



Driving Power MOSFETs in High-Current, Switch Mode Regulators

Author: Abid Hussain, Microchip Technology, Inc.

DRIVING THE MOSFET

The low on-resistance and high current carrying capability of power MOSFETs make them preferred switching devices in SMPS power supply design. However, designing with these devices is not as straightforward as with their bipolar counterparts.

Unlike bipolar transistors, power MOSFETs have a considerable gate capacitance that must be charged beyond the threshold voltage, VGS(TH), to achieve turn-on. The gate driver must provide a high enough output current to charge the equivalent gate capacitance, CEI, within the time required by the system design.

HOW MUCH GATE CURRENT?

The most common error in calculating gate current is confusing the MOSFET input capacitance, Ciss, for CEI and applying the equation....

I = C(dv/dt)

to calculate the required peak gate current. CEI is actually much higher, and must be derived from the MOSFET manufacturer's total gate charge, QG, specifications.

The total gate charge, QG, that must be dispensed into the equivalent gate capacitance of the MOSFET to achieve turn-on is given as:

QG = QGS + QGD + QOD

where:

- QG is the total gate charge
QGS is the gate-to-source charge
QGD is the gate-to-drain Miller charge
QOD is the "overdrive charge" after charging the Miller capacitance.

The curve of Figure 1 is typical of those supplied by MOSFET manufacturers. Notice that in order to achieve strong turn-on, a VGS well above that required to charge CEI (and well above VGS(TH)) is required. The equivalent gate capacitance is determined by dividing a given VGS into the corresponding total gate charge. The required gate drive current (for a transition within a specified time) is determined by dividing the total gate charge by the desired transition time.

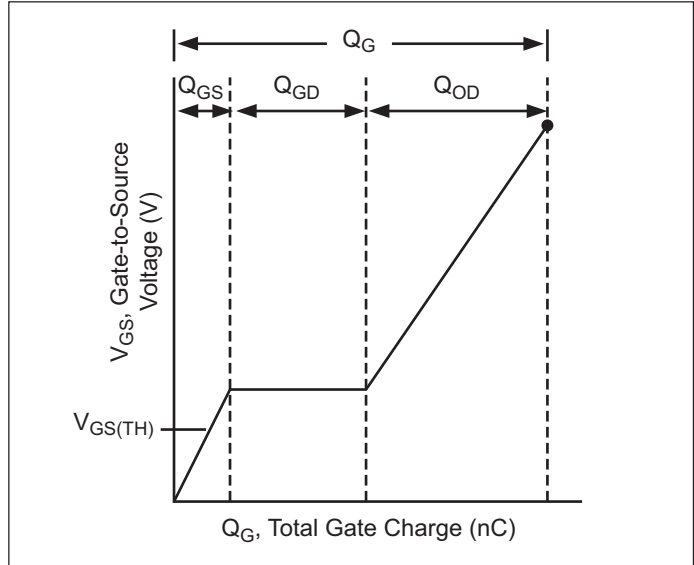


FIGURE 1: Gate charge characteristics.

In equation form:

QG = (CEI)(VGS)

and

IG = QG/t(transition)

where:

- QG is the total gate charge, as defined above
CEI is the equivalent gate capacitance
VGS is the gate-to-source voltage
IG is the gate current required to turn the MOSFET on in time period t(transition)
t(transition) is the desired transition time

For example:

- Given: N-Channel MOSFET
VGS = 10V
t (transition) = 25nsec

Find: Gate drive current, IG.

From the MOSFET manufacturer's specifications, QG = 50nC at VGS = 10V. Using IG = QG/t(transition):

IG = QG/t(transition) = 50 x 10^-9 / 25 x 10^-9 = 2.0A

AN786

Table 1 is a guideline for matching various Microchip MOSFET drivers to Industry-standard HEXFETs.

Device No.	Drive Current (Peak)	Output Number and Type		Rated Load (pF)	Rise Time @ Rated Load (nsec)	Fall Time @ Rated Load (nsec)	Rising Edge Prop. Delay (nsec)	Falling Edge Prop. Delay (nsec)	Latch-Up Proof	Input Protected to 5V Below GND Rail
		Inverting	Non-Invert.							
TC1410	0.5A	Single		500	25	25	30	30	Yes	Yes
TC1410N	0.5A		Single	500	25	25	30	30	Yes	Yes
TC1411	1.0A	Single		1000	25	25	30	30	Yes	Yes
TC1411N	1.0A		Single	1000	25	25	30	30	Yes	Yes
TC1426	1.2A	Dual		1000	23	17	36	43	Yes	No
TC1427	1.2A		Dual	1000	23	17	36	43	Yes	No
TC1428	1.2A	Single	Single	1000	23	17	36	43	Yes	No
TC4467	1.2A	— Quad NAND —		470	15	15	40	40	Yes	Yes
TC4468	1.2A	— Quad AND —		470	15	15	40	40	Yes	Yes
TC4469	1.2A	— Quad AND with INV—		470	15	15	40	40	Yes	Yes
TC4426	1.5A	Dual		1000	19	19	20	40	Yes	Yes
TC4426A	1.5A	Dual		1000	25	25	30	30	Yes	Yes
TC4427	1.5A		Dual	1000	19	19	20	40	Yes	Yes
TC4427A	1.5A		Dual	1000	25	25	30	30	Yes	Yes
TC4428	1.5A	Single	Single	1000	19	19	20	40	Yes	Yes
TC4428A	1.5A	Single	Single	1000	25	25	30	30	Yes	Yes
TC1412	2.0A	Single		1000	18	18	35	35	Yes	Yes
TC1412N	2.0A		Single	1000	18	18	35	35	Yes	Yes
TC1413	3.0A	Single		1800	20	20	35	35	Yes	Yes
TC1413N	3.0A		Single	1800	20	20	35	35	Yes	Yes
TC4423	3.0A	Dual		1800	23	25	33	38	Yes	Yes
TC4424	3.0A		Dual	1800	23	25	33	38	Yes	Yes
TC4425	3.0A	Single	Single	1800	23	25	33	38	Yes	Yes
TC4420	6.0A	Single		2500	25	25	55	55	Yes	Yes
TC4429	6.0A		Single	2500	25	25	55	55	Yes	Yes
TC4421	9.0A	Single		10000	60	60	30	33	Yes	Yes
TC4422	9.0A		Single	10000	60	60	30	33	Yes	Yes

Note: Typical values for $T_A = 25^\circ\text{C}$.

TABLE 1A: Selecting MOSFET drivers.

MOSFET Size	Die Size (mm)	C _{EI} of MOSFET (pF)	Suggested Driver Family (@ 12V)	Faster Rise/Fall Times
Hex 0	0.89 x 1.09	400	TC1426/4426/4469	
Hex 1	1.75 x 2.41	750	TC1426/4426/4469	
Hex 2	3.40 x 2.21	1500	TC1426/4426/4469	TC4423
Hex 3	4.44 x 2.79	3000	TC1426/4426	TC4423
Hex 4	7.04 x 4.32	6000	TC4423	TC4429
Hex 5	6.45 x 6.45	12,000	TC4423	TC4429
Hex 6	283 x 321 mil	15,000	TC4429/4420	TC4421/4422
Hex 7	283 x 348 mil	16,000	TC4429/4420	TC4421/4422
Parallel Modules	Various	Up to 48,000	TC4421/4422	

TABLE 1B: MOSFET die size vs. suggested drive family.

WHY DEDICATED MOSFET DRIVERS?

Traditional SMPS controllers have on-board drivers suitable for some applications. Typically, these drivers have peak output currents of 1A or less, limiting their scope of applications. In addition, the heat generated in these drivers causes the on-chip reference voltage to change.

The need for "smarter" power supplies are forcing SMPS controllers to grow in sophistication. Many newer SMPS controllers are fabricated in smaller geometry CMOS process technologies, precluding the use of high voltage (i.e. voltages greater than 12V). In such cases, the external MOSFET driver also acts as a level shifter, translating TTL-compatible levels to MOSFET drive voltages. A device like the TC4427A for example, furnishes a rail-to-rail output voltage swing (from a maximum V_{DD} of 18V) from an input swing of V_{IL} = 0.8V and V_{IH} = 2.4V.

Latch-up immunity is another consideration. Latch-up immunity is particularly important in that the driven MOSFETs typically drive inductive circuits that generate significant "kickback" currents. MOSFET drivers like the TC4427 can withstand as much as 0.5A of reverse output current without damage or upset.

Protection against shoot-through current is still another consideration, especially in higher speed SMPS designs. Shoot through currents are usually caused by excessively long driver rise, fall or propagational delay times; causing both the high side and low side MOSFETs to be on for a brief instant. Current "shoots through" (hence the name) from the supply input to ground, significantly degrading the overall supply efficiency. The use of dedicated MOSFET drivers minimizes this problem in two ways:

1. MOSFET gate drive rise and fall times must be symmetrical, and as short as possible. A driver like the TC4427 has a specified t_R and t_F of approximately 19nsec into a 1000pF load. A higher peak output current driver may be selected to achieve more aggressive rise and fall times if so desired.

2. The propagational delay times through the driver must be short (and matched for higher speed designs) to ensure symmetrical turn-on and turn-off delays of both the high side and low side MOSFET.

The TC4427A for example, has rising and falling edge propagation delay times matched to within 2nsec (see Figure 2). These delays track each other with both voltage and temperature. Microchip's 2nsec skew is among the best available (competing devices have skews at least 4 times larger; drivers integrated on board the SMPS controller are worse yet).

These concerns (and related cost and reliability concerns) usually point in the direction of an external, dedicated driver, as opposed to an integrated or external discrete component driver solution.

TYPICAL APPLICATIONS

Portable Computer Supply

One common application that exploits the design benefits of dedicated MOSFET drivers is a switching power supply for portable systems, such as those found in notebook computer applications. The circuit topology of a high efficiency, synchronous buck converter is shown in Figure 3. It accepts an input voltage range of 5V to 30V to accommodate AC/DC adapters (14V to 30V) or a battery supply (7.2V to 10.8V).

The TC1411N acts as a low side driver, and is powered from a +5V supply to minimize turn-off delay due to gate "overdrive charge." The high side driver in Figure 3 is a TC4431, which has a peak output current of 1.5A. The TC1411N has a peak output current capability of 1A. They can drive MOSFETs capable of 10A continuous drain current in 30nsec.

AN786

Desktop PC Power Supply

Desktop power supplies also benefit from the use of dedicated MOSFET drivers (Figure 4). The synchronous stepdown converter shown is common for CPUs requiring greater than 6A of DC current. It also accommodates custom voltages not accommodated by the current “silver box” supplies. Efficiency is not as large a concern, since this supply is line-powered.

The topology shown is simpler than that of Figure 3. The TC4428A serves as a high-side/low-side driver powered from the same V_{DD} . N-Channel MOSFETs are used to save cost. The TC4428A has sufficient output current to drive a 10A (continuous drain current) MOSFET active in 25nsec.

SUMMARY

Power MOSFETs are desirable as switching elements in SMPS designs because of their low on-resistance and high current carrying capability.

Using dedicated MOSFET drivers results in a more optimized SMPS design. Drivers integrated on-board the SMPS controller are advantageous only for low sophistication, low output power designs. External drivers fashioned from discrete active and passive components have neither the repeatable high performance, nor the low cost of a dedicated monolithic driver circuit. Dedicated drivers like those offered by Microchip feature fast rise, fall and delay times, and are available in a wide variety of topologies to suit virtually every application.

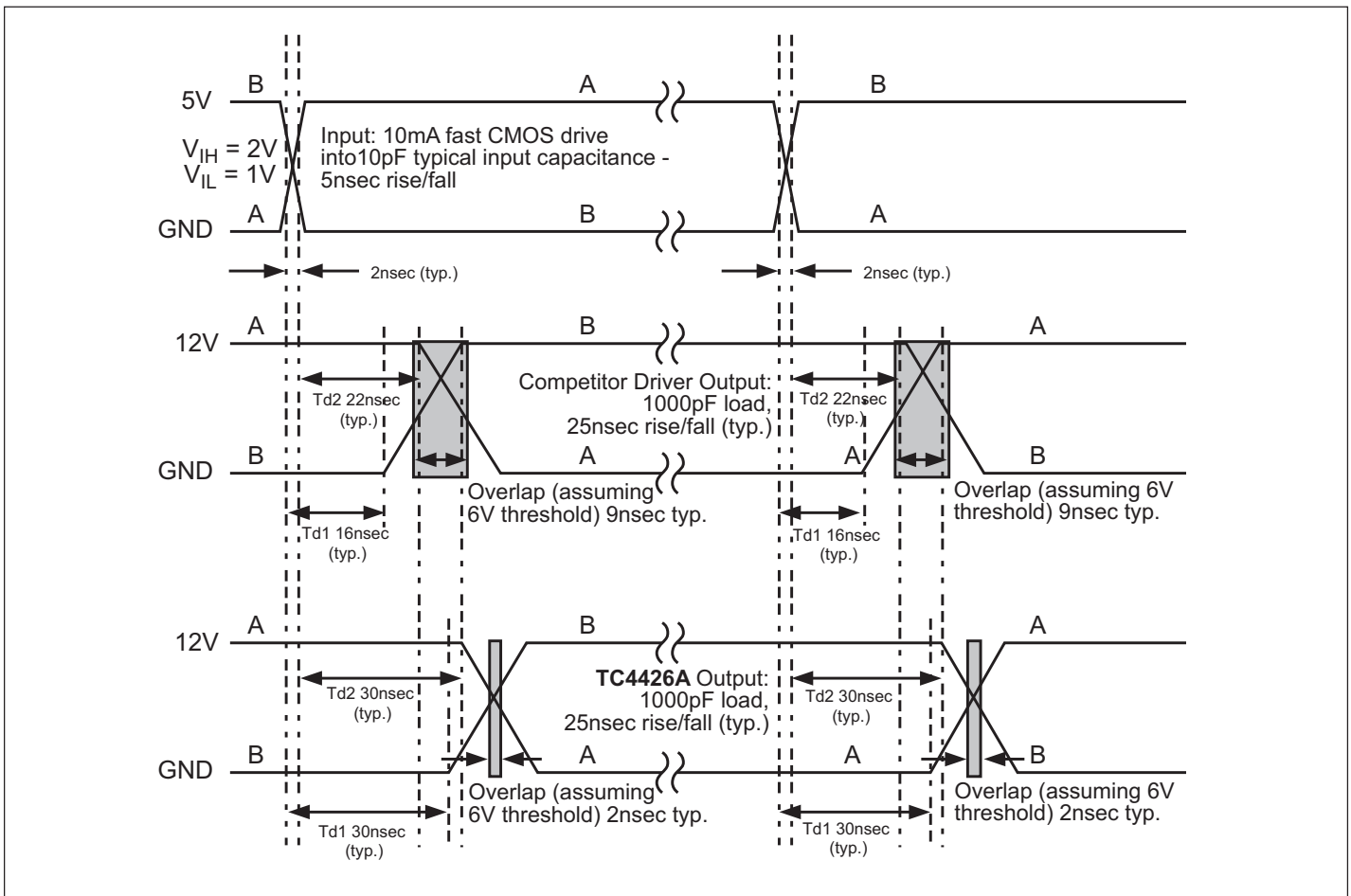


FIGURE 2: Matched delay times of the TC4426A reduce overlap times resulting in reduced shoot-through currents.

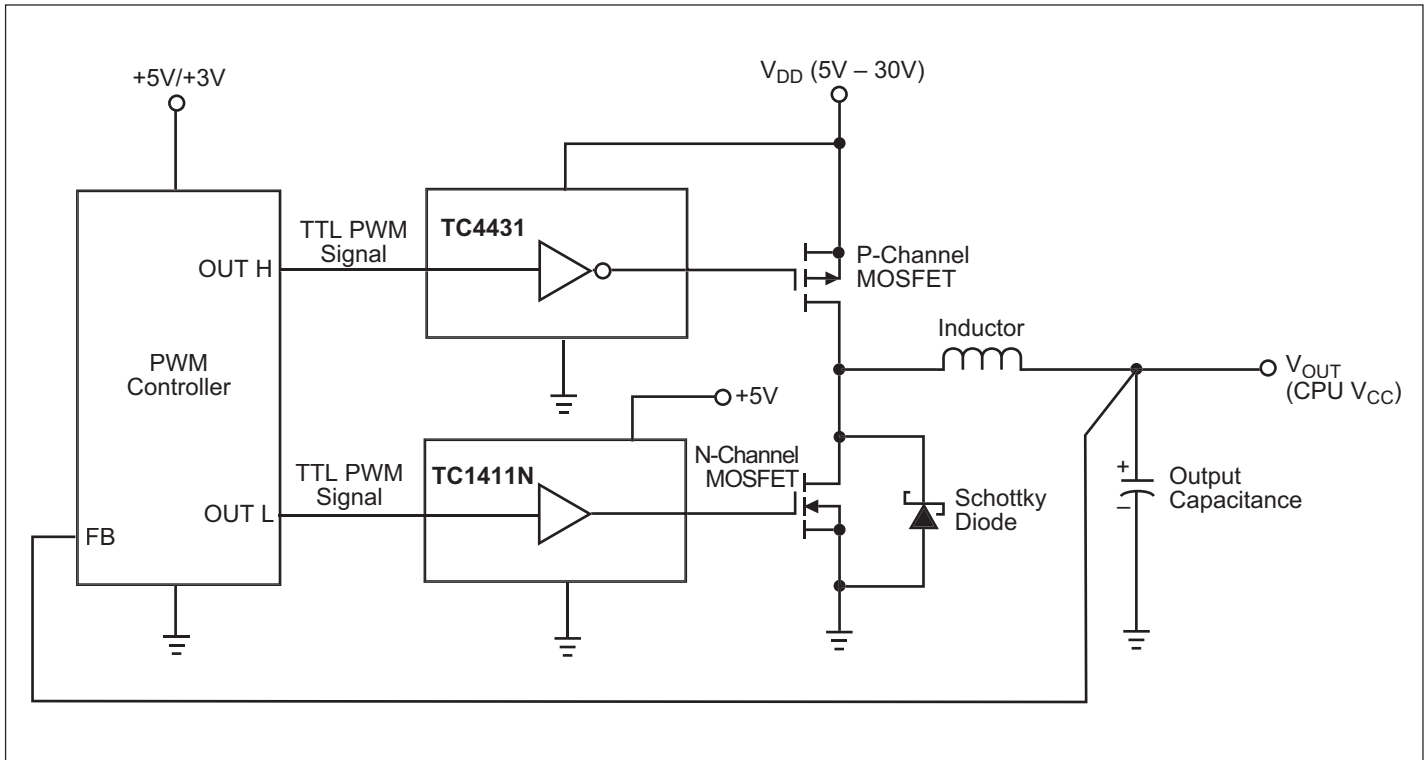


FIGURE 3: Portable CPU power supply.

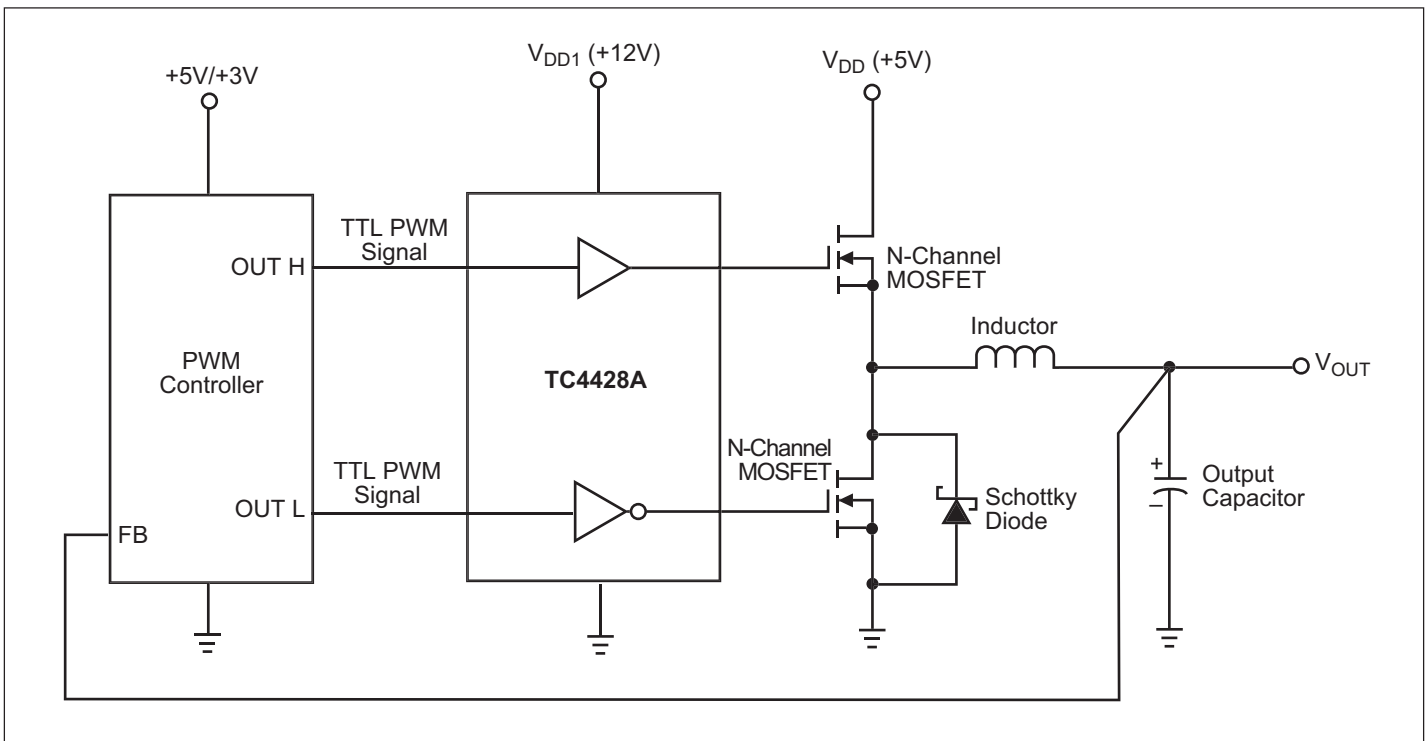


FIGURE 4: Desktop CPU power supply.

AN786

NOTES:

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks


The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.



Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELoq® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-692-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B
Atlanta, GA 30350
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202
Hauppauge, NY 11788
Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1315, 13/F, Shenzhen Kerry Centre,
Renminnan Lu
Shenzhen 518001, China
Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology Taiwan
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Gustav-Heinemann Ring 125
D-81739 Munich, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd.
505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02

