

Switched supplies with inductors

Basic principles

Basic information

- Switched supplies = supplies that works with an impulse (switched) regulation
- Stabilizer converts non-stabilized input (DC) to stabilized output DC voltage => DC-DC Converters
- Working frequency > 20kHz (above acoustic range), usually as high as possible (> 1 MHz) (dimensions, mass, output signal filtration)
- High requirements on electronic switch, accumulation inductor, impulse transformer, recuperation diode (high working frequency, short switch on and off time, low barrier capacitance)
- All impulse (switched) supplies works in feedback configuration
- Thyristor cannot be used as switching device (DC circuits)


Linear vs. switched

Disadvantages: linear stabilizer: big volume and mass of the stabilizer, low efficiency

Advantages: high efficiency of regulation, low voltage devices, voltage disturbances are filtered by line transformer

Basic principles



Switched supply with stabilization

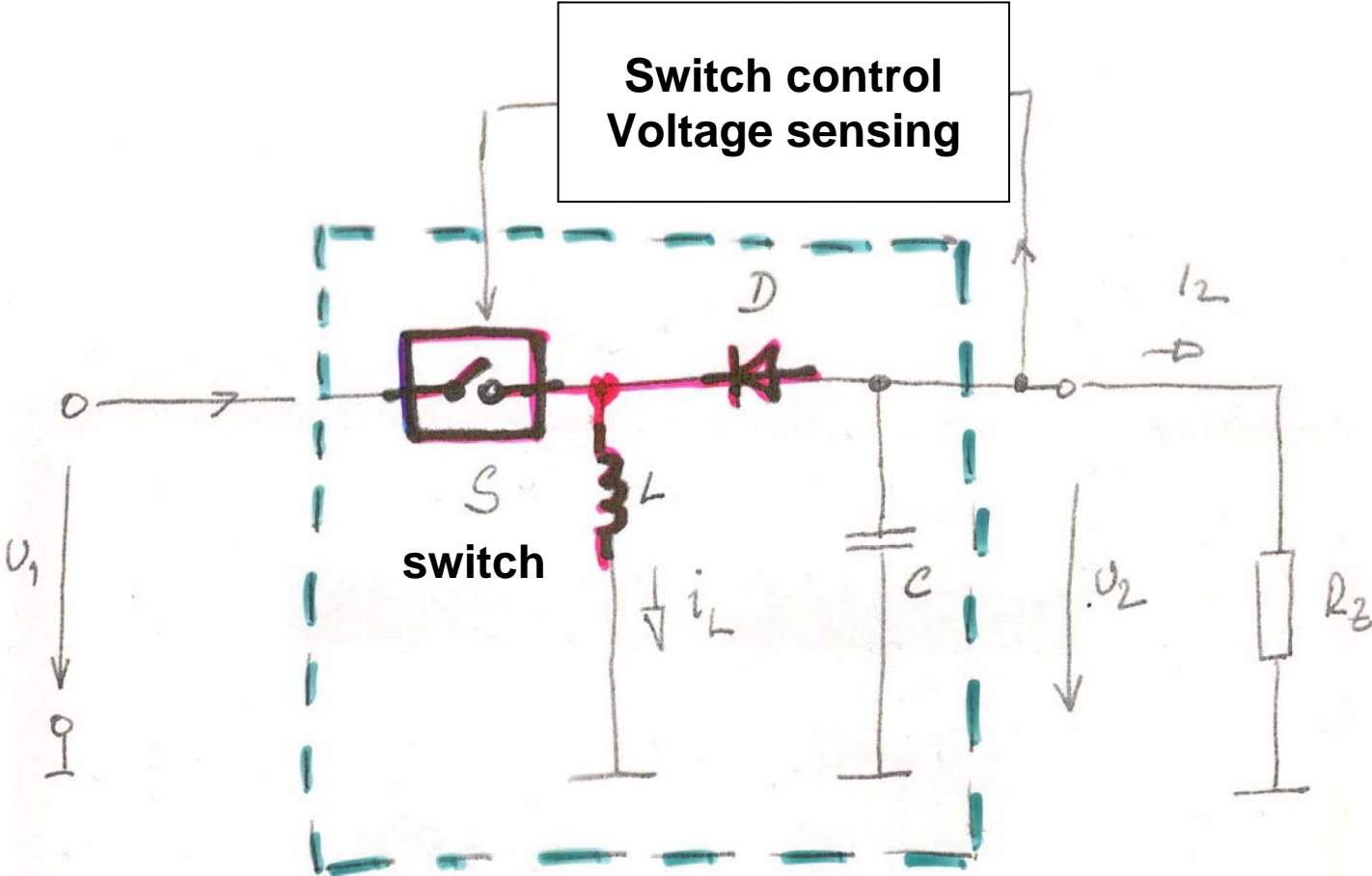

Accumulation filter


Switch

Simplified block circuit

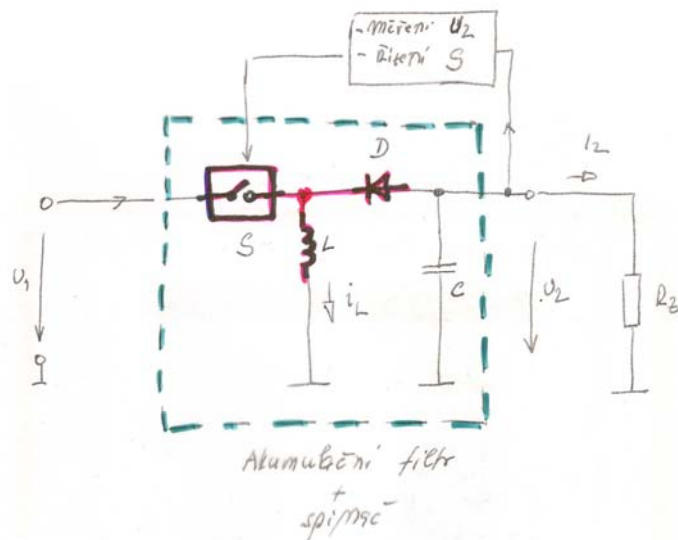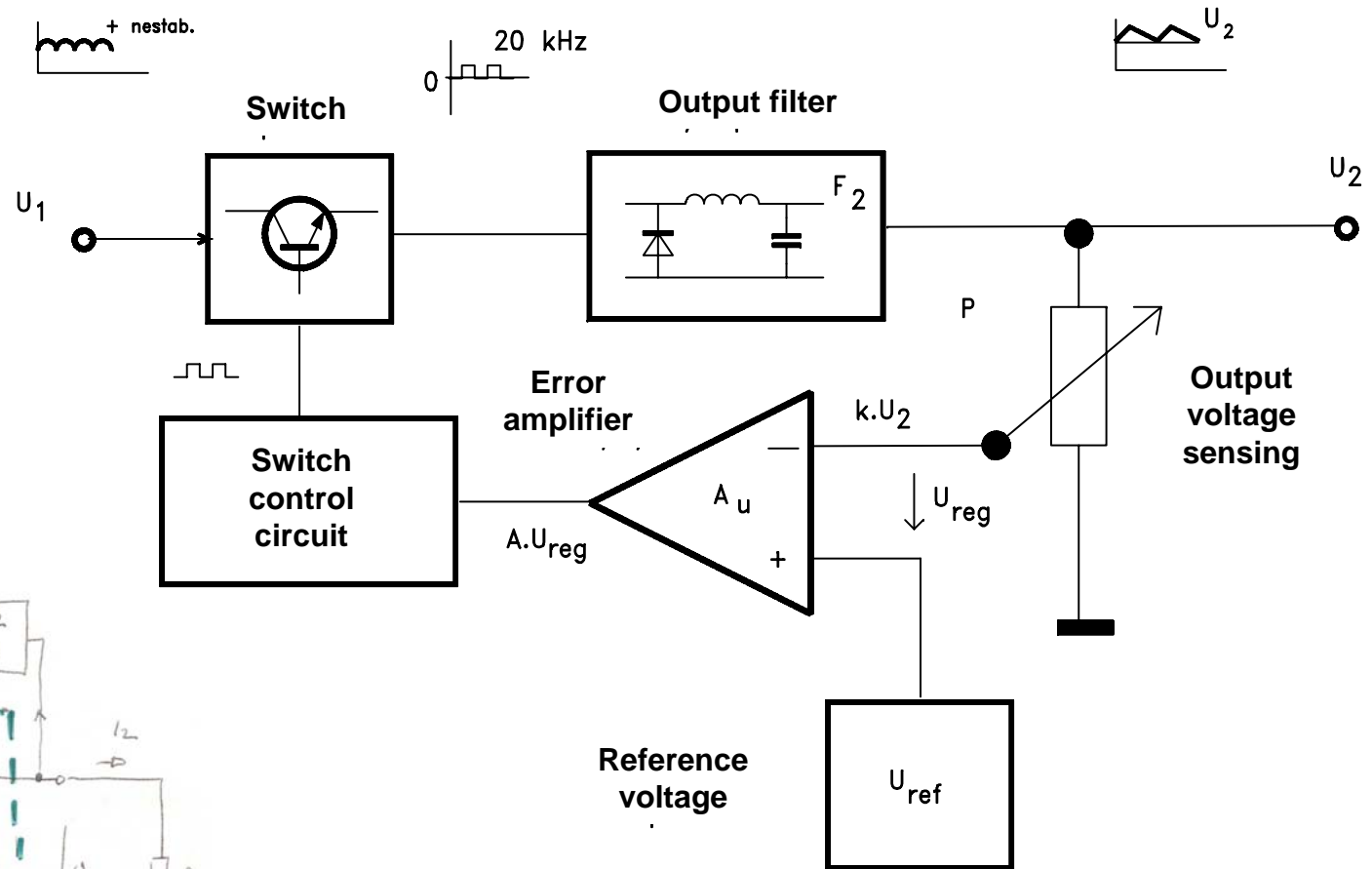


Switched supply with input transformer


Regulated on secondary part

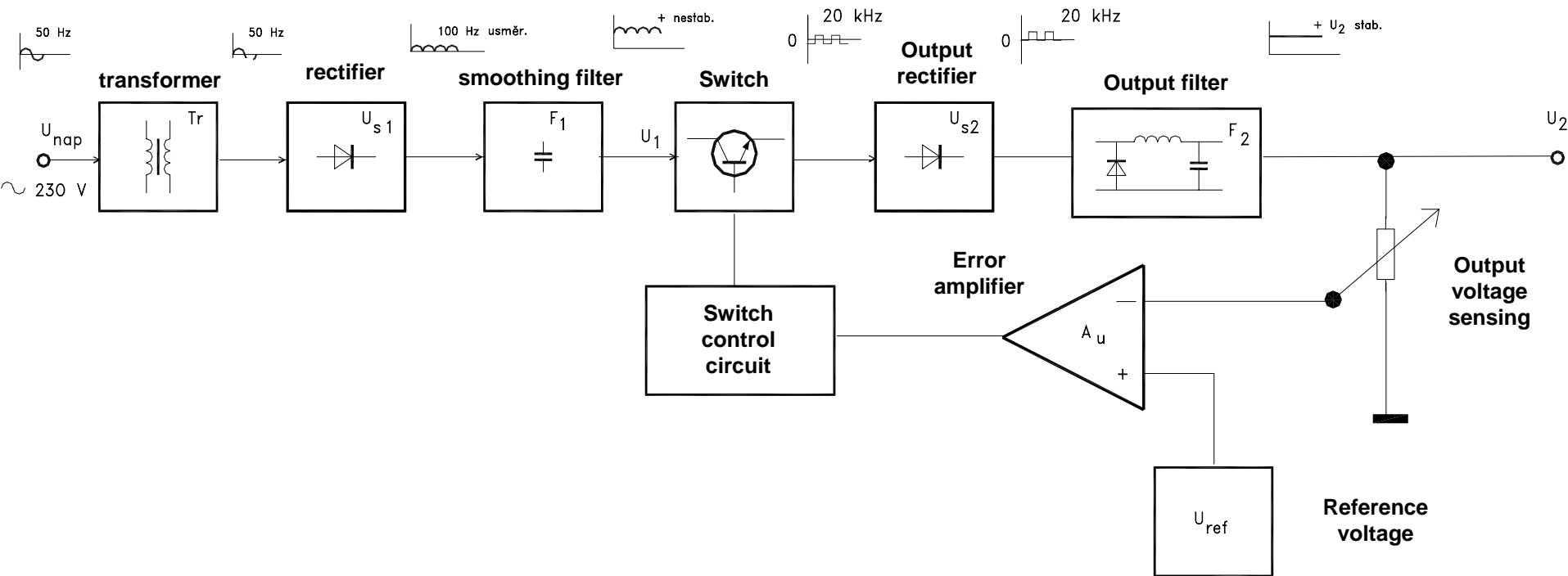

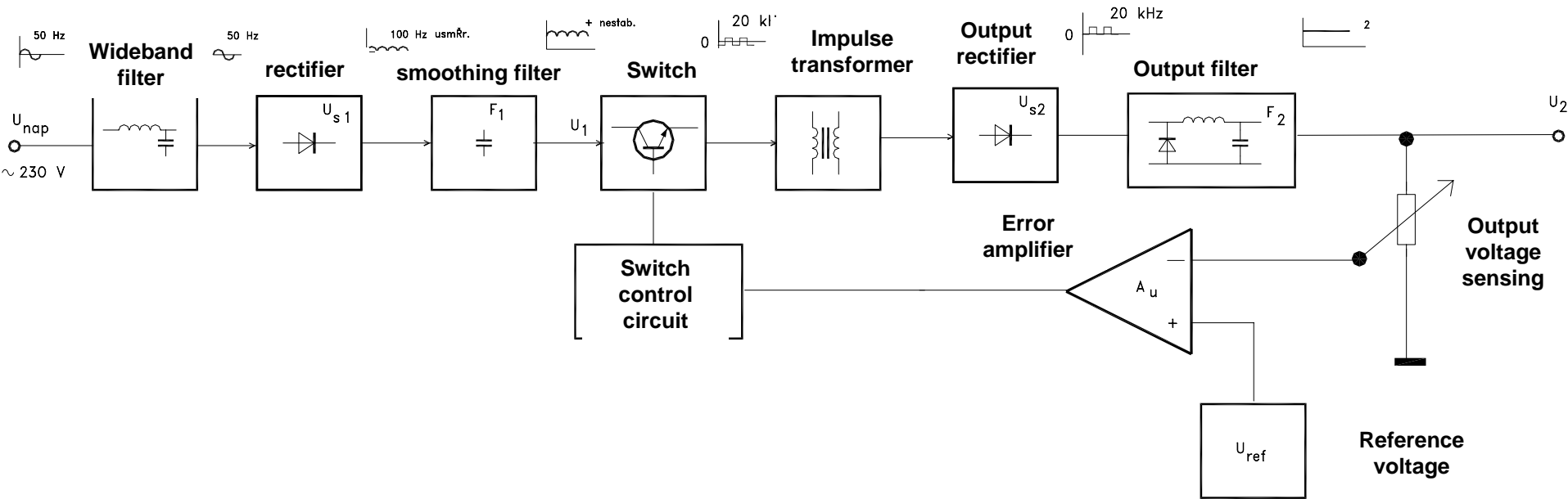
Switched supply without input transformer



DC/DC changer

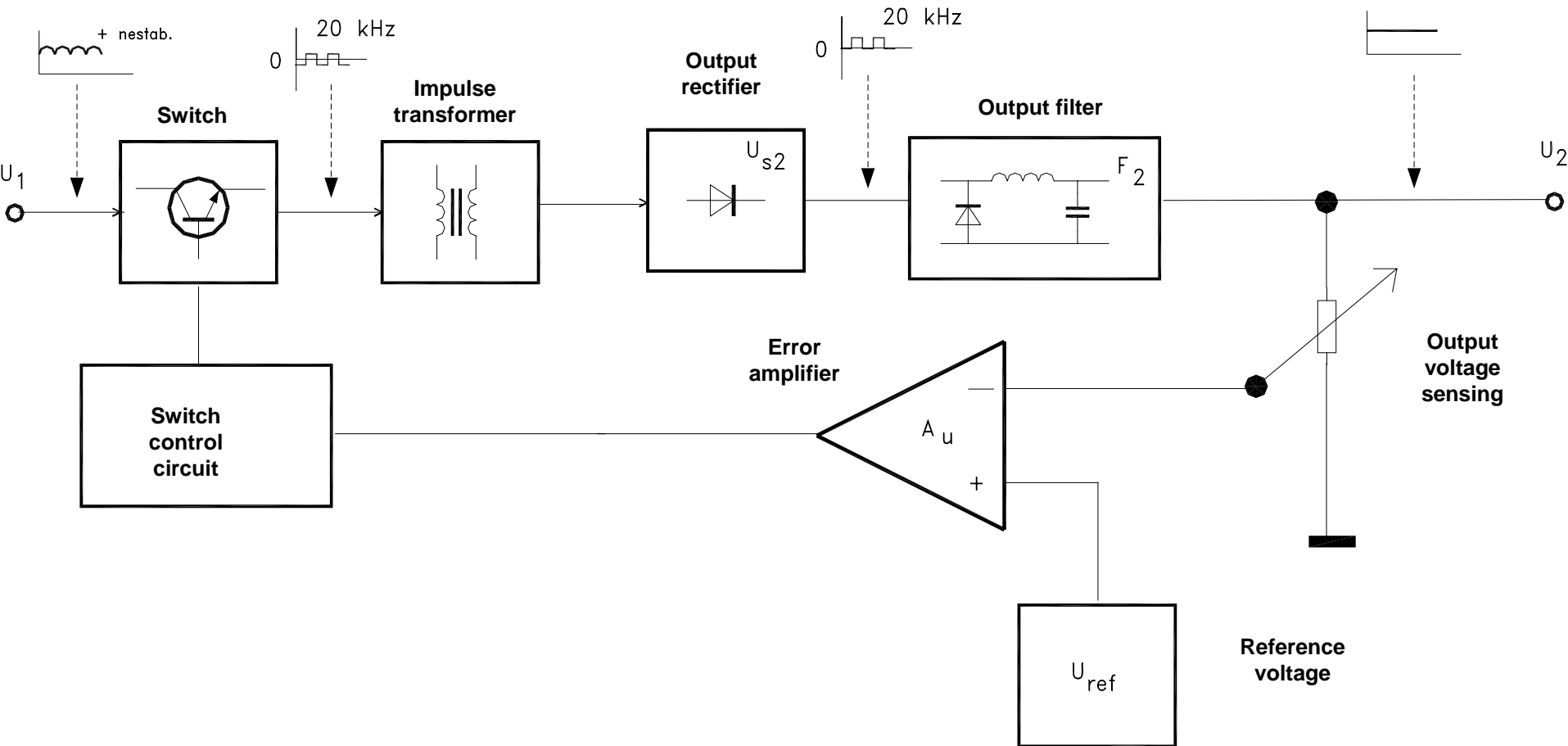

Switched stabilizer controlling

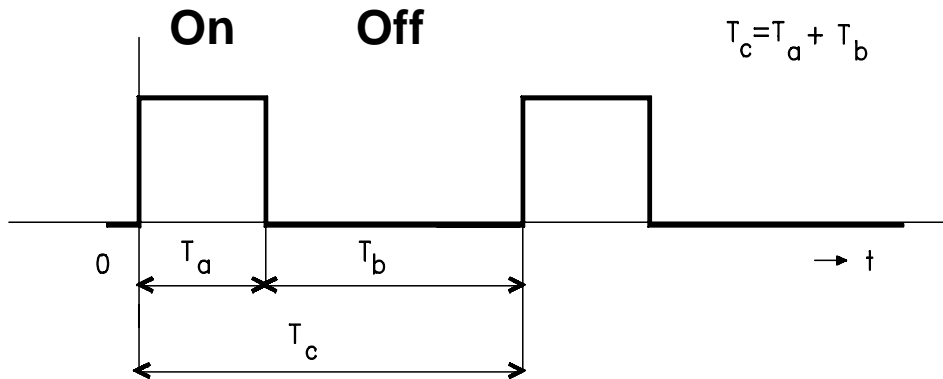

$$T_c = T_a + T_b$$


Duty cycle control

a) PFM: $T_a = \text{konst}$, $T \neq \text{konst}$, $T_b = g(I_z) \star f_c = g(I_z)$

b) PFM: $T_b = \text{konst}$, $T \neq \text{konst}$, $T_a = g(I_z) \star f_c = g(I_z)$

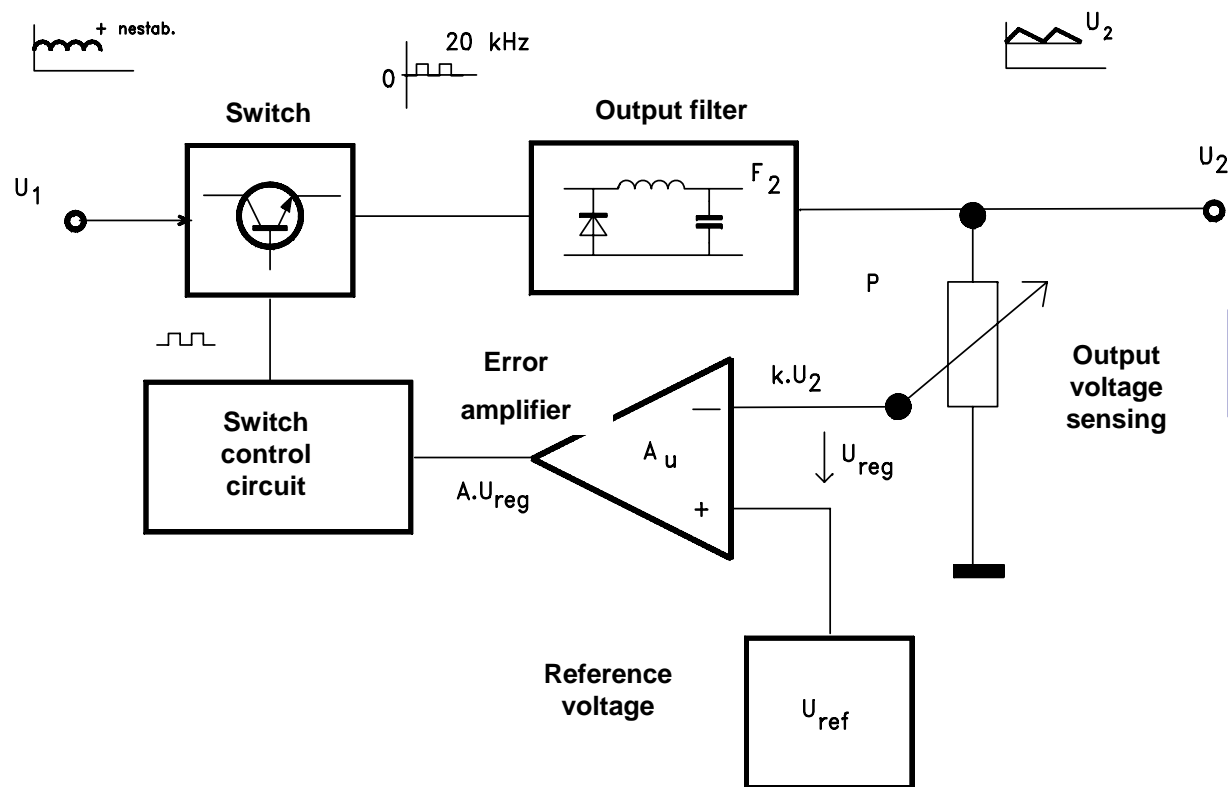c) PWM: $T_c = \text{konst}$, $T_a/T_b \neq \text{konst}$, $T_a/T_b = g(I_z) \star f_c = \text{konst}$

Impulse (switched) stabilizer – basic operation principle




$$U_{reg} = kU_2 - U_{ref}$$

$$U_2 = \frac{1}{k} U_{ref}$$

Basic problems of impulse (switched) regulation

Output filter has lag character, it causes delay between corrected voltage and deviation. For good dynamic parameters is required high switching frequency


Theoretical switching-regulator circuits

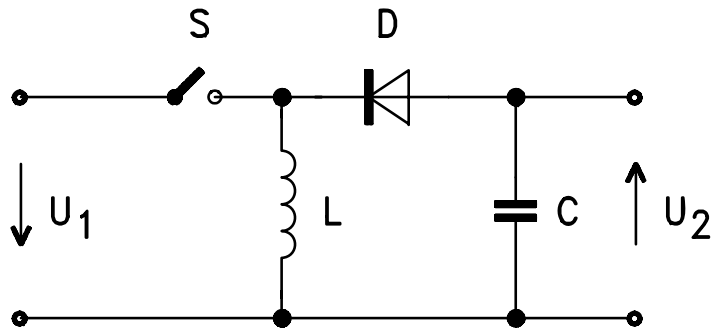

a)

BUCK - BOOST


$$U_2 \leq -U_1$$

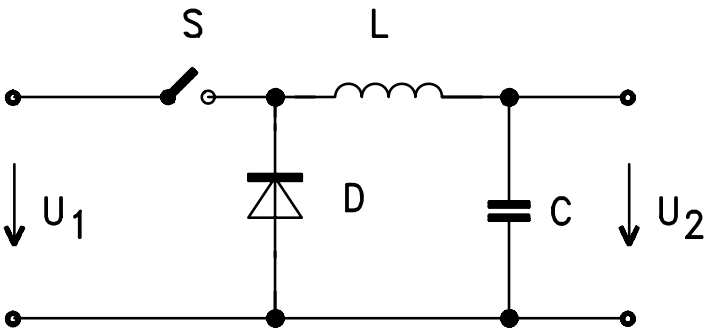

b)

BUCK

$$U_2 \leq U_1$$

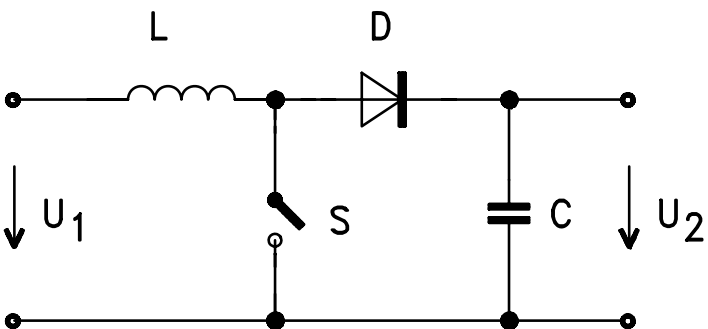

c)

BOOST

$$U_2 > U_1$$

There are used three basic devices in all theoretical circuits.

- switch
- accumulating inductor
- recuperating diode



In some cases, inductor can be changed by impulse transformer

T_a – switch ON time

T_b – switch OFF time

T_c – duty cycle

Inductor operating principle

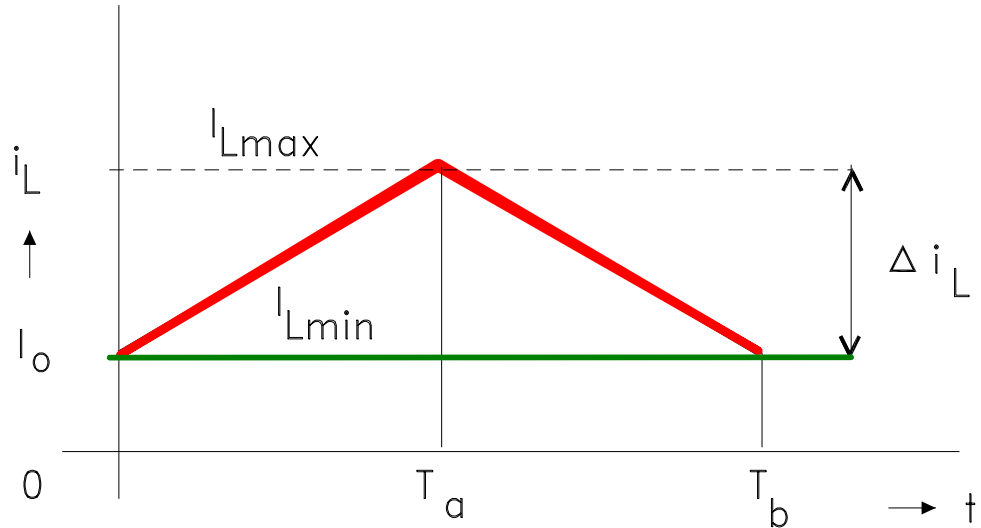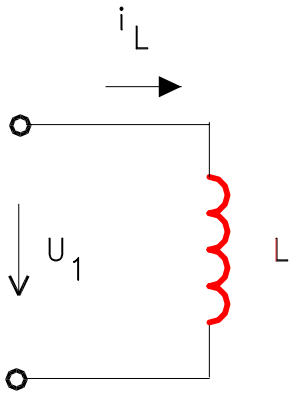

$$u_L = L \frac{di}{dt}$$

$$di = \frac{1}{L} u_L dt$$


$$I_{Lmax} = \int_0^{T_a} \frac{1}{L} u_L dt + I_o$$

$$I_{Lmax} = \frac{1}{L} U_1 T_a + I_o$$


$$\Delta i_{L_a} = I_{Lmax} - I_o$$

$$\Delta i_{L_a} = \frac{1}{L} U_1 T_a$$

BUCK-BOOST or inverting configuration

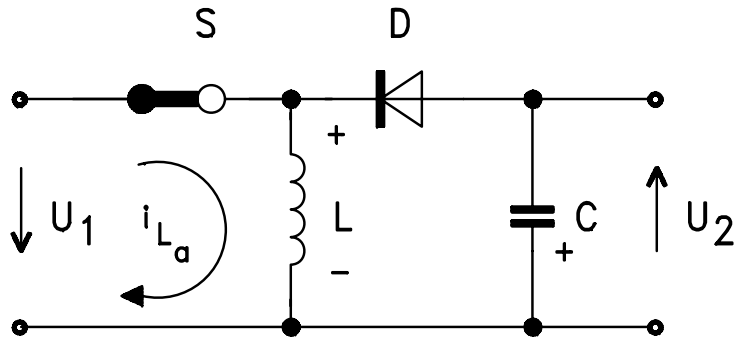


a) interval T_a

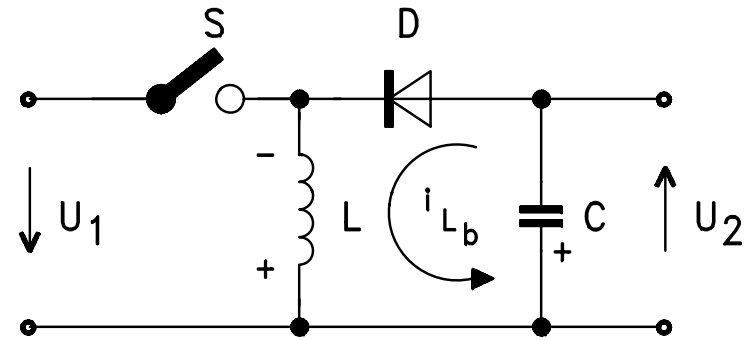

b) interval T_b

$$\Delta i_{L_a} = \frac{1}{L} U_1 T_a$$

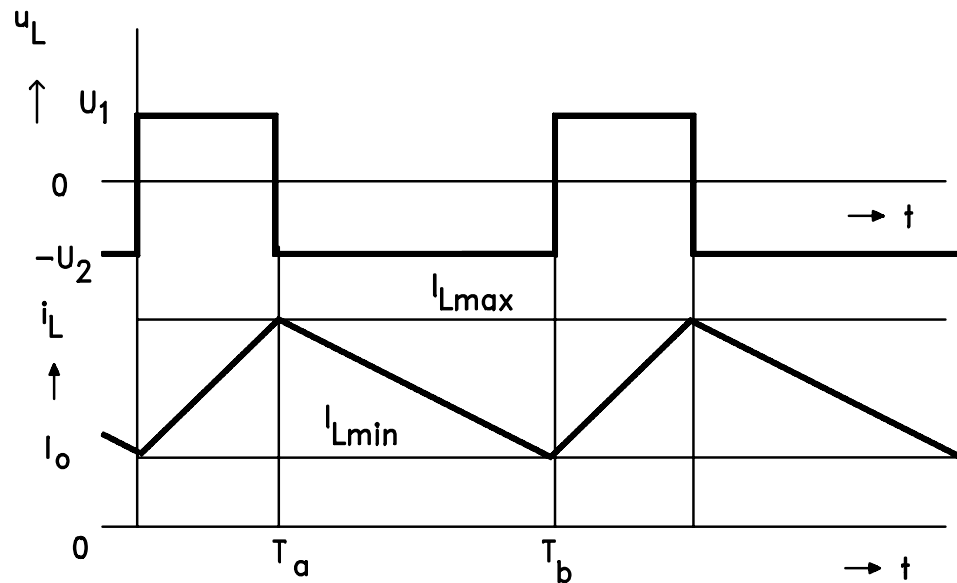

$$U_{2_{max}} \leq -U_1$$

c)

Operating principle of BUCK-BOOST configuration

Interval Ta

Switch is ON ,L accumulates magnetic field energy. Inductor current

$$i_L = \int_0^{T_a} u_L dt + I_o$$

$U_1 = \text{konst.}$,. For current increase at the end of T_a is:

$$\Delta i_{L_a} = \frac{U_1}{L} T_a$$

Peak current at the end of T_a


$$I_{L_{max}} = I_o + \Delta i_{L_a}$$

Accumulated energy W_a at the end of T_a


$$W_a = W_o + \Delta W_a$$

For energy of ideal changer in T_a and T_b


$$W_a = W_b$$

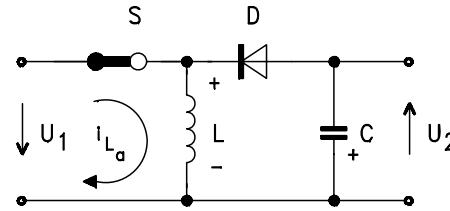

a) interval T_a

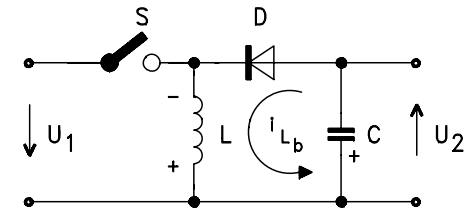

b) interval T_b

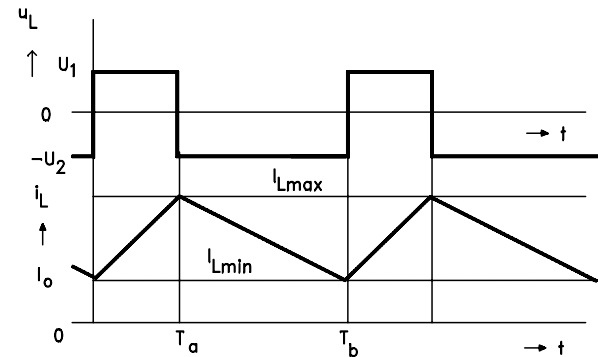

c)

Operating principle of BUCK-BOOST configuration

Interval Tb

When inductor is disconnected from U1, negative voltage is induced on their pins (due to...), inductor behaves as energy supply, and current flows through Diode and capacitor. At the beginning of Tb:


$$\Delta W_a = \Delta W_b$$

$$\Delta i_{L_a} = \Delta i_{L_b}$$


$$\Delta i_{L_a} = \frac{U_1}{L} T_a$$

$$\Delta i_{L_b} = \frac{U_2}{L} T_b$$

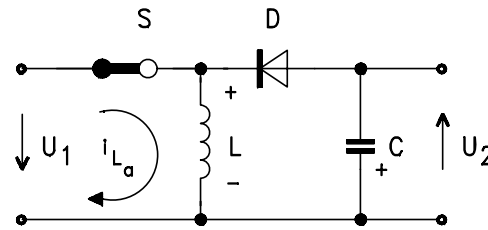
$$\frac{U_1}{L} T_a = \frac{U_2}{L} T_b \Rightarrow U_2 = U_1 \frac{T_a}{T_b}$$



a) interval Ta

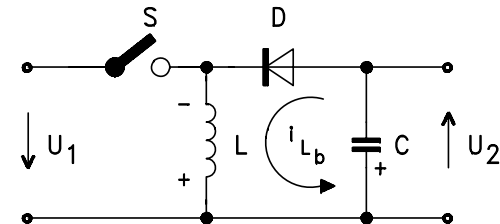


b) interval Tb

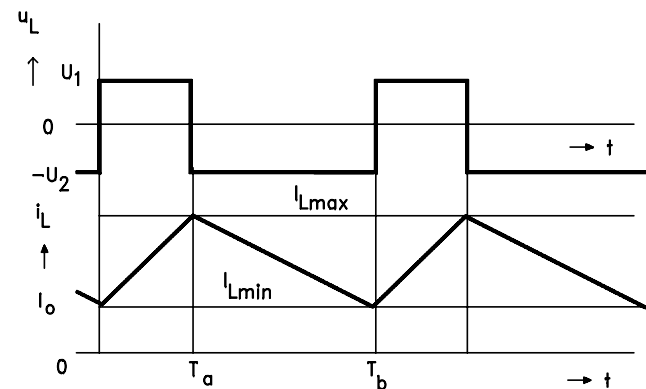

c)

Operating principle of BUCK-BOOST configuration

Minimum and maximum allowed load current

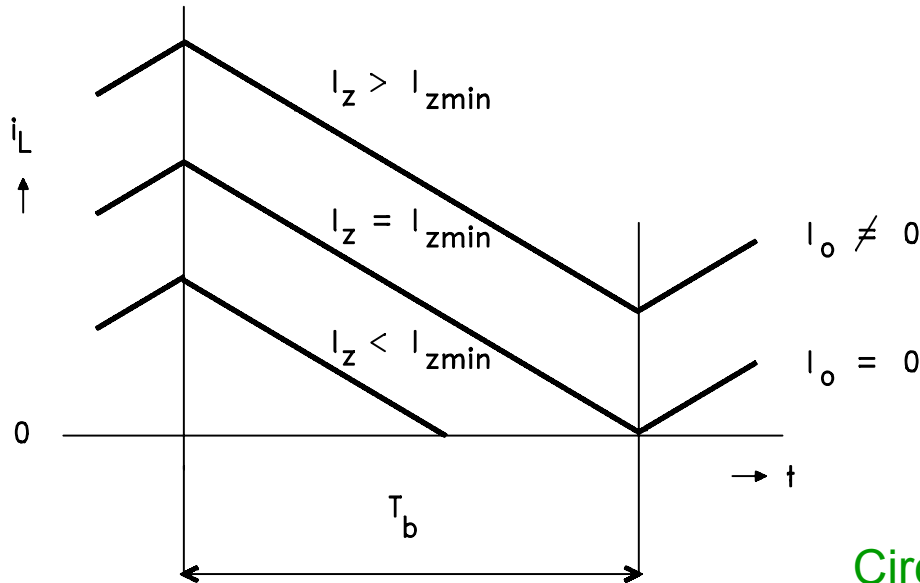


Min load current I_{zmin}

$$I_o = 0$$

$$I_z < I_{zmin} \Rightarrow W_a \neq W_b$$

Max load current I_{zmax}

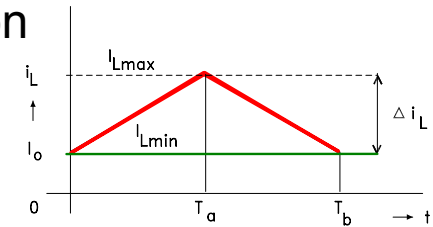- Limited by magnetic saturation of impulse transformer core
- IT is not allowed to be at saturation



Circuit disadvantages

- Relatively high output ripple ΔU_2 , especially at low output voltages and high load currents.

Reason:

- In T_a is load supplied just from C
- In T_b is C charged by high current impulses
- Voltage loss at diode, $U_{AK} \neq 0$.
- Parasitic R and L of real C.

Operating principle of BUCK-BOOST configuration

Design of capacity

- according to exponential discharging in T_a of RC circuit consist of load resistor and capacitor

Voltage on capacitor when switch is switched ON ($t=0$)


$$U_C(0) = U_2$$

Voltage on capacitor at the end of T_a , when ripple of output voltage is ΔU_2

$$U_C(T_a) = U_{Cmin}$$

Exponential discharging
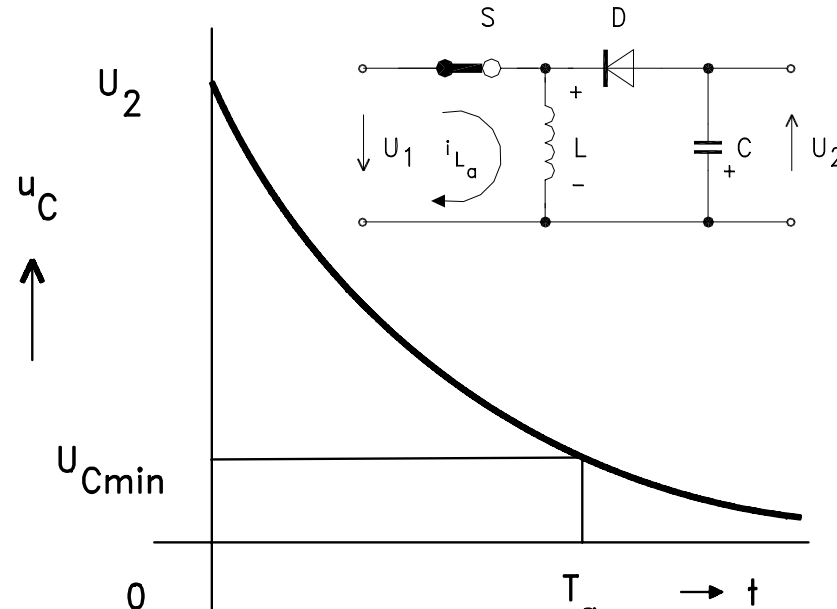
$$u_C = U_2 e^{-\frac{t}{\tau}} \quad \tau = R_z C$$



$$U_{Cmin} = U_2 e^{-\frac{T_a}{R_z C}}$$




$$C = \frac{T_a}{R_z \ln \frac{U_2}{U_{Cmin}}}$$

Output ripple is practically $< 20\%$, equation can be simplified

$$C \geq \frac{T_a}{R_z} \cdot \frac{U_2}{\Delta U_2} = \frac{T_a}{\Delta U_2} I_z$$

Circuit configuration with impulse transformer

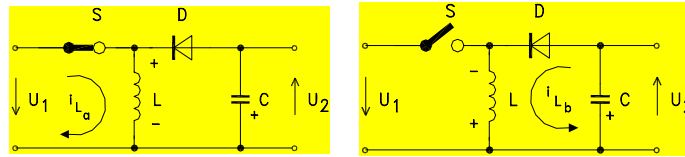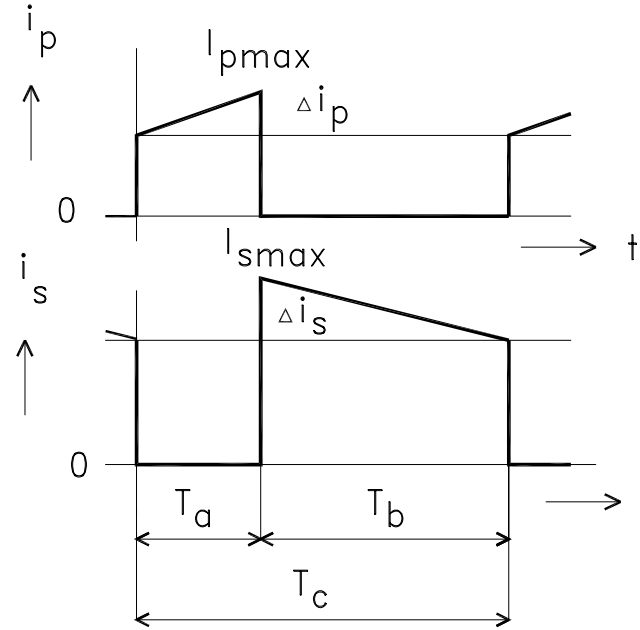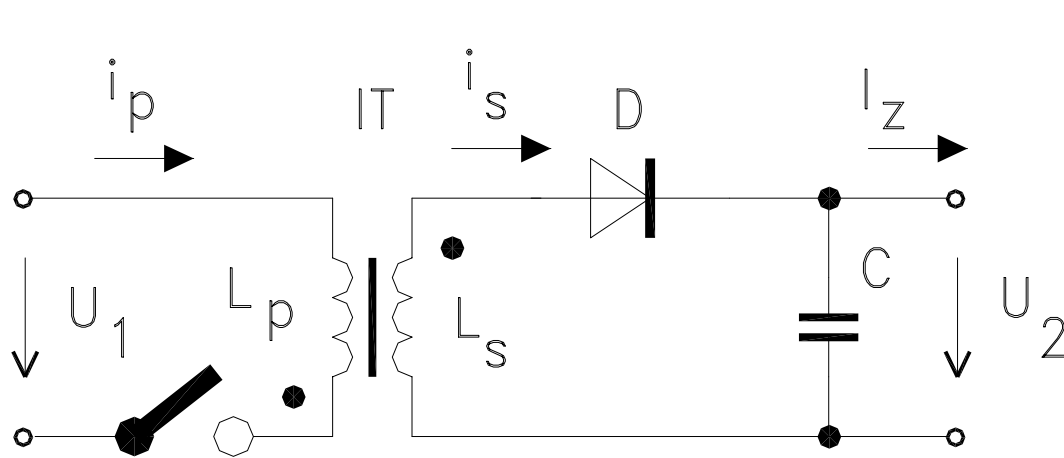Operating principle – inductor is replaced by impulse transformer



$$\Delta i_p = \frac{U_1 T_a}{L_p}$$

$$\Delta i_s = \frac{U_2 T_b}{L_s}$$

$$\frac{\Delta i_s}{\Delta i_p} = \frac{n_p}{n_s}$$

$$\frac{L_s}{L_p} = \left(\frac{n_s}{n_p}\right)^2$$

$$\Delta i_p = \frac{n_s}{n_p} \Delta i_s$$

$$\frac{U_1 T_a}{L_p} = \frac{n_s}{n_p} \cdot \frac{U_2 T_b}{L_s}$$

$$\frac{U_1 T_a}{L_p} = \frac{n_s}{n_p} U_2 T_b \frac{1}{L_p} \left(\frac{n_p}{n_s}\right)^2$$

$$U_2 = \frac{n_s}{n_p} \cdot \frac{T_a}{T_b} U_1$$

Circuit configuration with impulse transformer

Design example of buck boost switching regulator with impulse transformer

a) Design of transformer secondary coil L_s


Assumption - given U_2 and I_{zmin} . $I_z = I_o + \Delta i_s$ (average value). $I_o = 0$ for I_{zmin} .

$$I_{zmin} = \frac{\Delta i_s}{2} \cdot \frac{T_b}{T_c} \quad \leftarrow \quad \Delta i_s = \frac{U_2}{L_s} T_b$$

$$I_{zmin} = \frac{1}{2} \cdot \frac{U_2}{L_s} \cdot T_b \cdot \frac{T_b}{T_c}$$


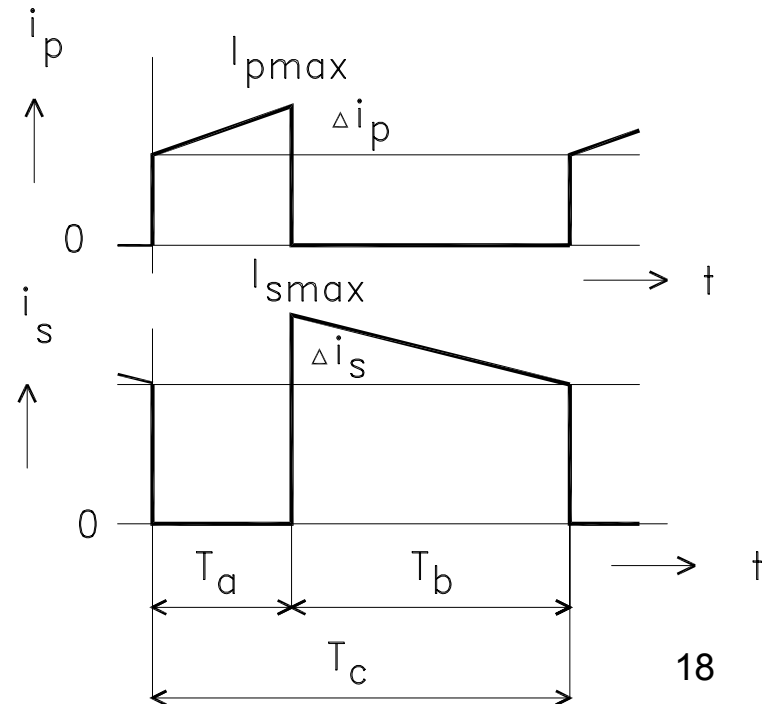
$$L_s = \frac{U_2}{2 I_{zmin}} \cdot \frac{T_b^2}{T_c}$$



Circuit configuration with impulse transformer

Design example of buck boost switching regulator with impulse transformer

b) Design of transformer primary

$$\frac{L_s}{L_p} = \left(\frac{n_s}{n_p}\right)^2 \longrightarrow L_p = L_s \left(\frac{n_p}{n_s}\right)^2$$

Ls from previous slide

$$L_s = \frac{U_2 \cdot T_b^2}{2 I_{zmin} T_c}$$

Instead of square of transformer ratio

$$U_2 = \frac{n_s}{n_p} \cdot \frac{T_a}{T_b} U_1$$

$$L_p = \left(\frac{U_2 \cdot T_b^2}{2 I_{zmin} T_c}\right) \cdot \left(\frac{U_1 \cdot T_a}{U_2 T_b}\right)^2$$



$$L_p = \frac{U_1^2}{2 U_2 I_{zmin}} \cdot \frac{T_a^2}{T_c}$$