

TRANSFORMER MEASUREMENT

I. $S_n = 440 \text{ VA}$

$V_{1n} = 220 \text{ V}, I_{1n} = 2 \text{ A}$

$V_{2n} = 110 \text{ V}, I_{2n} = 4 \text{ A}$


II. $S_n = 600 \text{ VA}$

$V_{1n} = 150 \text{ V}, I_{1n} = 4 \text{ A}$

$V_{2n} = 300 \text{ V}, I_{2n} = 2 \text{ A}$

1. Voltage – Current Characteristic (Volt – Ampere Ch.)

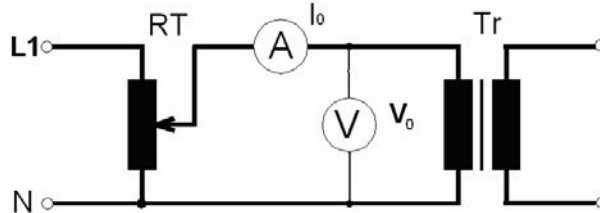Task: To measure $I_0 = f(V_0)$ dependence – for **NO-loaded** transformer. Plot the graph.



I. $V_{1n} = 110 \text{ V}$

V_0 [V]	30	60	90	120	150
I_0 [A]					


II. $V_{1n} = 150 \text{ V}$

V_0 [V]	40	80	120	160	180
I_0 [A]					

2. Loading Characteristic

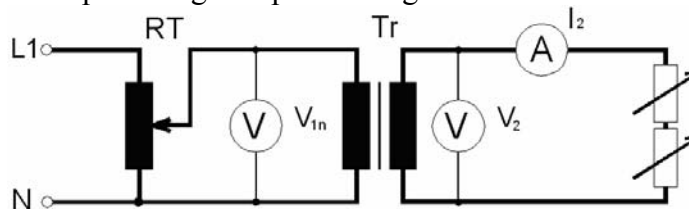Task:

- To measure – the Transformer Loading Characteristic $V_2 = f(I_2)$; and plot the graph.
- To calculate – the percentage drop of voltage Δv for the rated current I_n .




I. $V_{1n} = 220 \text{ V}$

I_2 [A]	0	1	2	3	4	5
V_2 [V]						

II. $V_{1n} = 150 \text{ V}$

I_2 [A]	0	1	1,5	2	2,5
V_2 [V]					
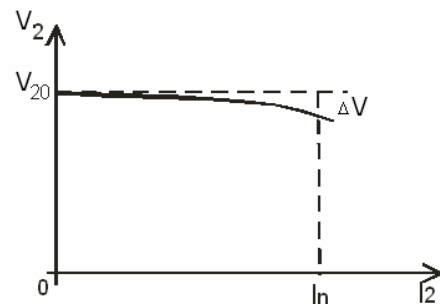
$$\Delta v = \frac{\Delta V}{V_{20}} 100 [\%]$$




3. As the measurement results – to determine the values for the **Efficiency η** Calculation; and for the **Relative Voltage Drop ε** Calculation - by the specific load.

Task:

- a) Using the Ohm's law method – to measure the primary winding Resistor **R_1** , and the secondary winding Resistor **R_2** .

b) **Open-circuit Test**

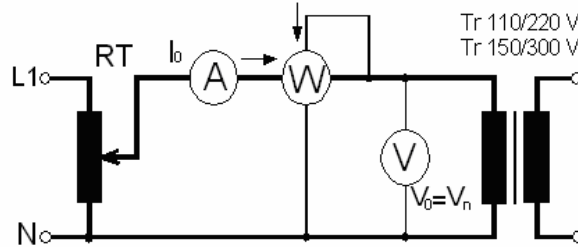


W : wattmetr 1 A; 150 V; $\cos\phi_W=0,2$

V_0 [V]	I_0 [A]	α [d]	k_w [W/d]	R_w [Ω]	R_v [Ω]	P' [W]	ΔP_0 [W]	$\cos\phi_0$ [-]
V_n								

$$P' = \frac{V_0^2}{R_w} + \frac{V_0^2}{R_v} \quad \Delta P_0 = \alpha \cdot k_w - P' \quad \cos\phi_0 = \frac{\Delta P_0}{V_0 \cdot I_0} \quad k_w = \frac{r_1 \cdot r_v}{d} \cos\phi_w$$

c) **Short-circuit Test**

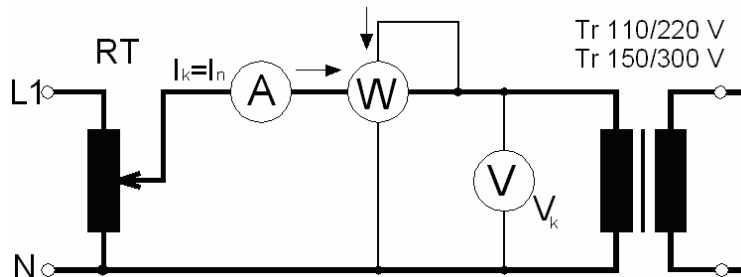

W : wattmetr 2 A; 75 V; $\cos\phi_W=0,2$

I_k [A]	V_k [V]	α [d]	k_w [W/d]	ΔP_k [W]	$\cos\phi_k$ [-]	v_k [%]
I_n						

$$\Delta P_k = \alpha \cdot k_w \quad \cos\phi_k = \frac{\Delta P_k}{V_k \cdot I_k} \quad v_k = 100 \frac{V_k}{V_n} \quad k_w = \frac{r_1 \cdot r_v}{d} \cos\phi_w$$

4. Being measured transformer (by open-circuit test; and by short-circuit test) – to calculate: the **Efficiency η [%]**; and the **Percentage Drop of Voltage ε [%]**.

(See textbook – only in Czech - Uhlřa a kol. : Elektrotechnika – laboratorní návody ; (El. Engineering – Labs Manuals) page 90 – 92).

Given parameters: $\cos\phi$... power factor for the load...(e.g.: $\cos\phi = 0,8$) ;
 $v = I_2/I_{2n}$... relative load ...(e.g.: $v = 1$) .

a) **Efficiency Calculus η [%]** for Transformer (by open-circuit test; and by short-circuit test)

$$\eta = 100 - \frac{1}{\cos \varphi} \left(\frac{\Delta p_0}{v} + v \Delta p_K \right)$$

$$\Delta p_0 = 100 \cdot \frac{\Delta P_0}{S_n} \dots\dots \text{percentage loss by open-circuit test}$$

$$\Delta P_0 [W] \dots\dots \text{the loss by open-circuit test for } V_{1a}$$

$$\Delta p_K = 100 \cdot \frac{\Delta P_{K75^\circ C}}{S_n} \dots\dots \text{percentage loss by short-circuit test}$$

$$\Delta P_{K75^\circ C} [W] \dots\dots \text{the loss by short-circuit test for } I_{1a} \text{ and } 75^\circ C$$

$$\Delta P_K = \Delta P_j + \Delta P_d$$

$$\Delta P_j = R_1 I_{1K}^2 + R_2 I_{2K}^2$$

$$I_{2K} = p \cdot I_{1K}$$

$$p = \frac{V_{1n}}{V_{2n}}$$

$$\Delta P_{K75^\circ C} = \Delta P_{j75^\circ C} + \Delta P_{d75^\circ C}$$

$$\Delta P_{j75^\circ C} = \Delta P_j \cdot \frac{75 + k}{t_0 + k}$$

$$\Delta P_{d75^\circ C} = \Delta P_d \cdot \frac{t_0 + k}{75 + k}$$

$$k = k_{Cu} = 235 \quad t_0 = 20^\circ C$$

b) **Voltage Drop Calculation ε [%]**

$$\varepsilon = v \left(v_{R75^\circ C} \cos \varphi + v_L \sin \varphi \right)$$

$$v_R = v_K \cdot \cos \varphi_K \dots \text{resistive part of } v_K \text{ in percentage}$$

$$v_{R75^\circ C} = v_K \cdot \frac{k + 75}{k + t_0}$$

$$v_L = v_K \cdot \sin \varphi_K \dots\dots \text{reactive part of } v_K \text{ in percentage}$$

$$v_K = 100 \cdot \frac{V_{1K}}{V_{1n}} \dots\dots \text{short circuit voltage in percentage}$$