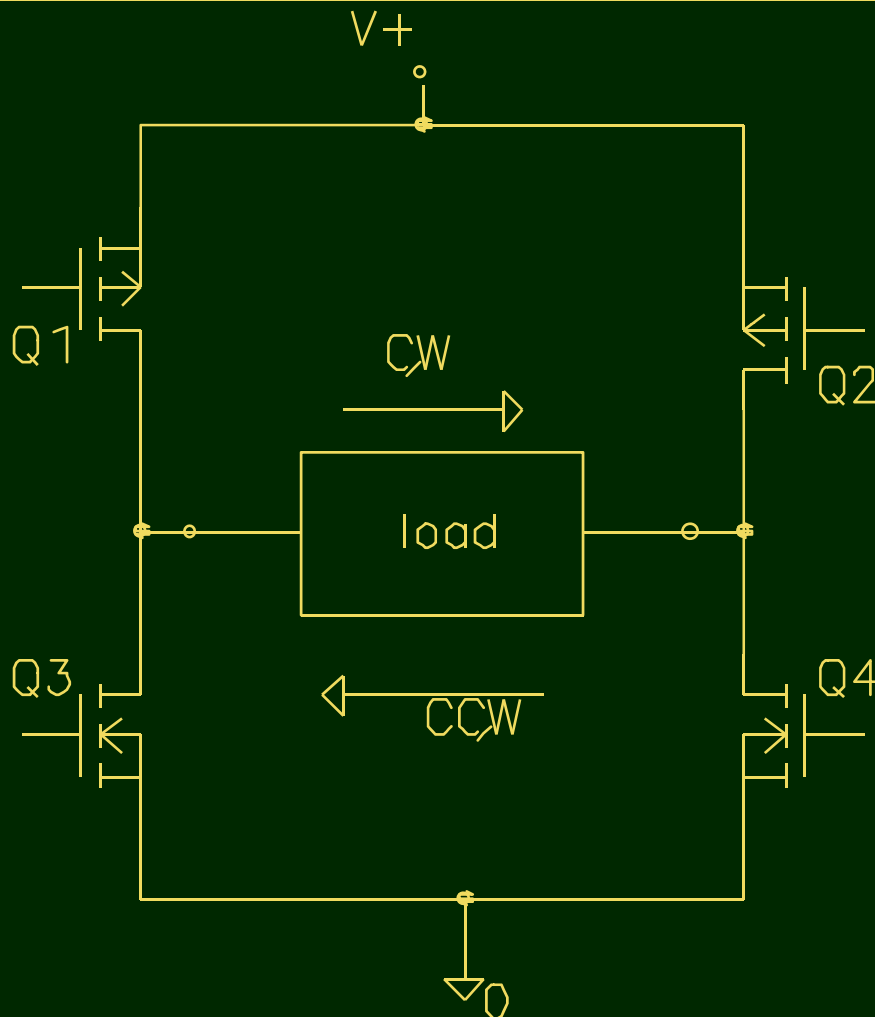


H Bridge



N channel

low side switch

$V_g = 0 \Rightarrow \text{OFF}$

$V_g > V_{th} \Rightarrow \text{ON}$

P channel

high side switch

$V_g = 0 \Rightarrow \text{ON}$

$V_g = V+ \Rightarrow \text{OFF}$


CW

$Q1 \ \& \ Q4 \ \text{on} \quad Q2 \ \& \ Q3 \ \text{off}$

CCW

$Q2 \ \& \ Q3 \ \text{on} \quad Q1 \ \& \ Q4 \ \text{off}$

H Bridge Logic Control

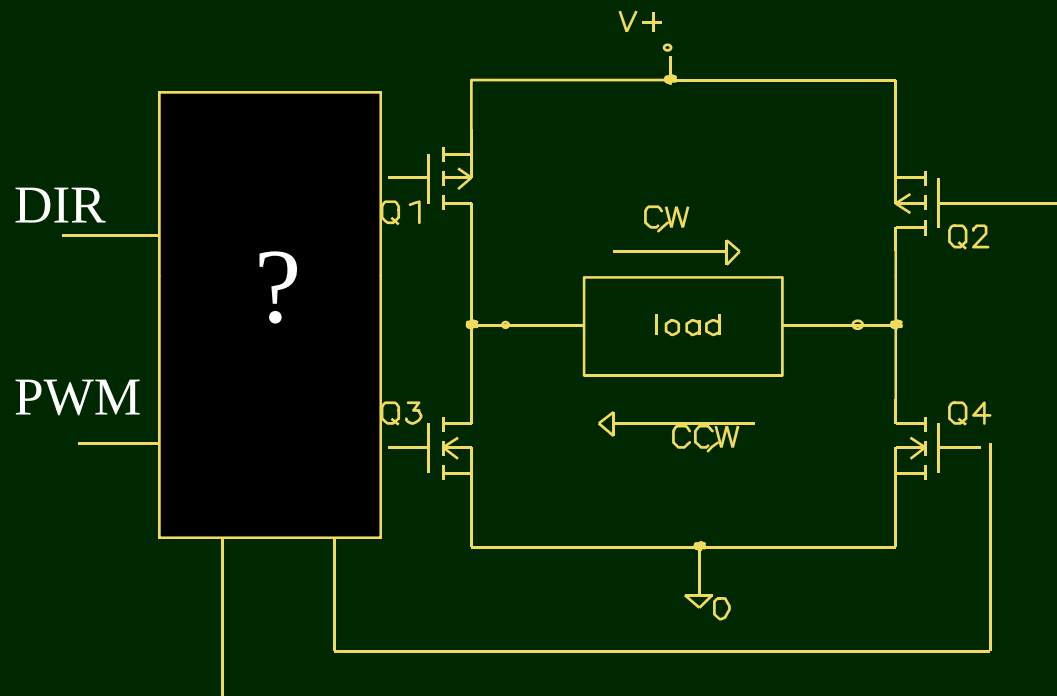

◆ DIR


- sets direction
- 0 => CW
- 1 => CCW

◆ PWM

- sets speed



H Bridge Logic Control

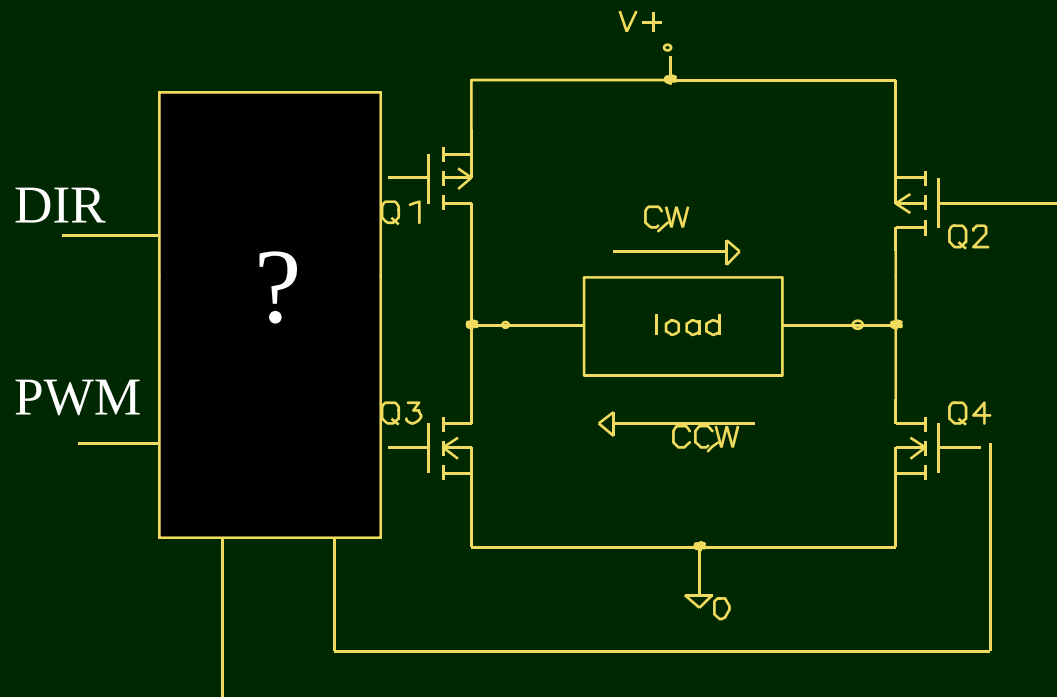

◆ DIR

- sets direction
- 0 => CW
- 1 => CCW

◆ PWM

- sets speed




D I R	c w / c c w	Q 1	Q 2	Q 3	Q 4
0					
1					



Add decoupling caps –
position *critical*

Connect to supply common

N Channel High Side Switches

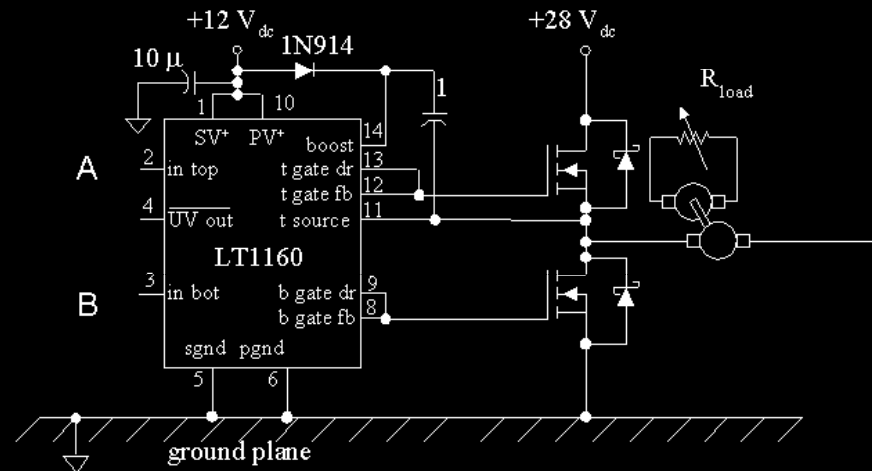


Add decoupling caps – position *critical*



One leg in one driver =>
Dead time control

Ground planes connected

Connect to supply common

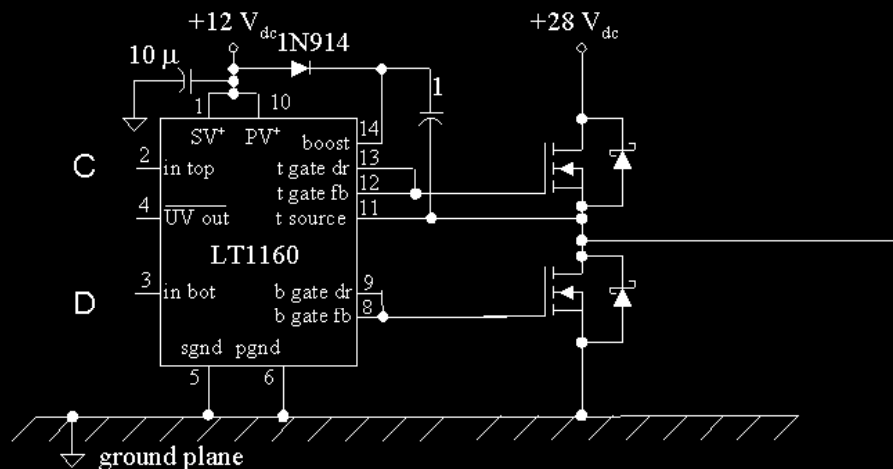

N Channel High Side Switches

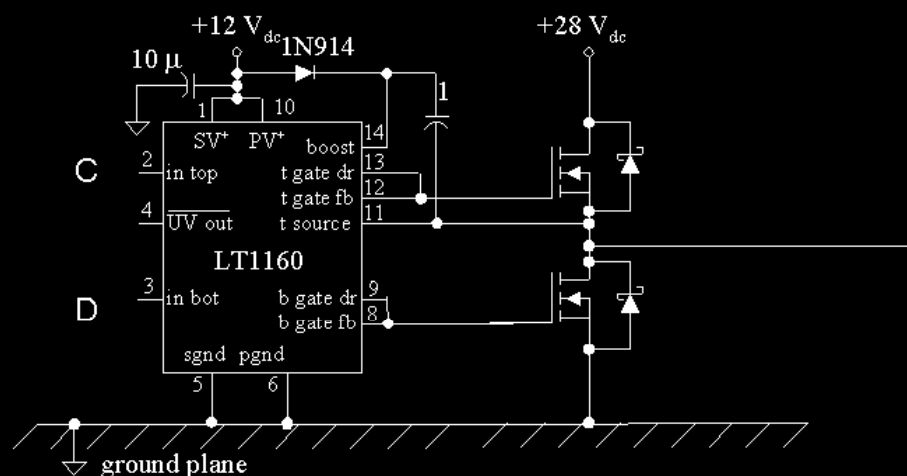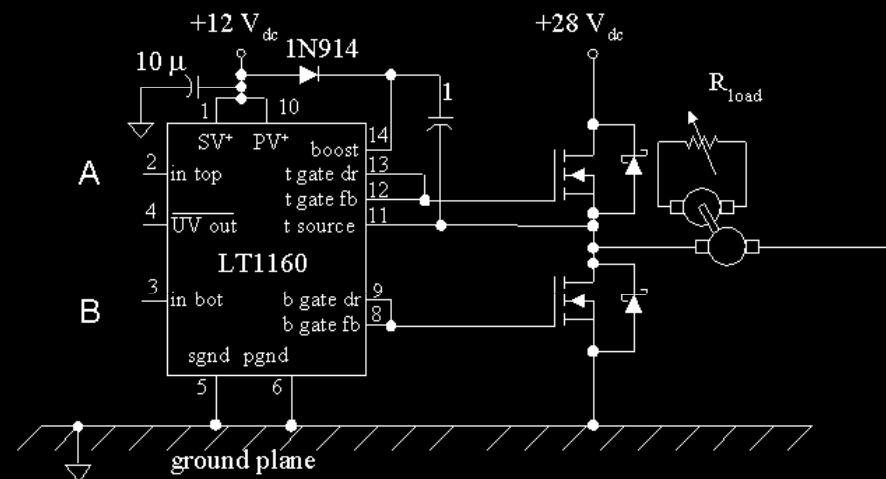


Dir	pwm	Q1	Q2	Q3	Q4
0	0				
0	1				
1	0				
1	1				

H Bridge IC

STMicroelectronics

L6225N

BLOCK DIAGRAM

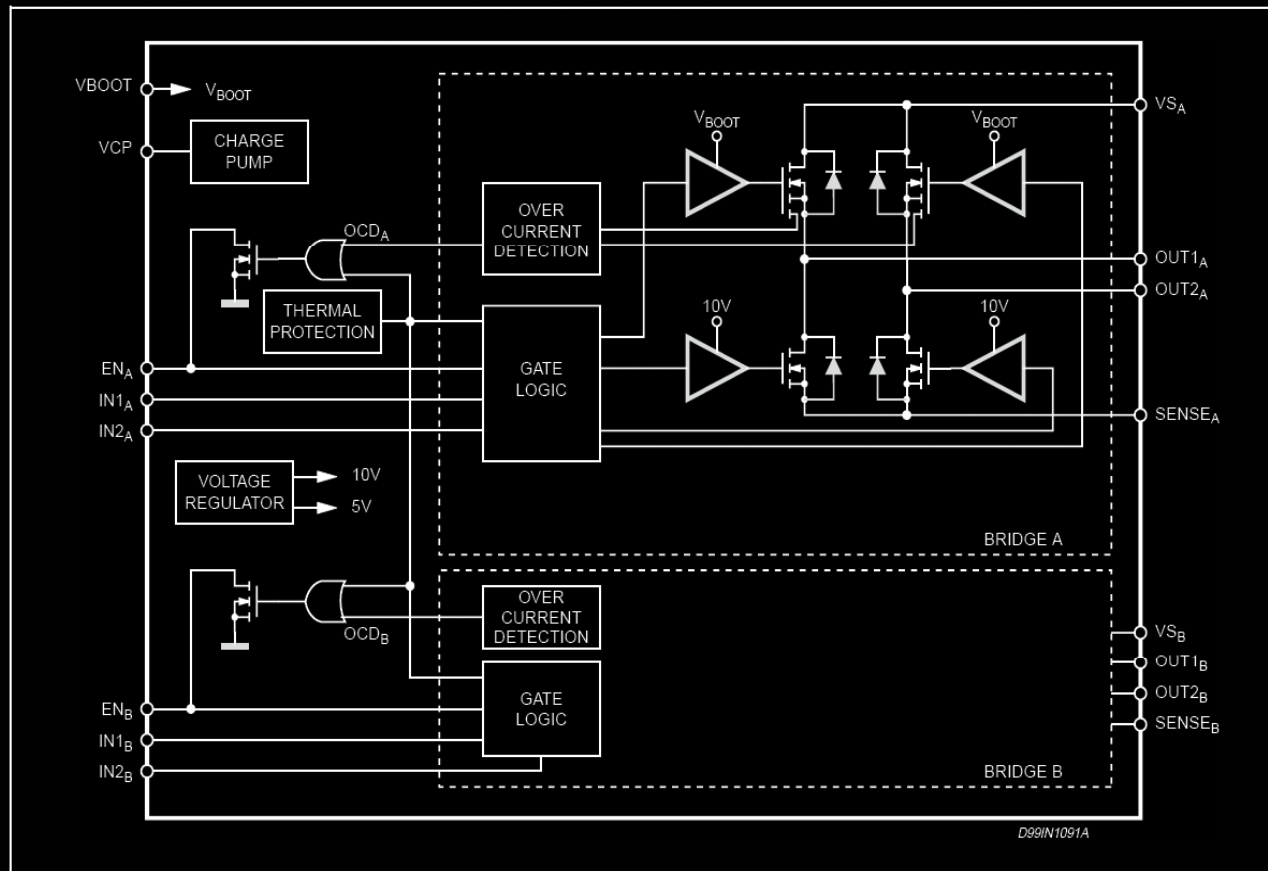

Load 8 V to 52 V

$$I_{load} \leq 1.4 A_{rms}$$

$$f < 100 \text{ kHz}$$

T_J & I_{load} shutdown

Dual

Power Calc

- $T_J < 125 \text{ C}$
- $\Theta_{JA \text{ bare}} = 57 \text{ C/W}$
- $R_{on} < 0.73 \Omega$

TRUTH TABLE

INPUTS			OUTPUTS	
EN	IN1	IN2	OUT1	OUT2
L	X	X	High Z	High Z
H	L	L	GND	GND
H	H	L	Vs	GND
H	L	H	GND	Vs
H	H	H	Vs	Vs

X = Don't care

High Z = High Impedance Output

<http://www.st.com/stonline/products/literature/ds/9451/l6225.pdf>

Purdue University

ECET 257

Power & RF Electronics