
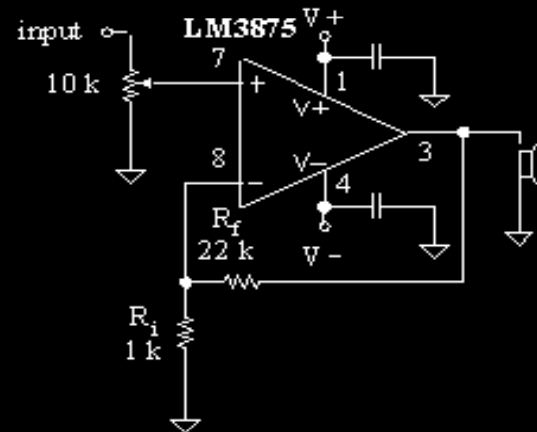
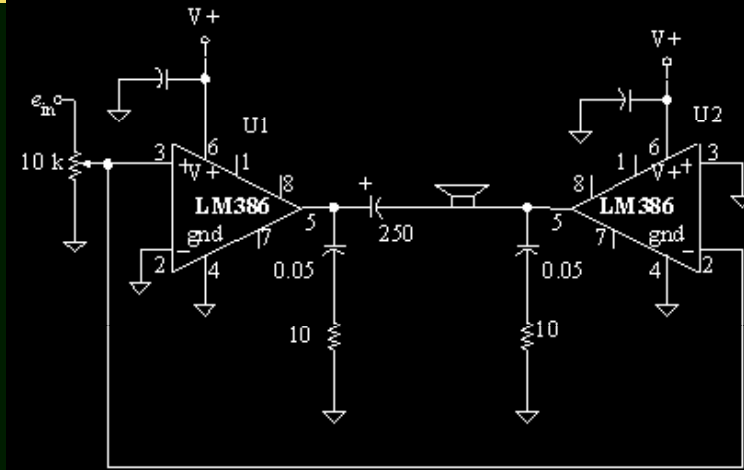


Audio ICs

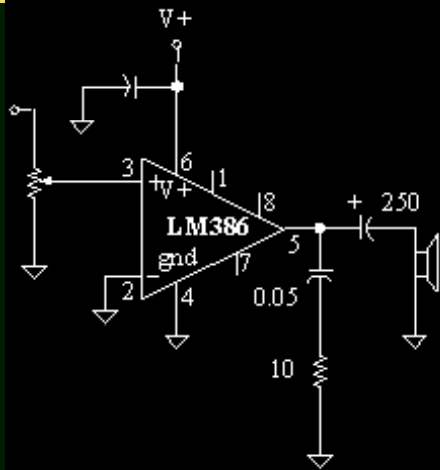


Power Electronics: Principles & Applications – Figure 4-19 - 22

Overview

- ◆ Low Power IC (1 W) LM386
 - Schematic
 - Characteristics
 - Calculations
- ◆ High Power IC (50W) LM3875
 - Schematic
 - Characteristics
 - Calculations

LM386 - characteristics

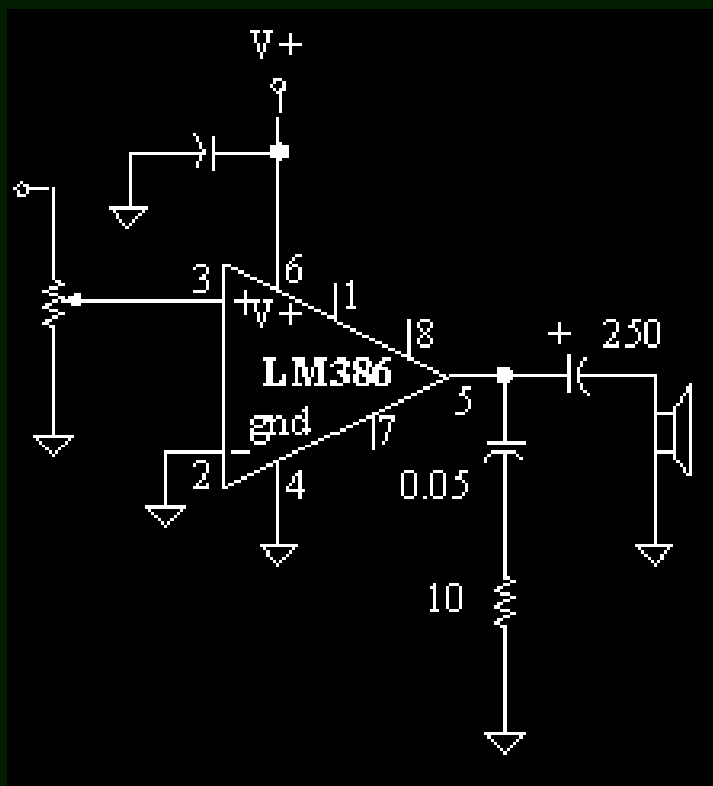

◆ Single supply:


- +4 V to +18 V
- Output automatically adjusted to $\frac{1}{2} V_+$
- No RC *input* coupling needed
- RC *output* coupling required

$$f_{-3\text{dB}} = 1/(2\pi R_{\text{load}} C_{\text{out}})$$

Power Electronics: Principles & Applications – Figure 4-19

LM386 - characteristics

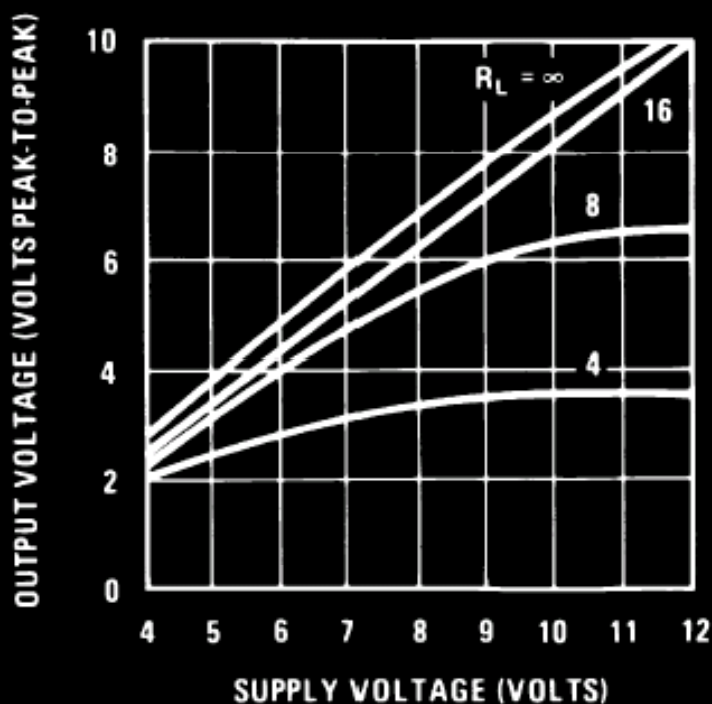Peak-to-Peak Output Voltage Swing vs Supply Voltage



<http://cache.national.com/ds/LM/LM386.pdf>

◆ Rails (8 Ω load):


$$- V_+ = 4V \Rightarrow V_{\text{sat}} = \pm 1V$$

$$- V_+ = 12V \Rightarrow V_{\text{sat}} = \pm 2.5V$$

LM386 - characteristics

◆ - feedback is *internal*:

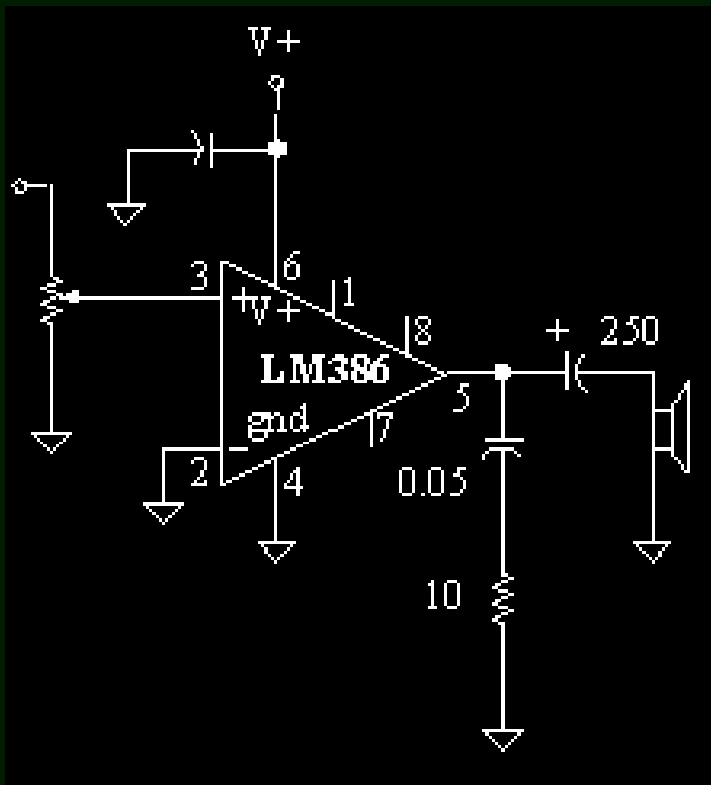
- $A_v \approx \pm 20$
- NI: drive pin 3, ground pin 2
- INV: drive pin 2, ground pin 3
- Leave *neither* open
- $R_{in} = 50 \text{ k}\Omega$
- $R_{input} < 10 \text{ k}\Omega$: drive straight from signal generator



Power Electronics: Principles & Applications – Figure 4-19

$$- e_{in} < \frac{V_p}{2} : V_+ = 12 V_{dc}$$

LM386 – max out calculations

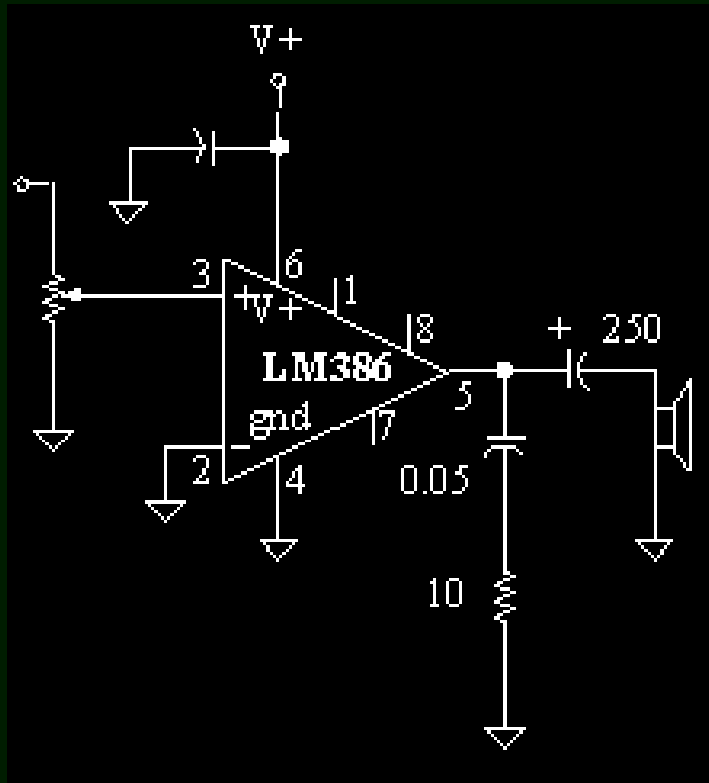

◆ $V_+ = 12\text{ V}$, $R_{\text{load}} = 8\ \Omega$, $98\text{ dB}_{\text{spl@ } 1\text{W@ } 1\text{ m}}$

◆ $V_{\text{out dc}} = \underline{\hspace{2cm}}$

◆ $V_{\text{out p max}} = \underline{\hspace{2cm}}$

◆ $V_{\text{load p max}} = \underline{\hspace{2cm}}$

◆ $P_{\text{load max}} = \underline{\hspace{2cm}}$


◆ $dBW_{\text{max}} = \underline{\hspace{2cm}}$

◆ $dB_{\text{spl @ } 1\text{ m}} = \underline{\hspace{2cm}}$

◆ $dB_{\text{spl @ } 3\text{ m}} = \underline{\hspace{2cm}}$

Power Electronics: Principles & Applications – Figure 4-19


LM386 – max out calculations

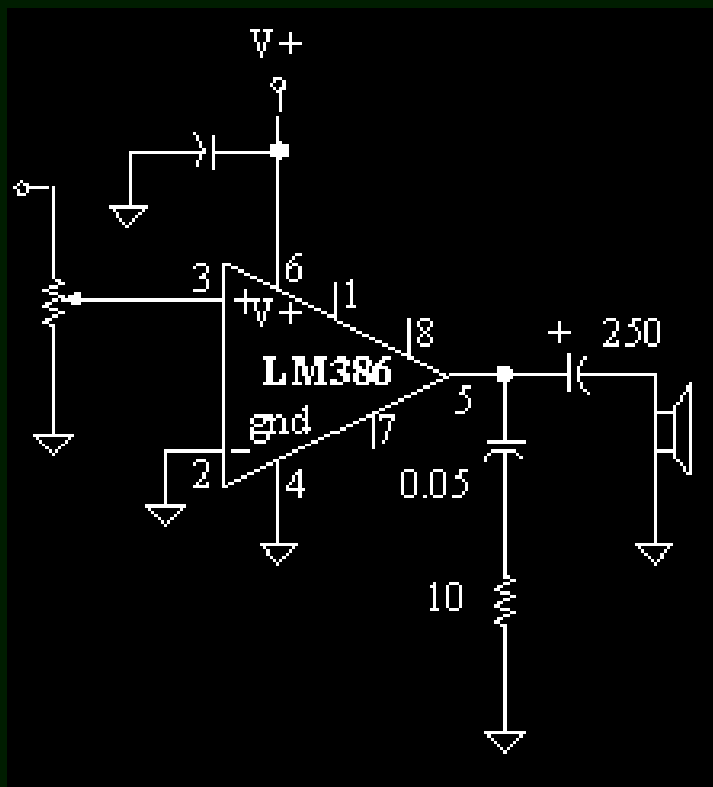

- ◆ $V_+ = 12\text{ V}$, $R_{\text{load}} = 8\ \Omega$, $98\text{ dB}_{\text{spl}} @ 1\text{W} @ 1\text{ m}$
- ◆ $V_{\text{out dc}} = 6 V_{\text{dc}}$
- ◆ $V_{\text{out p max}} = 9.25 V_{\text{p max}}$
- ◆ $V_{\text{load p max}} = 3.5 V_{\text{p}}$
- ◆ $P_{\text{load max}} = 660\text{ mW}$
- ◆ $\text{dBW}_{\text{max}} = -1.8\text{ dBW}$
- ◆ $\text{dB}_{\text{spl}} @ 1\text{ m} = 96.2\text{ dB}_{\text{spl}}$
- ◆ $\text{dB}_{\text{spl}} @ 3\text{ m} = 86.7\text{ dB}_{\text{spl}}$

Power Electronics: Principles & Applications – Figure 4-19

LM386 – bridged amp

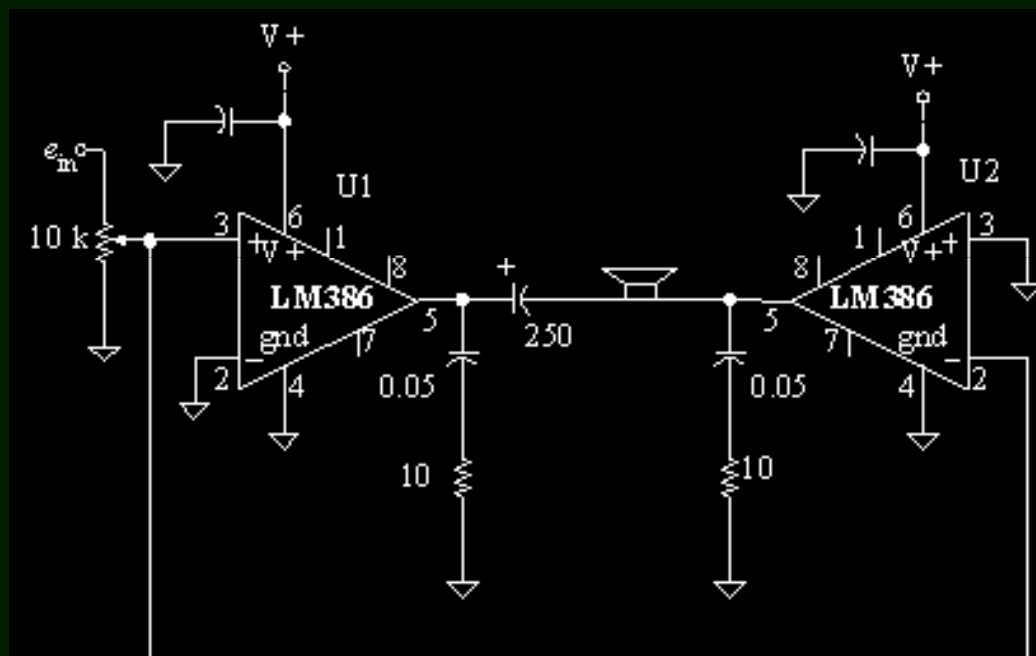

Power Electronics: Principles & Applications – Figure 4-21

- ◆ $V_{\text{load}} \uparrow \times 2$
- ◆ $P_{\text{load}} = (V_{\text{load rms}})^2 / R_{\text{load}}$
- ◆ $P_{\text{load}} \uparrow \times \underline{\hspace{2cm}}$
- ◆ *Beware!*
 $I_{\text{out p max}} \sim 400 \text{ mA}_p$
 may be the limiting factor.

Overview


◆ Low Power IC (1 W) LM386

- Schematic
- Characteristics
- Calculations


➔ High Power IC (50W) LM3875

- Schematic
- Characteristics
- Calculations

LM3875 - characteristics

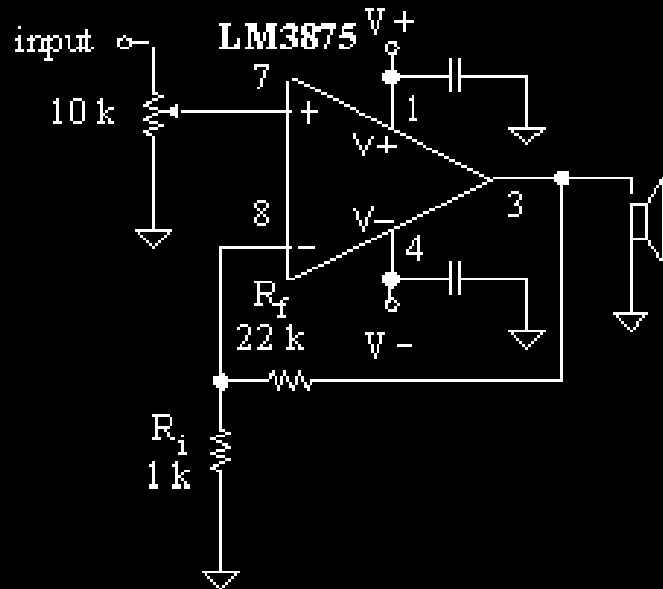

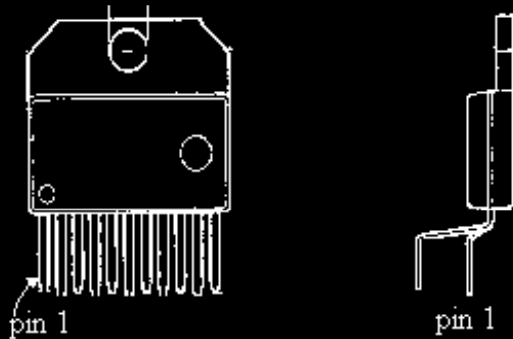
Power Electronics: Principles & Applications – Figure 4-22



Power Electronics: Principles & Applications – Figure 4-23

- ◆ $P_{\text{load}} \leq 56 \text{ W}$ into 8Ω
- ◆ $T_{\text{J max}}$ internally limited $165 \text{ }^\circ\text{C}$
- ◆ $\Theta_{\text{JC}} = 1 \text{ }^\circ\text{C/W}$
- ◆ $I_{\text{p max}} \leq 4 \text{ A}_\text{p}$
- ◆ V^+ to V^- : 20 V to 84 V
- ◆ $V_{\text{sat}} : \pm 5 \text{ V}$
- ◆ Use it like an op amp
 - R_f and R_i
 - GBW and slew rate concerns
- ◆ Layout is a *big deal*


LM3875 – design - @ max output

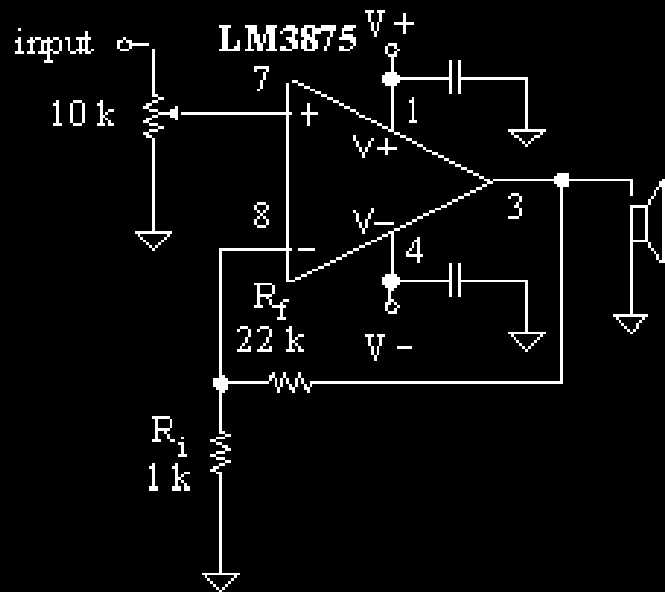

- ◆ $P_{\text{load}} \leq 30 \text{ W}$ into 8Ω , $e_{\text{in}} = 300 \text{ mV}_{\text{rms}}$
- ◆ $E_{\text{supply}} = \underline{\hspace{2cm}}$
- ◆ $I_{\text{supply max}} = \underline{\hspace{2cm}}$
- ◆ $A_o = \underline{\hspace{2cm}}$
- ◆ $R_f = \underline{\hspace{2cm}}$
- ◆ $\text{GBW} = \underline{\hspace{2cm}}$ ok ?
- ◆ $\text{Slew rate} = \underline{\hspace{2cm}}$ ok ?

Power Electronics: Principles & Applications – Figure 4-22


LM3875 – design - @ max output

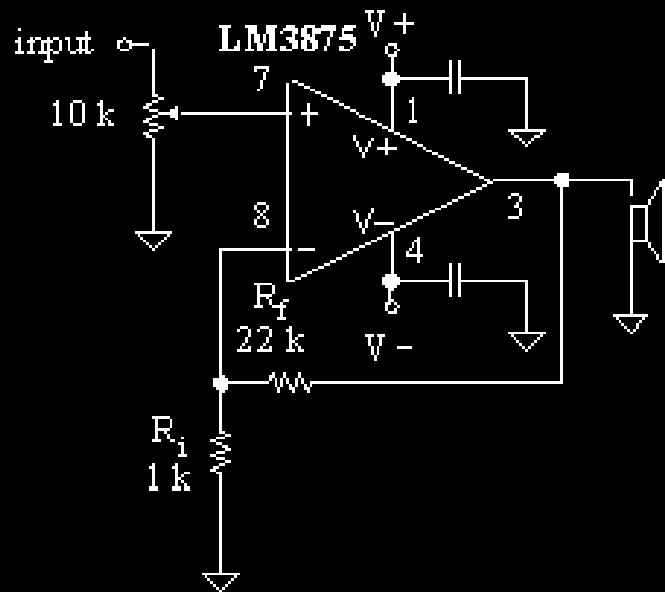

- ◆ $P_{\text{load}} \leq 30 \text{ W}$ into 8Ω , $e_{\text{in}} = 300 \text{ mV}_{\text{rms}}$
- ◆ $E_{\text{supply}} = \pm 28 \text{ V}_{\text{dc}}$
- ◆ $I_{\text{supply max}} = 2.75 \text{ A}$
- ◆ $A_o = 51.7$
- ◆ $R_f = 50.7 \text{ k}\Omega$
- ◆ $\text{GBW} = 1.03 \text{ MHz}$
- ◆ $\text{Slew rate} = 2.76 \text{ V}/\mu\text{s}$


Power Electronics: Principles & Applications – Figure 4-22

LM3875 – design - @ IC worst case

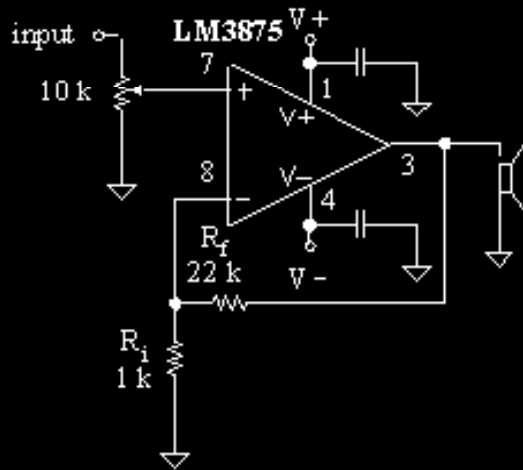

Power Electronics: Principles & Applications – Figure 4-22

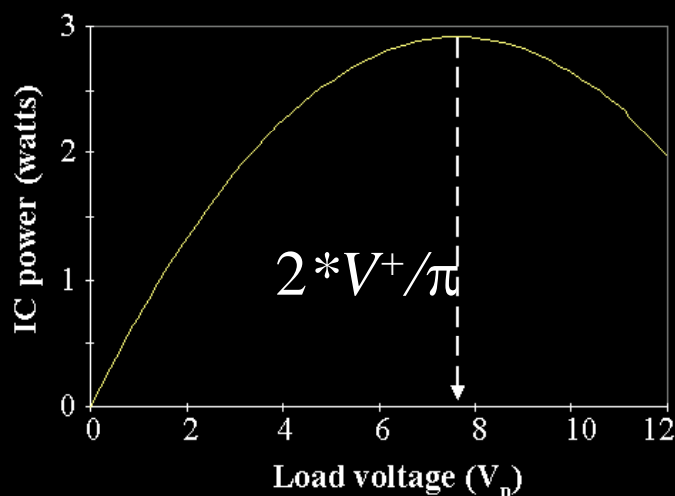- ◆ $P_{\text{load}} \leq 30 \text{ W}$ into 8Ω , $e_{\text{in}} = 300 \text{ mV}_{\text{rms}}$
- ◆ $V_{\text{load p w.c.}} = 17.8 \text{ V}_p$
- ◆ $I_{\text{load p w.c.}} = 2.2 \text{ A}_p$
- ◆ $P_{\text{supply w.c.}} = 39.2 \text{ W}$
- ◆ $P_{\text{load w.c.}} = 19.8 \text{ W}$
- ◆ $P_{\text{IC w.c.}} = 19.5 \text{ W}$
- ◆ $\Theta_{\text{JA w.c.}} = 5.2 \text{ deg C/W}$
- ◆ Heat sink : 4 deg C/W



Power Electronics: Principles & Applications – Figure 4-12