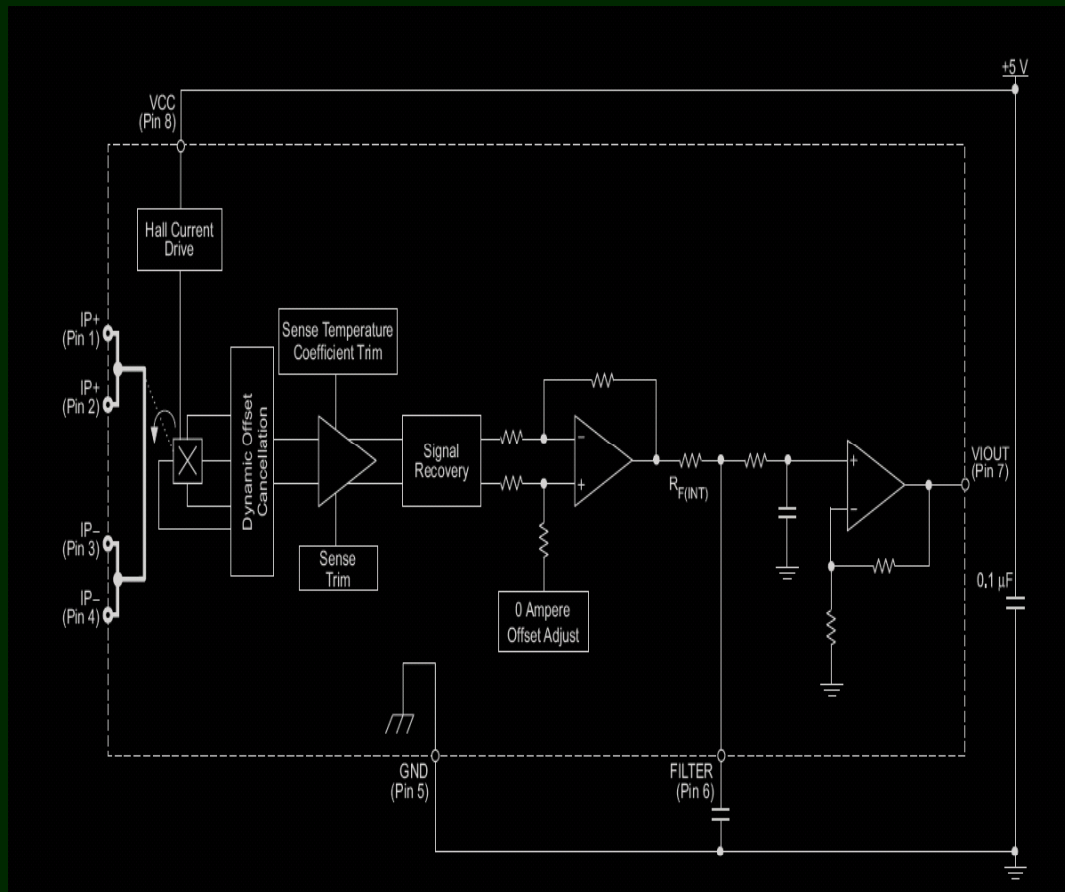


Amplifier Protection




http://www.allegromicro.com/en/Products/Part_Numbers/0712/0712.pdf

Purdue University

ECET 257

Power & RF Electronics

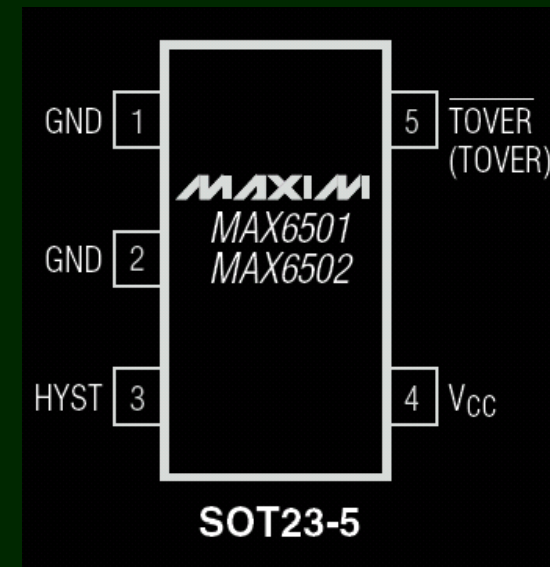

<http://datasheets.maxim-ic.com/en/ds/MAX6501-MAX6504.pdf>

Overview



Over Current Protection

- Hall Effect Sensor
- Current Limiting

◆ Temperature Sensor

- Case temperature
- IC switch

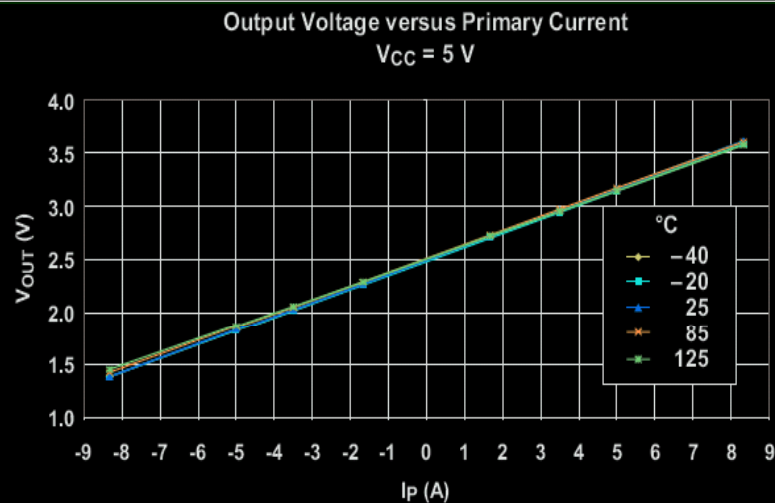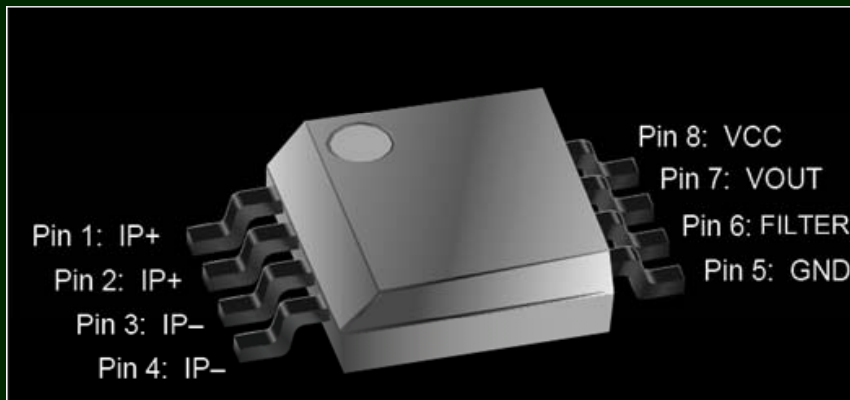
Over Current Protection – Hall Effect Sensor



http://www.allegromicro.com/en/Products/Part_Numbers/0712/0712.pdf

- ◆ ACS712ELCTR-05B-T
- ◆ $r_{IP+ \text{ to } IP-} = 0.0012\ \Omega$
- ◆ $V_{out @ IP = 0} = 2.5\text{ V}$
- ◆ Sensitivity = 185 mV/A

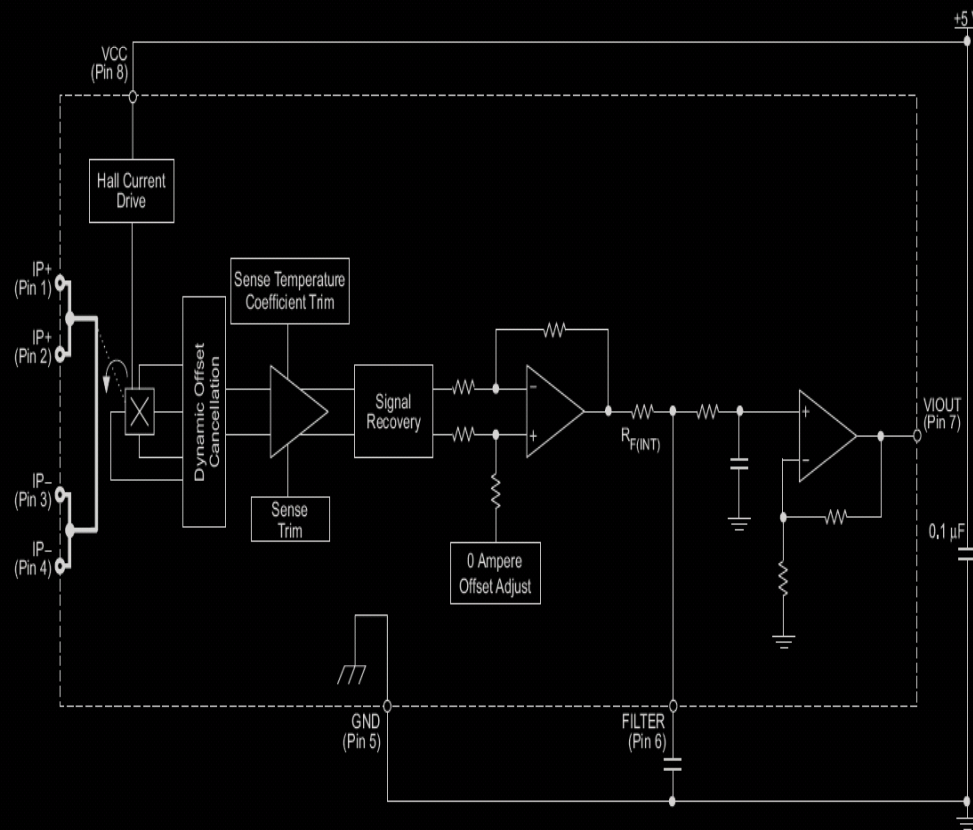Over Current Protection – Hall Effect Sensor



http://www.allegromicro.com/en/Products/Part_Numbers/0712/0712.pdf


- ◆ ACS712ELCTR-05B-T
- ◆ I_{P+} & I_{P-} isolated from V_{CC} , V_{out} , & GND
- ◆ Pins 3 & 4 = I_{out}
- ◆ Pins 1 & 2 = I_{in}
- ◆ Filter: $t_{rise} = 0.35/f_{-3dB}$

C_F (nF)	t_r (μ s)
0	6.6
1	7.7
4.7	17.4
10	32.1
22	68.2
47	88.2
100	291.3
220	623.0
470	1120.0


$$f_{-3dB} = 20 \text{ kHz}$$

$$C_f = ?$$

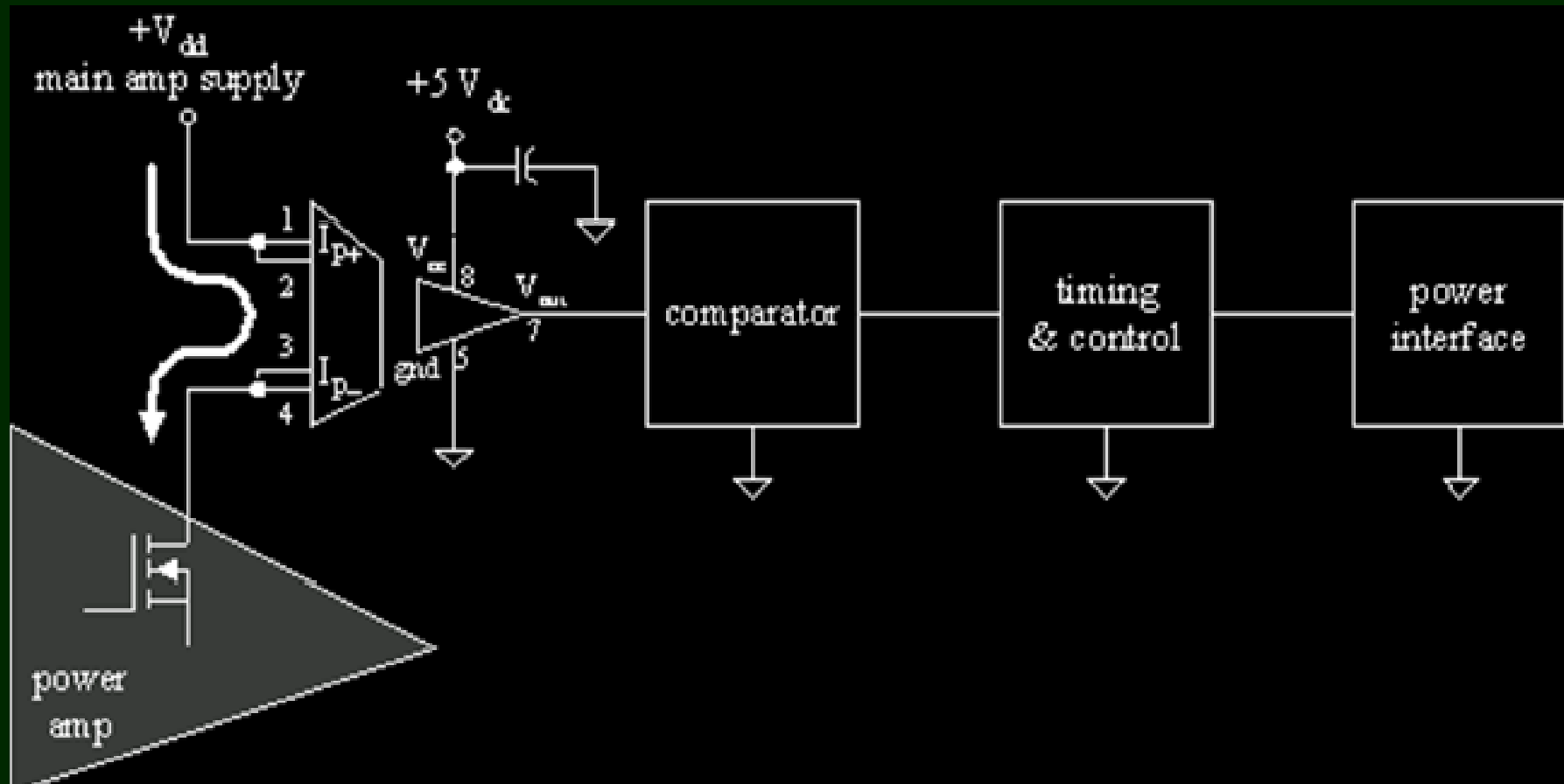
Over Current Protection – Signal Processing



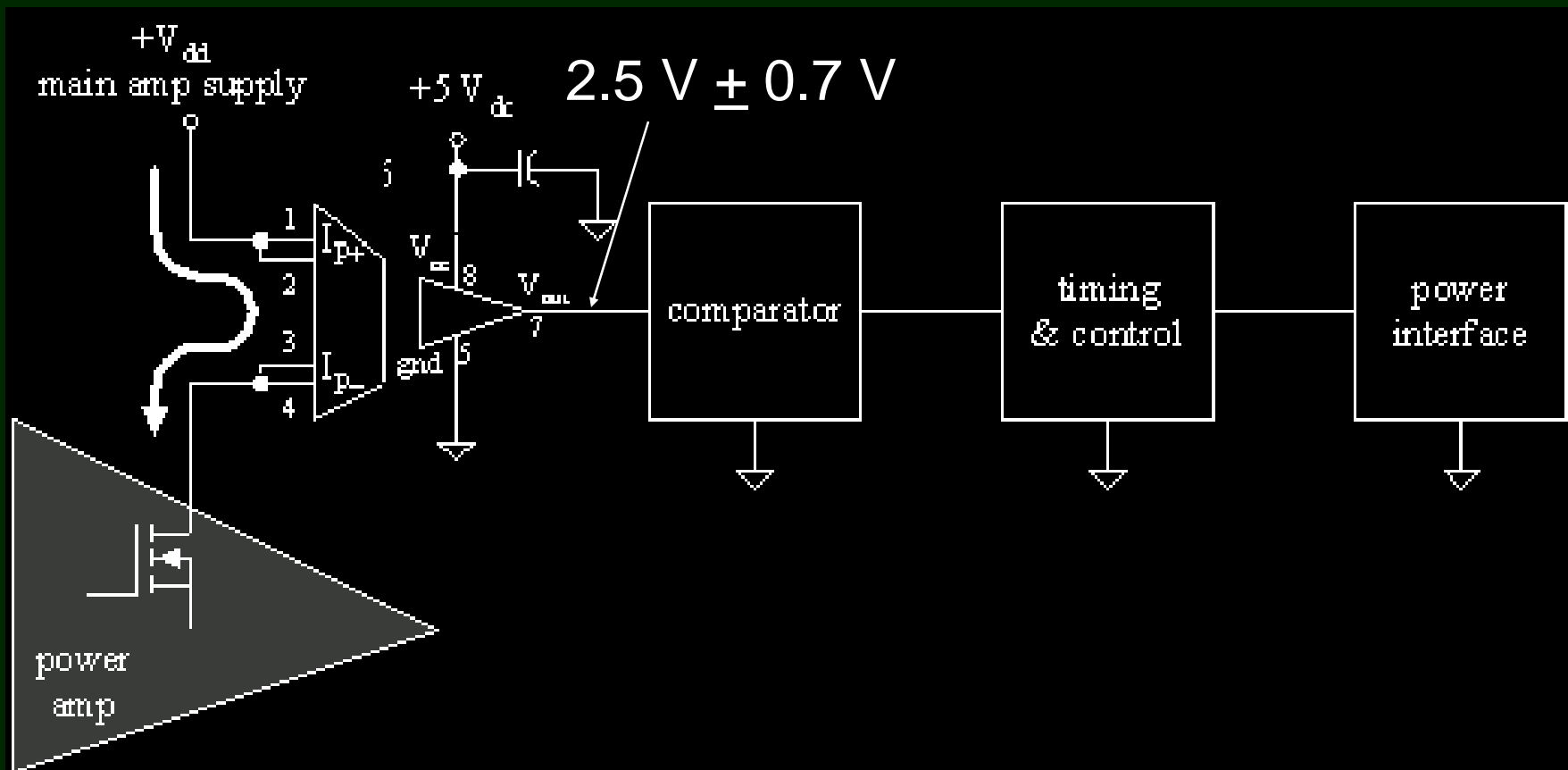
Over Current Protection – Signal Processing



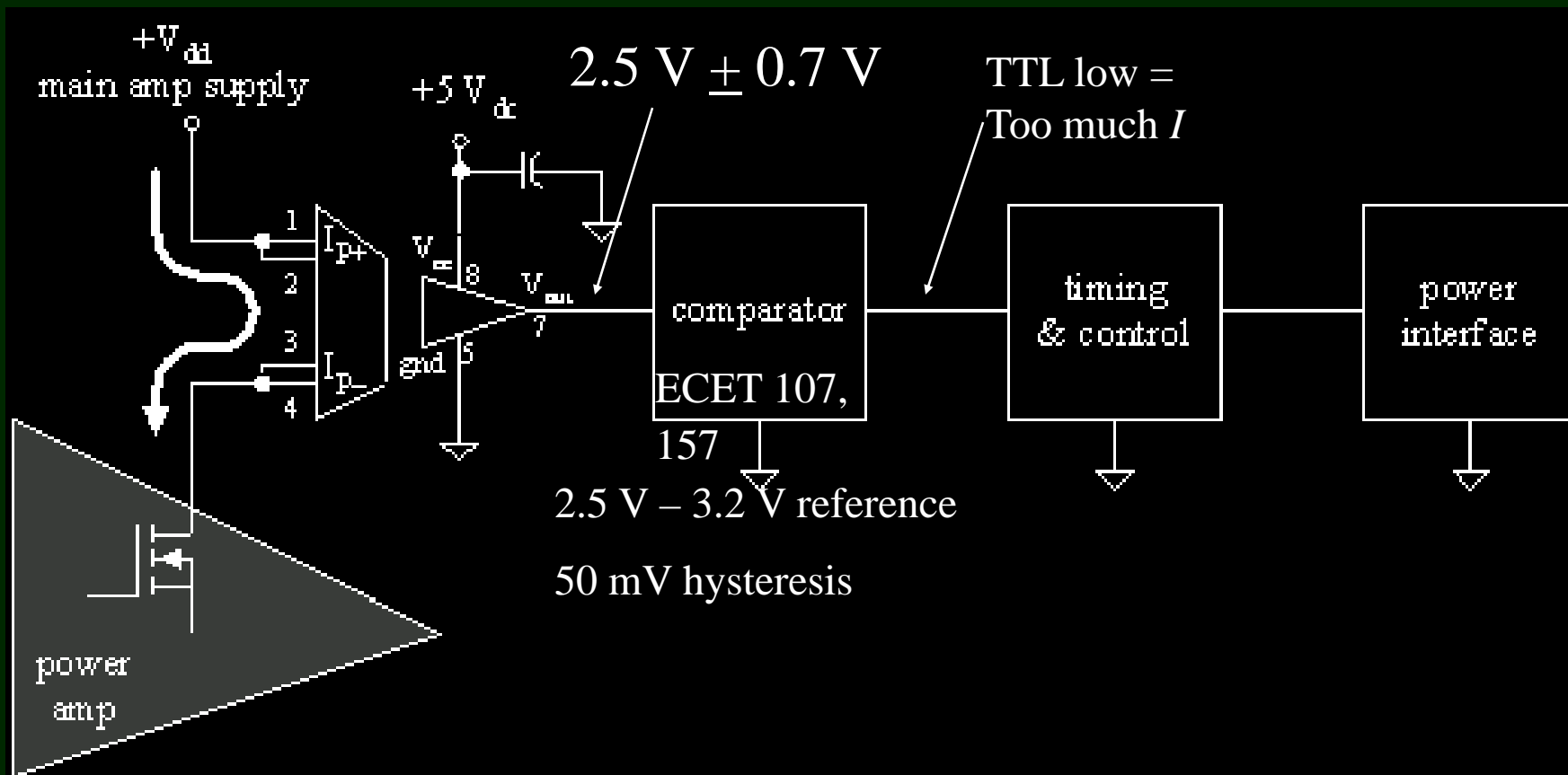
Over Current Protection – Signal Processing



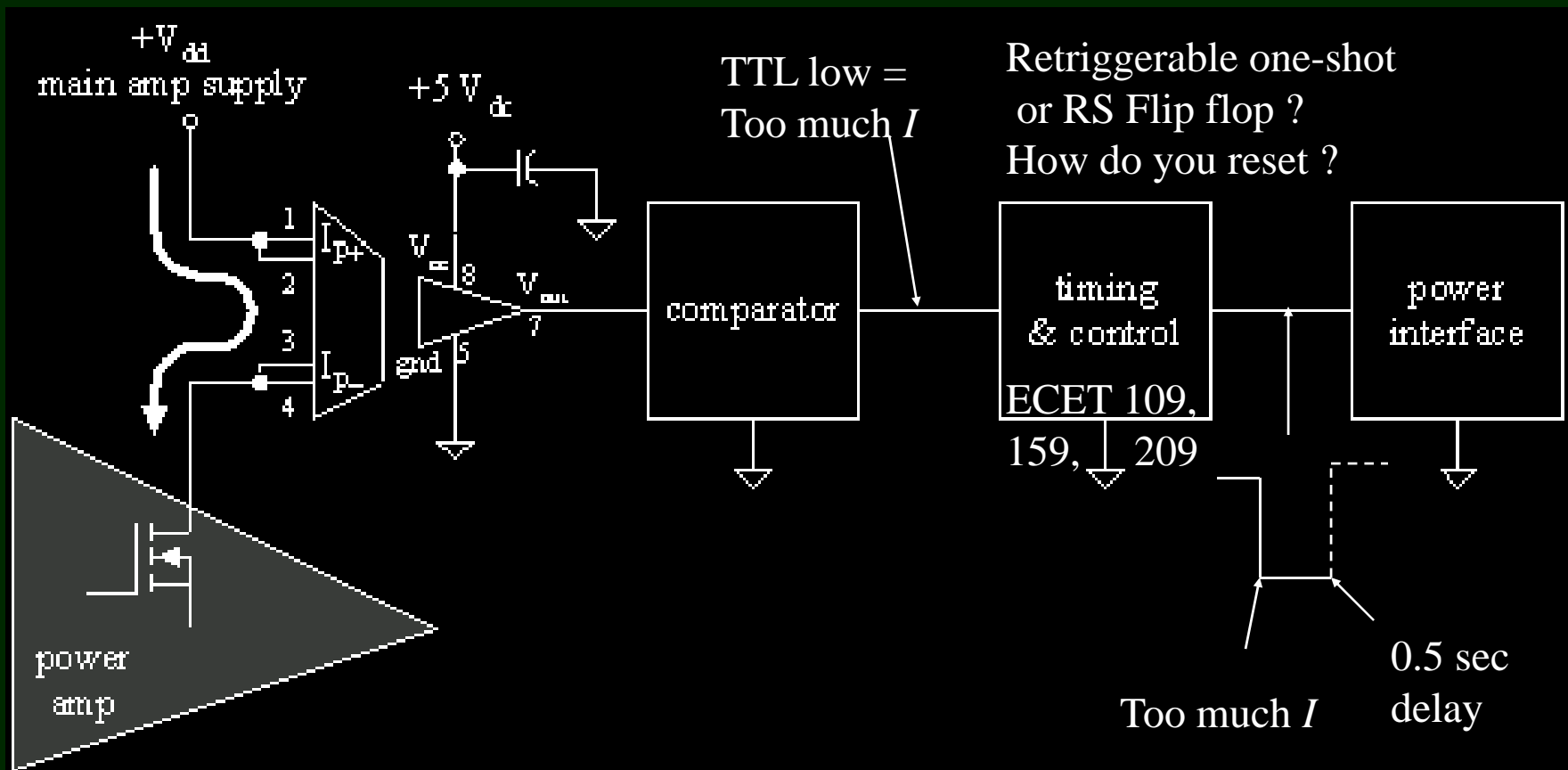
Over Current Protection – Signal Processing



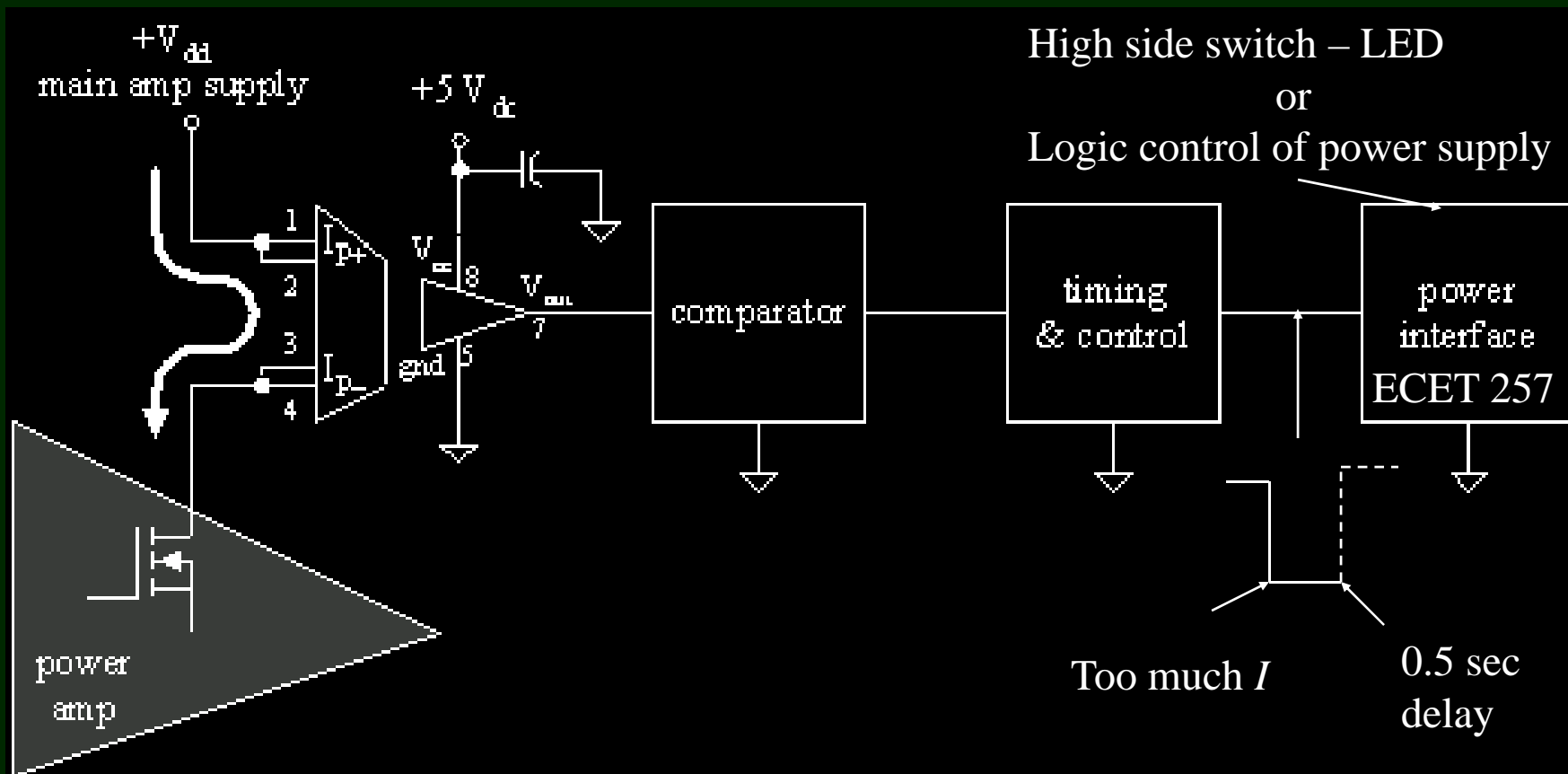
Over Current Protection – Signal Processing



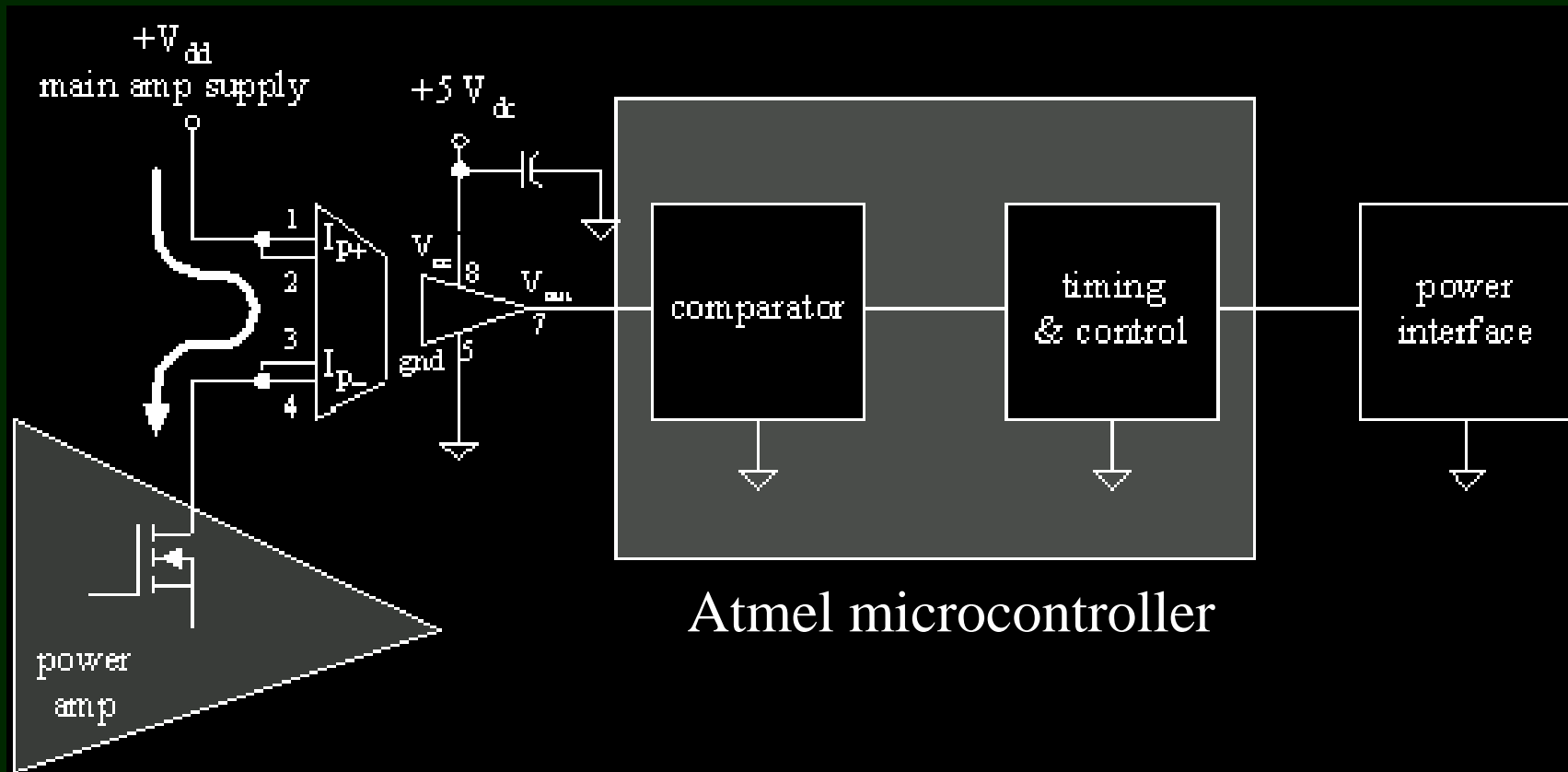Over Current Protection – Signal Processing



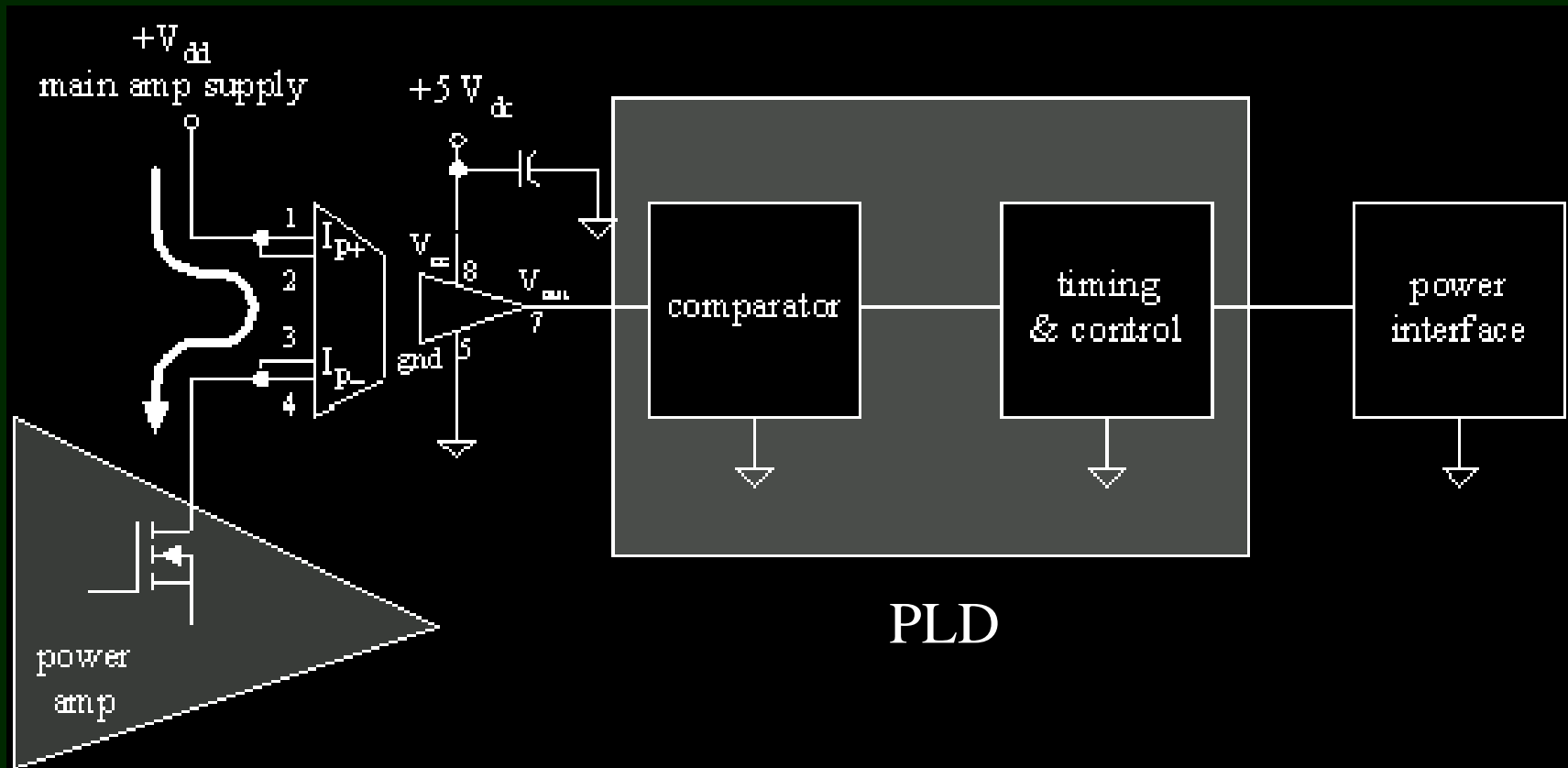
Over Current Protection – Signal Processing



Current Limiting - performance

low voltages out

=> whatever current R_{load} needs

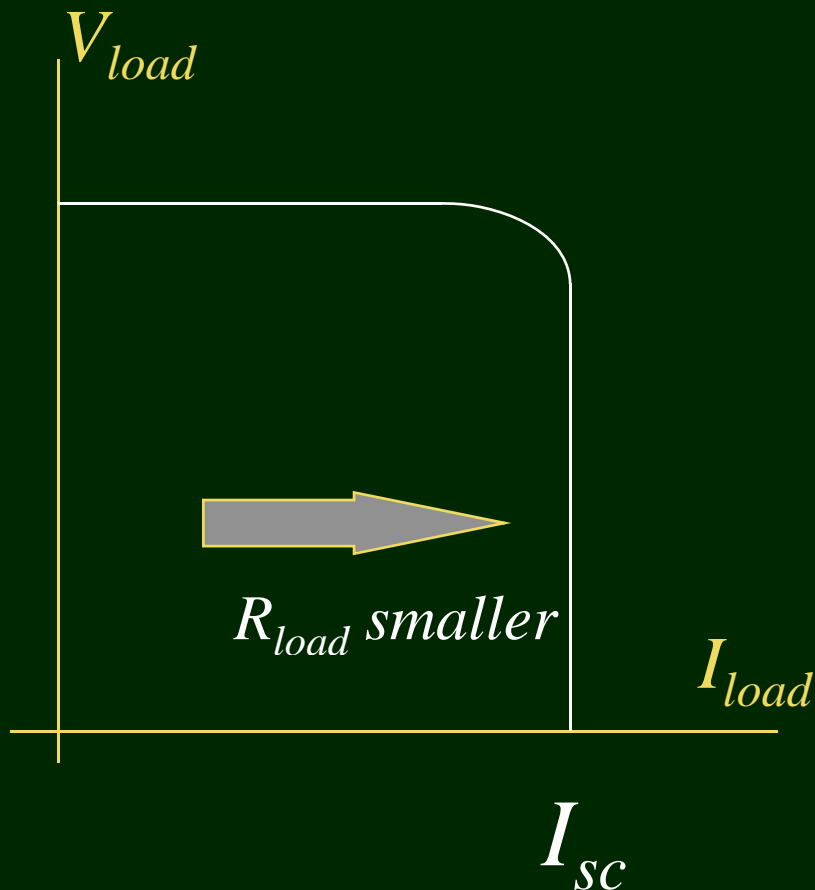


Current Limiting - performance

low voltages out

=> whatever current R_{load} needs

I demand too high

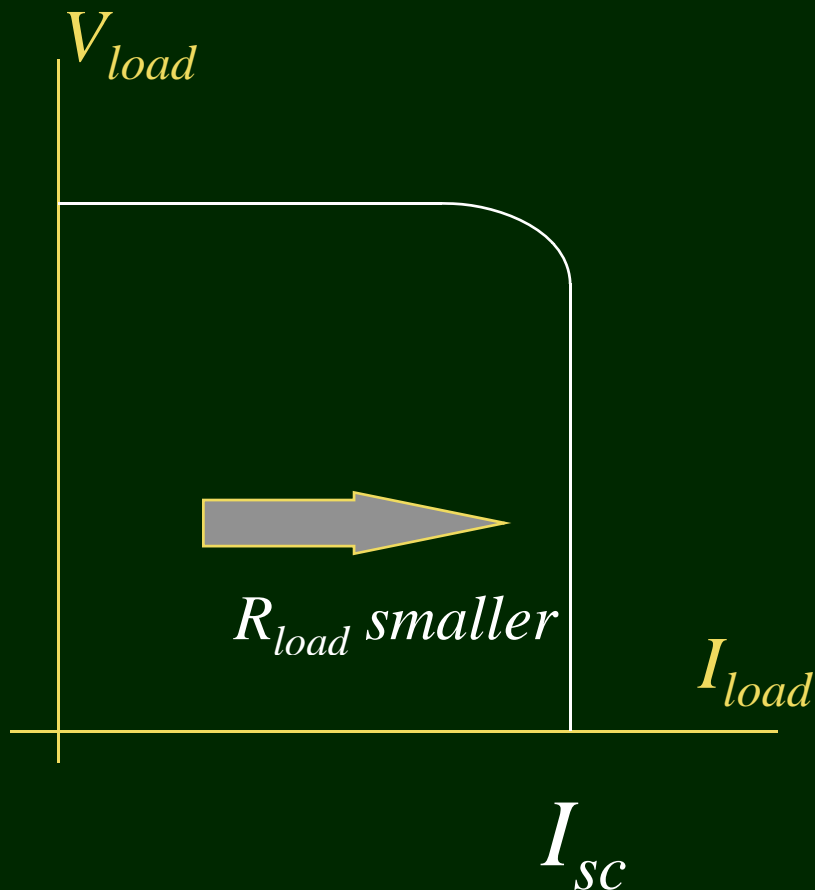


Current Limiting - performance

low voltages out

=> whatever current R_{load} needs

I demand too high

=> I_{load} limited to I_{sc}

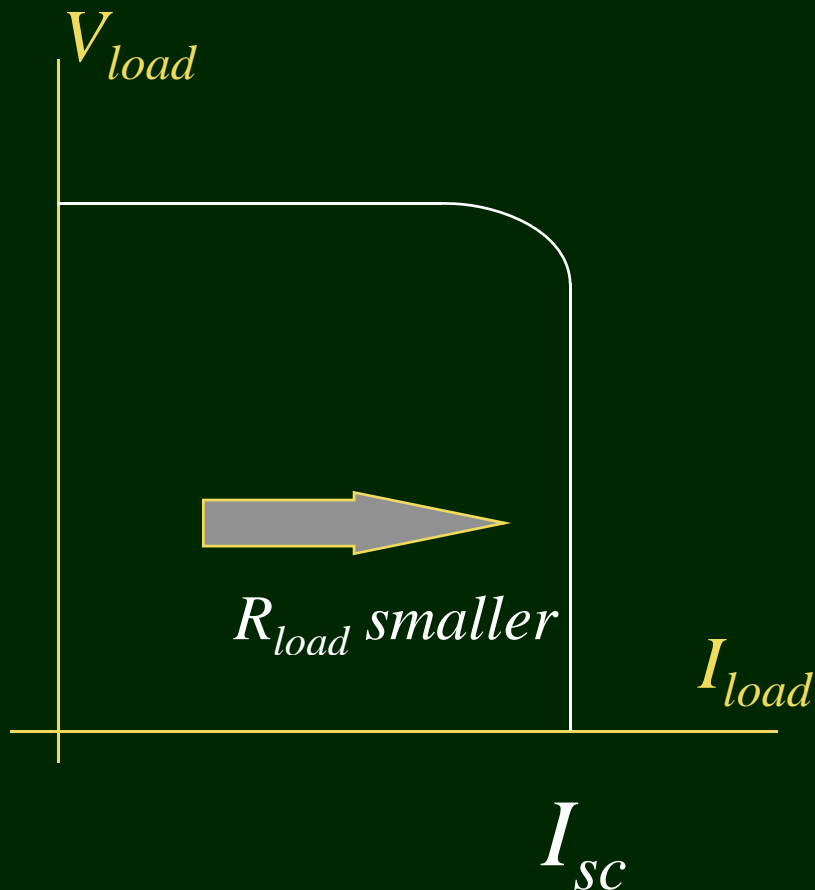

Current Limiting - performance


low voltages out

=> whatever current R_{load} needs

I demand too high

=> I_{load} limited to I_{sc}

& V_{load} dropped as set by R_{load}

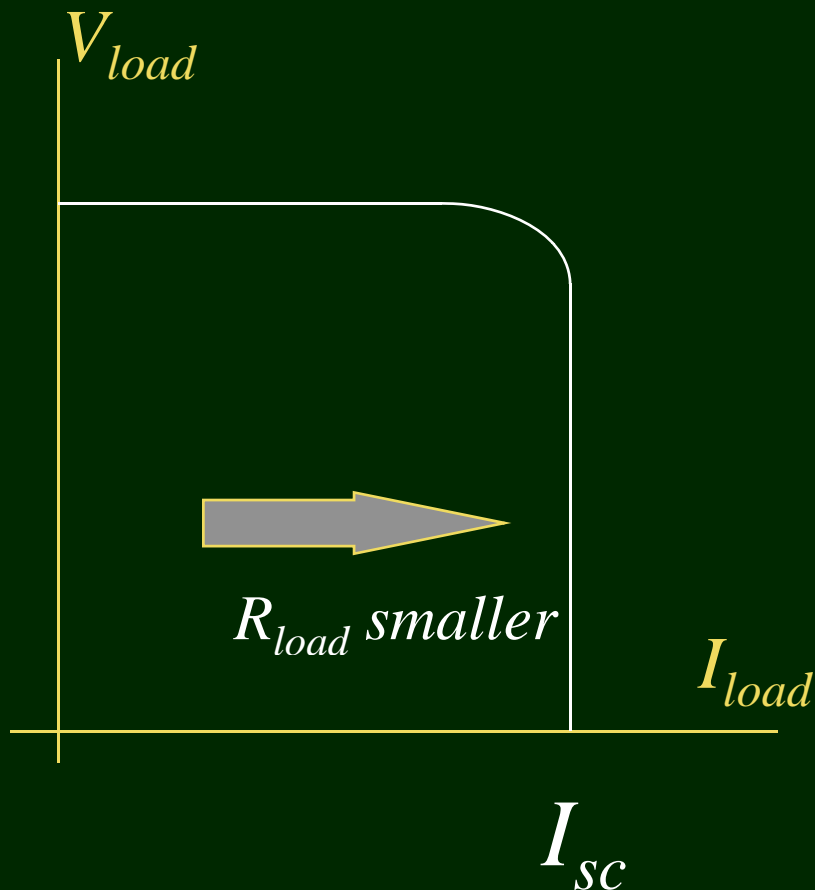

Current Limiting - performance

low voltages out


=> whatever current R_{load} needs

I demand too high


=> I_{load} limited to I_{sc}

& V_{load} dropped as set by R_{load}

$$V_{load} = I_{sc} * R_{load}$$

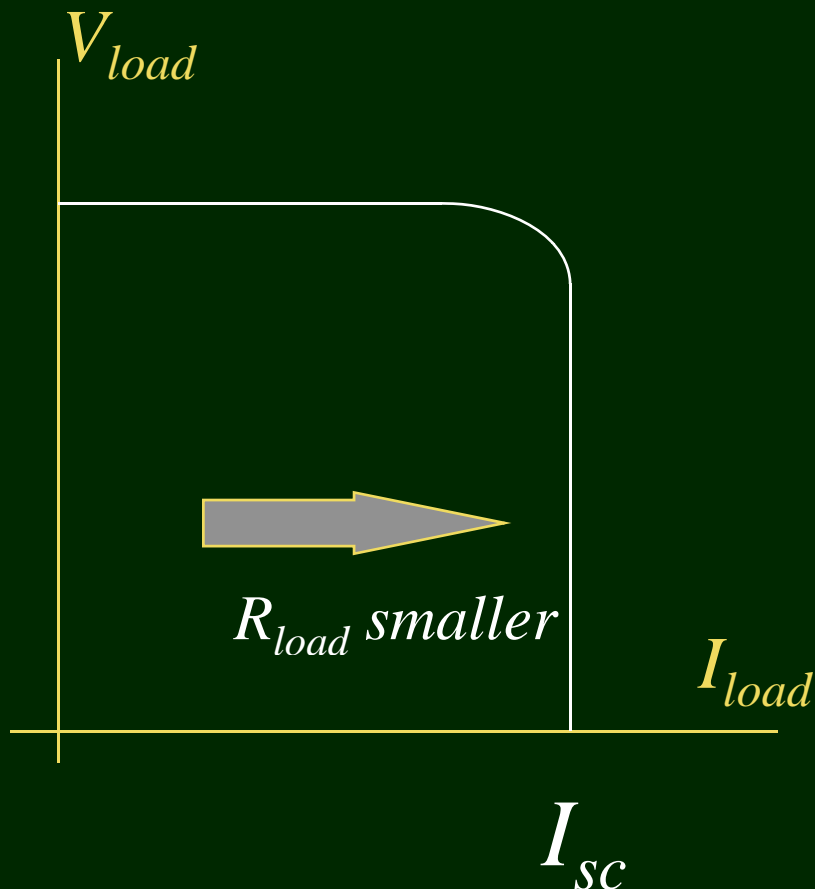

Current Limiting - performance

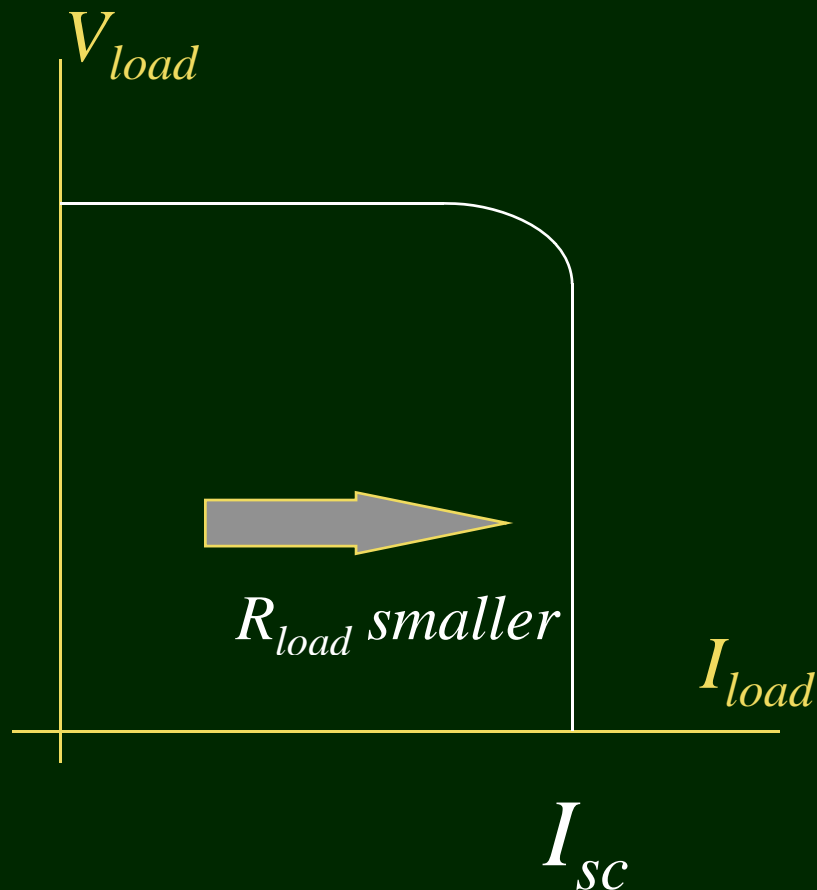

low voltages out

=> whatever current R_{load} needs

I demand too high

=> I_{load} limited to I_{sc}


& V_{load} dropped as set by R_{load}

$$V_{load} = I_{sc} * R_{load}$$

↓ constant



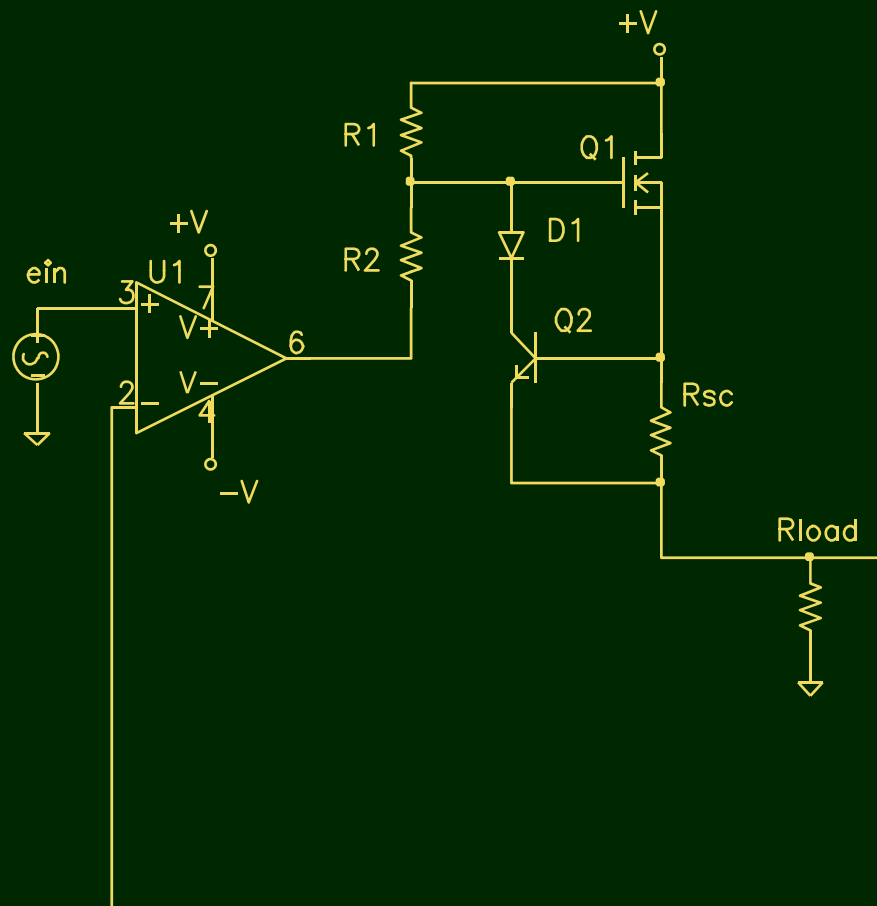Current Limiting - Positive side schematic




R_{sc} small $0.x \Omega$

normal operation

$$I_{load} < I_{sc}$$

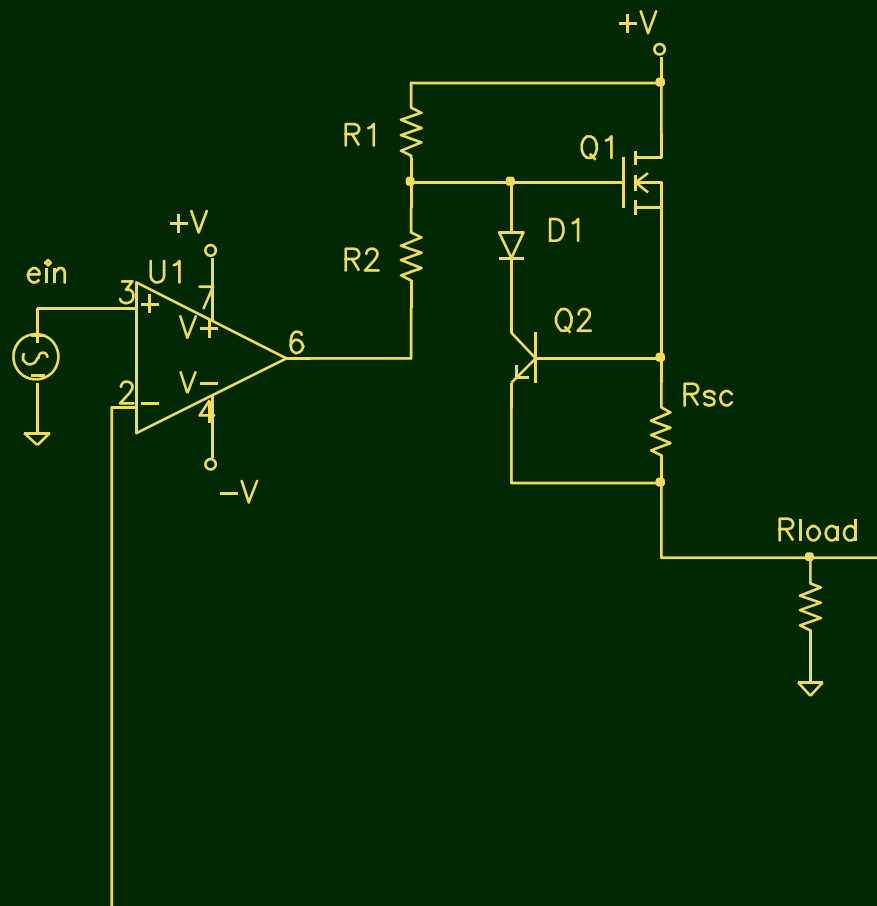Q2 off \Rightarrow no effect

Current Limiting - Positive side schematic



R_{sc} small $0.x \Omega$


normal operation

$$I_{load} < I_{sc}$$

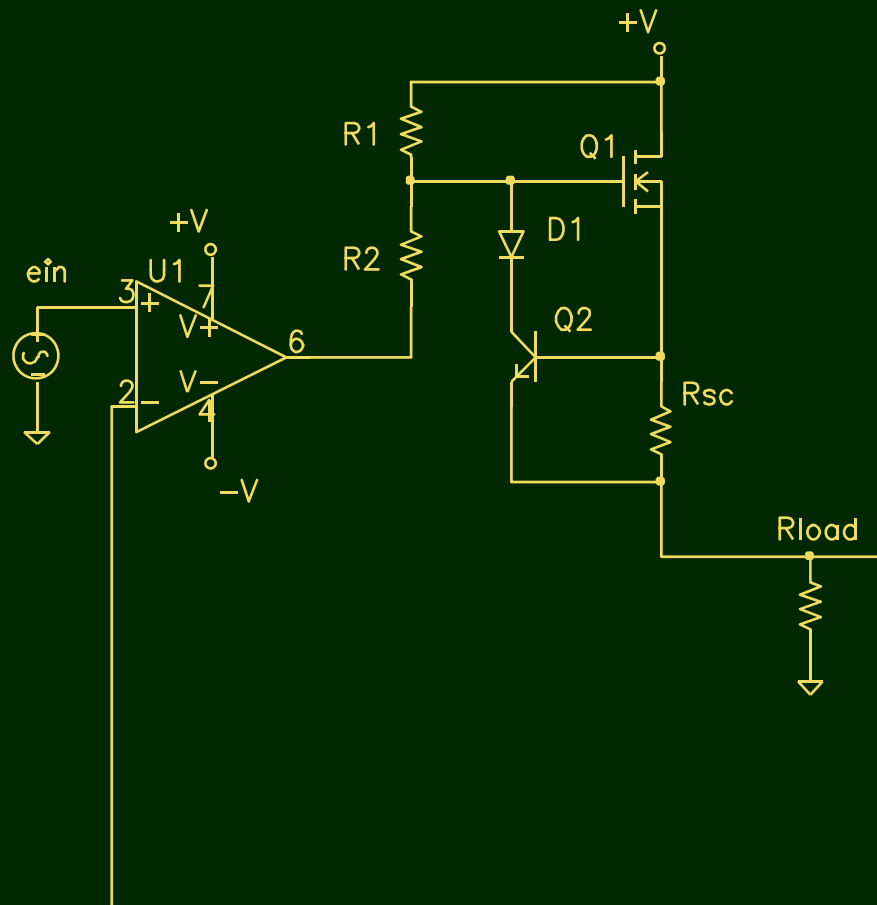Q2 off \Rightarrow no effect

$$I_{load} \uparrow \Rightarrow V_{R_{sc}} \uparrow$$

Current Limiting - Positive side schematic



R_{sc} small $0.x \Omega$

normal operation


$$I_{load} < I_{sc}$$

Q2 off \Rightarrow no effect

$$I_{load} \uparrow \Rightarrow V_{R_{sc}} \uparrow$$

$$V_{R_{sc}} = 0.7V \Rightarrow$$

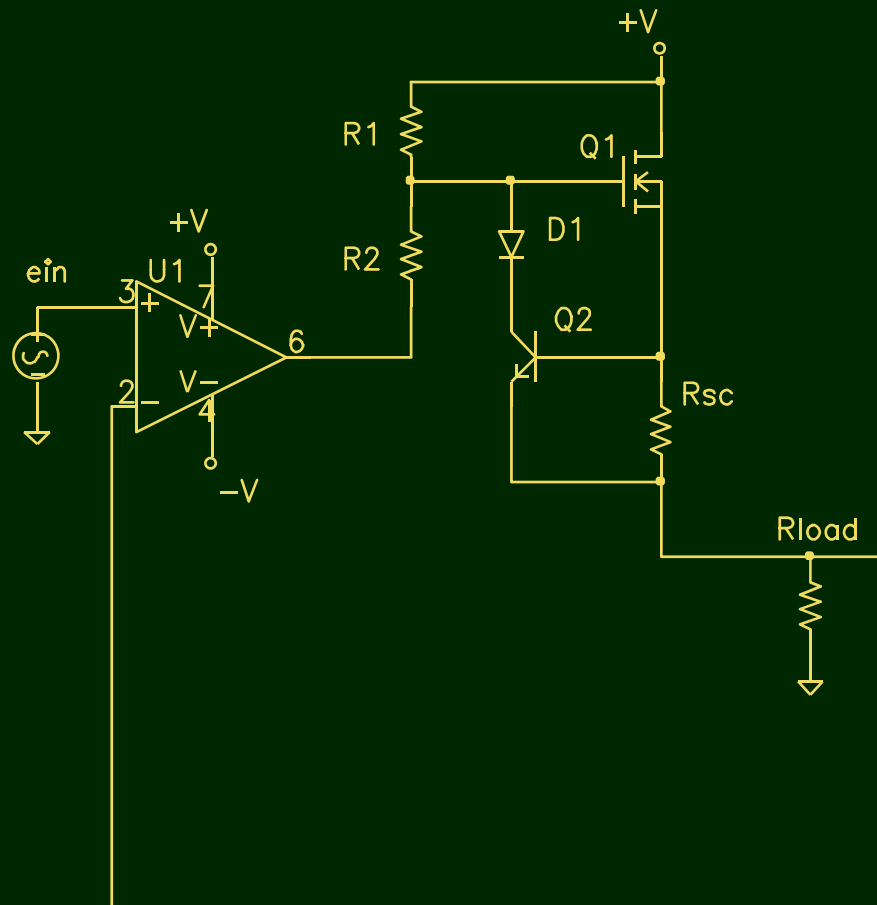Current Limiting - Positive side schematic



R_{sc} small $0.x \Omega$

normal operation

$$I_{load} < I_{sc}$$


Q2 off \Rightarrow no effect

$$I_{load} \uparrow \Rightarrow V_{R_{sc}} \uparrow$$

$$V_{R_{sc}} = 0.7V \Rightarrow$$

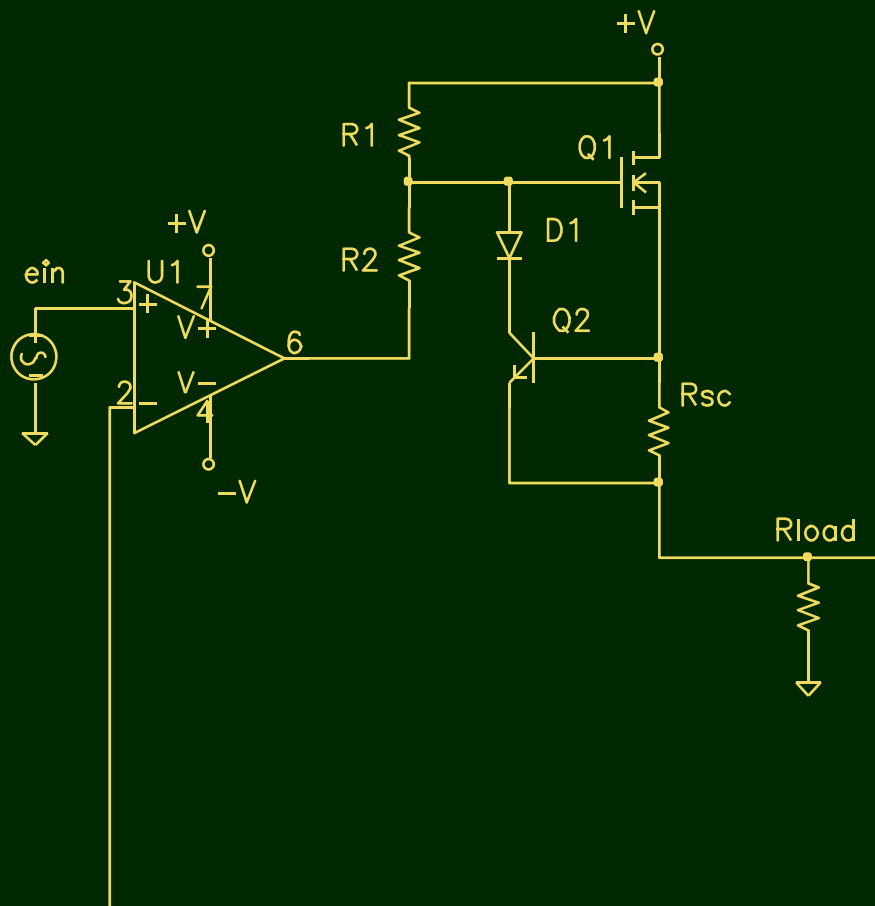Q2 on \Rightarrow Q1 V_{GS} shorted

Current Limiting - Positive side schematic



R_{sc} small $0.x \Omega$

normal operation

$$I_{load} < I_{sc}$$

Q2 off \Rightarrow no effect


$$I_{load} \uparrow \Rightarrow V_{R_{sc}} \uparrow$$

$$V_{R_{sc}} = 0.7V \Rightarrow$$

Q2 on \Rightarrow Q1 V_{GS} shorted

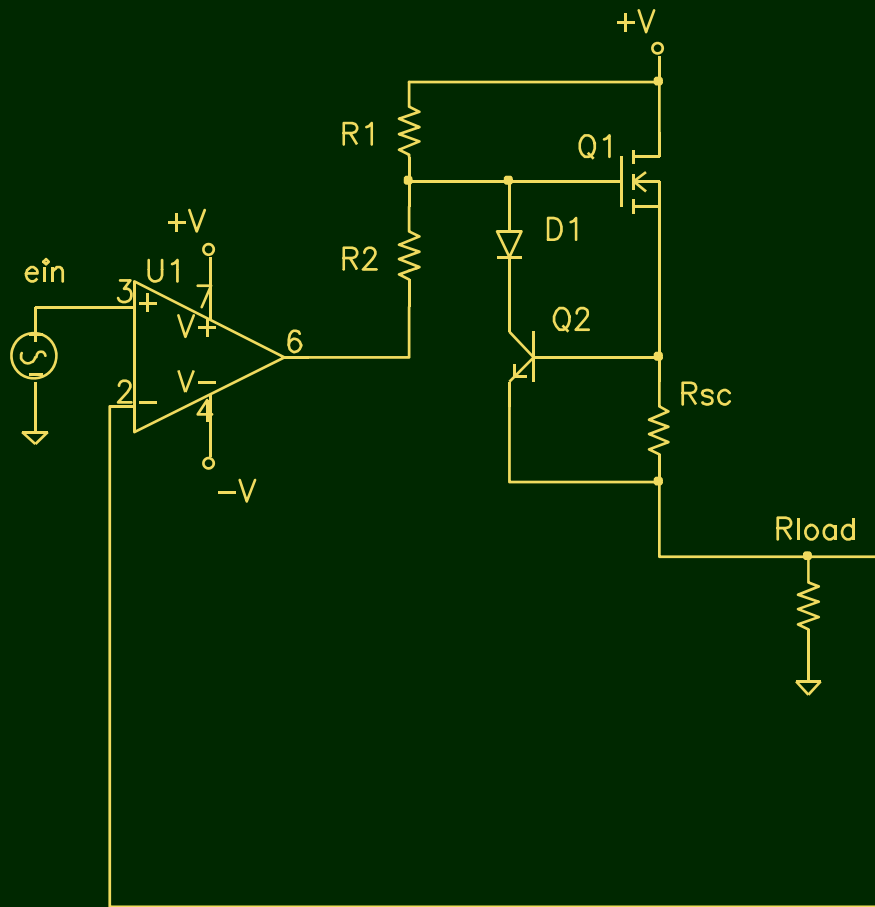Q1 off \Rightarrow $I_{load} \downarrow$

Current Limiting - Positive side schematic



R_{sc} small $0.x \Omega$

normal operation

$$I_{load} < I_{sc}$$

Q2 off \Rightarrow no effect

$$I_{load} \uparrow \Rightarrow V_{R_{sc}} \uparrow$$

$$V_{R_{sc}} = 0.7V \Rightarrow$$

Q2 on \Rightarrow Q1 V_{GS} shorted

Q1 off \Rightarrow $I_{load} \downarrow$

Current Limiting - Problem

$$V_{\text{supply}} = 30\text{V}$$

$$R_{\text{load}} = 8\Omega$$

$$V_{\text{load max}} = 20V_P$$

$$T_A = 50\text{ }^\circ\text{C}$$

$$\Theta_{JA} = 7.5\text{ }^\circ\text{C/W}$$

$$I_{SC} = ? \quad R_{SC} = ?$$

$$P_{Q \text{ shorted load}} = ?$$

$$T_J = ?$$

$$\begin{aligned} I_{SC} &> V_{\text{load P}} / R_{\text{load}} \\ &> 20V_P / 8\Omega = 2.5A_P \end{aligned}$$

$$\text{pick } I_{sc} = 2.8A$$

$$R_{SC} = 0.7V / 2.8A = 0.25\Omega$$

$$P_{Q \text{ short}} = (30V * 2.8A) / 2 = 42W$$

$$T_J = 50\text{ }^\circ\text{C} + 42W * 7.5\text{ }^\circ\text{C/W}$$

$$= 365\text{ }^\circ\text{C} \Rightarrow \text{smoke !}$$

Current Limiting - Problem

$$V_{\text{supply}} = 30\text{V}$$

$$R_{\text{load}} = 8\Omega$$

$$V_{\text{load max}} = 20\text{V}_P$$

$$T_A = 50\text{ }^\circ\text{C}$$

$$\Theta_{JA} = 7.5\text{ }^\circ\text{C/W}$$

$$I_{SC} = ? \quad R_{SC} = ?$$

$$P_{Q \text{ shorted load}} = ?$$

$$T_J = ?$$

$$I_{SC} > V_{\text{load P}} / R_{\text{load}}$$

$$\text{pick } I_{sc} = 2.8\text{A}$$

$$T_J = 365\text{ }^\circ\text{C} \Rightarrow \text{smoke !}$$

Why does it not burn up when the load is not shorted?

What are we going to do?

Overview

◆ Current Limiting

- performance positive side schematic
operation problem

Temperature Sensor


- Case temperature
- IC switch

Temperature Switch

$$T_J = T_S + P(\Theta_{JC} + \Theta_{CS})$$

$$T_S = T_J - P(\Theta_{JC} + \Theta_{CS})$$
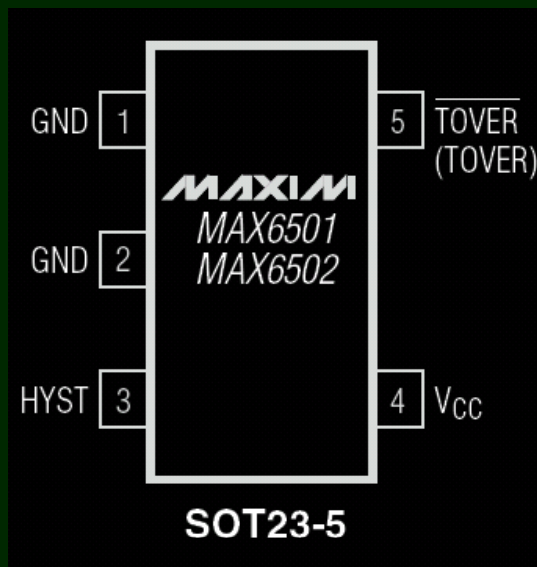
$$T_S = 130^\circ\text{C} - 19.5\text{W} \left(1.9 \frac{^\circ\text{C}}{\text{W}} + 0.2 \frac{^\circ\text{C}}{\text{W}} \right) = 89^\circ\text{C}$$



Heat sink temperature = ?

Temperature switch

MAX6501 - 95°C

$T_C < 95^\circ\text{C} \Rightarrow$ output open

3.3kΩ pullup to 5V

$T_C > 95^\circ\text{C} \Rightarrow$ output low

Hysteresis pin

$V_H \Rightarrow 10^\circ\text{C}$

85 °C to go high

Mounting ?