

## Registers and Counters

## Last Lecture

- Last time we looked at:
  - latches
  - flip flops
- We saw that these devices hold a value depending on their inputs.
- A data input value is loaded into the register on the rise of the clock edge.
- Some circuits have additional ~clear or ~reset inputs.




Positive edge-triggered flip-flop

|   | C | D | Q  |
|---|---|---|----|
| ↑ |   | 0 | 0  |
| ↑ |   | 1 | 1  |
| ↓ |   | ? | Qn |


## Registers from Latches

- Often want to read a group of data inputs into a set of latches at the same time (e.g. reading a 4 bit value off a computer bus)
- A group of latches can be combined to form a register
- A 4 bit register can be made from 4 latches

## Four bit Register

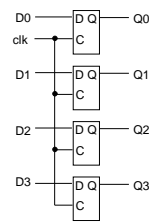


Circuit

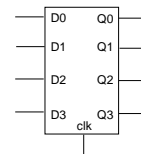

Symbol
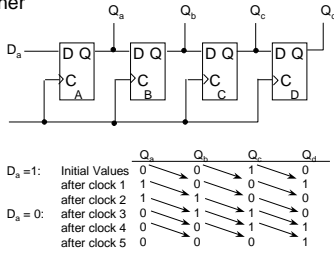
## Shift Registers

- Allow stored data to be moved from one bit position to another




## Shift Registers

### ■ Points to note:

- At every clock pulse, the first flip flop is loaded with the value of the data in stream
- The data that was in this flip flop is then loaded into the second and so on.
- The data can be taken out of the last flip flop in serial form or it can be taken from all outputs at the same time – parallel form.
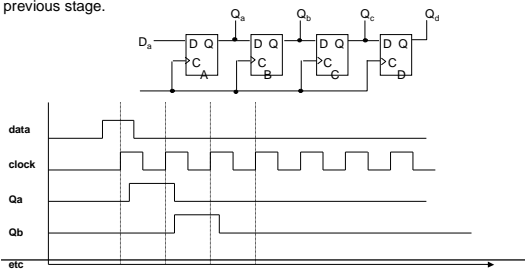
## Shift Registers

■ For each flip flop there is a delay between clock pulse and output. This delay provides time for the next flip flop in the chain to load the data from the previous stage.



## Shift Registers


- Shift registers can also be loaded using parallel input lines
- Therefore inputs can be parallel or serial
- Outputs can be parallel or serial
- Functions that shift registers can carry out include:
  - Serial Loading
  - Serial Output
  - Parallel Output
  - Parallel Loading
- This makes them suitable for a wide variety of tasks

## Shift Registers

- A large variety of integrated circuit (IC) shift registers are available with various combinations of
  - serial and/or parallel input
  - serial and/or parallel output
  - shift left and/or shift right
- Applications include:
  - Converting a parallel word into serial form or vice versa
  - performing a number of logical and arithmetic operations (binary multiplication/division involves shifting).
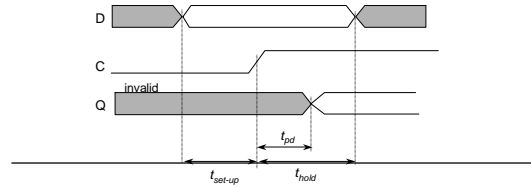
## Registers

- Timing characteristics for edge-triggered registers
  - propagation delay ( $t_{pd}$ ) defined as the time between the clock edge and the output changing
  - Set-up ( $t_{set-up}$ ) and hold ( $t_{hold}$ ) times are the times which the data must be held steady before and after the clock edge




## Counters

- Counters may be clocked by:
  - regular clock pulses to determine a certain time duration
  - random pulses to count the occurrences of a particular event
- Most common counters count natural binary sequence

| up counter | down counter |
|------------|--------------|
| 000        | 111          |
| 001        | 110          |
| 010        | 101          |
| 011        | 100          |
| 100        | 011          |
| 101        | 010          |
| 110        | 001          |
| 111        | 000          |
| 000        | 111          |
| ...        | ...          |
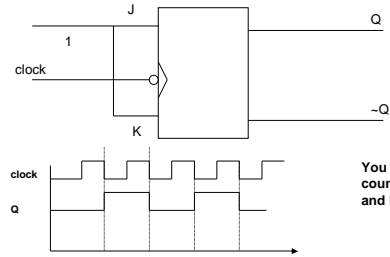
## JK Flip flop - recall

- A JK flip flop toggles when both inputs are 1. In this case it effectively counts every second clock pulse:



You can also say it counts from 0 to 1 and back again.

Sometimes called a "scale of 2 counter"

### Counters

- Connect two such flip flops together:

Complete the timing diagram for Q2

Outputs Q1 and Q2 cycle.

Q2Q1: 00 01 10 11 00

### Counters

- Ripple (asynchronous) Counter
  - e.g. A 3 bit ripple counter using negative edge triggered JK flip-flops
  - Asynchronous means each flip flop is triggered by the preceding one.

### Counters

- These propagation delays cause a number of sequence changes when going from one number to the next, which can be undesirable in a lot of situations.
- The counter can get the wrong value at a particular instant in time
- Operating speed is therefore limited.


### Counters

- Synchronous counters
  - Outputs of all the flip-flops change at the same time
  - e.g. a 2-bit synchronous counter

## Counters
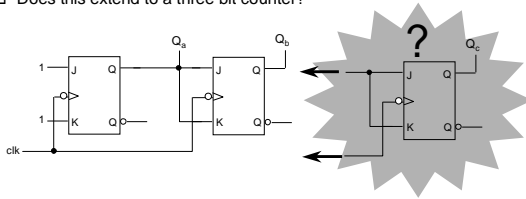
### ■ Synchronous counters

- Does this extend to a three bit counter?




- $Q_c$  should not toggle until both  $Q_a$  and  $Q_b$  are 1


## Counters

### □ Synchronous counters

- e.g. A three bit counter

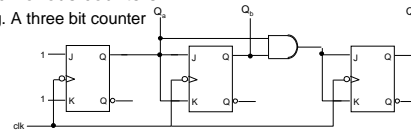


- e.g. A four bit counter

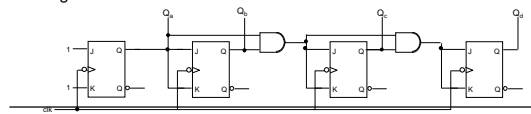

## Counters
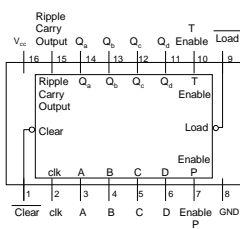
### □ An integrated circuit counter


- Many forms of counters available as integrated circuits
- e.g. 74163 - four bit synchronous binary up counter
- **Clock:** count advanced by 1 on  $\uparrow$
- **Clear:** when = 0 count reset to 0 on next clk
- **Load:** when = 0 count set to values on A-D on next clk
- **Enable T & P:** Counting disabled when either is equal 0
- $Q_a, Q_b, Q_c, Q_d$ : state of the counter
- **Ripple Carry output:** = 1 when count = 1111 otherwise 0



## Counters
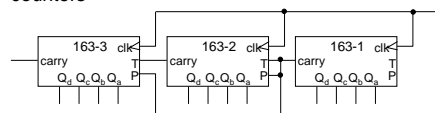
### ■ An integrated circuit counter


- In many cases more than 16 states required for counting
- counters like 163 can be cascaded to form larger counters




## Counters
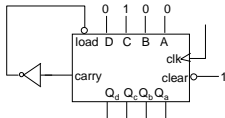
### □ Modulo-n counters

- A **modulo-n** counter generates n states before it repeats itself
- e.g. a 2 bit count is modulo 4 and a 4 bit counter is modulo 16
- Often a counter which has a modulo that is not a power of 2 is required e.g. modulo 12



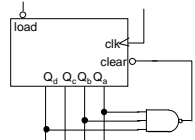Counts from 4 through to 15 before being set to 4 again




Counts from 0 through to 11 before being reset

## Counters
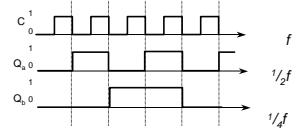
### ■ Frequency division

- Binary counters offer the possibility of frequency division



- Often used where clocks of different frequencies are required in a circuit or to produce a compact accurate low frequency oscillator (e.g. an oscillator for a digital watch)

## Registers/Shift registers and Counters

### ■ Summary

- Registers consist of a group of D-type latches or flip-flops which are clocked simultaneously to store a binary word
  - set-up and hold times must be observed
- Shift registers allow data to be moved from one bit position to another
  - used for parallel $\leftrightarrow$ serial conversion and some types of arithmetic operations
- Counting is a common requirement in sequential logic circuits
  - Counters can be asynchronous or synchronous
  - Many IC packages exist which implement counters

## What you should be able to do

- Explain the operation of a register
- Explain the propagation delays associated with registers
- Outline the use of registers for converting serial/parallel inputs/outputs.
- Explain the operation of ripple (asynchronous counters)
- Explain the operation of synchronous counters
- Outline the characteristics of modulo n counters.