



**School of Electronic
and Communications
Engineering**

Phase-Locked Loops (PLL)

Recommended Text: Gray, P.R. & Meyer. R.G.,
Analysis and Design of Analog Integrated Circuits (3rd
Edition), Wiley (1992) pp. 681-698

Introduction


- ❖ The phase-locked loop concept was first developed in the 1930s.⁴
- ❖ It has since been used in communications systems of many types, particularly in satellite communications systems.
- ❖ Until recently, however, phase-locked systems have been too complex and costly for use in most consumer and industrial systems, where performance requirements are more modest and other approaches are more economical.
- ❖ The PLL is particularly amenable to monolithic construction, however, and integrated-circuit phase-locked loops can now be fabricated at very low cost.
- ❖ Their use has become attractive for many applications such as FM demodulators, stereo demodulators, tone detectors, frequency synthesizers, and others.

Definition

- ❖ A PLL is a feedback system that includes a
 1. Voltage–Controlled Oscillator (VCO),
 2. phase detector, and
 3. low pass filter within its loop.
- ❖ Its purpose is to force the VCO to replicate and track the frequency and phase at the input when in lock.
- ❖ The PLL is a control system allowing one oscillator to track with another. It is possible to have a phase offset between input and output, but when locked, the frequencies must exactly track.

$$\phi_{out}(t) = \phi_{in}(t) + const.$$

$$\omega_{out}(t) = \omega_{in}(t)$$

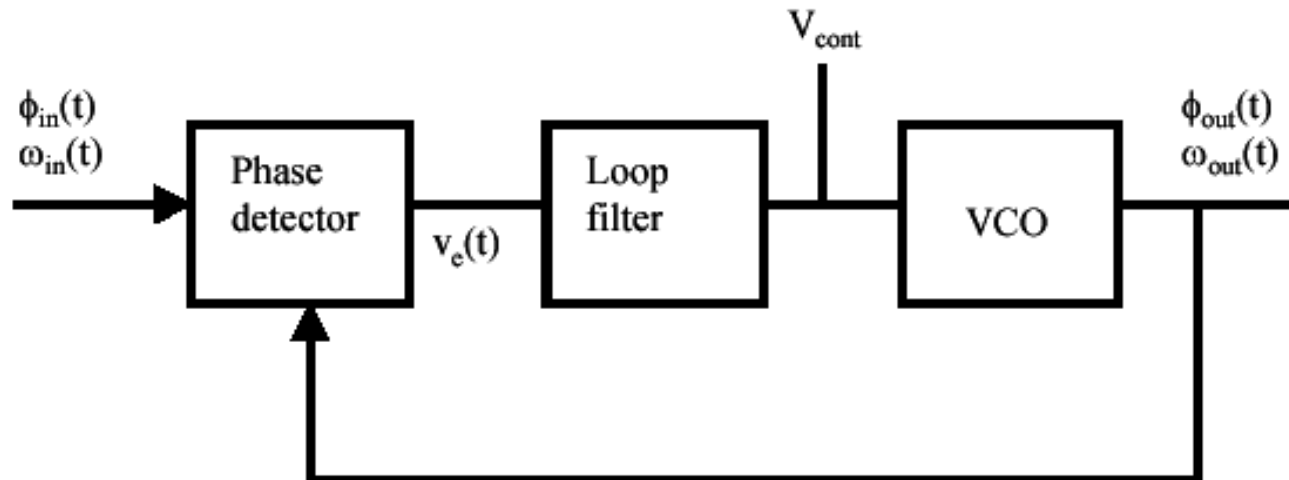

- ❖ The PLL output can be taken from either
 1. V_{cont} , the filtered (almost DC) VCO control voltage, or
 2. from the output of the VCO depending on the application.
- ❖ The former provides a baseband output that tracks the phase variation at the input.
- ❖ The VCO output can be used as a local oscillator or to generate a clock signal for a digital system.
- ❖ Either phase or frequency can be used as the input or output variables.
- ❖ Of course, phase and frequency are interrelated by:

$$\omega(t) = \frac{d\varphi}{dt} \quad \text{and} \quad \varphi(t) = \varphi(0) + \int \omega(t') dt'$$

Applications:

- ❖ There are many applications for the PLL:
 1. a. FM demodulator
 2. b. Frequency synthesizer
 3. c. Clock generation
- ❖ You should note that there will be different input and output variables and different design criteria for each case,
- ❖ but you can still use the same basic loop topology and analysis methods.

Phase detector:

- ❖ **Phase detector** compares the phase at each input and generates an error signal, $v_e(t)$, proportional to the phase difference between the two inputs. K_D is the gain of the phase detector (V/rad).

$$v_e(t) = K_D (\varphi_{out}(t) - \varphi_{in}(t))$$

- ❖ As one familiar circuit example, an analogue multiplier (Gilbert cell) can be used as a phase detector.
- ❖ Recall that the mixer takes the product of two inputs. $v_e(t) = A(t)B(t)$. If,

$$A(t) = A \cos(\omega_0 t + \varphi_A) \text{ and } B(t) = B \cos(\omega_0 t + \varphi_B)$$

$$A(t)B(t) = AB \cos(\omega_0 t + \varphi_A) \cos(\omega_0 t + \varphi_B) =$$


$$(AB / 2) [\cos(2\omega_0 t + \varphi_A + \varphi_B) + \cos(\varphi_A - \varphi_B)]$$

$$v_e(t) = (AB / 2) [\cos(2\omega_0 t + \varphi_A + \varphi_B) + \cos(\varphi_A - \varphi_B)]$$

- ❖ Since the two inputs are at the same frequency when the loop is locked, we have:
 1. one output at **twice** the input frequency and
 2. an output proportional to the cosine of the **phase difference**.
- ❖ The doubled frequency component must be removed by the lowpass loop filter.
- ❖ Any phase difference then shows up as the control voltage to the VCO, a DC or slowly varying AC signal after filtering.

Transfer Characteristic

 - ❖ The averaged transfer characteristic of such a phase detector is shown below.



- ❖ Note that in many implementations, the characteristic may be shifted up in voltage (single supply/single ended).
- ❖ If the phase difference is $\pi/2$, then the average or integrated output from the XOR-type phase detector will be zero (or $V_{DD}/2$ for single supply, digital XOR).
- ❖ The slope of the characteristic in either case is K_D .

Voltage-Controlled Oscillator (VCO)

- ❖ In PLL applications, the VCO is treated as a linear, time-invariant system.
- ❖ Excess phase of the VCO is the system output.

$$\varphi_{out} = K_O \int_{-\infty}^t V_{cont} dt'$$


- ❖ The VCO oscillates at an angular frequency, ω_{out} . Its frequency is set to a nominal ω_0 when the control voltage is zero.
- ❖ Frequency is assumed to be linearly proportional to the control voltage with a gain coefficient K_O or K_{VCO} (rad/s/v).

$$\omega_{out} = \omega_0 + K_O V_{cont}$$


- ❖ Thus, to obtain an arbitrary output frequency (within the VCO tuning range), a finite V_{cont} is required.
- ❖ Let's define $\varphi_{out} - \varphi_{in} = \Delta\varphi$.

VCO (cont.)

 - ❖ In the figure below, the two inputs to the phase detector are depicted as square waves.
- ❖ The XOR function produces an output pulse whenever there is a phase misalignment.
- ❖ Suppose that an output frequency ω_1 is needed. From the upper right figure, we see that a control voltage V_1 will be necessary to produce this output frequency.



(a)

 

(h)

VCO (cont.)


- ❖ The phase detector can produce this $V1$ only by maintaining a phase offset ϕ_0 at its input.
- ❖ In order to minimize the required phase offset or error, the PLL loop gain, $K_D K_O$, should be maximized, since

$$\phi_0 = \frac{V1}{K_D} = \frac{\omega_1 - \omega_0}{K_D K_O}$$

- ❖ Thus, a high loop gain is beneficial for reducing phase errors.

PLL dynamic response

 - ❖ To see how the PLL works, suppose that we introduce phase step at the input at $t = t_1$. So that, $\phi_{in} = \omega_1 t + \phi_0 + \phi_1 u(t - t_1)$
- ❖ Since we have a step in phase, it is clear that the initial and final frequencies must be identical: ω_1 .
- ❖ But, a temporary change in frequency is necessary to shift the phase by ϕ_1 .



Dynamic Response ($\Delta\phi$)




- ❖ The area under ω_{out} gives the additional phase because V_{cont} is proportional to frequency.

$$\phi_1 = \int_{t_1}^{\infty} \omega_{out} dt = \int_{t_1}^{\infty} K_O V_{cont}(t) dt$$

- ❖ After settling, all parameters are as before since the initial and final frequencies are the same.
- ❖ This shows that $V_{cont}(t)$ can be used to monitor the dynamic phase response of the PLL.

Dynamic Response ($\Delta\omega$)

- ❖ Now, let's investigate the behaviour during a frequency step: $\phi_2 = \phi_1 + \Delta\phi$
- ❖ This will cause the phase difference to grow with time
- ❖ This in turn causes the control voltage, V_{cont} , to increase, moving the frequency step will cause the phase difference to grow with time since a frequency step is a phase ramp.
- ❖ This in turn causes the V_{cont} to increase, moving the VCO frequency up to catch up with the input reference signal.

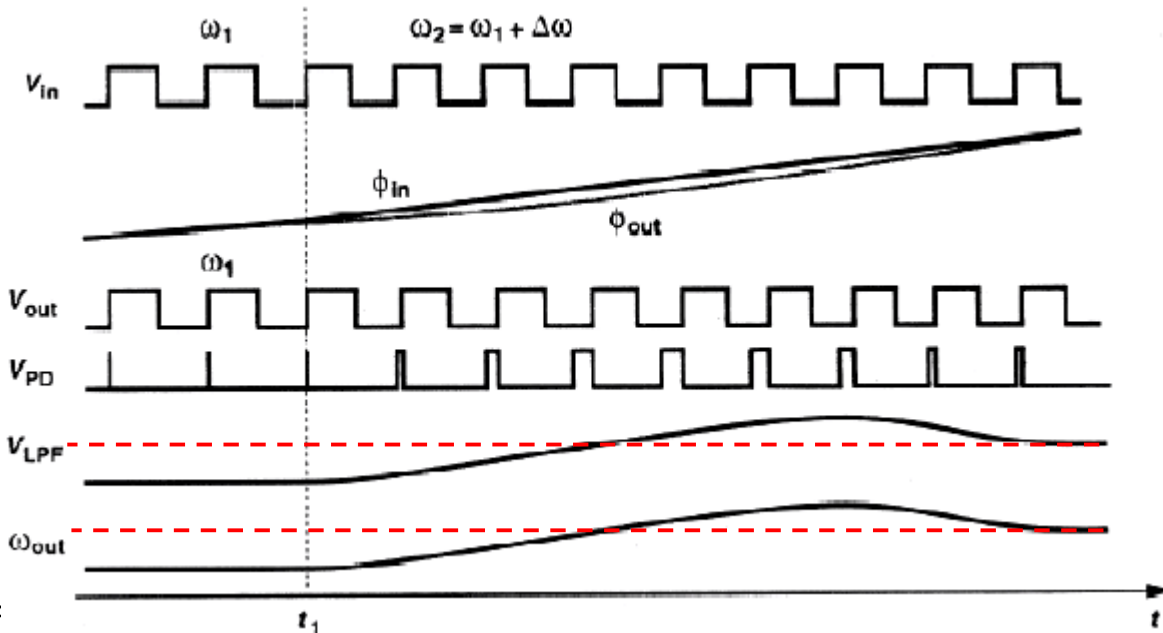

In this case, we have a permanent change in ω_{out} since a higher V_{cont} is required to sustain a higher ω_{out} .

If the frequency step is too large, the PLL will lose lock.

PLL in Locked Condition

- ❖ **Approach:** We will discuss the details of phase detectors and loop filters as we proceed.
- ❖ But, at this point, we will treat the PLL as a linear feedback system.
- ❖ We assume that it is already “locked” to the reference signal, and examine how the output varies with the loop transfer function and input.
- ❖ A frequency domain approach will be used, specifically describing transfer functions in the s-domain.

$$V_e(s)/\Delta\varphi = K_D \quad \text{and} \quad \varphi_{out}(s)/V_{cont}(s) = K_O/s$$


- ❖ Note that the VCO performs an integration of the control voltage and thus provides a factor of $1/s$ in the loop transfer function.
- ❖ Because of this, a PLL is always at least a first order feedback system.

PLL as Feedback System.

❖ **Loop Gain:** $T(s) = K_{FWD}(s)K_{FB}(s)$

❖ **Transfer Function:**
 
$$\frac{OUT(s)}{IN(s)} = H(s) = \frac{K_{FWD}(s)}{1 + T(s)}$$



❖ The Loop gain can be described as a polynomial:

$$T(s) = \frac{K'(s+a)(s+b)\dots}{s^n(s+\alpha)(s+\beta)\dots}$$

❖ **ORDER** = the order of the polynomial in the denominator

❖ **TYPE** = n (the exponent of the s factor in the denominator)

❖ **PHASE ERROR** $\epsilon(s) = IN(s) / [1 + T(s)]$

❖ **STEADY STATE ERROR** $\epsilon_{SS} = \lim_{s \rightarrow 0} [s\epsilon(s)] = \lim_{t \rightarrow \infty} \epsilon(t)$

❖ SS error is a characteristic of feedback control systems.

❖ This is the error remaining in the loop at the phase detector output after all transients have died out. Large loop gain leads to small error

PLL as a first-order filter

The closed-loop gain transfer function is given by

$$\frac{V_o}{\phi_i} = \frac{K_D F(s) A}{1 + K_D F(s) A \cdot (K_O / s)}$$

Assuming

$$\omega_i = \frac{d\phi_i}{dt} \quad \text{then} \quad \omega_i = s\phi_i(s)$$


The transfer function in terms of frequency variations therefore can be expressed as:

$$\frac{V_o}{\omega_i} = \frac{1}{s} \frac{V_o}{\phi_i} = \frac{K_D F(s) A}{s + K_D F(s) A \cdot K_O}$$

Assuming that LP is removed and $K_v = K_O K_D A$, hence

$$\frac{V_o}{\omega_i} = \frac{K_v}{s + K_v} \cdot \frac{1}{K_O}$$

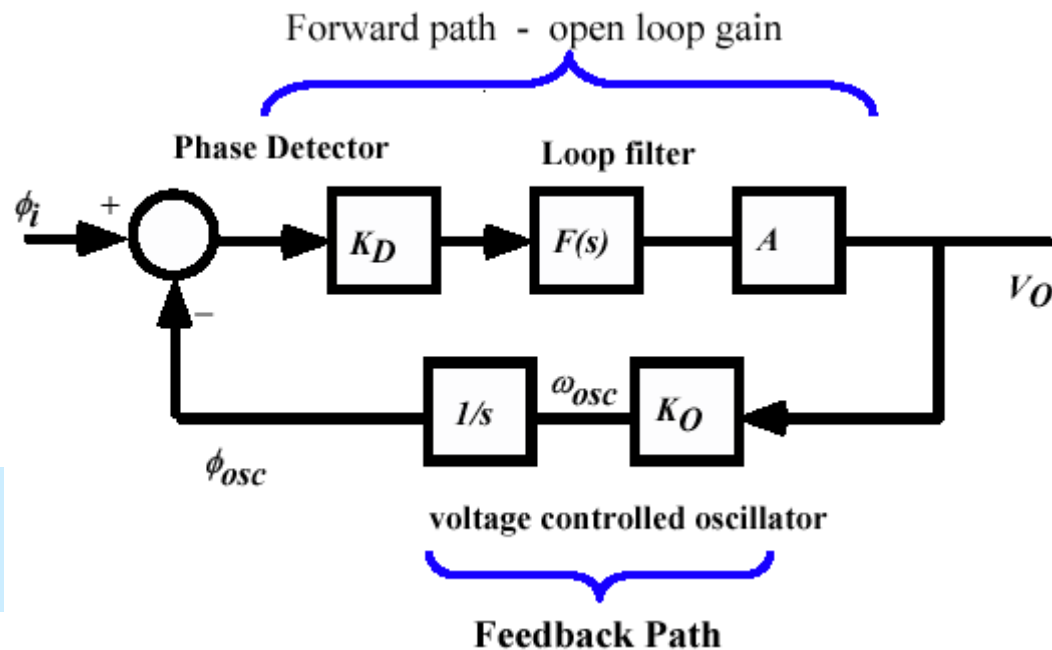Thus the loop inherently produces a first order low-pass transfer characteristic





PLL as a first-order filter

$$\frac{V_o}{\omega_i} = \frac{1}{s} \frac{V_o}{\phi_i} = \frac{K_D F(s) A}{s + K_D F(s) A \cdot K_O}$$

$$\frac{V_o}{\omega_i} = \frac{K_v}{s + K_v} \frac{1}{K_O}$$

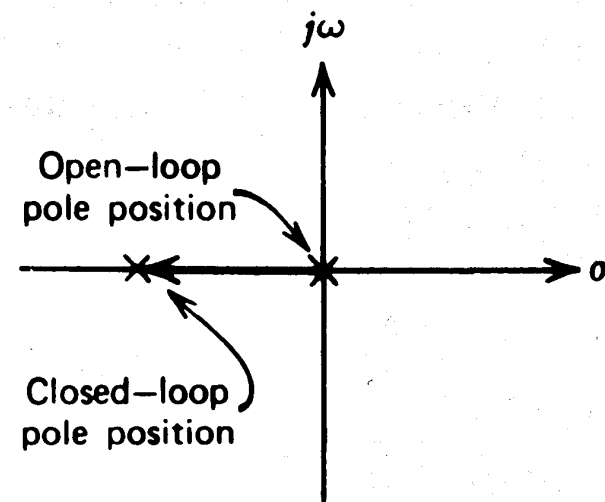 - ❖ Assuming that LP is removed and $K_v = K_O K_D A$, hence
- ❖ Thus the loop inherently produces a first order low-pass transfer characteristic.



Example

- ❖ A PLL has a K_O of 2π (1kHz/V), a K_V of 500 s^{-1} and a free-running frequency of 500Hz. Find V_O for a constant input signal frequency of 250 Hz and 1 kHz
- ❖ Sketch the response of V_O


$$V_O = (\omega_i - \omega_o) / K_O$$

- ❖ At 250 Hz ,

$$V_O = (2\pi(250) - 2\pi(500)) / 2\pi(1\text{kHz} / V) = -0.25V$$

- ❖ At 500 Hz
 
$$V_O = (2\pi(1000) - 2\pi(500)) / 2\pi(1\text{kHz} / V) = 0.5V$$




PLL as a first-order filter

- ❖ This example shows that PLL can operate with no loop filter
- ❖ Nevertheless it has several practical drawbacks.
- ❖ Since the phase detector is really a multiplier, it produces a **sum frequency** component at its output as well as the **difference frequency** component.
- ❖ This component at twice the carrier frequency will be fed directly to the output if there is no loop filter.
- ❖ Also, all the out-of-band interfering signals present at the input will appear, shifted in frequency, at the output.
- ❖ Thus, a loop filter is very desirable in applications where interfering signals are present.

Second-order PLL

- ❖ The most common configuration for integrated circuit PLLs is the second-order loop.
- ❖ Here, loop filter $F(s)$ is simply a single-pole, low-pass filter, usually realized with a single resistor and capacitor. Thus

$$F(s) = \frac{1}{1 + s / \omega_1}$$

 

- ❖ Substituting this into


$$\frac{V_o}{\omega_i} = \frac{1}{s} \frac{V_o}{\phi_i} = \frac{K_D F(s) A}{s + K_D F(s) A \cdot K_O}$$

- ❖ It gives:

$$\frac{V_o}{\omega_i} = \frac{1}{K_O} \frac{1}{1 + s / K_v + s^2 / \omega_1 K_v}$$

- ❖ The roots of this transfer function are
 
$$s_{1,2} = -\frac{\omega_1}{2} \left(1 \pm \sqrt{1 - \frac{4K_v}{\omega_1}} \right)$$



Damping Factor


- ❖ This transfer function
- ❖ can be also expressed as:

$$\frac{V_o}{\omega_i} = \frac{1}{K_o} \frac{1}{\frac{s^2}{\omega_n^2} + \frac{2\zeta}{\omega_n} s + 1}$$

$\omega_n = \sqrt{\omega_1 K_v}$ is crossover frequency

$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_v}}$ is damping factor

 - ❖ We can have a very underdamped response when $\omega_1 \ll K_v$.
- ❖ Think about the inverse Laplace transform of the complex conjugate pole pair.



- ❖ The inverse Laplace transform of the complex conjugate pole pair.

$$s_{1,2} = -\frac{\omega_1}{2} \left(1 \pm \sqrt{1 - \frac{4K_v}{\omega_1}} \right)$$


- ❖ Gives

$$v(t) = e^{-\frac{\omega_1 t}{2}} \sin \left(\frac{\omega_1}{2} \sqrt{1 - \frac{4K_v}{\omega_1}} t \right)$$


- ❖ A good compromise is using a maximally flat low-pass pole configuration in For this response, the damping factor should be equal to $1/\sqrt{2}$
- ❖ Thus

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_v}} = \frac{1}{\sqrt{2}} \text{ and } \omega_1 = 2K_v$$

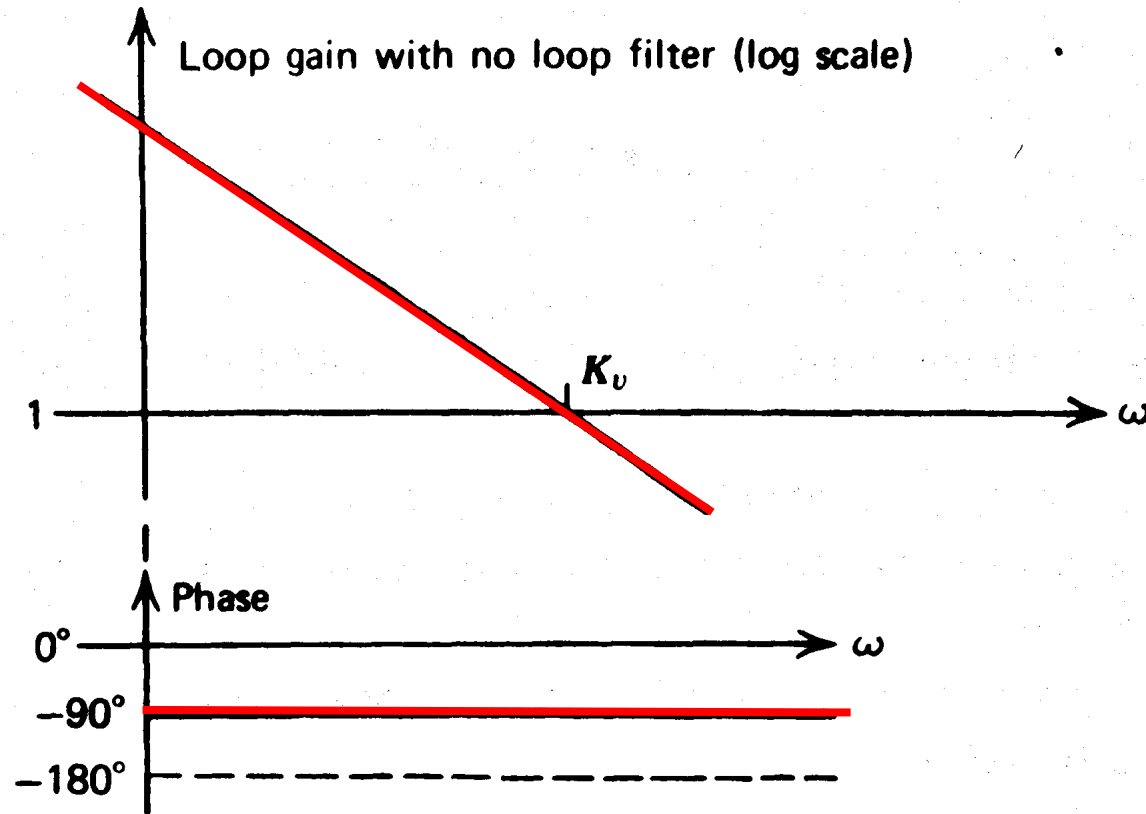PLL open-loop response with no loop filter




 
PLL open-loop response with a single-pole filter



PLL open-loop response with zero added in loop filter

- Adding a resistor to the lowpass loop filter contributes a zero to its transfer function
  
$$F(s) = \frac{1 + s / \omega_2}{1 + s / \omega_1}$$




$$\omega_2 = \frac{1}{R_2 C}$$

$$\omega_1 = \frac{1}{(R_1 + R_2) C}$$

Thus, the zero frequency is always higher than the pole frequency, $\omega_2 > \omega_1$.

Lock Range

 - ❖ **Lock Range.** Range of input signal frequencies over which the loop remains locked once it has captured the input signal. This can be limited either by the
- ❖ (a) phase detector or
- ❖ (b) the VCO frequency range.
- ❖ If limited by phase detector: $0 < \phi < \pi$ is the active range where lock can be maintained.




Lock Range

- ❖ For the phase detector type shown (Gilbert multiplier or mixer), the voltage vs. phase slope reverses outside this range.
- ❖ Thus the frequency would change in the opposite direction to that required to maintain the locked condition. $V_{e-max} = \pm K_D \pi / 2$
- ❖ When the phase detector output voltage is applied through the loop filter to the VCO, $\Delta\omega_{out-max} = \pm K_V \pi / 2 = \omega_L$ (lock range)
- ❖ where $K_V = K_O K_D$, the product of the phase detector and VCO gains.
- ❖ This is the frequency range around the free running frequency that the loop can track.
- ❖ Doesn't depend on the loop filter
- ❖ Does depend on DC loop gain
- ❖ b. The lock range could also be limited by the tuning range of the VCO.
- ❖ Oscillator tuning range is limited by capacitance ratios or current ratios and is finite. In many cases, the VCO can set the maximum lock range.

Capture Range

- ❖ **Capture range:** Range of input frequencies around the VCO centre frequency onto which the loop will lock when starting from an unlocked condition.
- ❖ The **capture range** is the range of input frequencies for which the initially unlocked loop will lock on an input signal and is always **less** than the **lock range**.
- ❖ the capture range is difficult to predict analytically. As a very rough rule of thumb, the approximate capture range can be estimated using the following procedure:
- ❖ When the input frequency is swept through a range around the center frequency, the output voltage as a function of input frequency displays a hysteresis effect.

Capture Range

 

- ❖ Assume that the loop is opened at the loop-amplifier output and that a signal with a frequency not equal to the free-running VCO frequency is applied at the input of the PLL.
- ❖ The sinusoidal *difference* frequency component that appears at the output of the phase detector has the value

$$V_p(t) = \frac{\pi}{2} K_D \cos(\omega_i - \omega_{ocs})t$$

Capture Range

- ❖ The output from the loop amplifier thus consists of a sinusoid at the difference frequency whose *amplitude* is reduced by the loop filter.
- ❖ This component is passed through the loop filter, and the output from the loop amplifier resulting from this component is

$$V_o(t) = \frac{\pi}{2} K_D A \cdot |F(j(\omega_i - \omega_{ocs}))| \cdot \cos((\omega_i - \omega_{ocs})t - \varphi)$$

where φ is $\varphi = \angle F(j(\omega_i - \omega_{ocs}))$

- ❖ In order for capture to occur, the magnitude of the voltage that must be applied to the **VCO** input is

$$V_{osc}(t) = \frac{\omega_i - \omega_{ocs}}{K_O}$$

- ❖ Capture is likely to occur when $V_{osc}(t) < V_o(t)$ Therefore:

$$\omega_i - \omega_{ocs} < \frac{\pi}{2} \cdot K_D K_O A \cdot |F(j(\omega_i - \omega_{ocs}))|$$

- ❖ Sometimes a frequency detector is added to the phase detector to assist in initial acquisition of lock.

Typical Question

- The 2nd-order phase-locked loop (PLL) system illustrated in Fig. 2 contains sub-elements with corresponding gain values as shown in Table 1. The amplifier gain may be assumed to be constant.

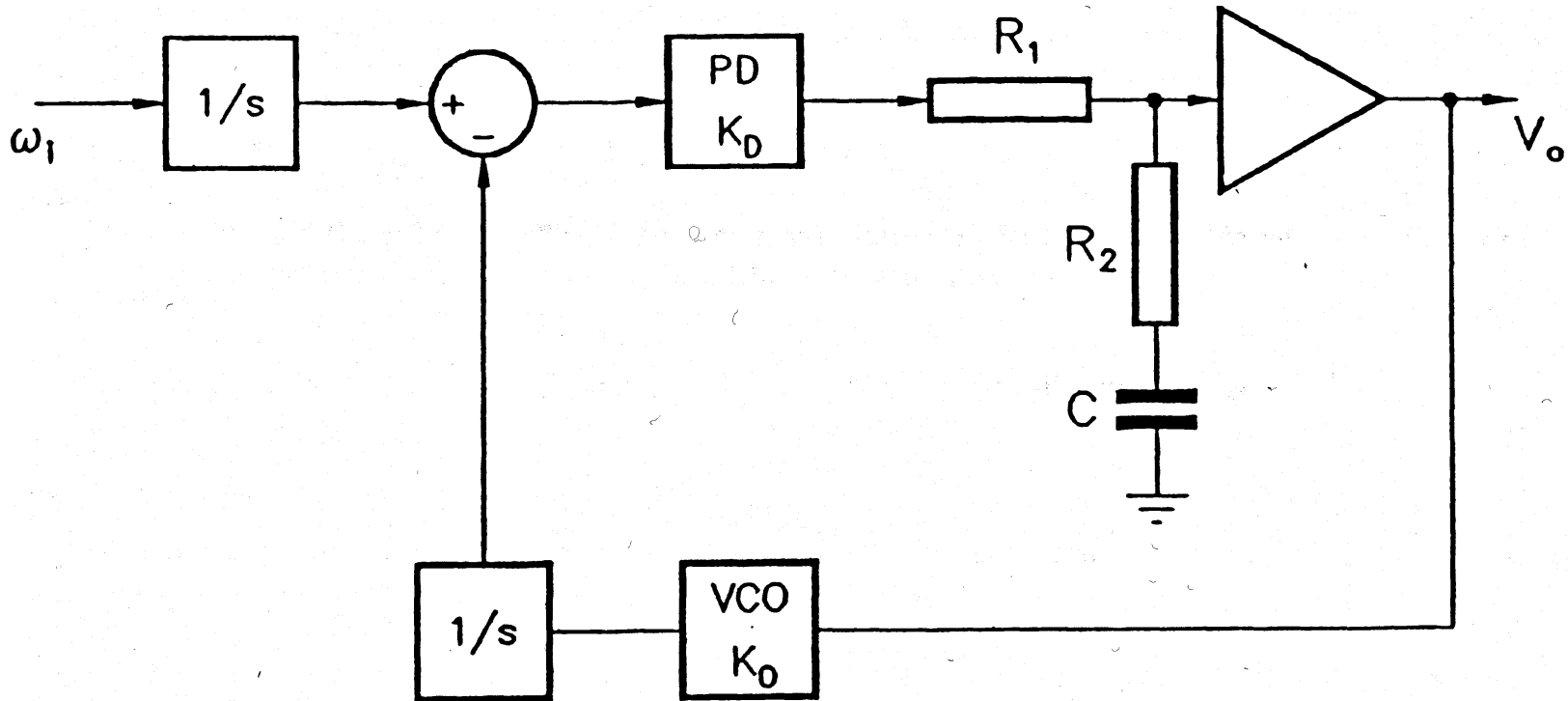


Table of Gains

| Component | Symbol | Value | Units |
|----------------|--------|--------|------------------|
| Phase Detector | K_D | 50 | volts/radian |
| VCO | K_O | 10^6 | Radians/sec/volt |
| Amplifier | A | 20 | dB |

- ❖ Given loop-filter component values $R_1 = 5.6 \text{ k}\Omega$, $R_2 = 330 \text{ }\Omega$ and $C = 1 \text{ nF}$, sketch
 - ❖ (a) the asymptotic closed-loop (V_o/ω_1) PLL frequency response and estimate the bandwidth and
 - ❖ (b) the asymptotic loop-gain response and graphically or otherwise, determine the 0 dB intercept frequency