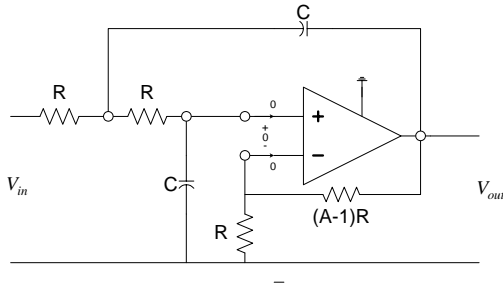


## Second-Order Sallen-Key Filters

### S.K. Low-Pass Filter




$$\omega_c = \frac{1}{RC},$$

$$A_v = A,$$

$$Q = \frac{1}{3-A}$$

### S.K. High-Pass Filter

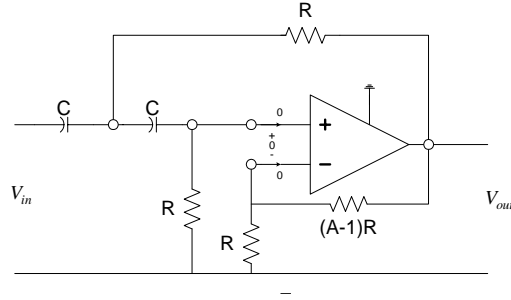


$$\omega_c = \frac{1}{RC},$$

$$A_v = A,$$

$$Q = \frac{1}{3-A}$$

### S.K. Band-Pass Filter

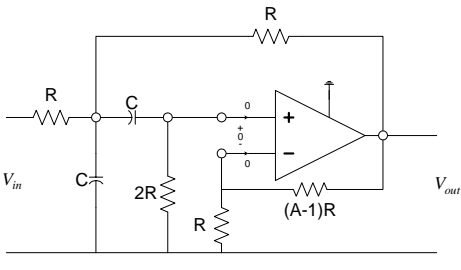


$$\omega_o = \frac{1}{RC}$$

$$Q = \frac{1}{3-A}$$

$$A_v = AQ$$

### S.K. Band-Reject Filter

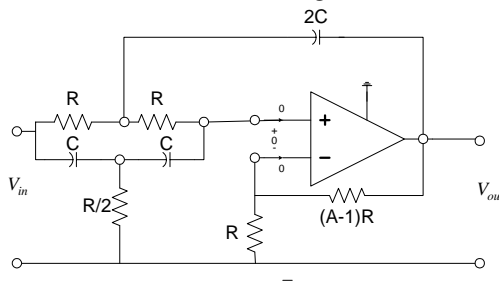

$$\omega_o = \frac{1}{RC}$$

$$Q = \frac{1}{4-2A}$$

$$A_v = A$$

### Properties of Sallen-Key Filters:


1. **Simplicity of the design**
2. **Non-Inverting Amplifier (positive Gain)**
3. **Replication of elements**

### Limitations of Sallen-Key Filters:

1. **The Gain and Q are related**
2. **Q must be > 1/2, since A must be > 1**


## Other Active Filters

### Band Pass 1:

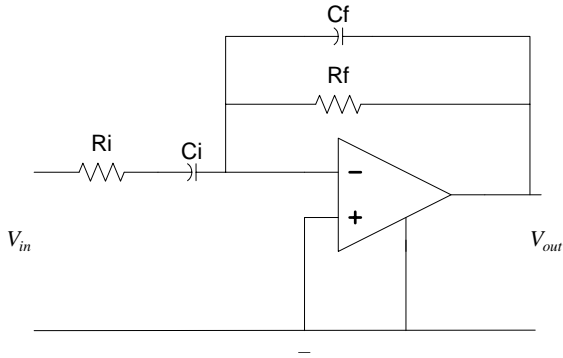


$$H(s) = -\frac{R_f}{R_i} \frac{\frac{1}{R_f C_f} s}{s^2 + \left( \frac{1}{R_f C_f} + \frac{1}{R_i C_i} \right) s + \frac{1}{R_i C_i R_f C_f}}$$

### Band Pass 2:

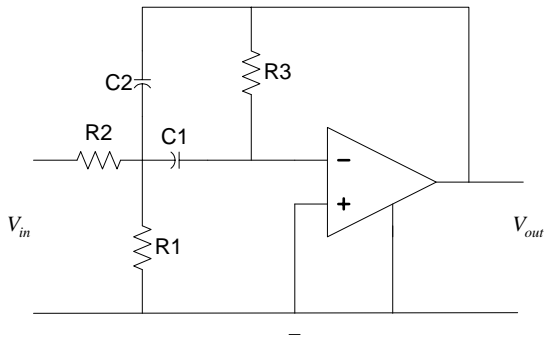


$$H(s) = \frac{-\frac{1}{R_2 C_2} s}{s^2 + \left( \frac{C_1 + C_2}{R_3 C_1 C_2} \right) s + \frac{1}{(R_1 \parallel R_2) R_3 C_1 C_2}}$$

### Band Pass 3:

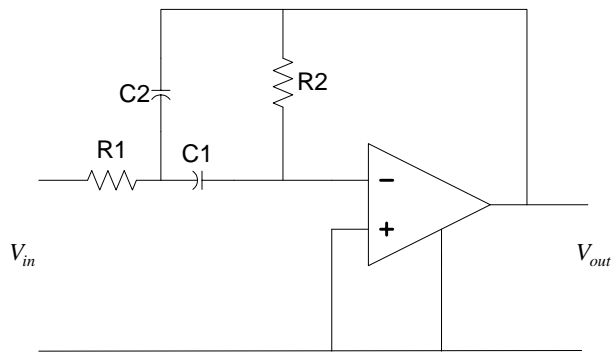

$$H(s) = \frac{-\frac{1}{R_1 C_2} s}{s^2 + \left( \frac{C_1 + C_2}{R_2 C_1 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

### Band Reject 1:

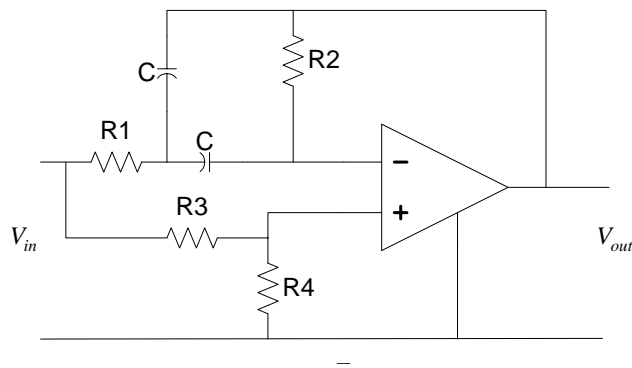

$$H(s) = \frac{R_4}{R_3 + R_4} \frac{s^2 + s \left( \frac{2}{R_2 C} - \frac{R_3}{R_1 R_4 C} \right) + \frac{1}{C^2 R_1 R_2}}{s^2 + s \frac{2}{R_2 C} + \frac{1}{C^2 R_1 R_2}}$$

## Other Active Filters

### Properties & Design Hints

- These amplifiers are “inverting amplifiers” (negative gain)
- BPF1 is restricted to  $Q > 1/2$ .
- BPF2 can have a  $Q < 1/2$  if  $C_1 \neq C_2$ .
- Both gain and  $Q$  can be controlled with the circuit elements.
- BRF1 does not have a true zero on the imaginary axis unless  $\frac{R_3}{R_1 R_4} = \frac{2}{R_2}$ .
- A design may not require a true null, but a notch. The zero can be adjusted to control the “dip” in the response.
- Typical design: Specify the gain,  $Q$ , and resonant frequency, and then solve for the circuit elements.
  - Requires some assumptions for the values of  $R$ 's and  $C$ 's (problem is under-determined). Choose  $R$  to be large ( $> 1$  k) when possible. Possibly choose relationships (such as  $C_1 = k \times C_2$ ).
  - Equations for remaining elements can be non-linear.
  - Not all values of  $Q$ ,  $A_v$ , and  $\omega_o$  are necessarily possible.
  - Gain may not be as important as  $Q$  and resonant frequency if the amplifier is one stage of a system design.