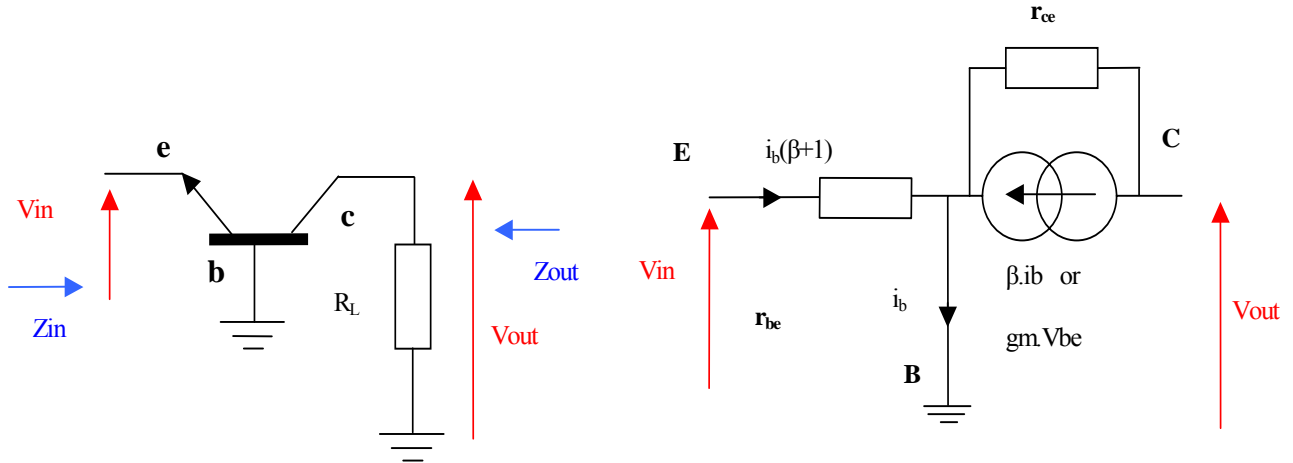


Common-Base/Gate Circuits

Common-Base BJT circuit


The figure below shows the simplified 'Pi' model of a common-base BJT.



$$R_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{i_b(\beta+1) \cdot r_{be}}{i_b(\beta+1)} = r_{be} = \frac{1}{g_m} \quad \text{where } g_m = \frac{I_{CQ}}{V_T}$$

$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{\beta \cdot i_b \cdot r_{ce}}{i_b(\beta+1)r_{be}} = \frac{\beta \cdot r_{ce}}{(\beta+1)r_{be}} \approx \frac{r_{ce}}{r_{be}} = \frac{I_{CQ}}{V_T} \cdot \frac{V_A}{I_{CQ}} = \frac{V_A}{V_T} \quad \left(\text{as } \frac{1}{g_m} = r_{ce}\right)$$
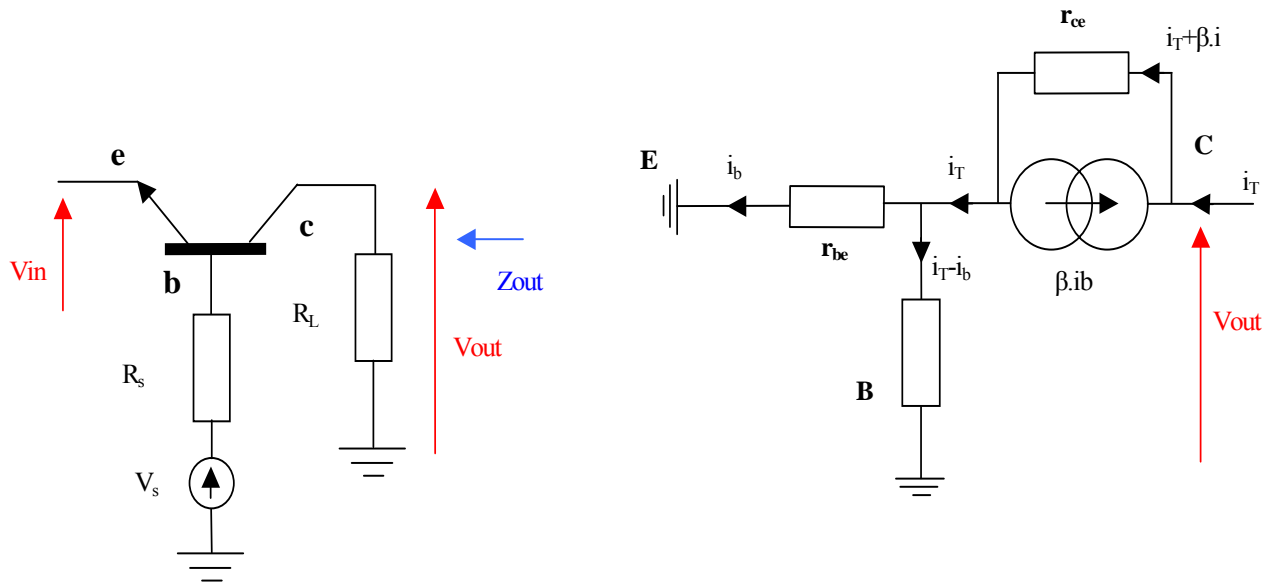
$$A_i = \frac{I_{OUT}}{I_{IN}} = \frac{\beta \cdot i_b}{i_b(\beta+1)} = \frac{\beta}{\beta+1} \approx 1$$



To determine the Output impedance of the circuit we can connect a voltage source ($V_s + R_s$) to the base and ground the input ie the emitter. We then have to resistances in parallel connected to the current source $\beta \cdot i_b$.

$$R_{OUT} = \frac{V_{OUT}}{i_T}$$

$$V_{OUT} = (i_T + \beta \cdot i_b) r_{ce} + i_b \cdot r_{be}$$

Also $i_b = i_T \frac{R_s}{r_{be} + R_s}$ sub into above equation



$$V_{OUT} = \left(i_T + \beta \cdot i_T \frac{R_s}{r_{be} + R_s} \right) r_{ce} + i_T \frac{R_s}{r_{be} + R_s} \cdot r_{be}$$

$$R_{OUT} = \frac{V_{OUT}}{i_T} = r_{ce} + \beta \cdot r_{ce} \frac{R_s}{r_{be} + R_s} + \frac{R_s \cdot r_{be}}{r_{be} + R_s}$$

If $R_s = 0$ then $R_{OUT} = r_{ce}$

If $R_s = \text{large}$ then $R_{OUT} = r_{ce} + \beta \cdot r_{ce} + 1 = (\beta + 1) r_{ce}$

Common-Gate MOSFET Circuit

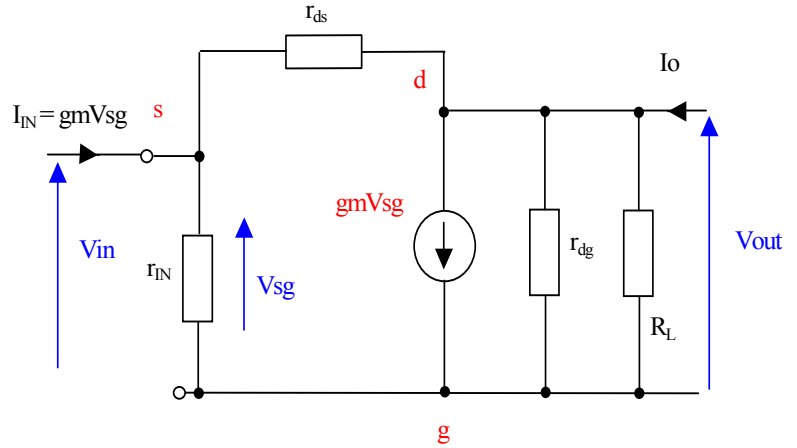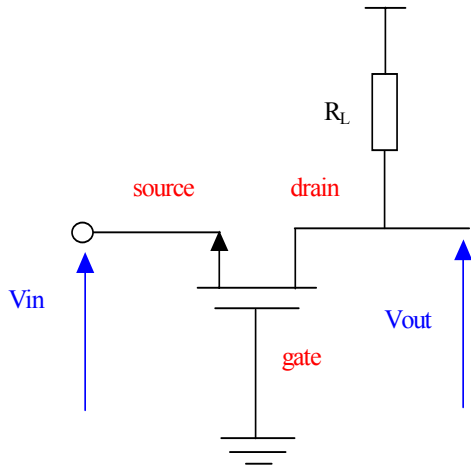

Voltage Gain A_v

$$A_v = \frac{V_o}{V_{IN}} \quad V_{IN} = V_{sg}$$

$$V_o = gmV_{sg}(r_{dg} // R_L) \quad A_v = gm \left(\frac{r_{dg} \cdot R_L}{r_{dg} + R_L} \right)$$

Input Resistance

$$R_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{V_{gs}}{gmV_{gs}} = \frac{1}{gm} = I_D \lambda$$

Output Resistance

As the source is low impedance ie close to ground for $R_{OUT} - r_{ds}$ appears to be connected across r_{ds} to ground.

$$R_{OUT} = \frac{V_o}{I_o} = r_{dg} // r_{ds}$$

Current Gain A_i

$$A_i = 1$$