

CpE358/CS381

**Switching Theory and
Logical Design**


Class 3

Today

- Fundamental concepts of digital systems (Mano Chapter 1)
- Binary codes, number systems, and arithmetic (Ch 1)
- Boolean algebra (Ch 2)
- **Simplification of switching equations (Ch 3)**
- Digital device characteristics (e.g., TTL, CMOS)/design considerations (Ch 10)
- Combinatoric logical design including LSI implementation (Chapter 4)
- Hazards, Races, and time related issues in digital design (Ch 9)
- Flip-flops and state memory elements (Ch 5)
- Sequential logic analysis and design (Ch 5)
- Synchronous vs. asynchronous design (Ch 9)
- Counters, shift register circuits (Ch 6)
- Memory and Programmable logic (Ch 7)
- Minimization of sequential systems
- Introduction to Finite Automata

Boolean Functions in Terms of Minterms

 - A logical function is TRUE if any of it's minterms are true:



- Algebraic manipulation of the literal expression of the function is one way to minimize it, manipulation of minterms is another

Two Variable Minterm Map

- Represent Boolean functions in terms of minterms in a Karnaugh map:

m_0	m_1
m_2	m_3

		y		\underline{y}
			0	1
x	0	$x'y'$	$x'y$	
	1	xy'	xy	

Two Variable Minterm Map

- Represent Boolean functions in terms of a Karnaugh map:

m_0	m_1
m_2	m_3

		y	\underline{y}
		0	1
x	0	$x'y'$	$x'y$
	1	xy'	xy

- Consider the XOR function

$$F(x, y) = x \oplus y = x'y + xy' = m_1 + m_2$$

		y		\underline{y}
			0	1
x	0			1
	1	1		

Two Variable Minterm Map

- Represent Boolean functions in terms of a Karnaugh map:

m_0	m_1
m_2	m_3

		y		\underline{y}
			0	1
x		0	$x'y'$	$x'y$
		1	xy'	xy

- Consider the XOR function

$$F(x, y) = x \oplus y = x'y + xy' = m_1 + m_2$$

		y		\underline{y}
			0	1
x		0		1
		1	1	

		y		\underline{y}
			0	1
x		0	0	1
		1	1	0

Set the non-asserted minterms to zero

Minimizing Function of Two Variables

		y		<u>y</u>	
		0		1	
x	0	x'y'	x'y		
	1	xy'	xy		

$$\begin{aligned}
 F(x, y) &= xy' + xy = m_2 + m_3 \\
 &= x(y' + y) \\
 &= x
 \end{aligned}$$

- Covering “adjacent” minterms with a single region defines the variables needed to represent the function

		y		<u>y</u>	
		0		1	
x	0	0	0		
	1	1	1		

Minimizing Function of Three Variables

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		yz		y	
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

- Minterms are numbered in Gray code order – adjacent minterms differ in only one variable
- If the function is asserted (i.e., TRUE) for both of these adjacent minterms, then the terms defined by those minterms do not depend on the variable that is changing between them

Three Variable Map

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		yz		y	
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

- Consider $F(x,y,z)=\Sigma(1,3,7)$

$$F(x, y, z) = m_1 + m_3 + m_7$$

$$\begin{aligned}
 F(x, y, z) &= x'y'z + x'yz + xyz \\
 &= x'y'z + x'yz + x'yz + xyz \\
 &= x'(y' + y)z + (x' + x)yz \\
 &= x'z + yz
 \end{aligned}$$

		yz		y	
		00	01	11	10
x	0	0	1	1	0
x	1	0	0	1	0
		z			

Diagram illustrating the Karnaugh map for $F(x,y,z) = \Sigma(1,3,7)$. The map shows the function values for all combinations of x, y, z . The function is 1 for the minterms m_1, m_3, m_7 and 0 otherwise. The map is used to derive the simplified expression $F(x,y,z) = x'z + yz$ by grouping the 1s. The group $x'z$ is highlighted in orange, and the group yz is highlighted in orange.

Three Variable Map

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		yz		y	
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

• Observations:

- All minterms must be covered
- Number of variables defining a sum term inversely proportional to number of minterms covered
- Number of sum terms required to define function equal to number of separate regions

→ Maximize region size

→ Minimize number of regions

		yz		y	
		00	01	11	10
x	0	0	1	1	0
x	1	0	0	1	0
		z			

Diagram illustrating a three-variable map with two regions circled in orange:

- A region circled in orange, labeled $x'z$, covers the cells $(x=0, y=0, z=1)$ and $(x=0, y=1, z=1)$.
- A region circled in orange, labeled yz , covers the cells $(x=0, y=1, z=1)$ and $(x=1, y=1, z=1)$.

Three Variable Map

- For a 3-variable map:
 - Covering 4 minterms with one 4-minterm region defines the function in terms of a single variable
 - Covering the same 4 minterms with 2 2-minterm regions defines the function in terms of two terms, each requiring two variables.

		yz		<u>y</u>	
		00	01	11	10
x	0	0	1	1	0
x	1	0	1	1	0

z

z

		yz		<u>y</u>	
		00	01	11	10
x	0	0	1	1	0
x	1	0	1	1	0

z

yz

y'z

Three Variable Map

- “Adjacency” sometimes exists in subtle ways:


- These four minterms are obviously adjacent to each other.

		yz		y	
		00	01	11	10
x	0	1	0	1	1
x	1	1	0	1	1
		z			


Three Variable Map

- “Adjacency” sometimes exists in subtle ways:

 
- These four minterms are obviously adjacent to each other.



 - But so are these, if we consider the map to wrap around on itself




Four Variable Map

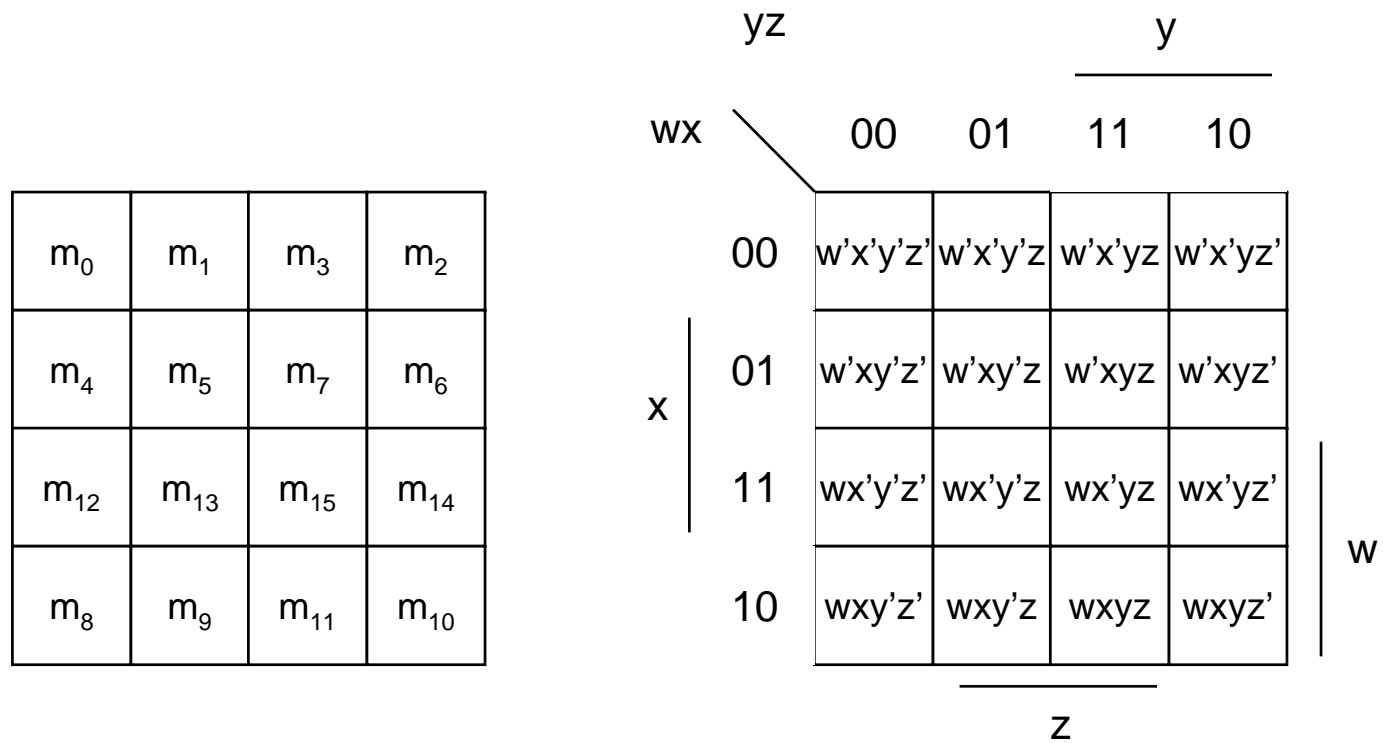

- The 4-variable map extends the concept of the 2- and 3-variable map

Minimizing Four Variable Map

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

 

- Minimize $F(w,x,y,z) = \Sigma(0,2,3,5,7,8,10,11,13,15)$
- $F(w,x,y,z) = xz + x'z' + yz$


Five Variable Map

		yz		<u>y</u>					
				00	01	11	10		
wx	x	00	m ₀	m ₁	m ₃	m ₂	w		
		01	m ₄	m ₅	m ₇	m ₆			
		11	m ₁₂	m ₁₃	m ₁₅	m ₁₄			
		10	m ₈	m ₉	m ₁₁	m ₁₀			
				<u>z</u>					
						v=0			

		yz		<u>y</u>					
				00	01	11	10		
wx	x	00	m ₁₆	m ₁₇	m ₁₉	m ₁₈	w		
		01	m ₂₀	m ₂₁	m ₂₃	m ₂₂			
		11	m ₂₈	m ₂₉	m ₃₁	m ₃₀			
		10	m ₂₄	m ₂₅	m ₂₇	m ₂₆			
				<u>z</u>					
						v=1			

- 5-variable map is extension of 4-variable map, adjacency must be considered between pairs of 4-variable maps

Minimizing Five Variable Map

 

- Minimize $F(v,w,x,y,z) = \Sigma(0,8,9,11,16,17,24,25,27,29,31)$
- $F(v,w,x,y,z) = wz + x'y'z' + vx'y'$

Six Variable Map

- Keeping track of what minterms are adjacent becomes tedious
- Ensuring the maximum coverage for each term is challenging
- 6-variable maps usable, but perhaps the design needs to be modularized instead

yz y

wx 00 01 11 10

00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

x

z

v=0

u=0

w

yz y

wx 00 01 11 10

00	m ₃₂	m ₃₃	m ₃₅	m ₃₄
01	m ₃₆	m ₃₇	m ₃₉	m ₃₈
11	m ₄₄	m ₄₅	m ₄₇	m ₄₆
10	m ₄₀	m ₄₁	m ₄₃	m ₄₂

x

z

v=1

w

yz y

wx 00 01 11 10

00	m ₀	m ₁	m ₃	m ₂
01	m ₄	m ₅	m ₇	m ₆
11	m ₁₂	m ₁₃	m ₁₅	m ₁₄
10	m ₈	m ₉	m ₁₁	m ₁₀

x

z

u=1

w

yz y

wx 00 01 11 10

00	m ₄₈	m ₄₉	m ₅₁	m ₅₀
01	m ₅₂	m ₅₃	m ₅₅	m ₅₄
11	m ₆₀	m ₆₁	m ₆₃	m ₆₂
10	m ₅₆	m ₅₇	m ₅₉	m ₅₈

x

z

w

Product of Sums – Covering 0's Instead of 1's

- A function of N variables, $F(v_1, v_2, \dots, v_N)$, can be represented by a Karnaugh map with 2^N cells. $(v_1, v_2, \dots, v_N) = (0, 0, \dots, 0), (0, 1, \dots, 0), \dots, (1, 1, \dots, 1)$
- $F()$, and its Karnaugh map have K minterms (1's) and $2^N - K$ maxterms (0's)
- If $K > 2^N - K$, it might be easier to cover the maxterms rather than the minterms.
E.g.:

		yz						yz			
	wx	00	01	11	10		wx	00	01	11	10
	00	1	1	1	0		00	1	1	1	0
	01	0	1	1	1		01	0	0	1	1
	11	1	1	1	1		11	1	1	1	1
	10	1	0	1	1		10	1	0	1	1
		v=0						v=1			

Product of Sums – Covering 0's Instead of 1's

	yz				
wx		00	01	11	10
00		1	1	1	0
01		0	1	1	1
11		1	1	1	1
10		1	0	1	1

v=0

	yz				
wx		00	01	11	10
00		1	1	1	0
01		0	0	1	1
11		1	1	1	1
10		1	0	1	1

v=1

$F(v,w,x,y,z)'$ has 4 terms

$$F(v,w,x,y,z)' = w'x'yz' + w'xy'z' + vw'xy' + wx'y'z$$

	yz				
wx		00	01	11	10
00		1	1	1	0
01		0	1	1	1
11		1	1	1	1
10		1	0	1	1

v=0

	yz				
wx		00	01	11	10
00		1	1	1	0
01		0	0	1	1
11		1	1	1	1
10		1	0	1	1


v=1

$F(v,w,x,y,z)$ has 7 terms

$$F(v,w,x,y,z) = w'x'y' + yz + v'xz + xy + wx + wy'z' + wy$$

Don't Care Conditions

 - Sometimes, not all possible output values are specified in system design, e.g.:



- Consider the horizontal line in the middle of the display (segment g):
 $F_g(w,x,y,z) = \Sigma(2,3,4,5,6,8,9)$, but we don't care what happens to minterms 10, 11, 12, 13, 14, or 15, since the display will not be sent those states

Don't Care Conditions

wx\yz	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	X	X	X	X
10	1	1	X	X

$$F(w,x,y,z) = xy + xz' + xy' + w$$

wx\yz	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	X	X	X	X
10	1	1	X	X

$$F'(w,x,y,z) = w'x'y' + xyz$$



- We are free to assign whatever values we want to for minterms 10, 11, 12, 13, 14, and 15. Assign them a value X to indicate they may be covered, or not, whichever results in the simplest expression

Logical Completeness

1. AND, OR, NOT can implement any Boolean function – They form a “Logically Complete” set of operators



Logical Completeness

  1. AND, OR, NOT can implement any Boolean function – They form a “Logically Complete” set of operators
2. NAND can implement AND and NOT directly:




Logical Completeness

  1. AND, OR, NOT can implement any Boolean function – They form a “Logically Complete” set of operators
2. NAND can implement AND and NOT directly:



 
3. NAND can implement OR by DeMorgan's Law:



→ NAND is logically complete (so is NOR)


NAND Implementation of Sum of Products

- Consider an arbitrary Sum of Products:

 


NAND Implementation of Sum of Products

 - Consider an arbitrary Sum of Products:
- Add inversions at each term. This is allowed, since $(x')' = x$





NAND Implementation of Sum of Products

 - Consider an arbitrary Sum of Products:
- Add inversions at each term. This is allowed, since $(x')' = x$
- Convert output gate by DeMorgan's Law:



Wired-AND and Open Collector

 
 
- Typical TTL “totem-pole” output circuit:




- TTL with Open Collector output circuit

Wired-AND and Open Collector

  - Each gate asserts 0-output – with no pull-up transistor, no gate can cause output to become “1.” External “pull-up” resistor needed
- Used for wiring multiple devices together on bus, but speed is limited





XOR Function

 

Exclusive OR
(XOR)

		x	
	\oplus	0	1
y	0	0	1
	1	1	0

$$x \oplus y = x' \cdot y + x \cdot y'$$

  


$$w \oplus x \oplus y \oplus z = ((w \oplus x) \oplus y) \oplus z = (w \oplus x) \oplus (y \oplus z)$$

- XOR applications:

- Addition, parity, data scramblers, encryption, shift register sequences

N-input XOR

 

$$w \oplus x \oplus y \oplus z = ((w \oplus x) \oplus y) \oplus z = (w \oplus x) \oplus (y \oplus z)$$

- These three designs are all logically equivalent (for static signals)

Hard To Minimize Functions

- Consider this map:

		yz			
wx		00	01	11	10
00		1	0	1	0
01		0	1	0	1
11		1	0	1	0
10		1	0	1	1

v=0

		yz			
wx		00	01	11	10
00		0	1	0	1
01		1	0	1	0
11		0	1	0	1
10		1	0	1	1

v=1

Isolated minterms
cannot be grouped

Hard To Minimize Functions

- Consider this map:

Cover part of the map with XOR

Treat the rest normally

		yz						yz			
		00	01	11	10			00	01	11	10
wx	00	1	0	1	0	wx	00	0	1	0	1
	01	0	1	0	1		01	1	0	1	0
	11	1	0	1	0		11	0	1	0	1
	10	1	0	1	1		10	1	0	1	1
v=0						v=1					

$$F(v, w, x, y, z) = (wx')' \cdot (v \oplus w \oplus x \oplus y \oplus z) + wx' y' z' + wx' y$$

Hard To Minimize Functions


- Consider this map:

Cover part of the map with XOR

Treat the rest normally

		yz						yz			
		wx	00	01	11			10	wx	00	01
	00	1	0	1	0	00	0	1	0	1	
	01	0	1	0	1	01	1	0	1	0	
	11	1	0	1	0	11	0	1	0	1	
	10	1	0	1	1	10	1	0	1	1	
		v=0						v=1			
 
$$F(v, w, x, y, z) = (wx')' \cdot (v \oplus w \oplus x \oplus y \oplus z) + wx' y' z' + wx' y$$



Summary

- Fundamental concepts of digital systems (Mano Chapter 1)
- Binary codes, number systems, and arithmetic (Ch 1)
- Boolean algebra (Ch 2)
- **Simplification of switching equations (Ch 3)**
- Digital device characteristics (e.g., TTL, CMOS)/design considerations (Ch 10)
- Combinatoric logical design including LSI implementation (Chapter 4)
- Hazards, Races, and time related issues in digital design (Ch 9)
- Flip-flops and state memory elements (Ch 5)
- Sequential logic analysis and design (Ch 5)
- Synchronous vs. asynchronous design (Ch 9)
- Counters, shift register circuits (Ch 6)
- Memory and Programmable logic (Ch 7)
- Minimization of sequential systems
- Introduction to Finite Automata

Homework 3 – due in Class 5

As always, show all work:

- Problems 3-5, 3-7, 3-18.
- Design a BCD to seven segment decoder for any 2 of the 6 segments (a-f) we did not discuss in class.