

## EMITTER FOLLOWER or VOLTAGE FOLLOWER

PHYS321

The transistor can be configured in a unity gain situation. This is called the emitter follower or voltage follower.  $V_{out}$  is taken from the emitter junction and follows the input voltage  $V_{in}$ . In essence it is a current amplifier with unit gain.

The input impedance  $R_{in}$  is high and  $R_{out}$  is proportional to the driving source's output impedance  $R_{source}$


$$V_E = V_B - 0.6V \quad \text{or} \quad \delta V_E = \delta V_B \quad \mathbf{V_{out} \sim V_{in}} \quad (1)$$

$$\mathbf{I_E = \delta V_E / R_E = \delta V_B / R_E} \quad (2)$$

$$\mathbf{I_E = I_C + I_B = \beta I_B + I_B = (1 + \beta) I_B = \delta V_B / R_E} \quad (3)$$

$$\text{Looking in to the base} \quad \mathbf{R_{in} = R_B = \delta V_B / I_B = I_E R_E / I_B = R_E (1 + \beta) \sim \beta R_E} \quad (4)$$
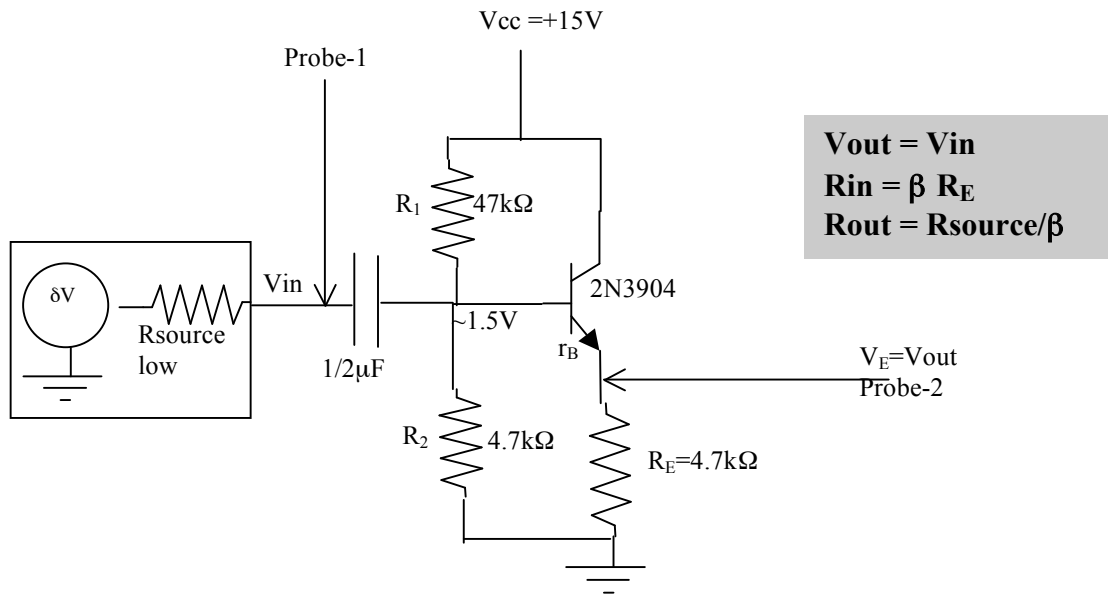
$$\text{Looking out from the emitter} \quad \mathbf{R_{out} = R_1 + (\beta / R_{source} + 1 / R_E)^{-1} \sim R_{source} / \beta} \quad (5)$$



Construct the Voltage follower circuit. Drive it with the smallest sine wave from your generator at  $f = 1\text{kHz}$ . Measure  $V_{in}$  (Vpp) on your oscilloscope channel-1. Measure  $V_{out}$  (Vpp) on channel-2 of your oscilloscope. Record these values.

$V_{in} =$  \_\_\_\_\_

$V_{out} =$  \_\_\_\_\_

Check the frequency response of the voltage follower by sweeping the frequencies between 10Hz and 1MHz.

$f$ (Hz)	10	100	1K	10K	100K	1M
V <sub>out</sub> (V)						
V <sub>in</sub> (V)						
gain						
$\Delta\phi$						

**Question#1-** Does the output signal replicate the input signal? Explain why or why not in terms of transistor function.

**Question#2-** Is there a phase change between input and output signal?

**Question#3-** What is the input and output impedance of your emitter-follower?

R<sub>in</sub> = \_\_\_\_\_

R<sub>out</sub> = \_\_\_\_\_

## TRANSISTOR SWITCH

PHYS321


One of the main uses of a discrete transistor is that of a switch. Often one needs to control a large current source from a small current source. We create a high impedance source by placing a  $10\text{k}\Omega$  resistor in series with our  $50\Omega$  signal generator.

Thus a high impedance source (low current) drives a low impedance output LED. On the positive half-cycle the transistor conducts  $I_C > 0$  and the LED is turned on. On the negative half-cycle the transistor cuts off and the LED goes off.

The LED takes about 1.6 volts to turn so about 10.4 V is dropped across the  $470\Omega$   $R_C$ .  $R_C$  limits the current through the LED or it may burn out if the current is too high.

$$I_B = 5\text{V}/10\text{k}\Omega = 0.5\text{mA} \quad (1)$$
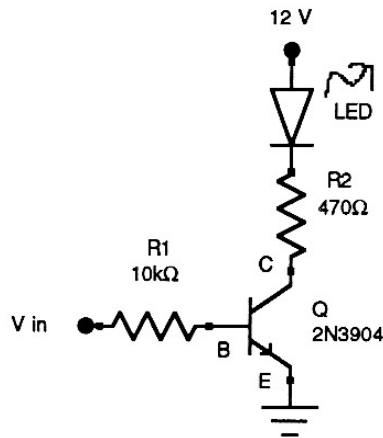
$$I_C = (12 - 1.6)/470\Omega = 10.4\text{V}/470\Omega = 22\text{mA} \quad (2)$$



(1) Construct the transistor switch circuit with your 2N3904.

(2) Apply a +DC voltage to the input  $V_{in} = 0\text{-}5\text{V}$  nominal value to determine when the LED just turns on. Record this voltage. Then increase the voltage to  $\sim 5\text{V}$ , the LED should be ON.

$$V_{ON} = \underline{\hspace{2cm}}$$

(3) Measure the voltage drops along the Collector-Emitter-Ground path.

$$V_{CC} = +12\text{ V} \quad \Delta V_{LED} = \underline{\hspace{2cm}} \text{ V} \quad \Delta V_{R2} = \underline{\hspace{2cm}} \text{ V}$$

$$\Delta V_{2N3904} = \underline{\hspace{2cm}} \text{ V}$$

(4) Do the individual drops and total correspond to what you expect? Calculate  $I_C$  from your measurement as in Eq (2).

$$I_C = \underline{\hspace{2cm}} \text{ A}$$

(5) Apply a  $10\text{Vpp}$  sine wave to  $V_{in}$ . Explain the LED behavior.