
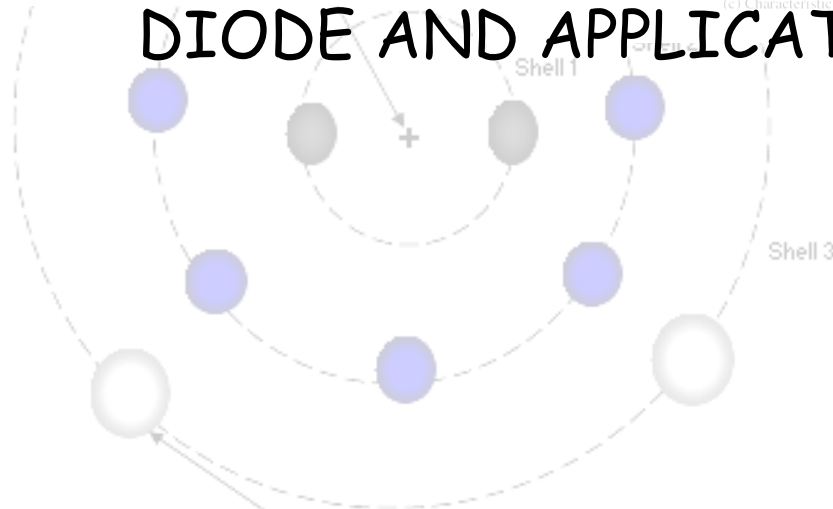
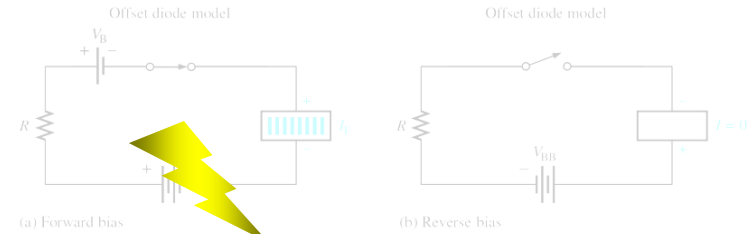



Electronic Devices

CHAPTER 2B:

DIODE AND APPLICATIONS

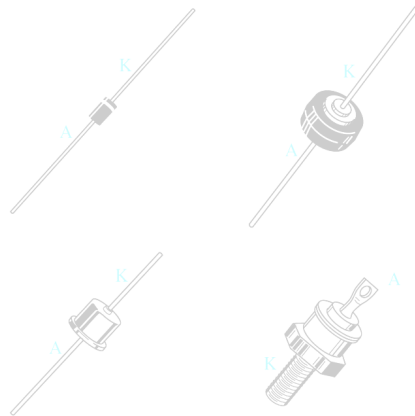


Negatively charged electrons orbit the nucleus in discrete energy levels.

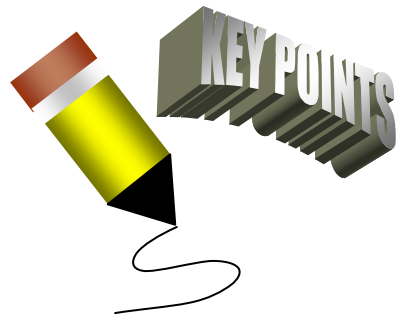

CHAPTER 2B: OBJECTIVES



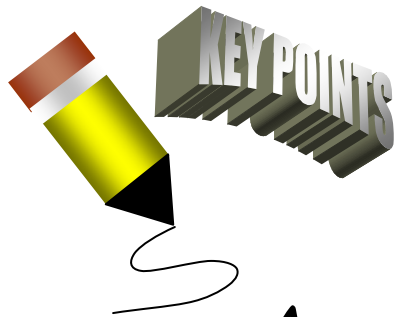- Analyze the operation of 3 basic types of rectifiers
- Describe the operation of rectifier filters and IC regulators
- Analyze the operation of diode limiters and clampers





HALF WAVE RECTIFIERS

Electronic Devices 1

- A rectifier is an electronic circuit that converts AC into pulsating DC.
- The voltage conversion process is known as half-wave rectification.
- When the sinusoidal input voltage goes positive, the diode is forward-biased and conducts current to the electrical load (resistor in **Figure 2-15(a)**)

FIGURE 2-15 Operation of half-wave rectifier. The diode is considered ideal.

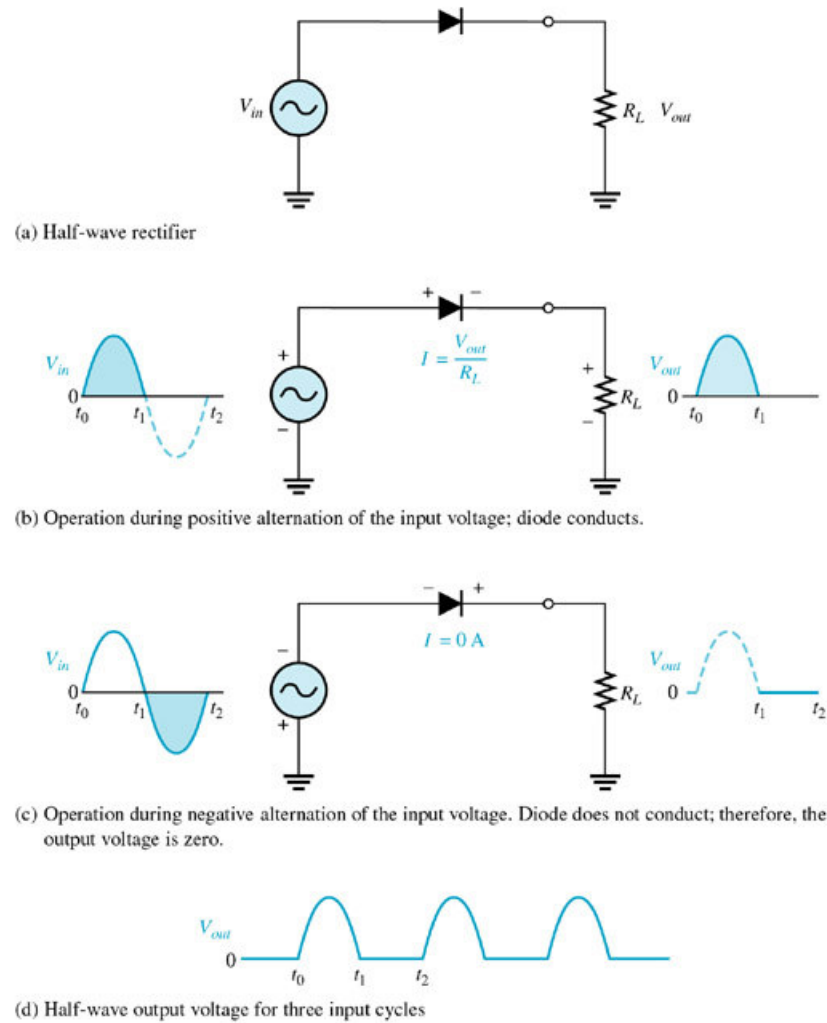

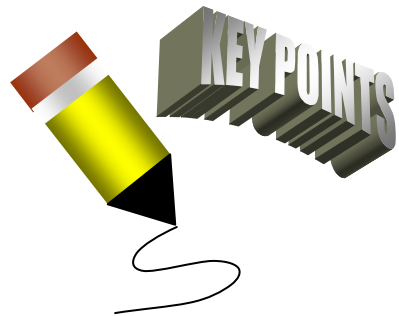


HALF WAVE RECTIFIERS...

- The output voltage is equal to the peak voltage less one diode drop.

$$\text{EQ1: } V_p(\text{out}) = V_p(\text{in}) - 0.7\text{V}$$

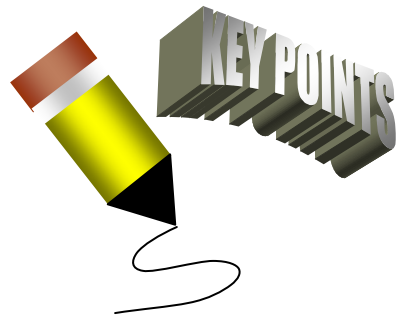
- The current produces a voltage across the load, which has the same shape as the positive half-cycle of the input voltage.



HALF WAVE RECTIFIERS...

Electronic Devices 1

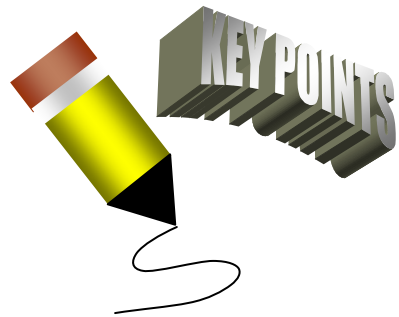- In working with diode circuits, it is sometimes practical to neglect the diode drop when the peak value is much greater than the barrier potential.
- This analysis technique is equivalent to the using the Ideal diode model for electronic product diagnostics and validation.



FULL WAVE RECTIFIERS

- The difference between Full Wave and Half wave rectification is the full wave rectifier allows unidirectional current to the load during the entire input cycle.
- The half wave rectifier allows current only during one-half of the cycle.
- The result of the full wave rectification is a dc output voltage that pulsates every half cycle of the input. (See **Figure 2-18.**)

FIGURE 2-18 Full-wave rectification.



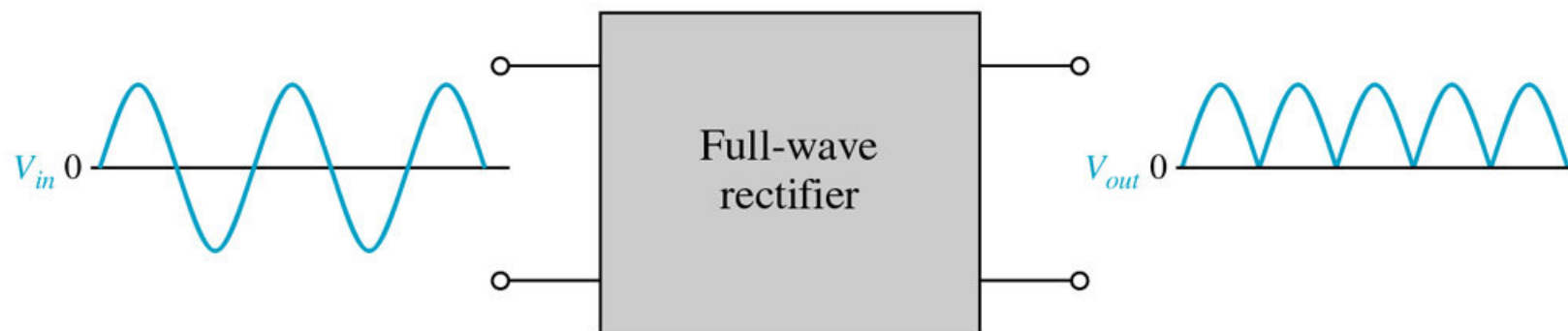


FIGURE 2-16

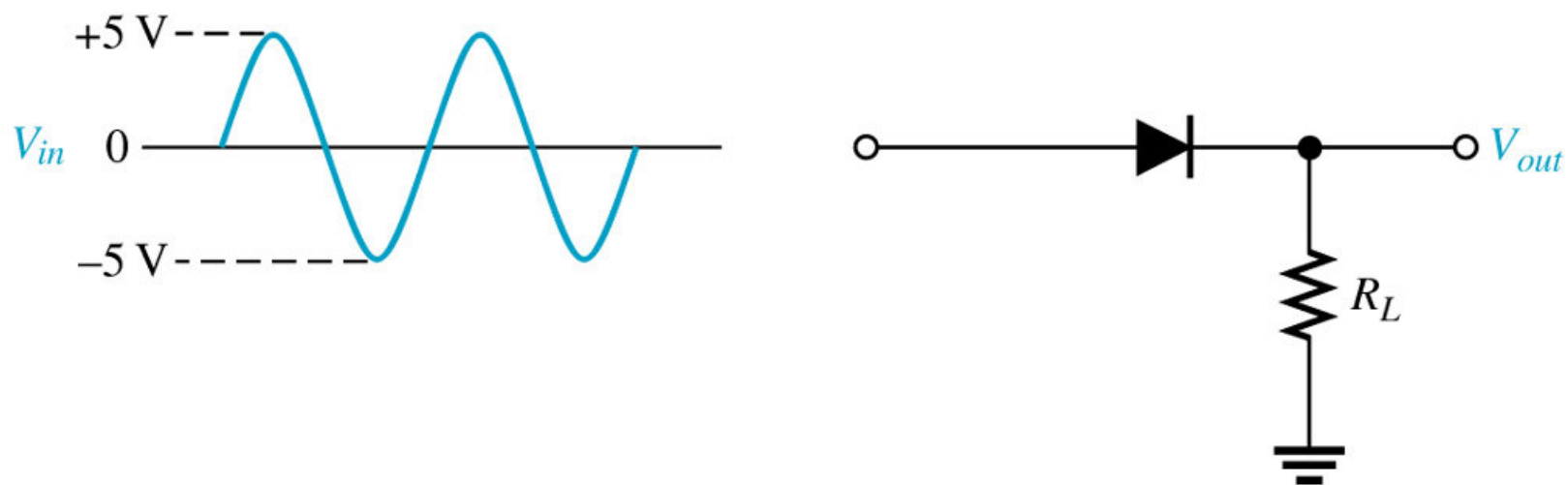


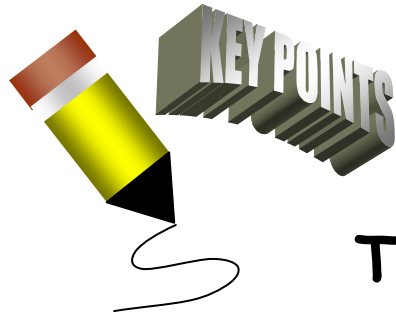


THE CENTER-TAPPED FULL WAVE RECTIFIER

- The center-tapped (CT) full wave rectifier uses 2 diodes connected to the secondary of a center-tapped transformer (See **Figure 2-19**).
- The input signal is coupled through the transformer (AC Electronics) to the secondary.
- Half of the total secondary voltage appears between the center tap and each of the secondary windings as shown in **Figure 2-19**.


FIGURE 2-19 A center-tapped (CT) full-wave rectifier.

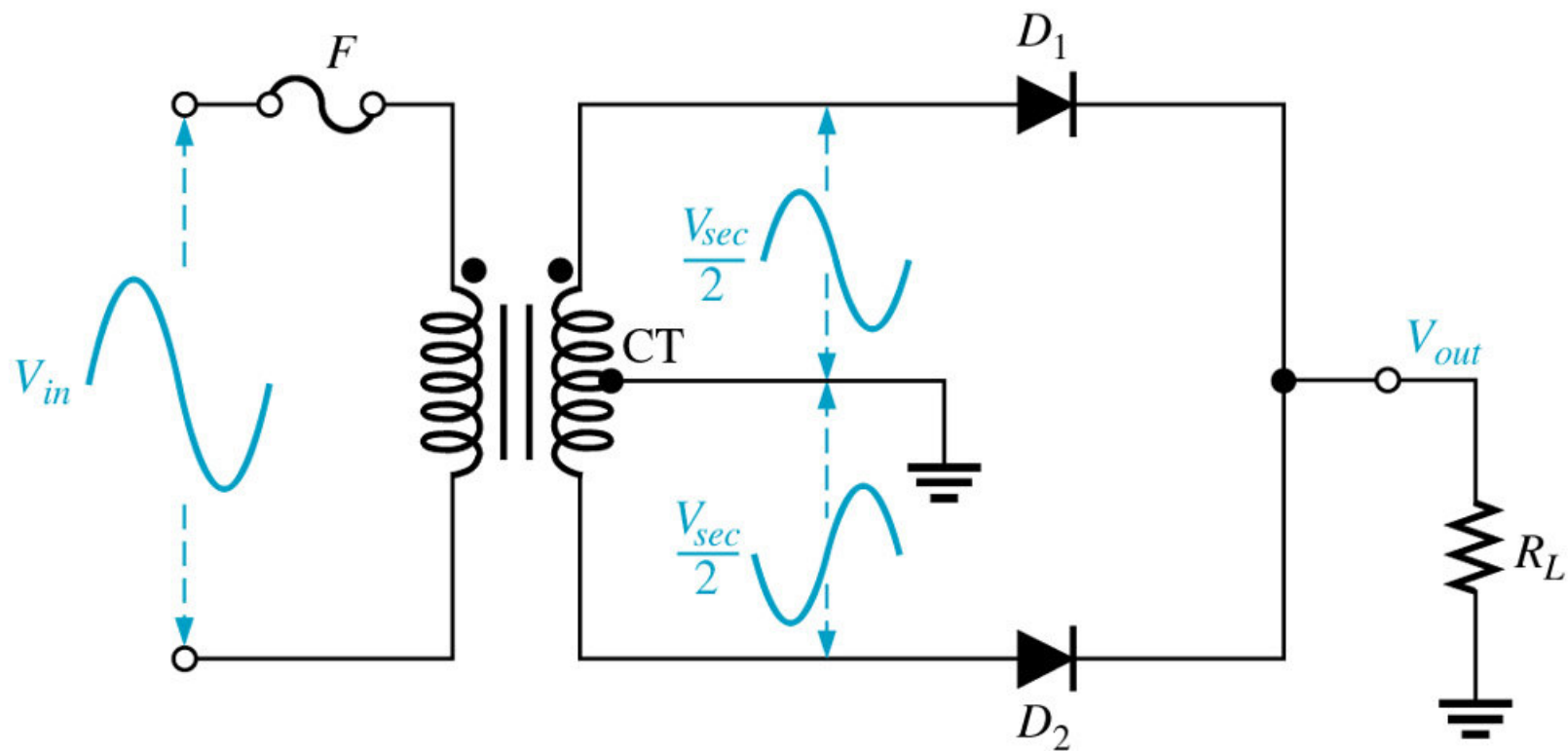

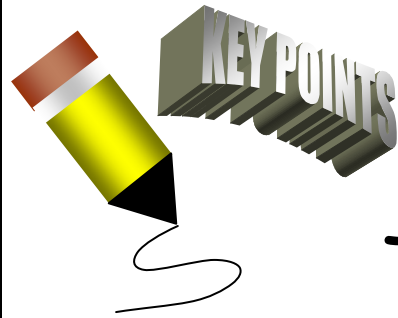

EFFECTS OF THE TURN RATIO ON THE FULL WAVE OUTPUT VOLTAGE


- If the turns ratio of the transformer is 1, the peak value of the rectified output equals half the peak value of the primary input voltage less one diode drop.
- Value occurs because half of the input voltage appears across each half of the secondary voltage.
- In order to obtain a peak output voltage equal to the peak input voltage (less the barrier potential), a step up transformer with a turns ratio of 2 (1:2) is used.

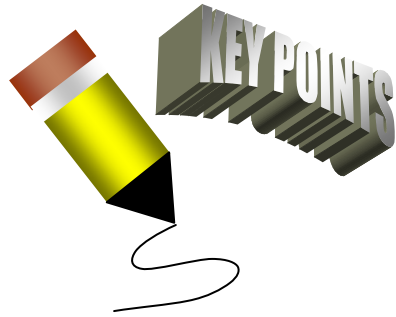

PEAK INVERSE VOLTAGE

- Each diode in the full wave rectifier is alternatively forward-biased and then reversed biased.
- The maximum reverse voltage that each diode must withstand is the peak value of the total secondary voltage (V_{sec}).
- The peak inverse voltage either diode in the center tapped full wave rectifier is:


$$\text{EQ2: PIV} = V_p(\text{out})$$

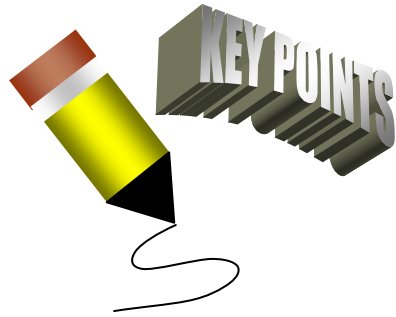


BRIDGE RECTIFIERS

- The bridge rectifier uses 4 diodes as shown in **Figure 2-23**.
- The most popular arrangement for power supplies because it does not require a center-tapped transformer.
- The four diodes are available in a single package, already wired in a bridge configuration.
- The bridge rectifier is a type of full wave rectifier because each half of the sine wave contributes to the output.


FIGURE 2-23 Operation of the full-wave rectifier. Conducting paths in the secondary are shown in color.

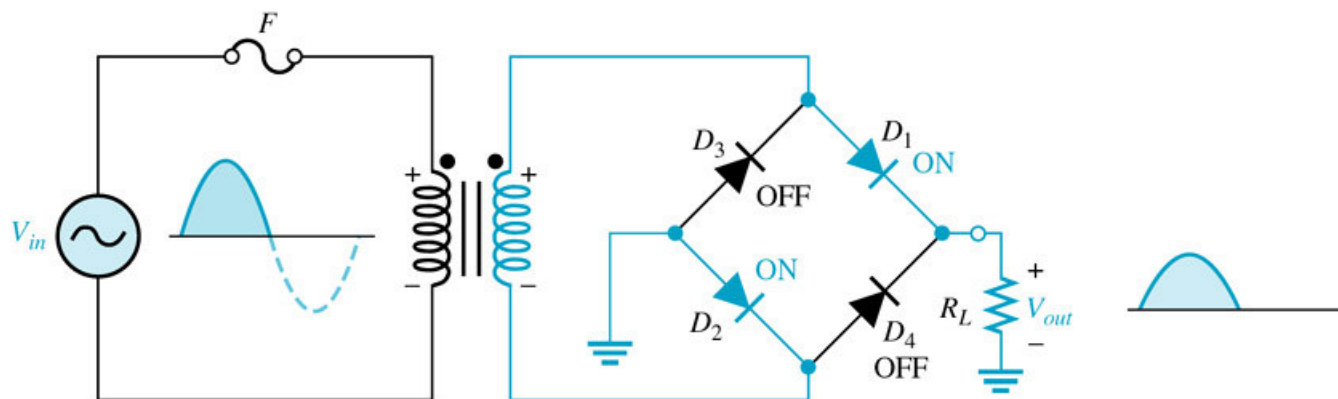

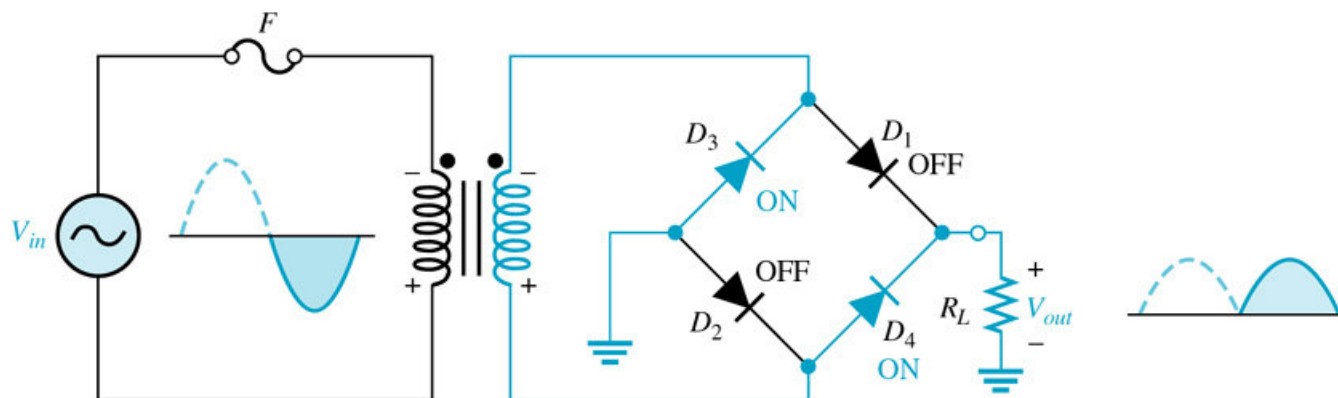(a) During positive half-cycle of the input, D_1 and D_2 are forward-biased and conduct current. D_3 and D_4 are reverse-biased.



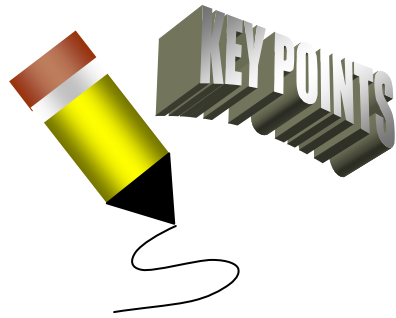(b) During negative half-cycle of the input, D_3 and D_4 are forward-biased and conduct current. D_1 and D_2 are reverse-biased.




BRIDGE OUTPUT VOLTAGE

- Neglecting the diode drops, the total secondary voltage, V_{sec} appears across the electrical load.

$$\text{EQ3: } V_{out} = V_{sec}$$

- If these diode drops are taken into account, the output voltage (with Si diodes) is:
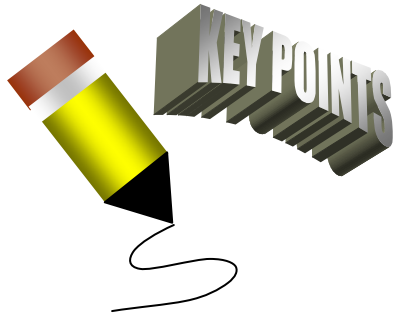
$$\text{EQ4: } V_{out} = V_{sec} - 0.7V$$



PEAK INVERSE VOLTAGE (PIV)

- When D_1 and D_2 are forward bias, the reverse voltage is across D_3 and D_4 .
- Visualizing D_1 and D_2 as shorts (ideally), the PIV is equal to the peak secondary voltage.


$$\text{EQ5: PIV} = V_p(\text{out})$$




CAPACITOR-INPUT FILTER

- A half wave rectifier with a capacitor input filter is shown in **Figure 2-24**.
- During the positive first quarter-cycle of the input, the diode is forward biased, allowing the capacitor to charge to within a diode drop of the input peak.
- When the input begins to decrease below its peak, the capacitor retains its charge and the diode becomes reverse bias.
- During the remaining part of the cycle and the beginning of the next cycle, the capacitor can discharge only through the load resistance at a rate determined by the RC time constant.


FIGURE 2-24 Operation of a half-wave rectifier with a capacitor-input filter.

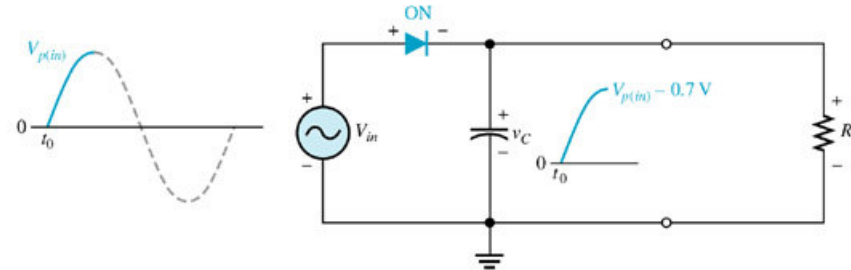

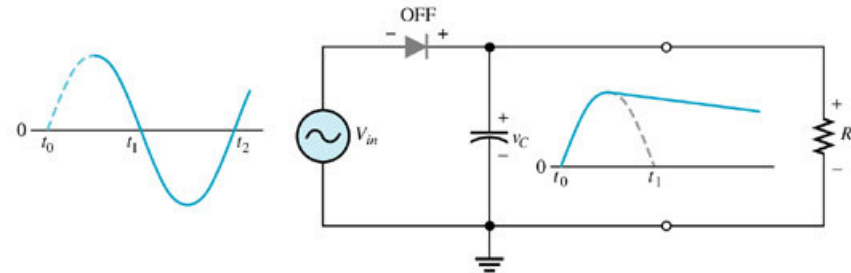
(a) Initial charging of capacitor (diode is forward-biased) happens only once when power is turned on.



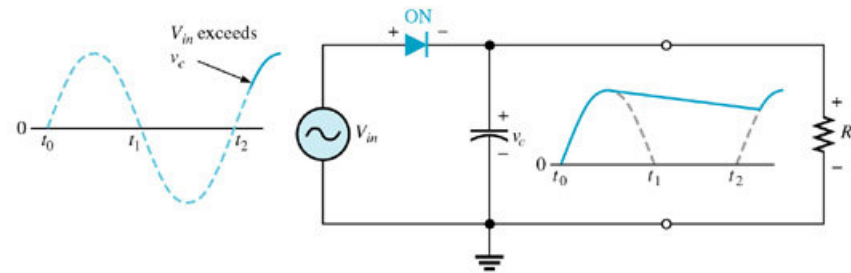(b) The capacitor discharges through R_L after peak of positive alternation when the diode is reverse-biased. This discharging occurs during the portion of the input voltage indicated by the solid colored curve.



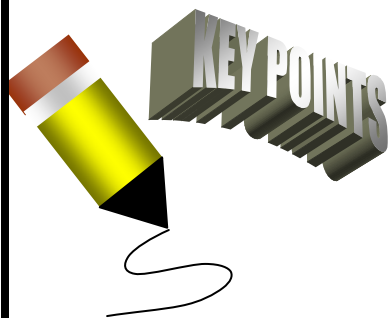
(c) The capacitor charges back to peak of input when the diode becomes forward-biased. This charging occurs during the portion of the input voltage indicated by the solid colored curve. Notice that the diode is not forward-biased on the second cycle until the capacitor voltage is overcome.




RIPPLE VOLTAGE

- The variation in the capacitor voltage due to the charging and discharging is called the **ripple voltage**.
- The smaller the ripple voltage, the better the filtering action.
- For a given input frequency, the output frequency of a full wave rectifier is twice that of a half wave rectifier.
- As a result, a full wave rectifier is easier to filter because of the shorter time between peaks.

FIGURE 2-25 Comparison of ripple voltages for half-wave and full-wave rectifier outputs with the same filter capacitor and derived from the same sinusoidal input.

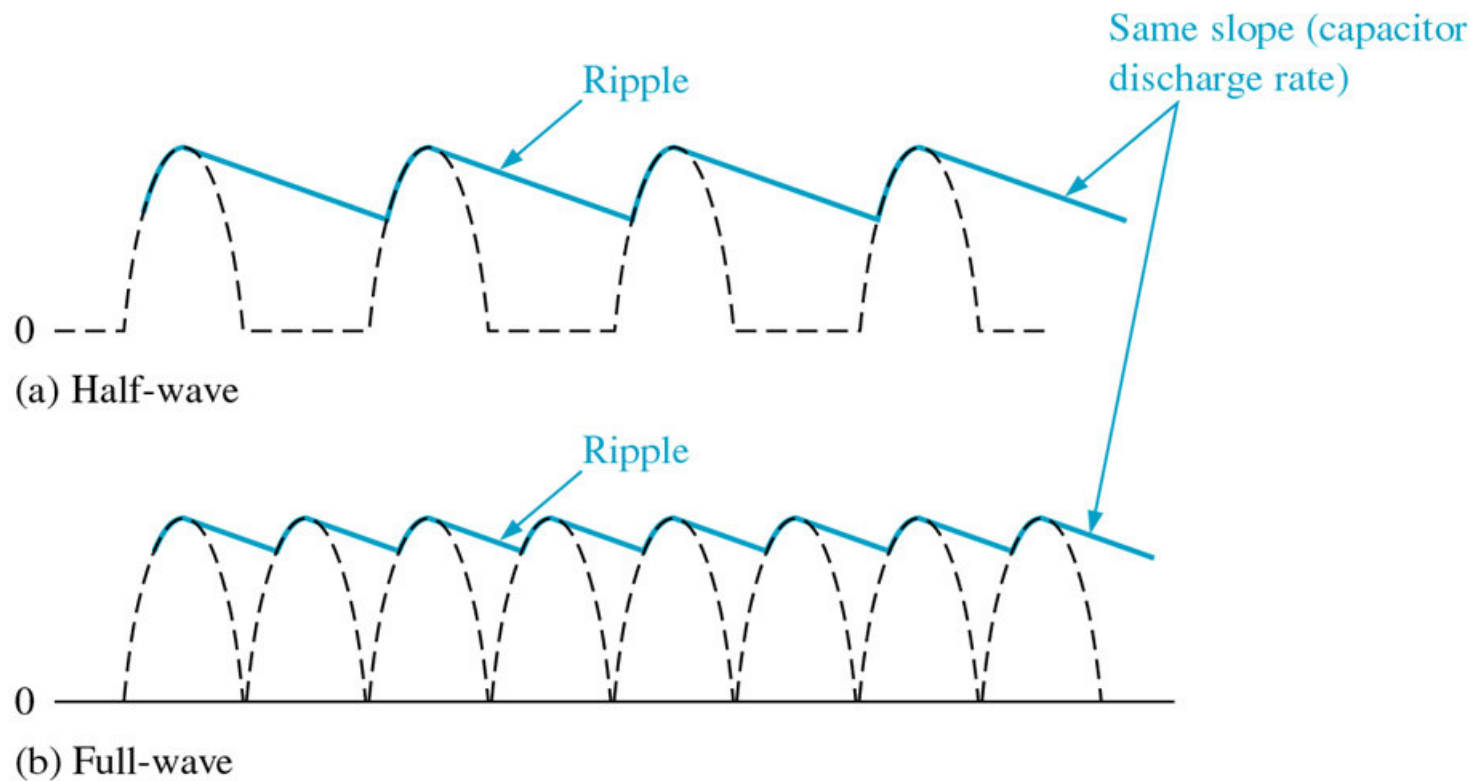


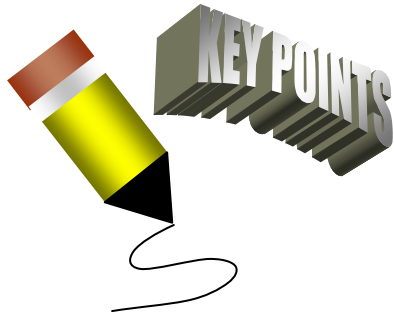


SURGE CURRENT IN THE CAPACITOR INPUT FILTER

- When the power is first applied to a power supply, the filter capacitor is uncharged..
- At the instant the switch is closed, voltage is connected to the rectifier and the uncharged capacitor appears as a short.
- This case is illustrated for a bridge circuit in **Figure 2-26(a)**.
- An initial surge of current is produced through the forward-biased diodes.


FIGURE 2-26 Surge current in a capacitor-input filter follows the path drawn in color.

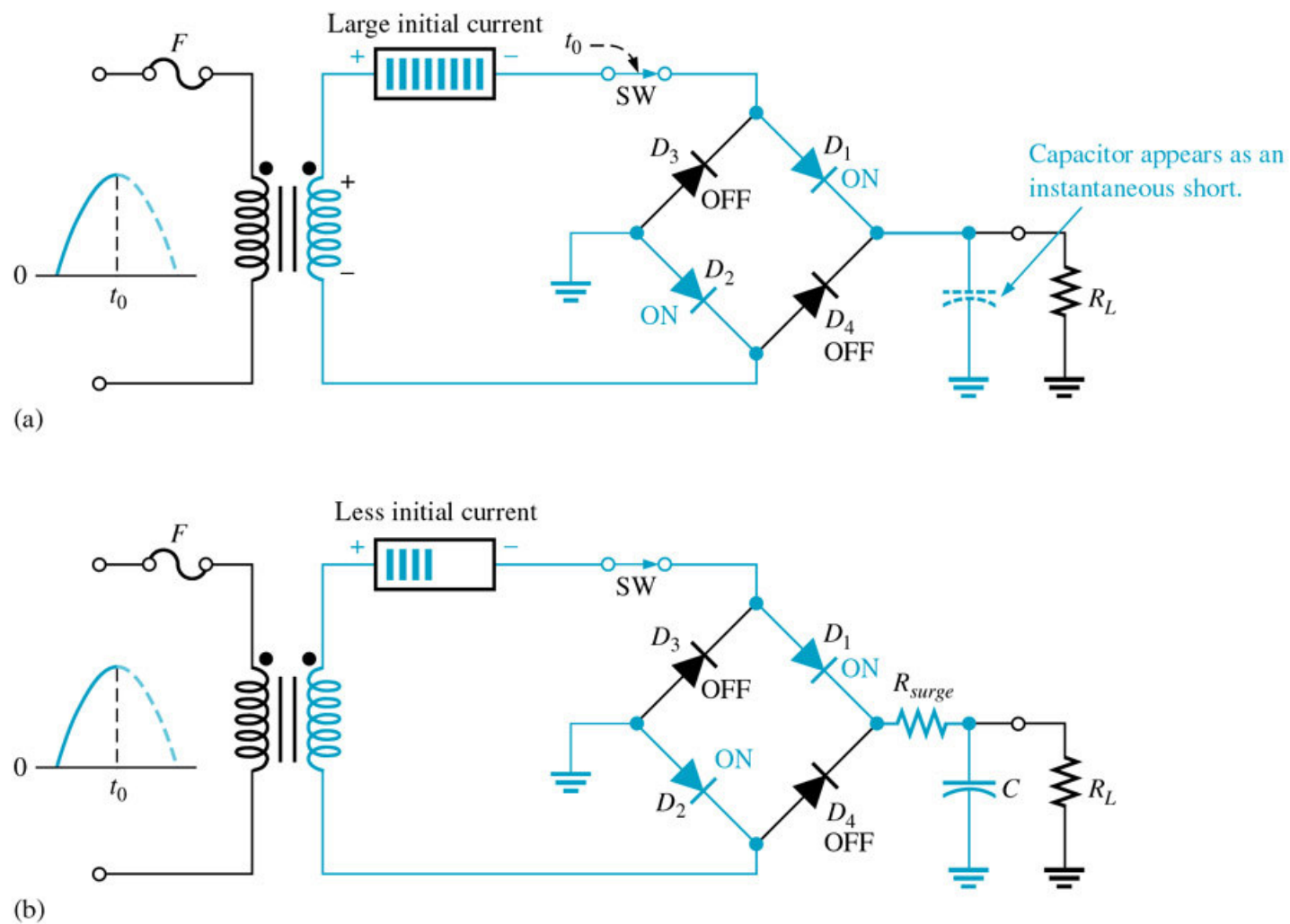

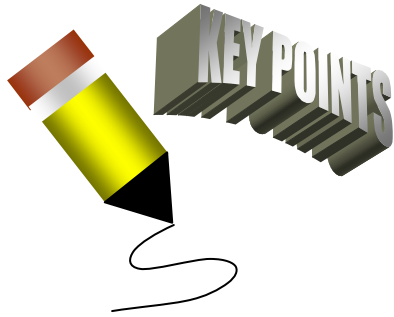

SURGE CURRENT IN THE CAPACITOR INPUT FILTER...

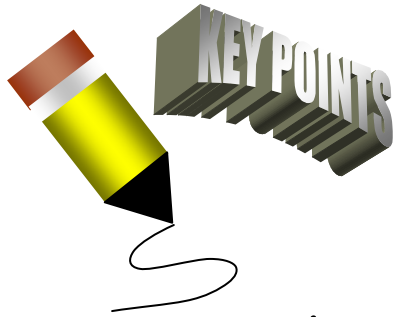
- It is possible that the surge current could destroy the diodes, for this reason a surge-limiting resistor R_{surge} , is sometimes connected. (See **Figure 2-26(b)**).
- The value of this resistor must be small to avoid a significant voltage drop across it.
- The diode must have a forward current rating that can handle the momentary surge of current.



IC REGULATORS

- The most effective filter is a combination of a capacitor-input filter with an IC regulator.
- In general, an IC (Integrated Circuit) is a complete functional circuit constructed on a single, tiny chip of silicon.
- An integrated circuit regulator is an IC that is connected to the output of rectifier and maintains a constant output voltage or current despite changes in the input.


FIGURE 2-27 The 7800 series three-terminal fixed positive voltage regulators.

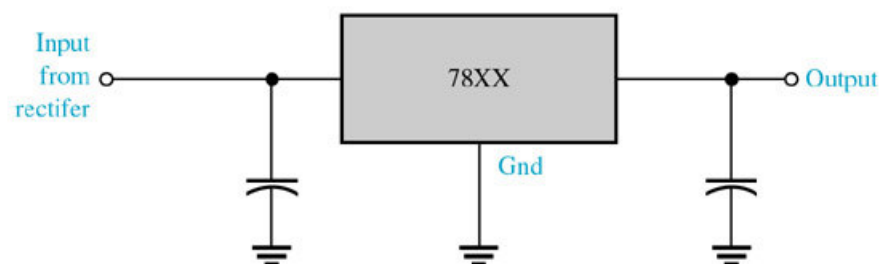

(a) Standard configuration



Type number	Output voltage
7805	+5.0 V
7806	+6.0 V
7808	+8.0 V
7809	+9.0 V
7812	+12.0 V
7815	+15.0 V
7818	+18.0 V
7824	+24.0 V

(b) The 7800 series

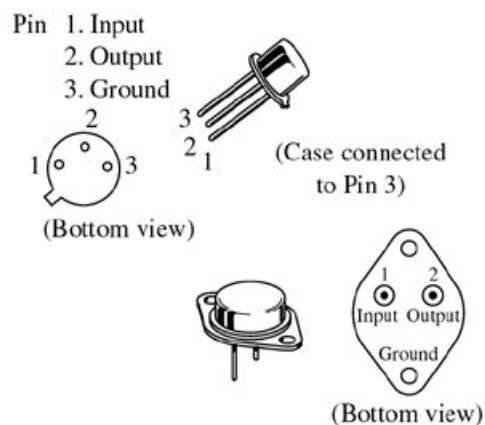

Pins 1 and 2 are electrically isolated from case.
Case is third electrical connection.

(c) Typical metal and plastic packages

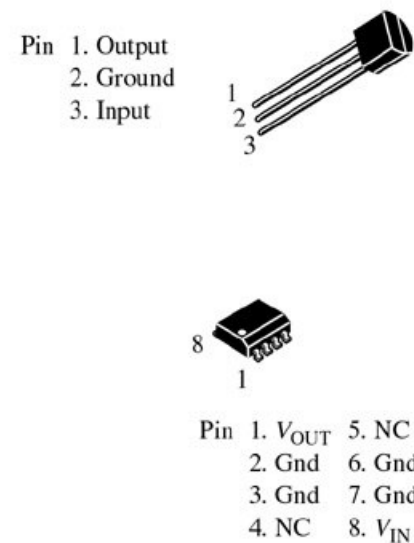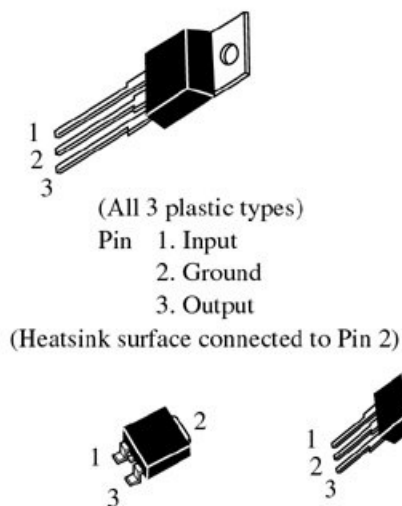



IC REGULATORS...

- Three terminal regulators designed for a fixed output voltage require only external capacitors to complete the regulation portion of the power (See **Figure 2-27(a)**).
- Filtering is accomplished by a large-value capacitor between the input voltage and ground.
- Sometimes a second smaller-value input capacitor is connected in parallel, especially if the filter capacitor is not close to the IC regulator to prevent transients and internal oscillation.

FIGURE 2-28 A basic +5.0 V(**fixed**) power supply.

IC REGULATORS: 7805


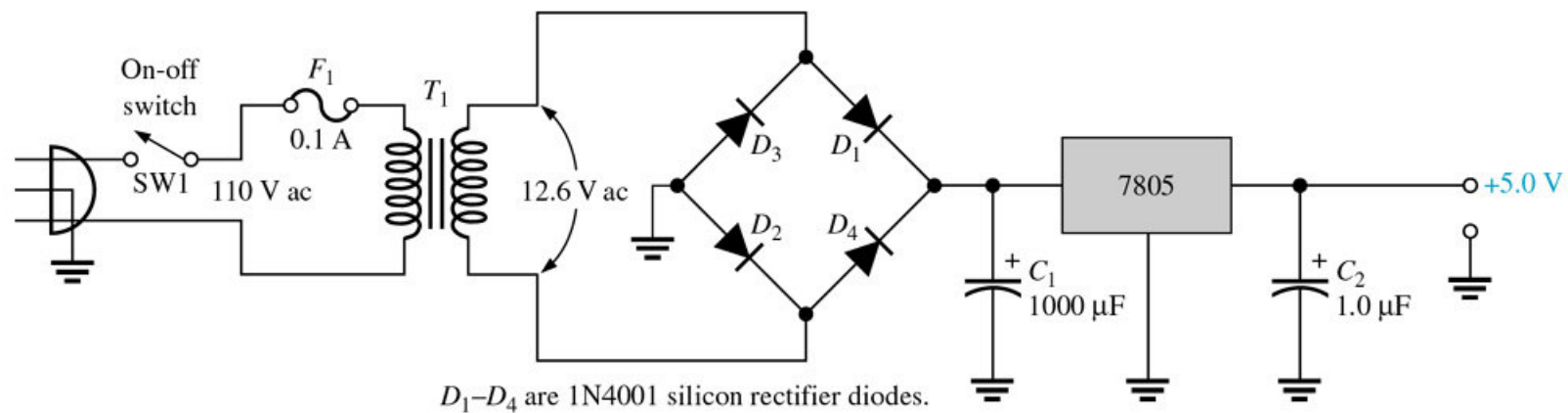


FIGURE 2-29 A basic power supply with a **variable** output voltage (from 1.25 V to 6.5V).


IC REGULATORS: LM317

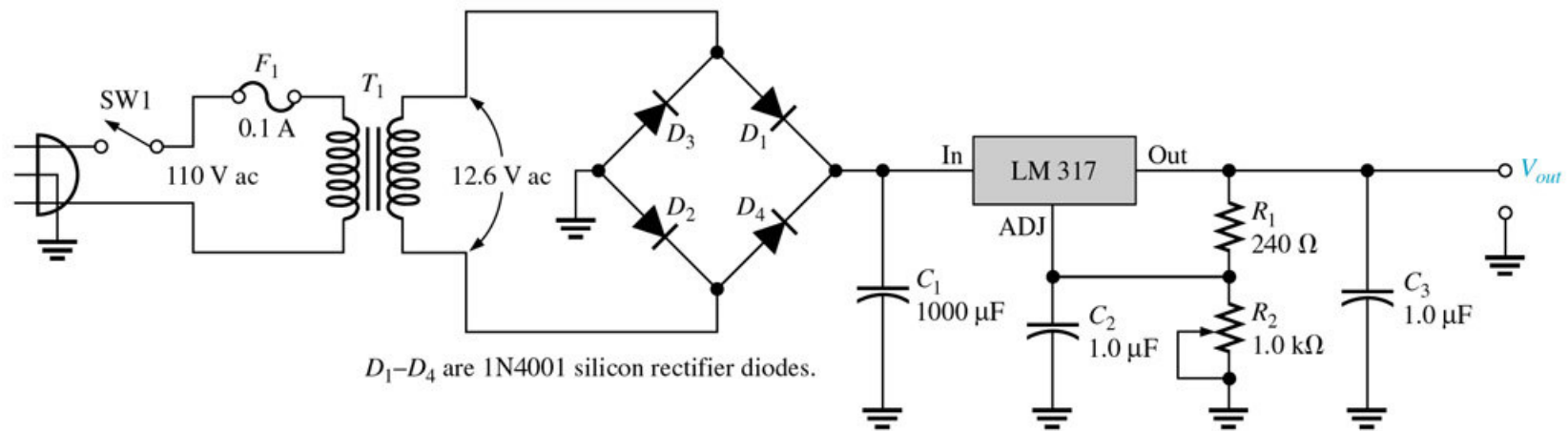



DIODE LIMITING AND CLIPPING CIRCUITS

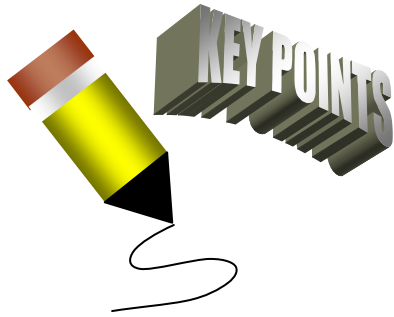- Diode circuits, called limiters, or clippers are sometimes used to clip off portions of the signal voltages above or below certain levels.
- Another type of diode circuit, called a clamper, is used to restore a dc level to an electrical signal.




DIODE LIMITERS


Diode Limiter is an electronic circuit that limits or clips off the positive or negative part of the input signal See **Figures 2-30(a) and (b)**.

- The negative or positive signal limiting function is based on if the diode is wired in a forward or reverse biased mode .


FIGURE 2-30 Diode limiting (clipping circuits).

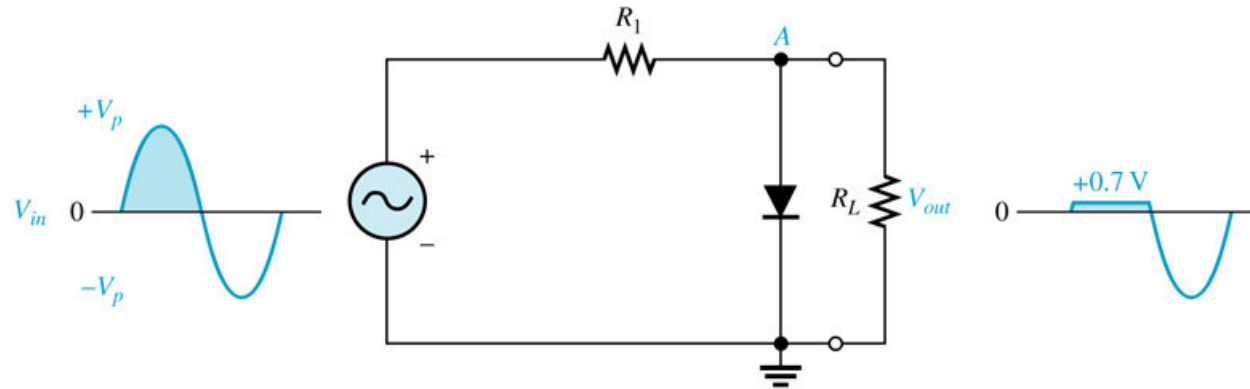

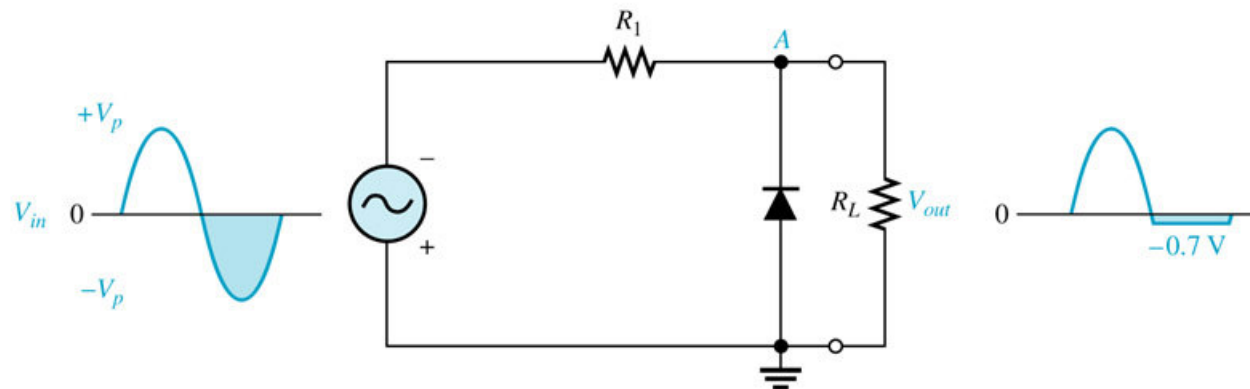(a) Limiting of the positive alternation; diode conducts on positive alternation.



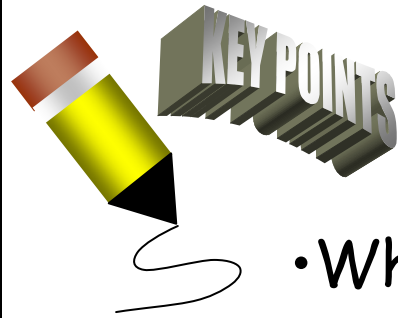(b) Limiting of the negative alternation; diode conducts on negative alternation.




DETERMING V_{OUT}

- Whenever the input is below 0.7V, the diode is reversed biased and appears as an open.
- The output voltage V_{OUT} looks like the negative part of the input, but with a magnitude determined by the voltage divider formed by R_1 and R_L , as follows:

$$\text{EQ5: } V_{OUT} = (R_L / (R_1 + R_L)) \times V_{IN}$$

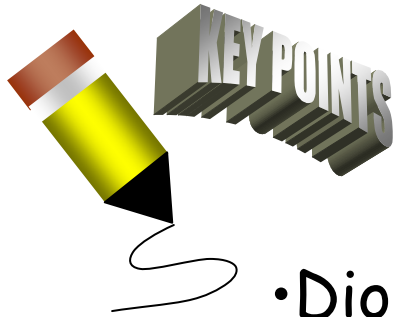- If R_1 is small compared to R_L , then $V_{OUT} \approx V_{IN}$



DIODE CLAMPERS

- Diode Clamper adds a dc level to an ac signal.
- Clampers are sometimes known as dc restorers
See **Figure 2-40**.
- The net effect of the clamping action is the capacitor retains a charge approximately equal to the peak value of the input less the diode drop.

FIGURE 2-40 Positive clamping. The diode allows the capacitor to charge rapidly. The capacitor can discharge only through R_L .

