
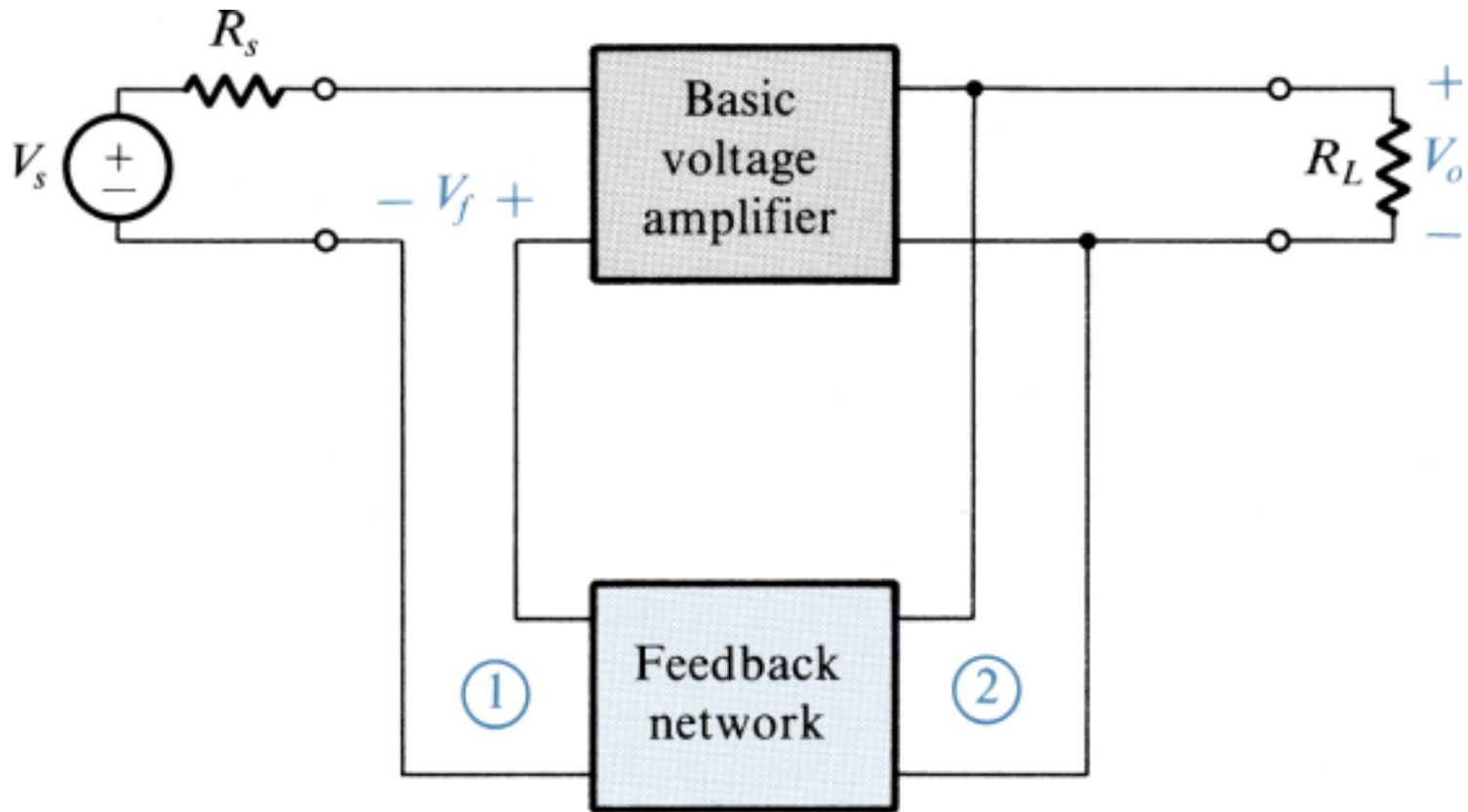


EE-4232


# Feedback Topologies

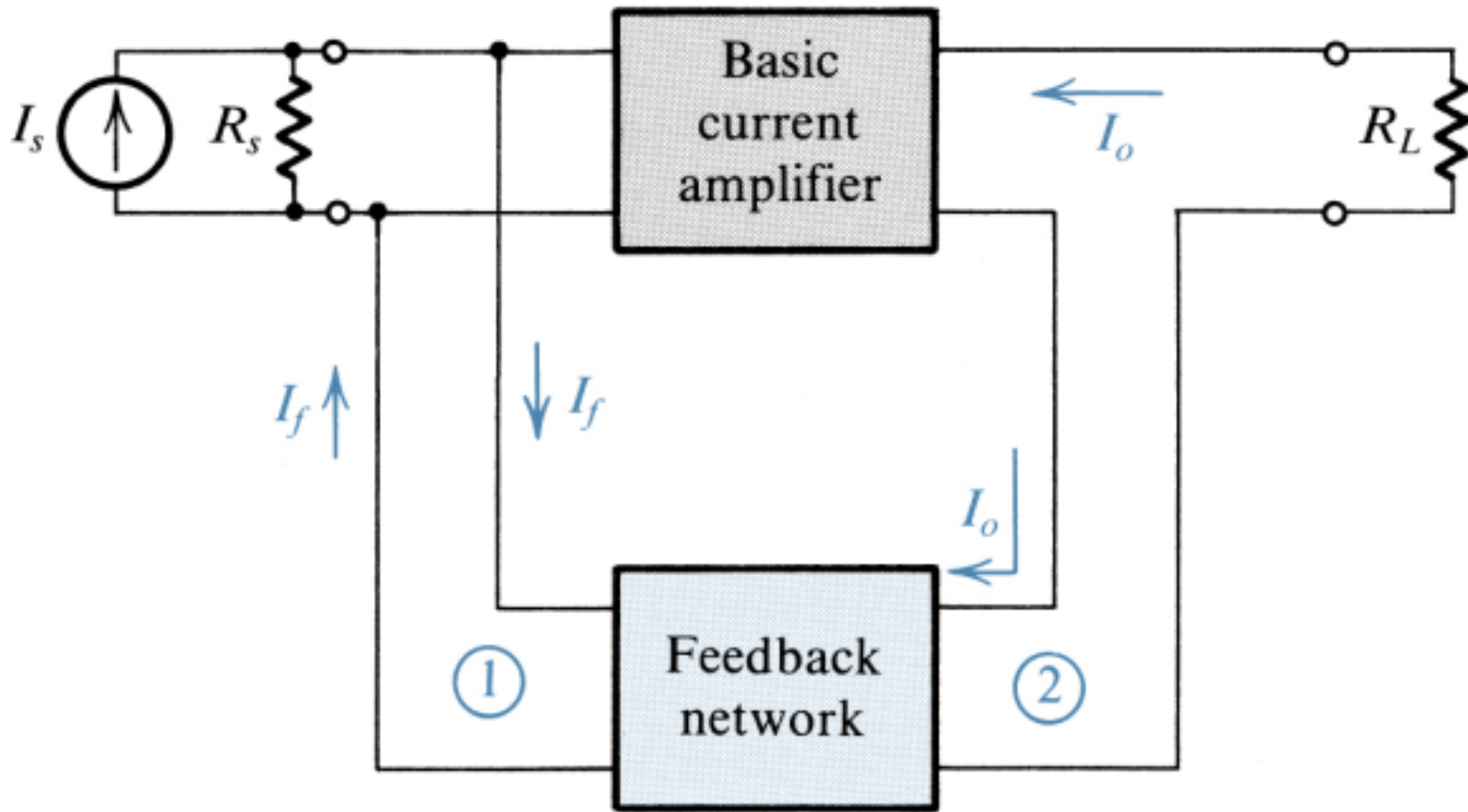


The four basic feedback topologies: voltage-sampling series-mixing (series-shunt) topology




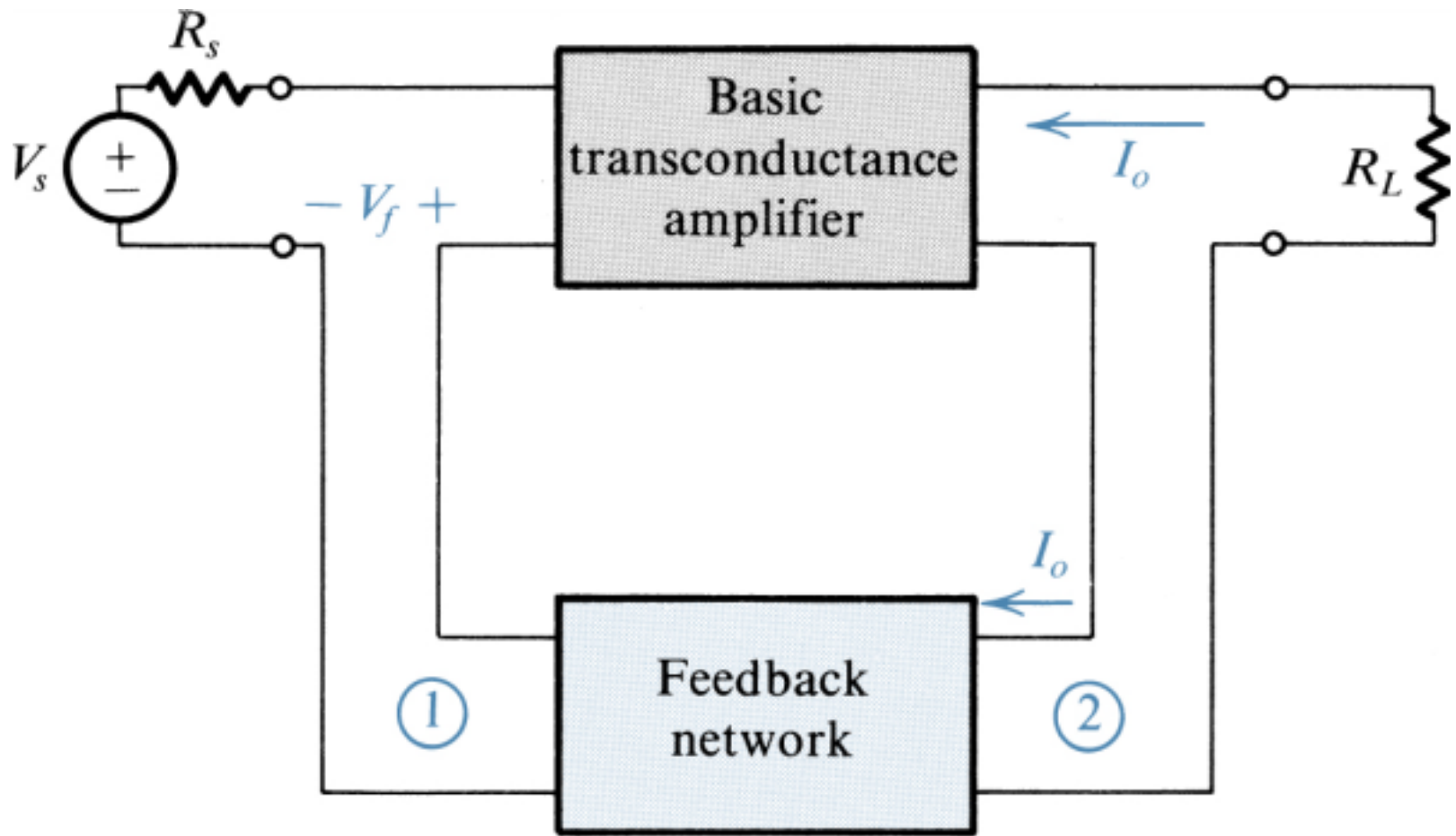
The four basic feedback topologies: current-sampling shunt-mixing (shunt-series) topology



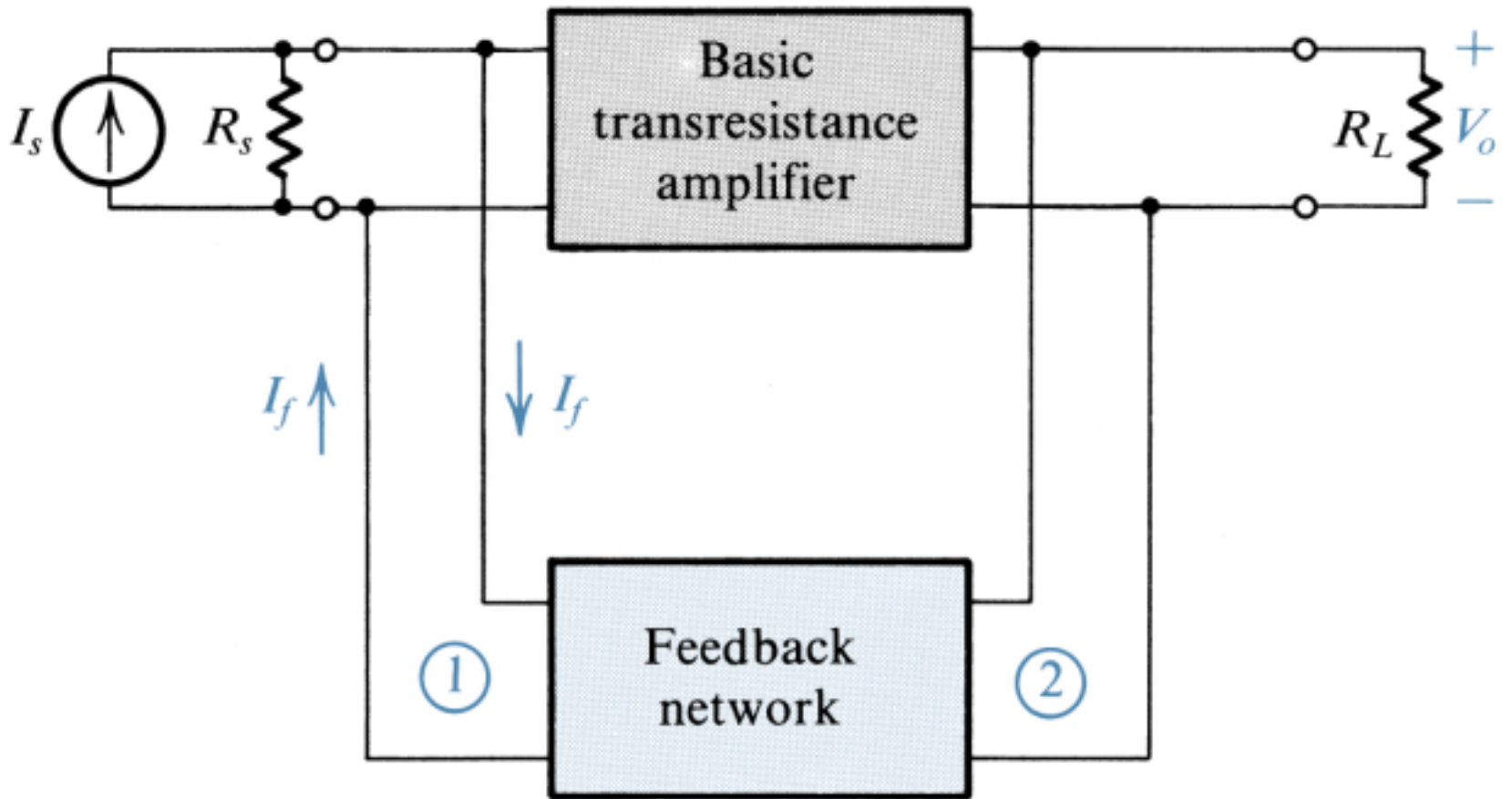
The four basic feedback topologies: current-sampling series-mixing (series-series) topology



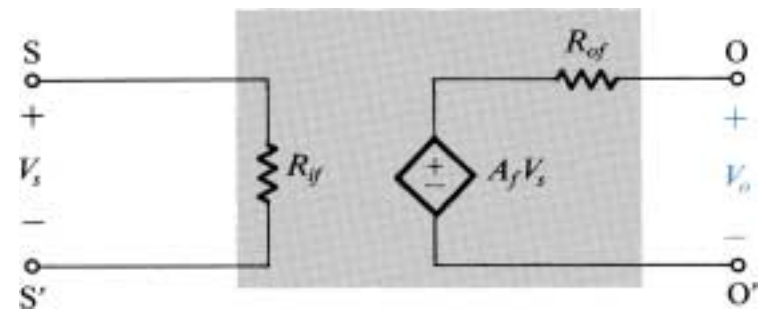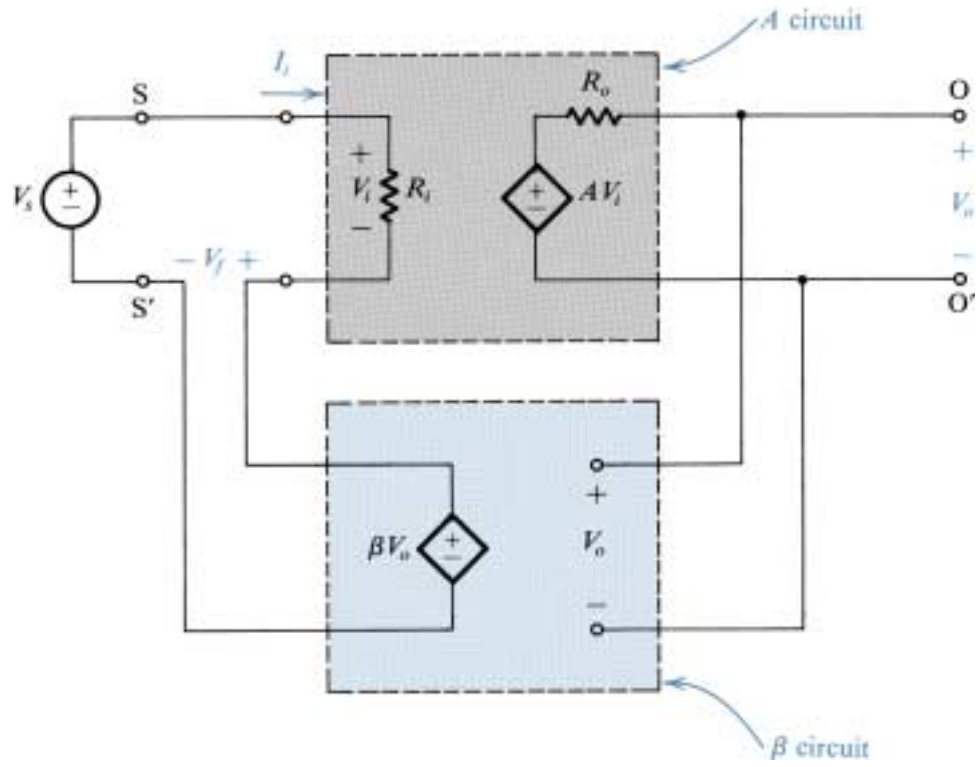
The four basic feedback topologies: voltage-sampling shunt-mixing (shunt-shunt) topology



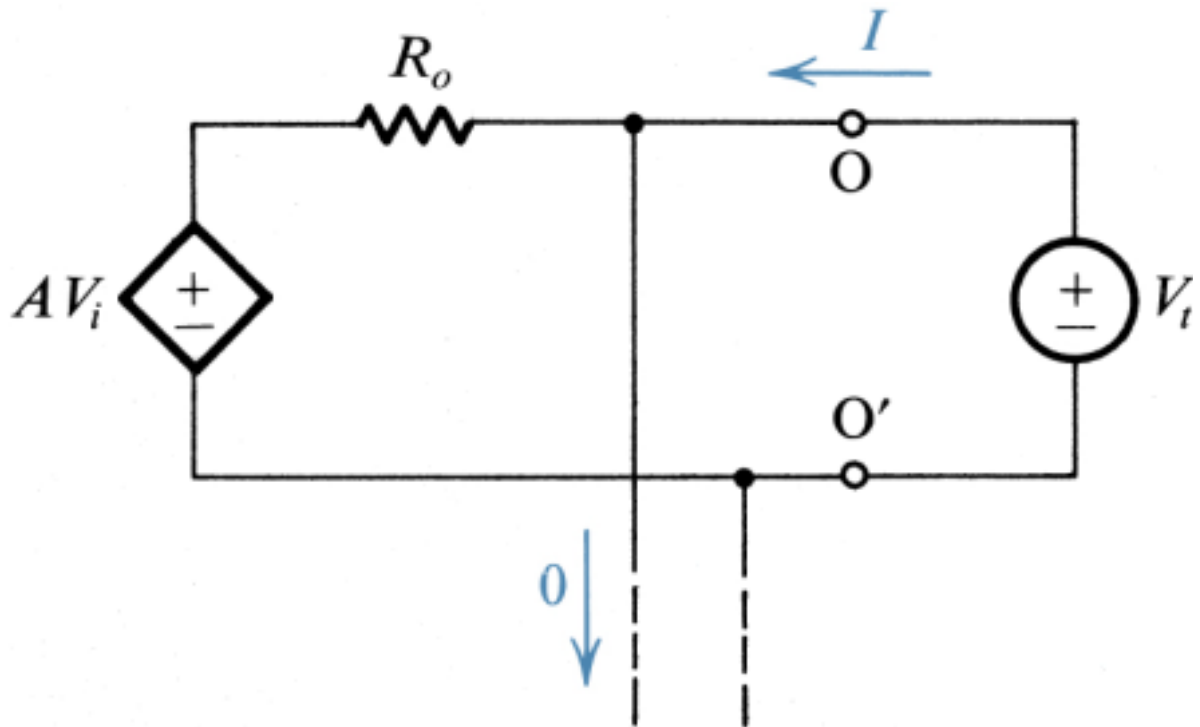The series-shunt feedback amplifier: (a) ideal structure; (b) equivalent circuit.




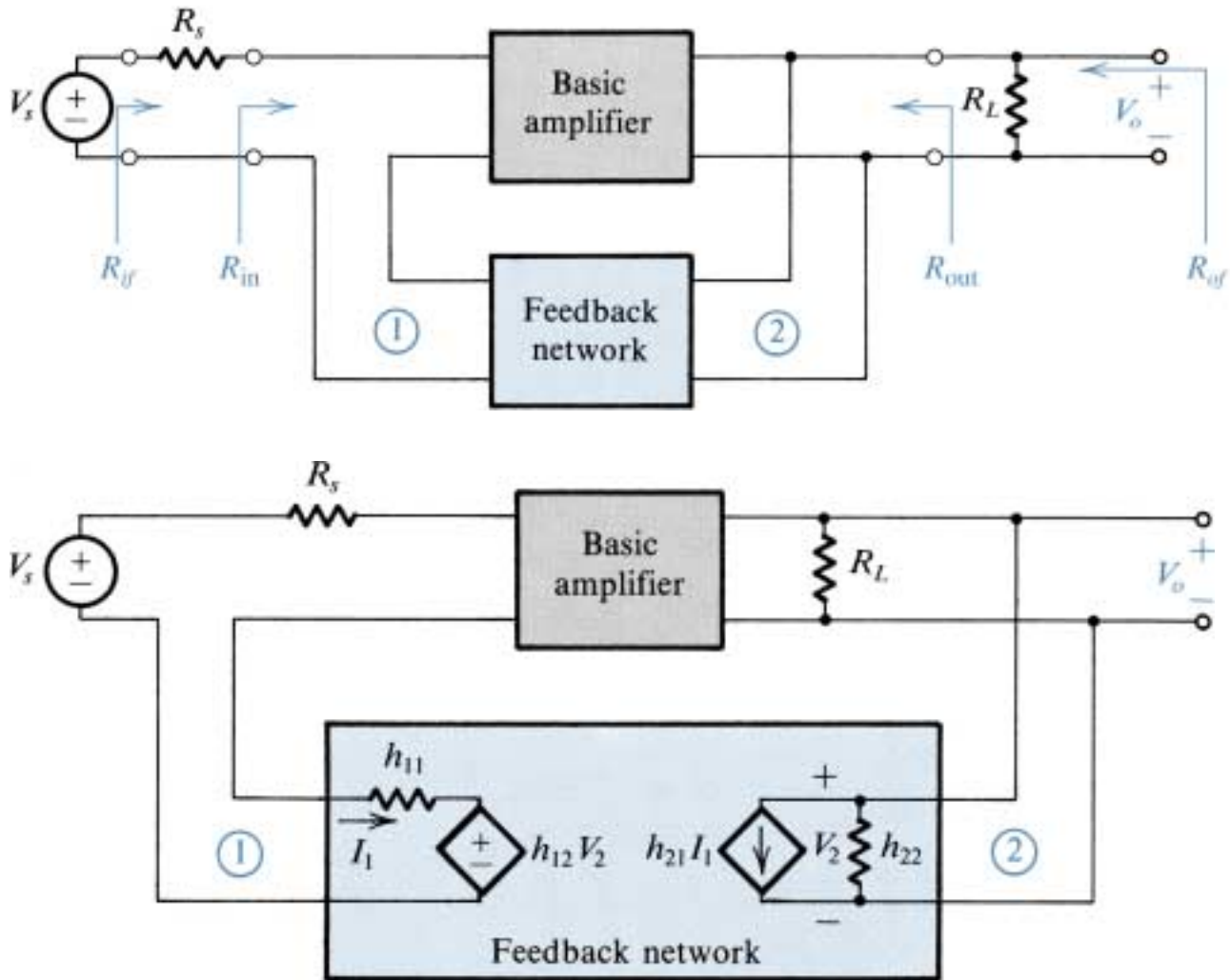Measuring the output resistance of the feedback amplifier of Fig. (a):  $R_{of} \equiv V_t/I$ .




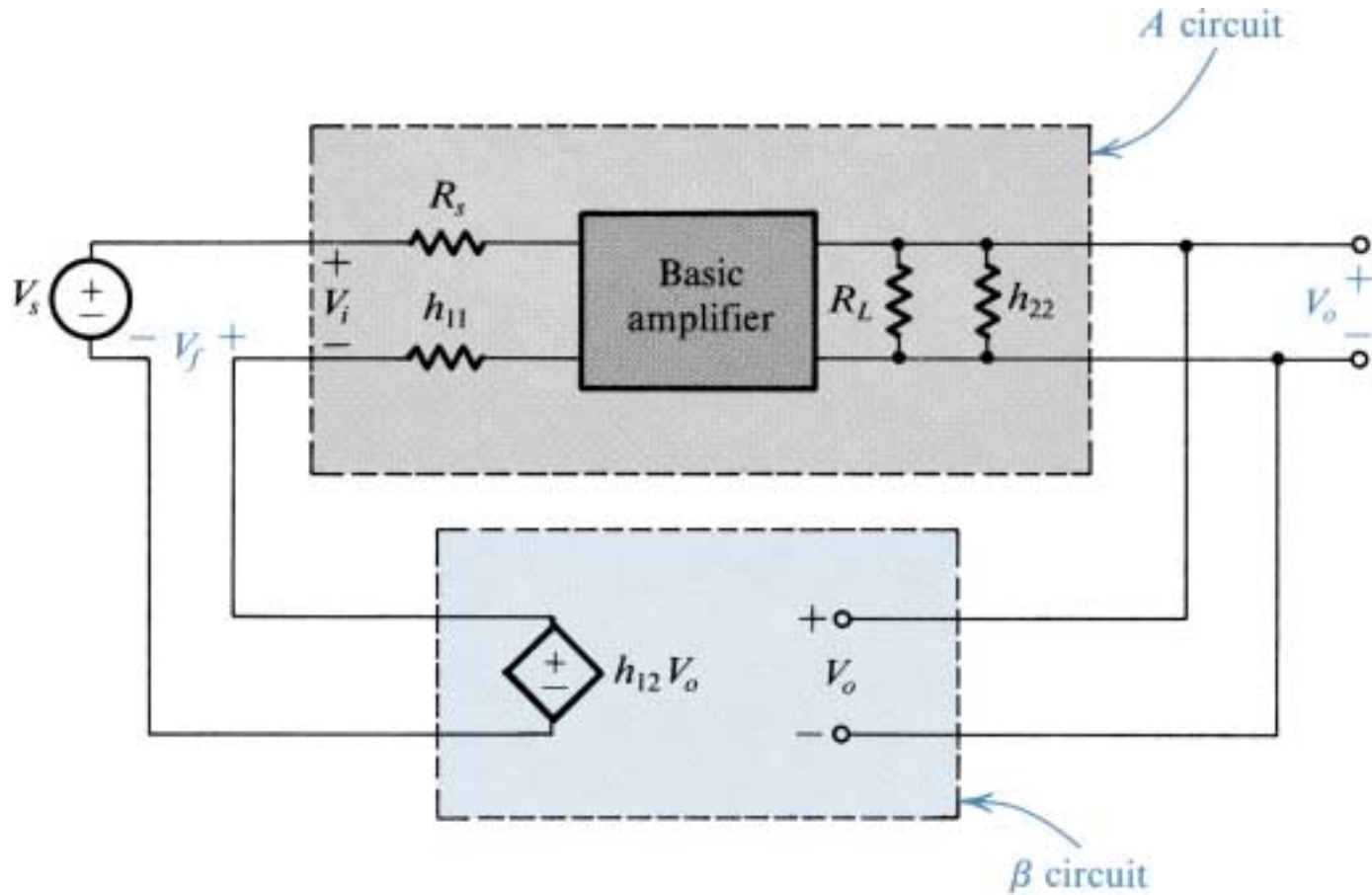Derivation of the  $A$  circuit and  $\beta$  circuit for the series-shunt feedback amplifier. (a) Block diagram of a practical series-shunt feedback amplifier. (b) The circuit in (a) with the feedback network represented by its  $h$  parameters.










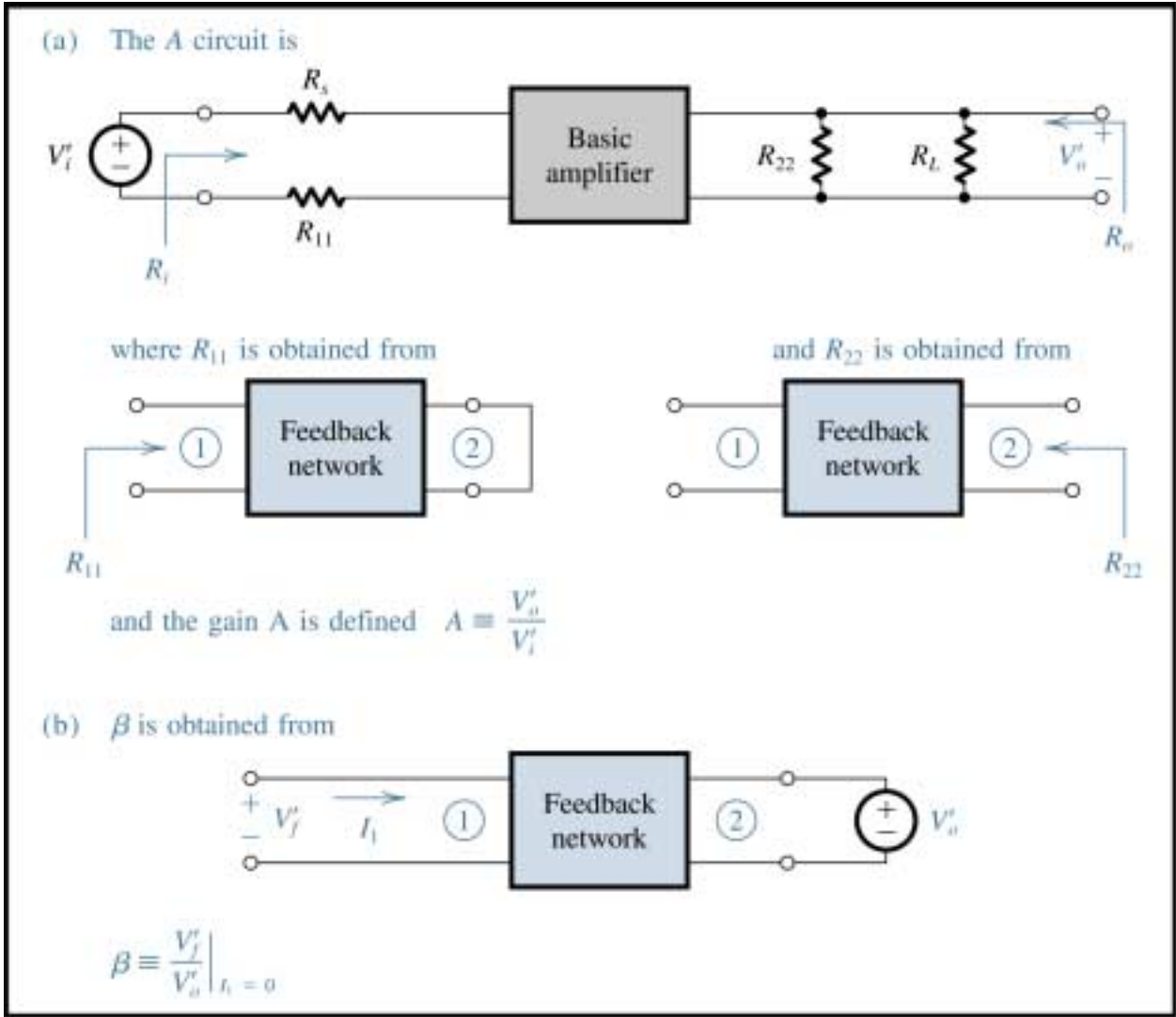Derivation of the  $A$  circuit and  $\beta$  circuit for the series-shunt feedback amplifier. (c) The circuit in (b) after neglecting  $h_{21}$ .




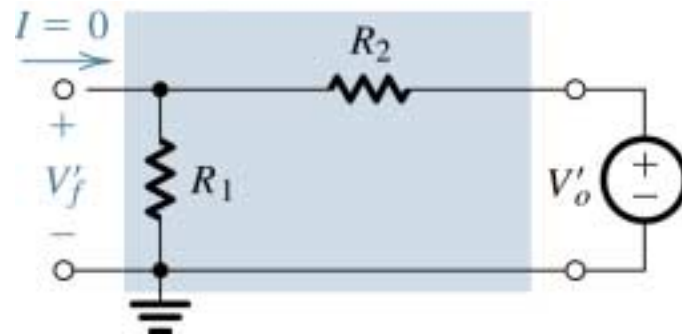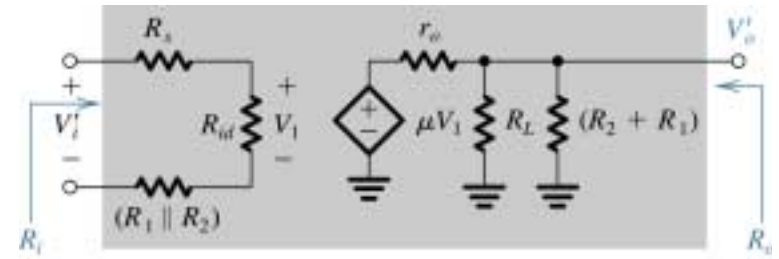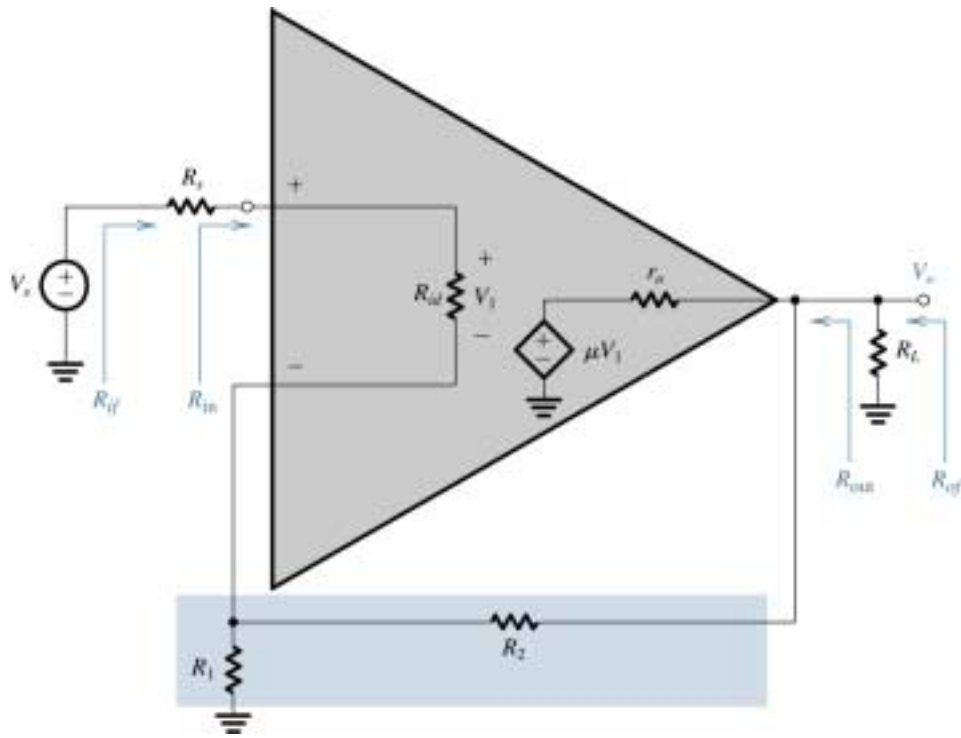Summary of the rules for finding the  $A$  circuit and  $\beta$  for the voltage-sampling series-mixing case.




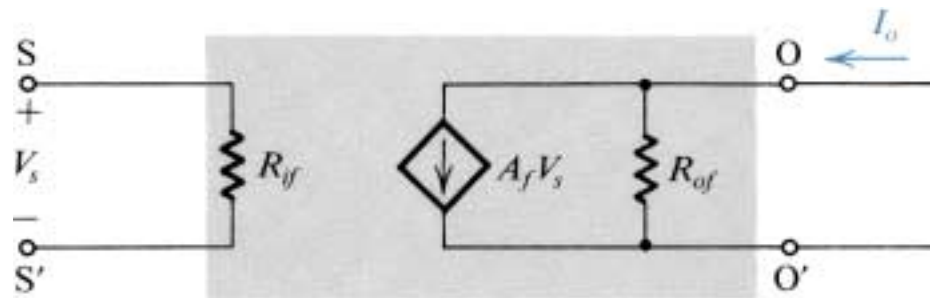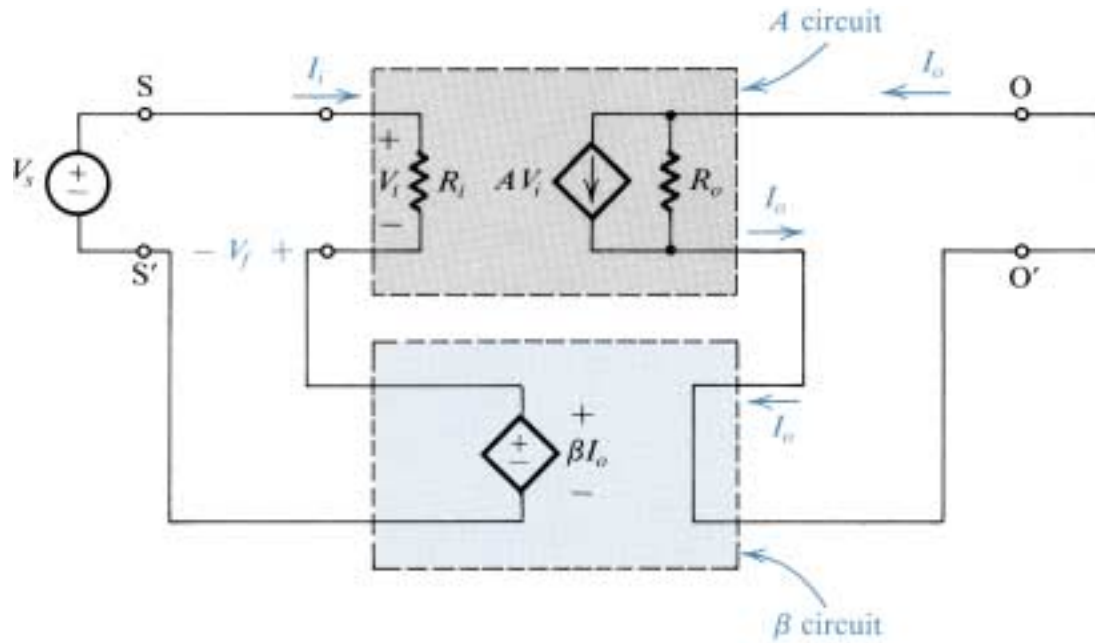

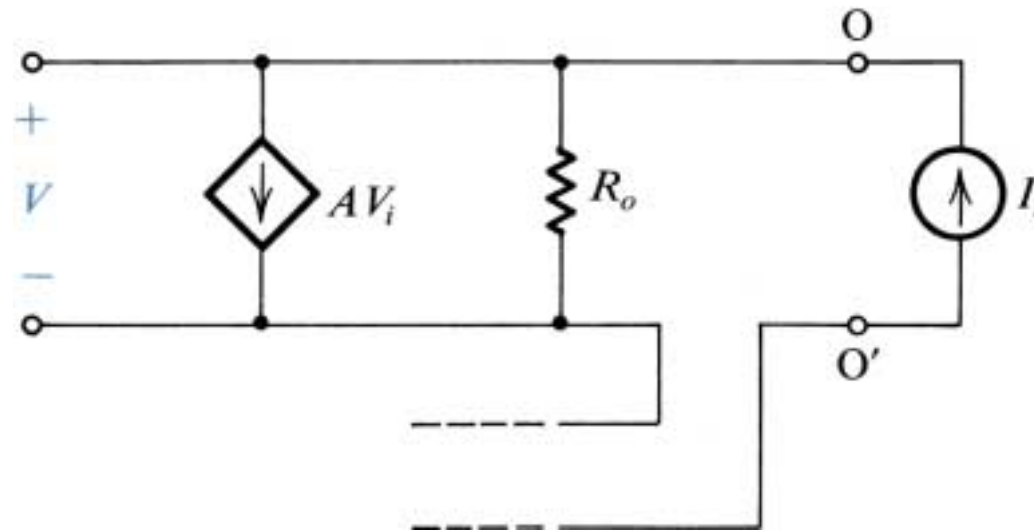
The series-series feedback amplifier: (a) ideal structure; (b) equivalent circuit.



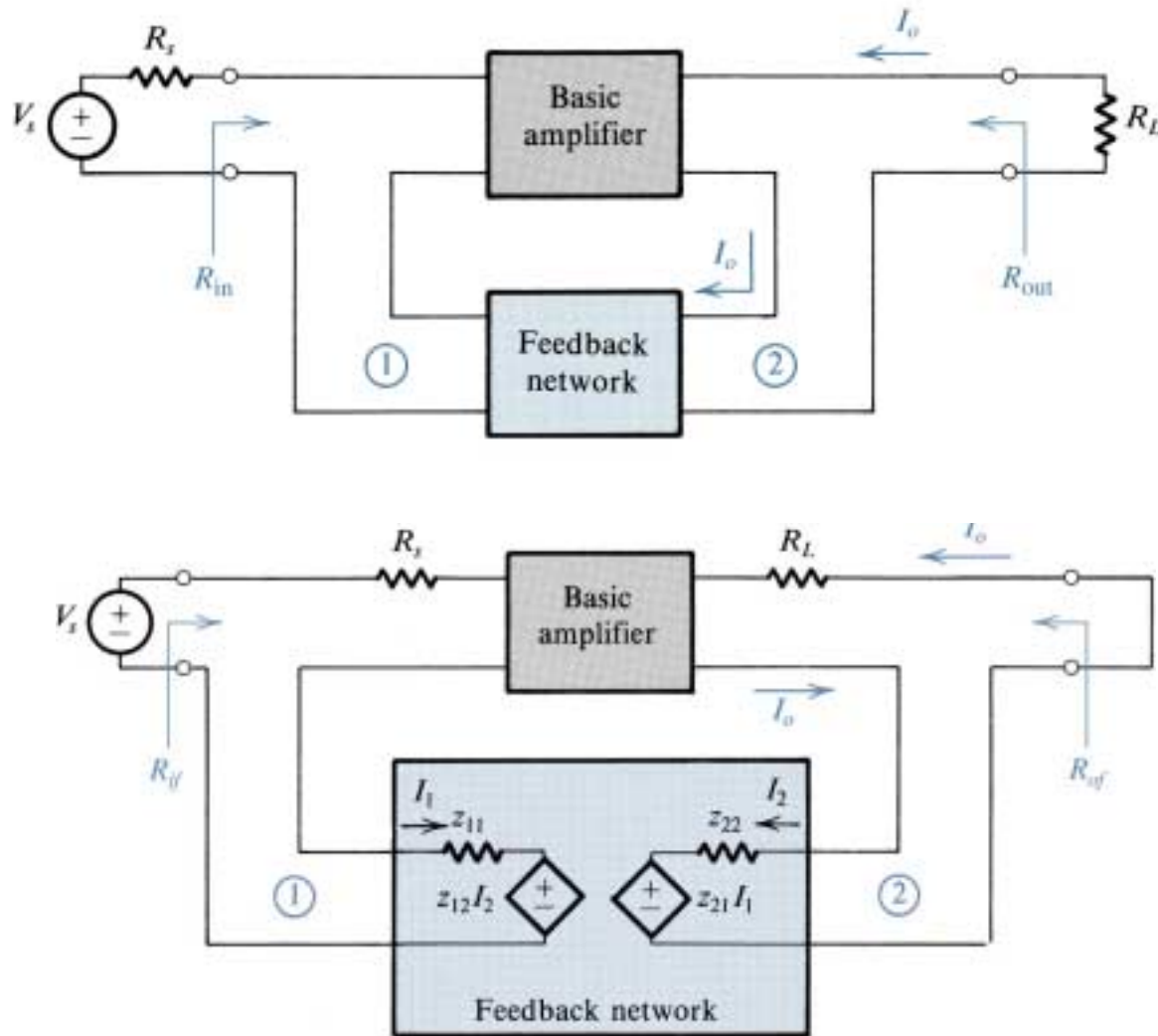
Measuring the output resistance  $R_{of}$  of the series-series feedback amplifier.



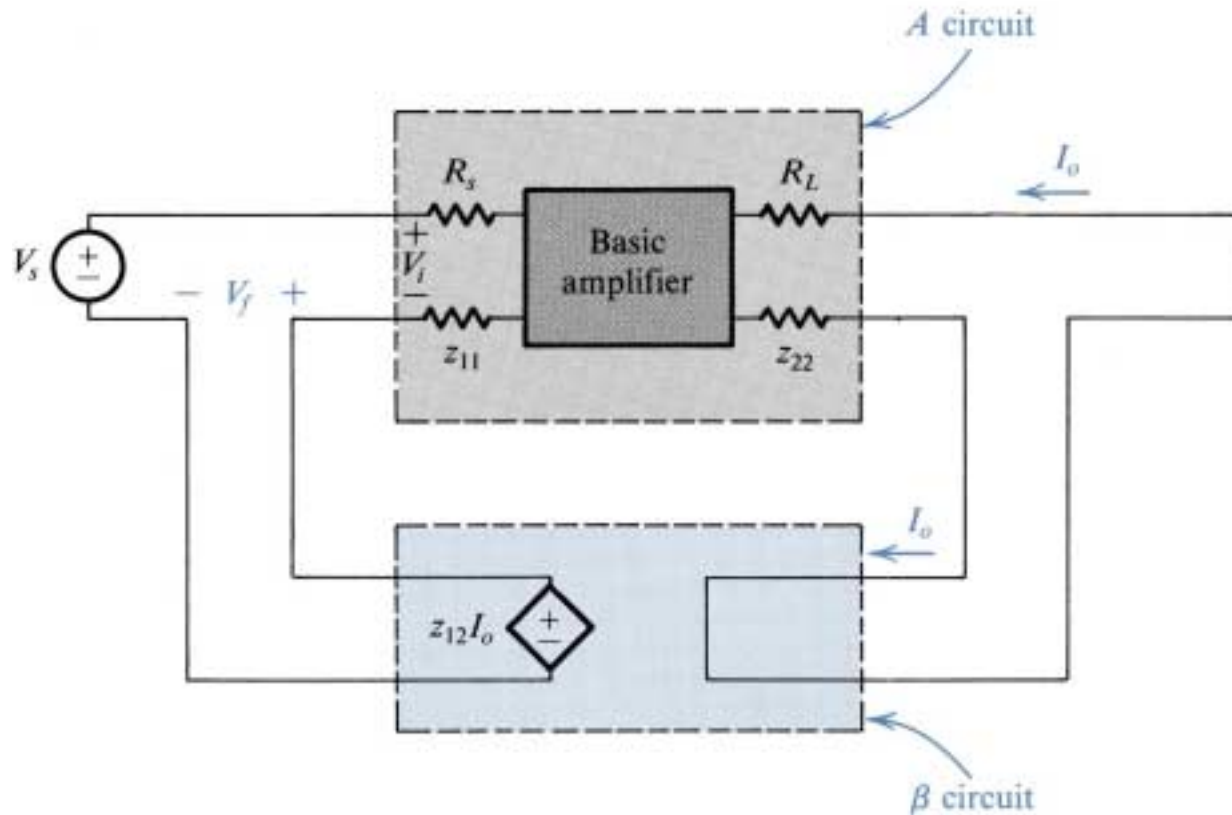Derivation of the  $A$  circuit and  $\beta$  circuit for the series-series feedback amplifiers. (a) A series-series feedback amplifier. (b) The circuit of (a) with the feedback network represented by its  $z$  parameters.







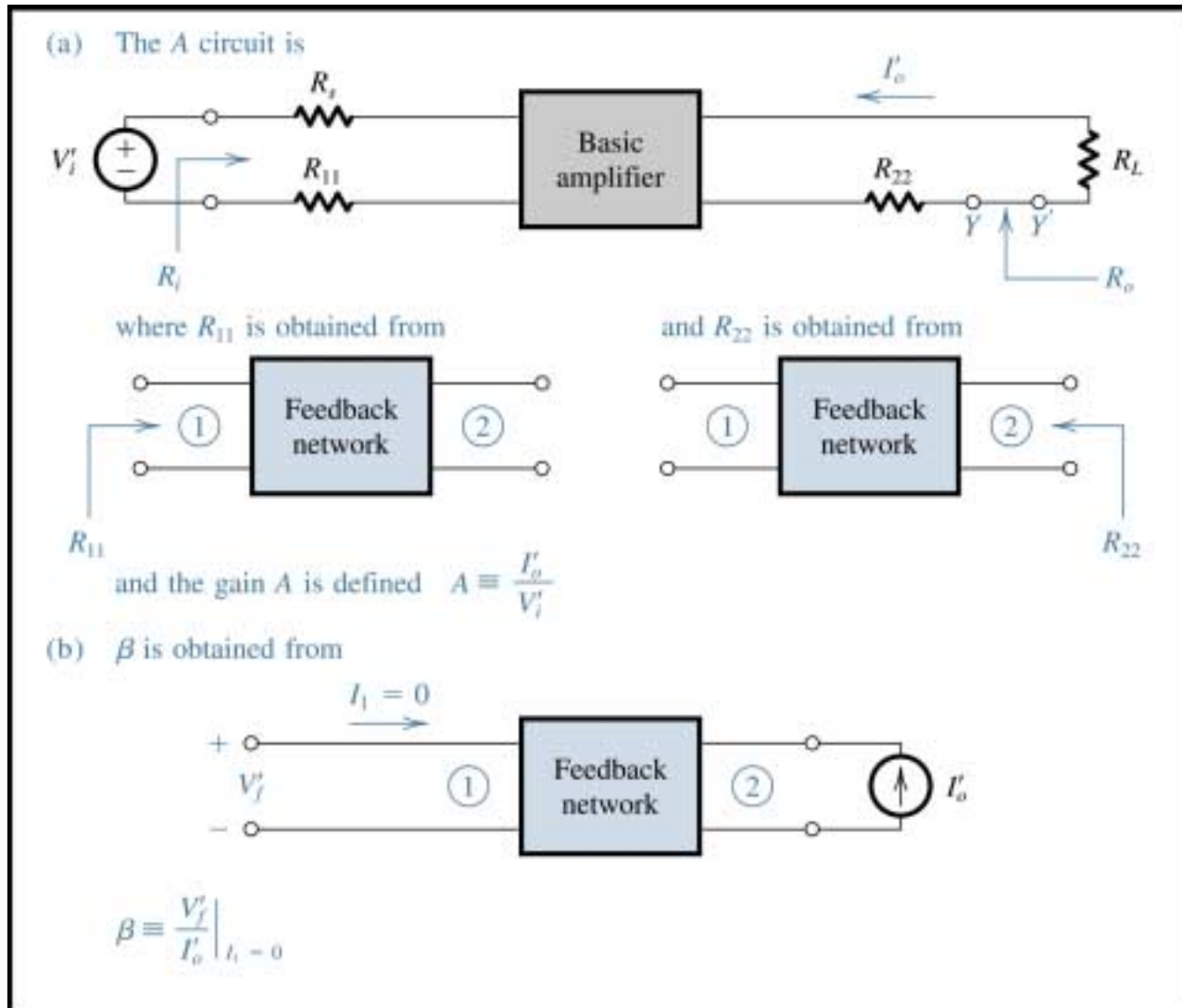
Derivation of the A circuit and  $\beta$  circuit for the series-series feedback amplifiers. (c) A redrawing of the circuit in (b) after neglecting  $z_{21}$ .



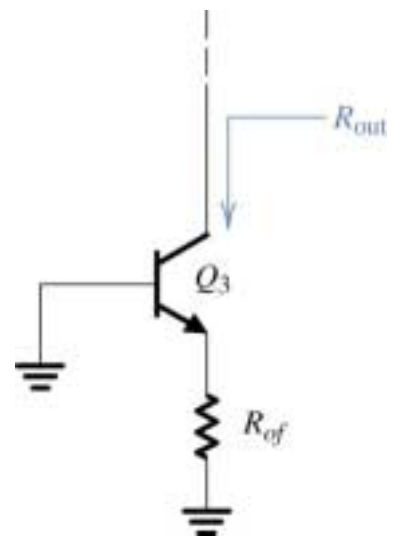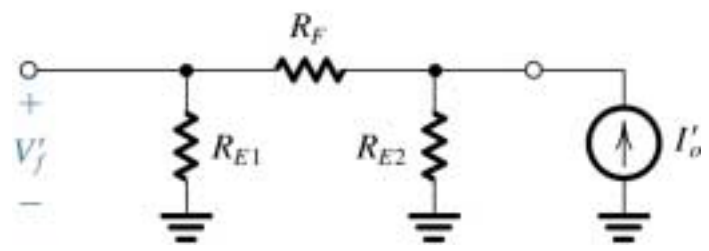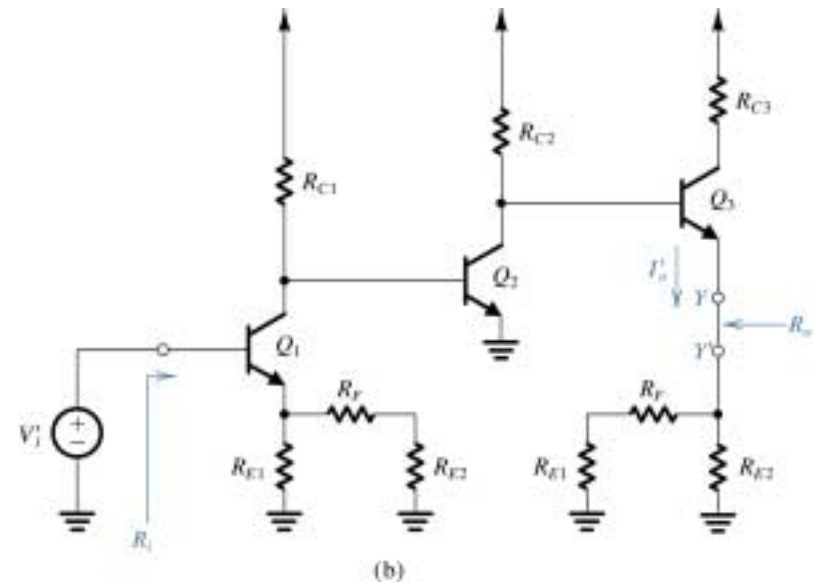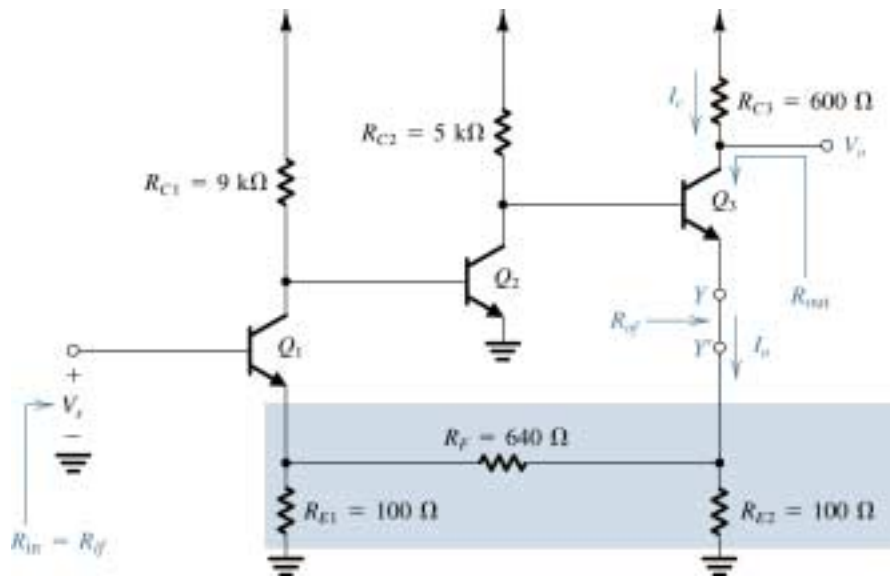
Finding the A circuit and  $\beta$  for the current-sampling series-mixing (series-series) case.






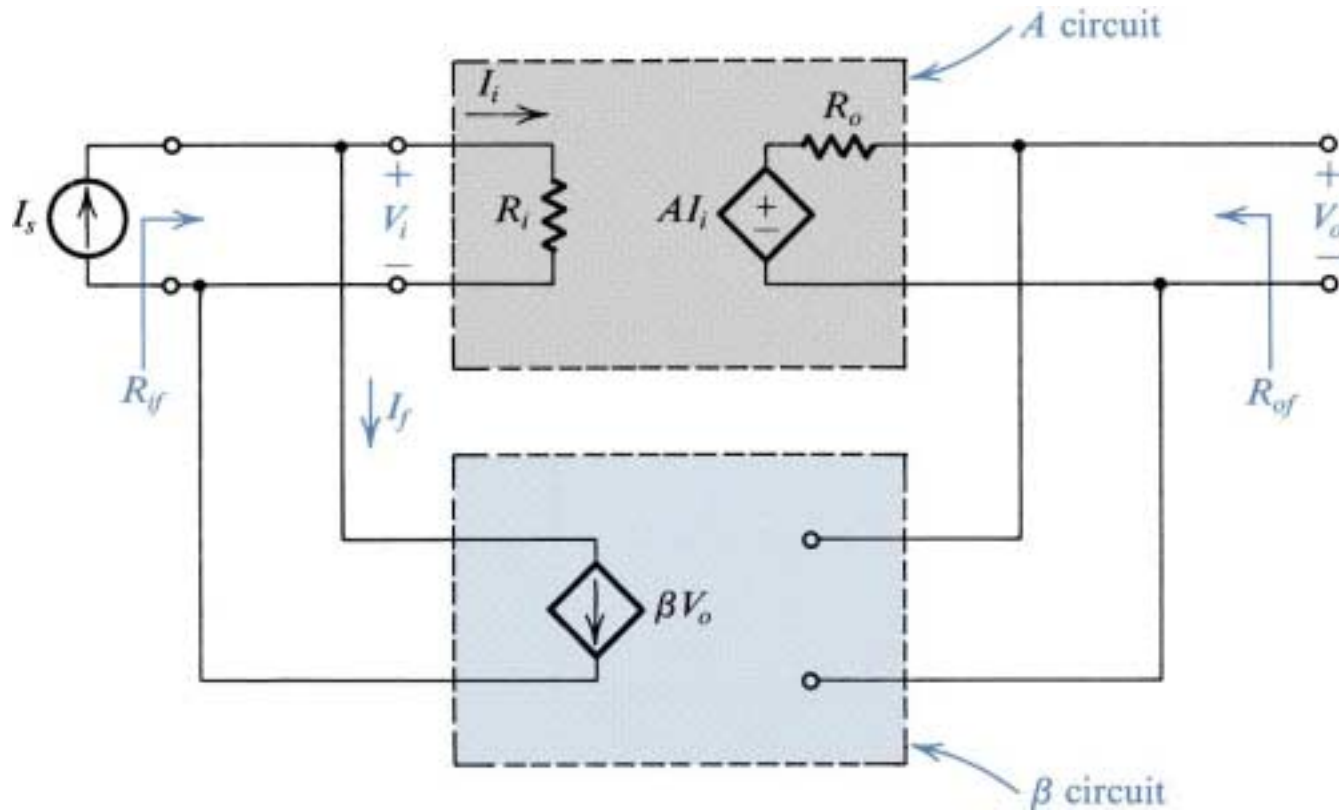

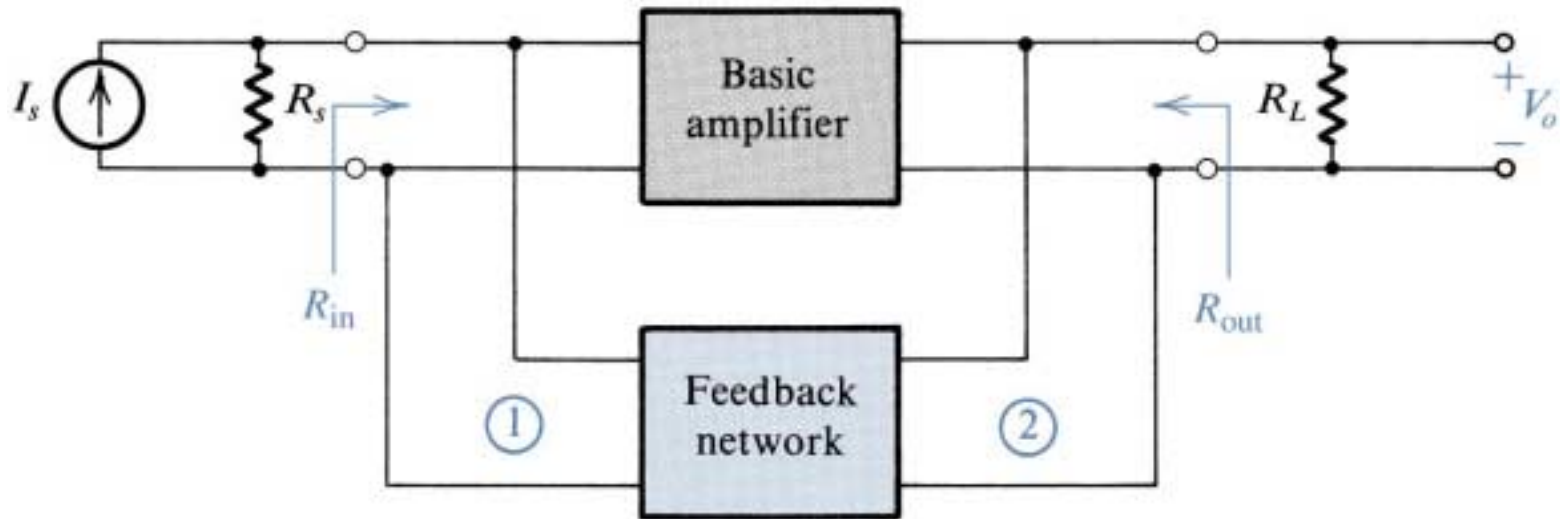
Ideal structure for the shunt-shunt feedback amplifier.



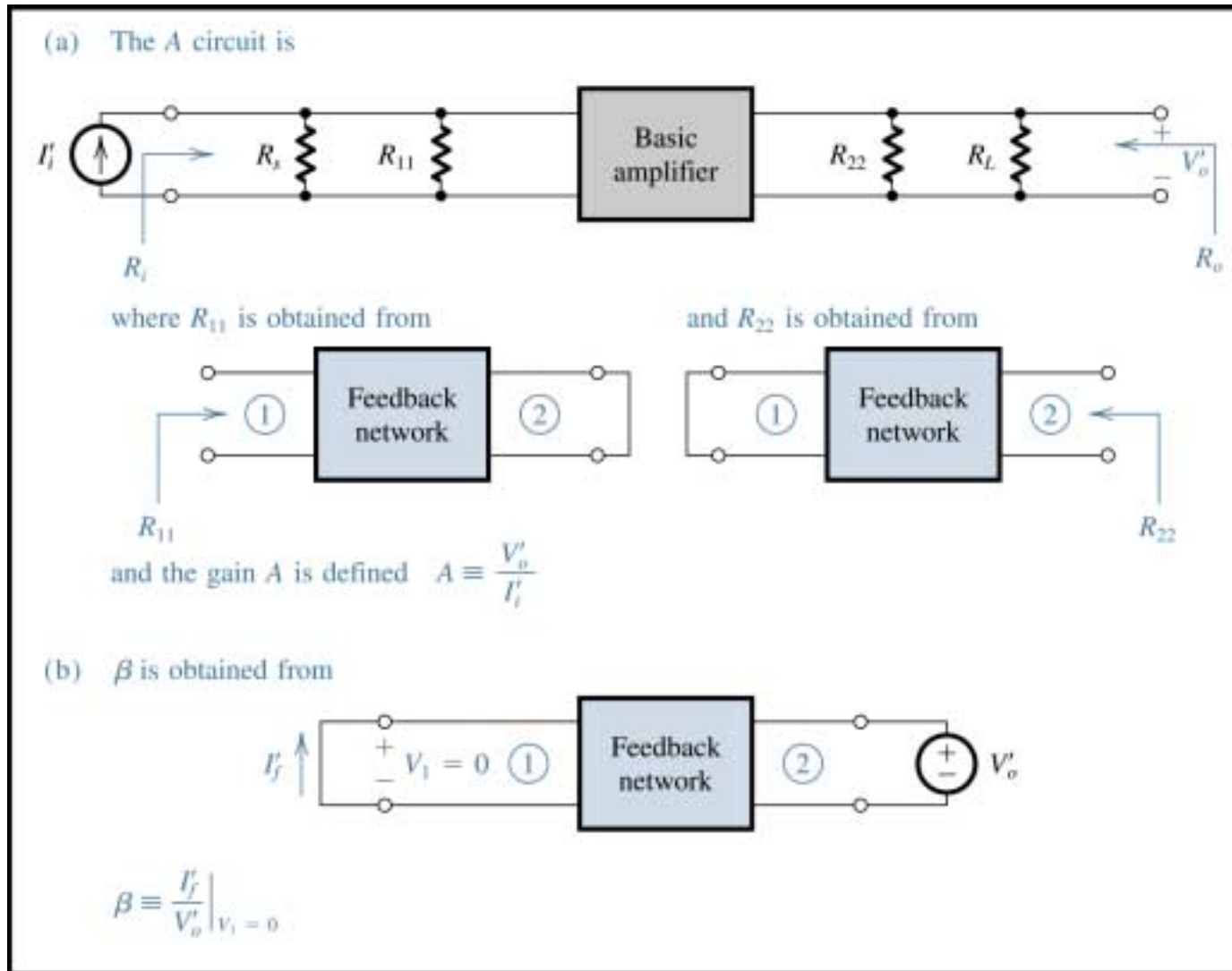
Block diagram for a practical shunt-shunt feedback amplifier.



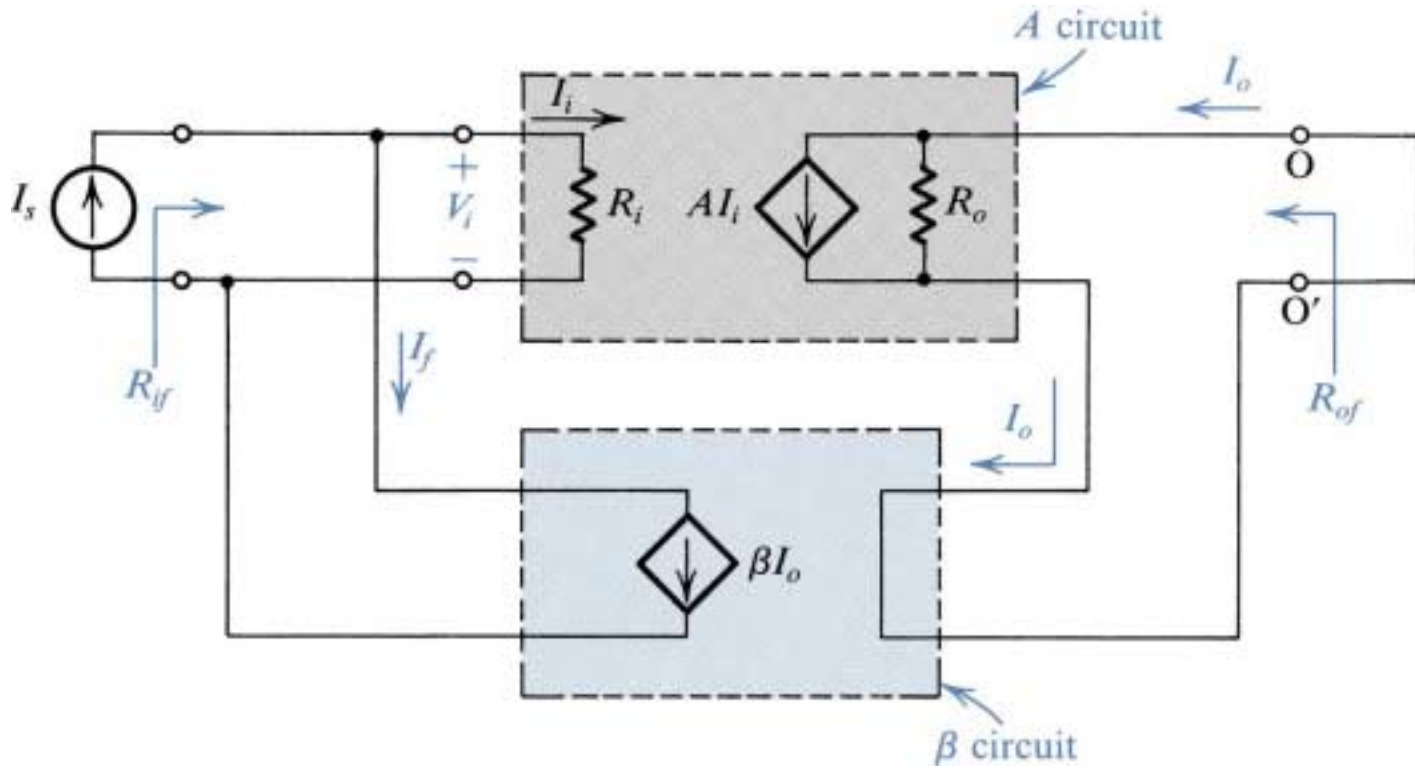
Finding the  $A$  circuit and  $\beta$  for the voltage-sampling shunt-mixing (shunt-shunt) case.




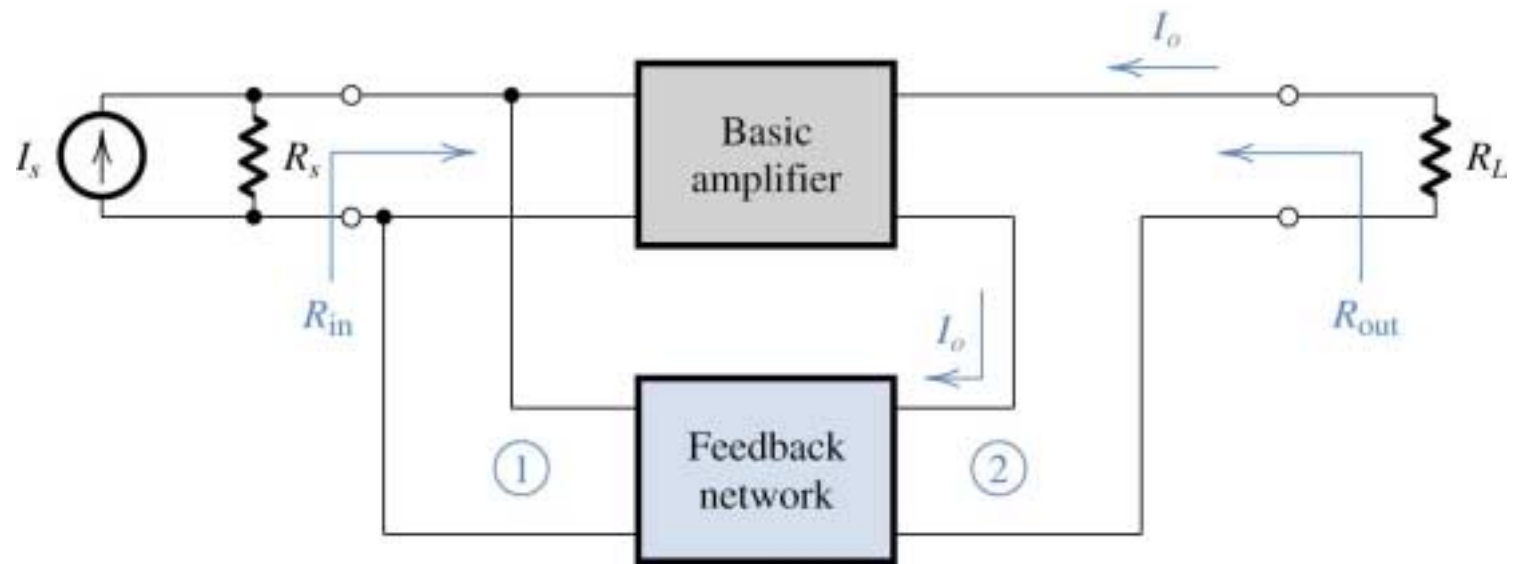
Ideal structure for the shunt-series feedback amplifier.





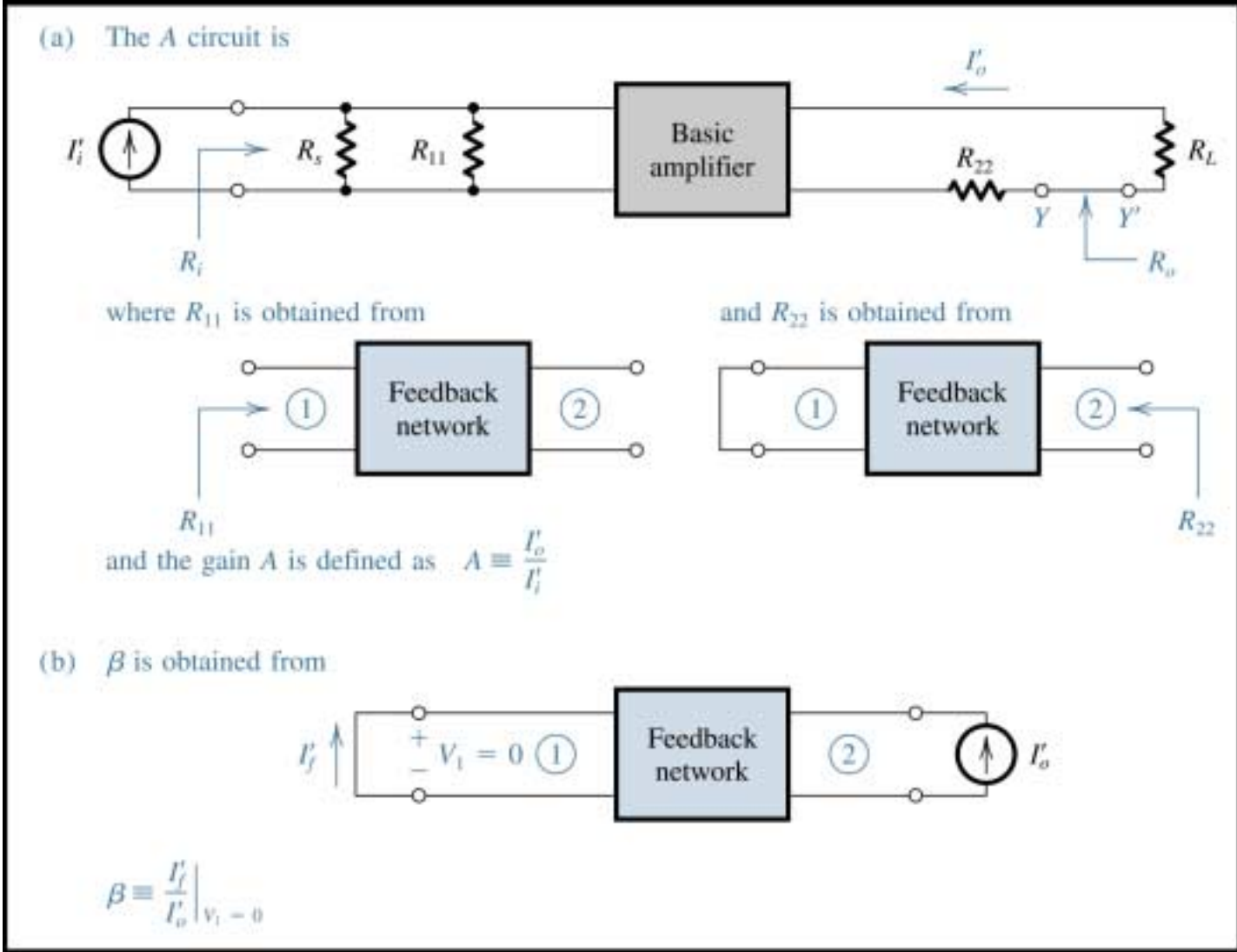
Block diagram for practical shunt-series feedback amplifier




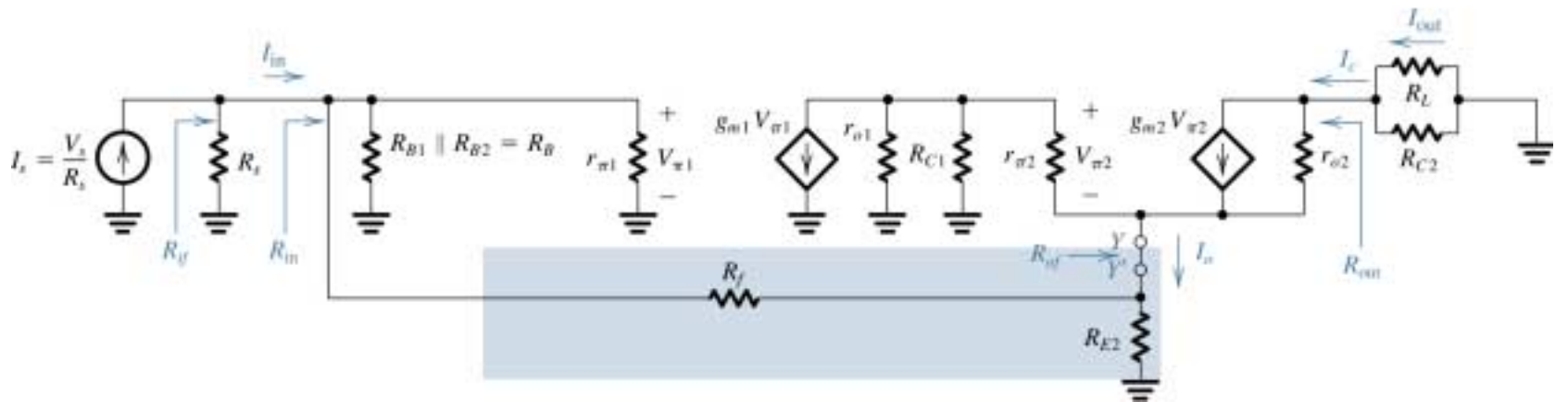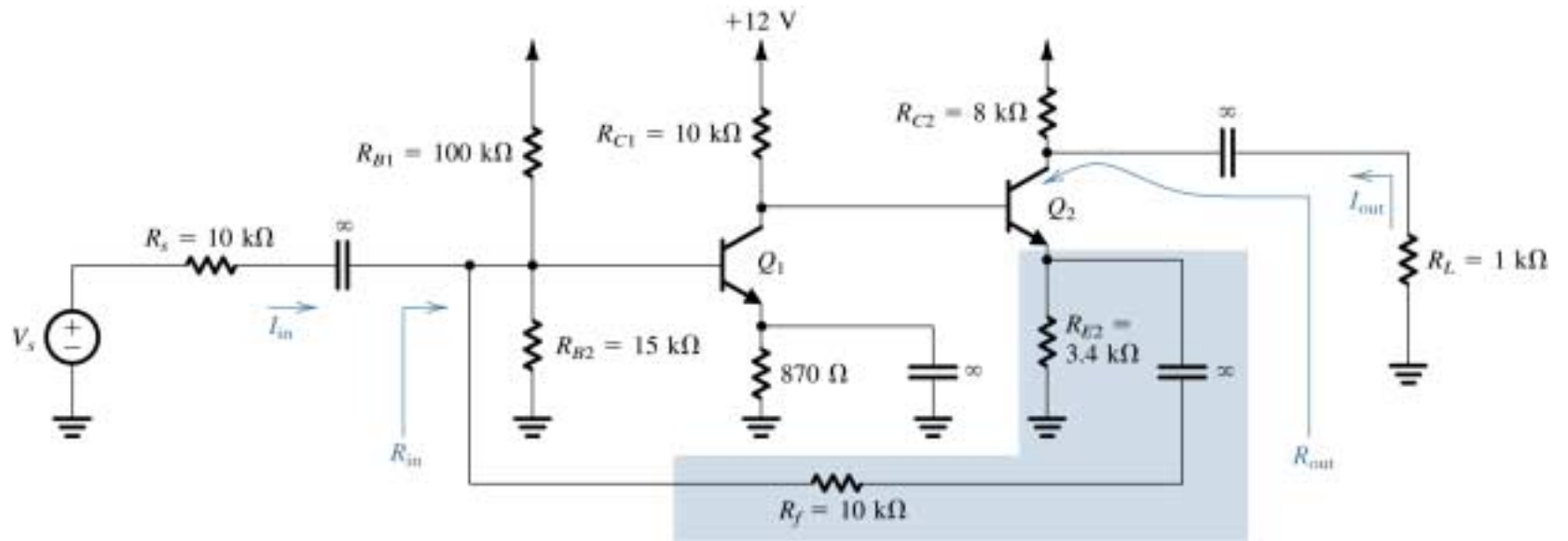Finding the A circuit and  $\beta$  for the current-sampling shunt-mixing (shunt-series) case.






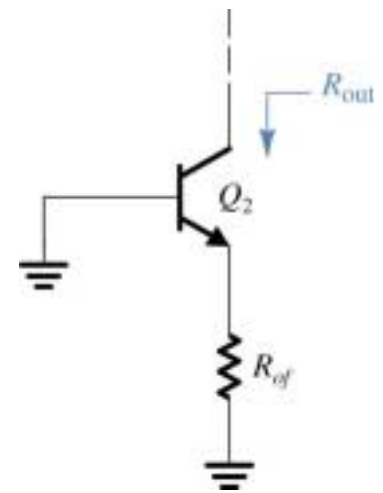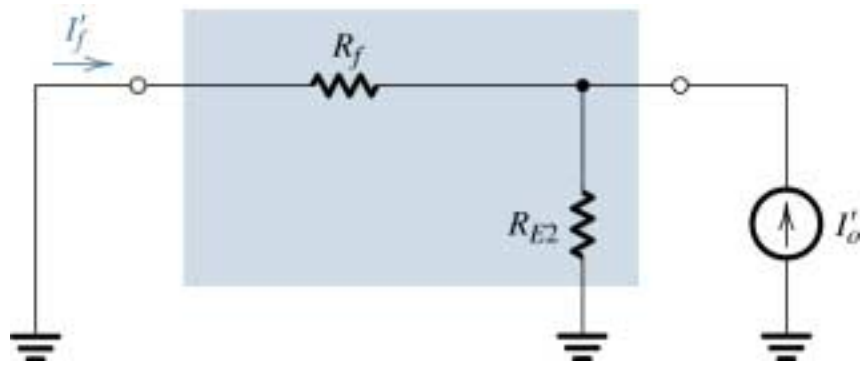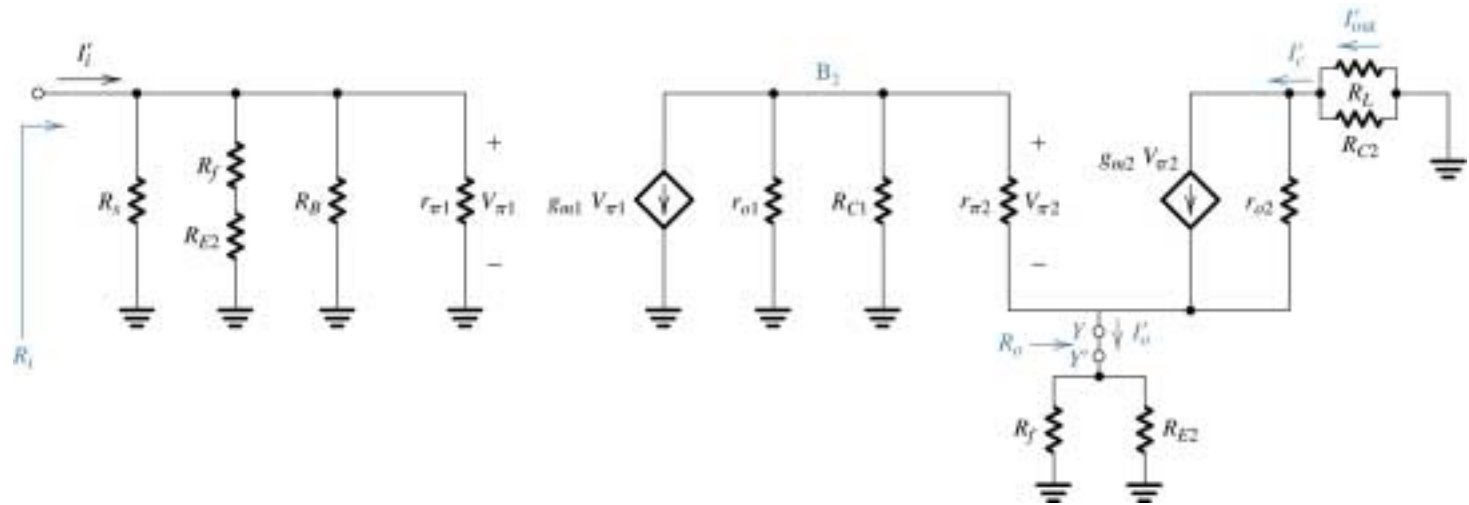


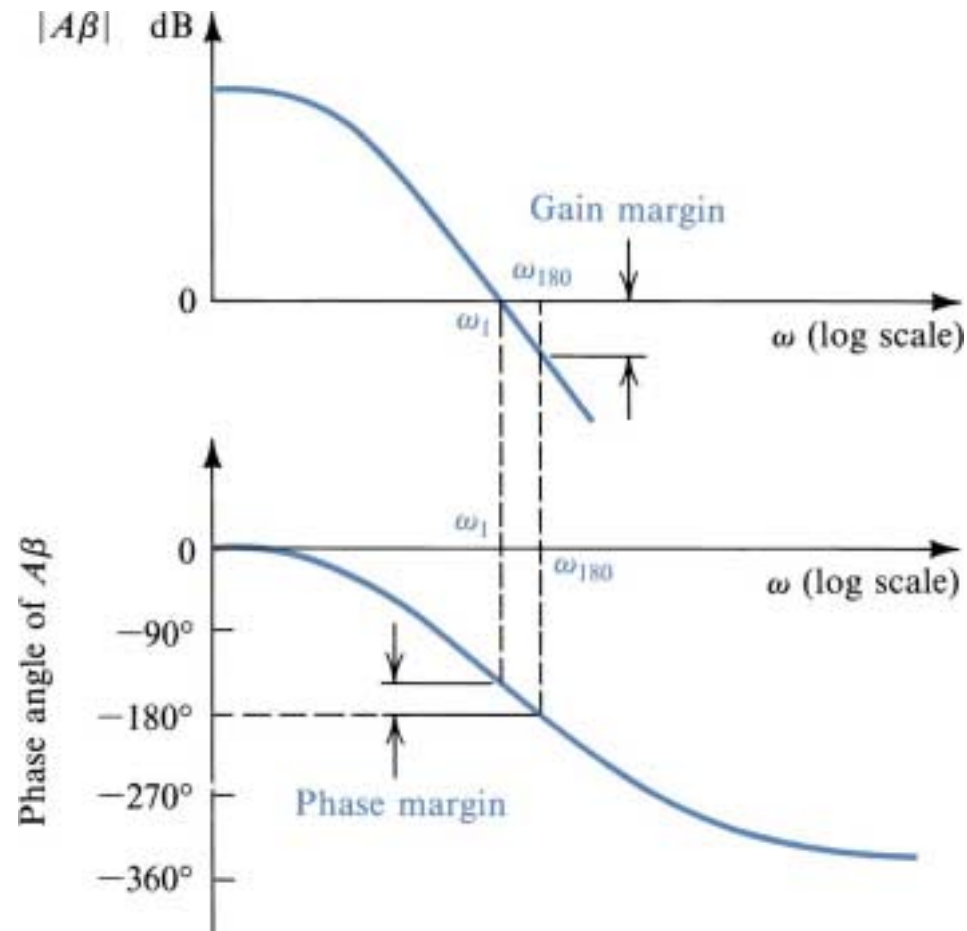

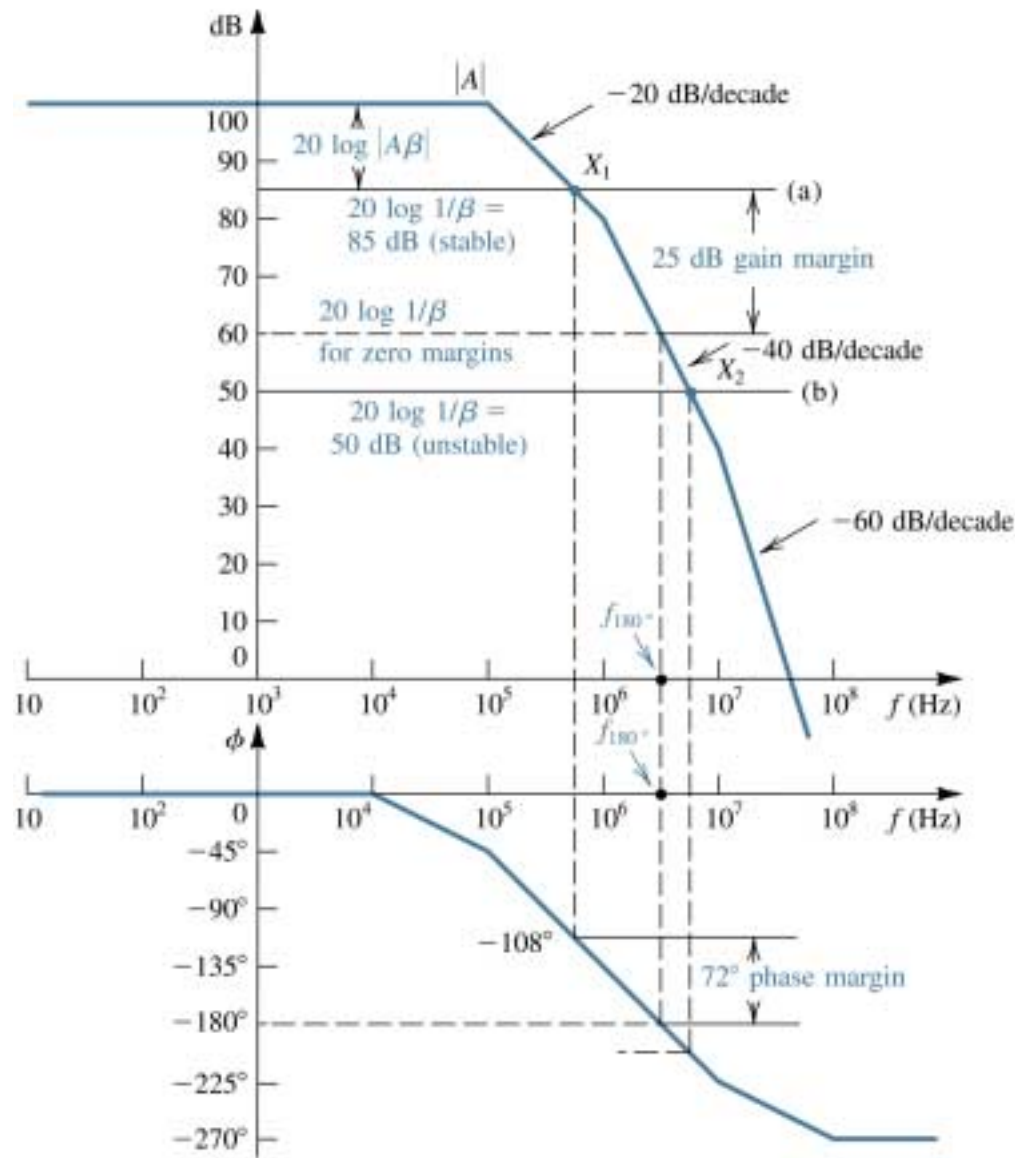Bode plot for the loop gain  $A\beta$  illustrating the definitions of the gain and phase margins.



Stability analysis using Bode plot of  $|A|$ .

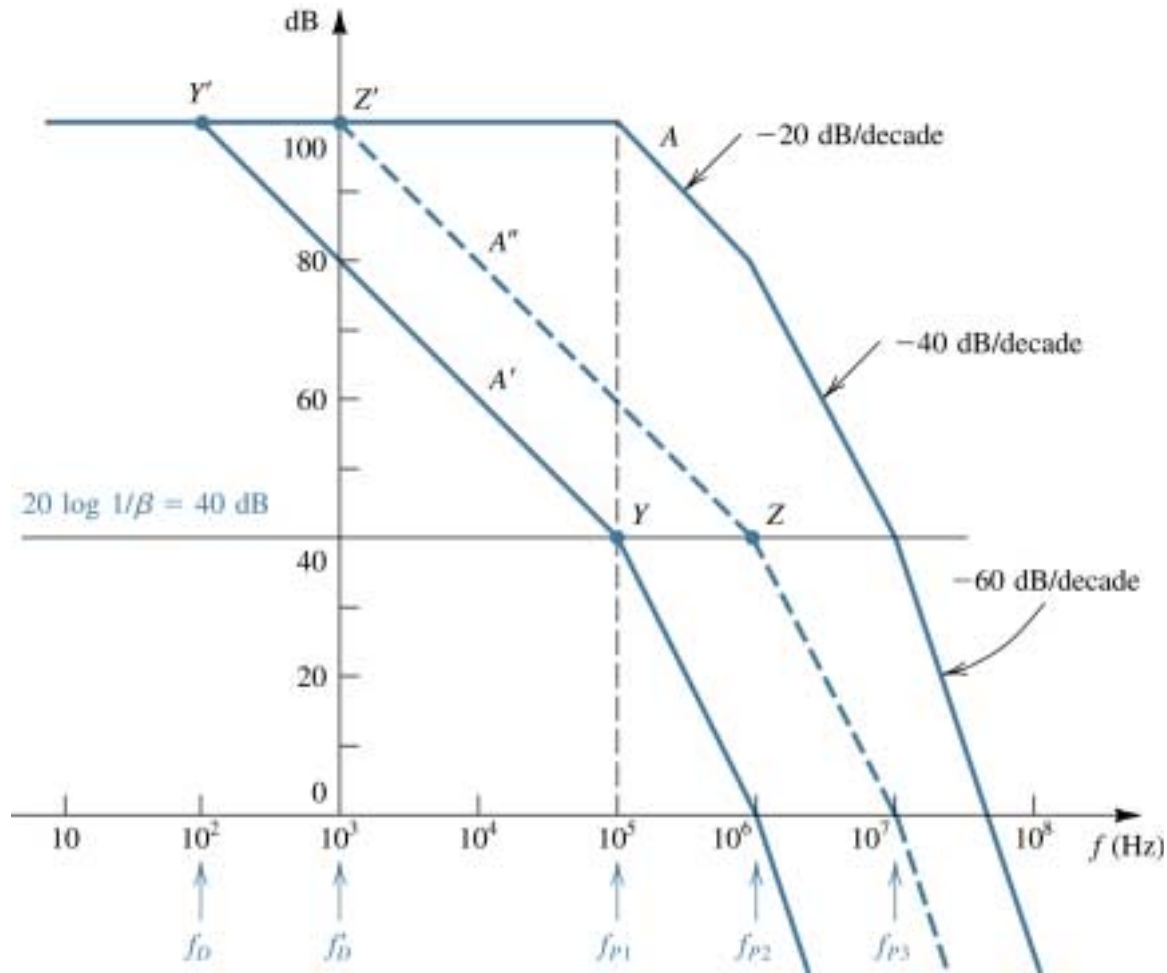

Frequency compensation for  $\beta = 10^{-2}$ . The response labeled  $A'$  is obtained by introducing an additional pole at  $f_D$ . The  $A''$  response is obtained by moving the original low-frequency pole to  $f_D'$ .

# References

- *Electronics* by A. Hambley
- *Microelectronics Circuits* by Sedra & Smith
- Other books on Electronics