

## **EXPERIMENT 2:**

### **Voltage and Current Division**

#### **Objective:**

Verify the voltage and current division properties.

#### **Equipment:**

- NI – ELVIS board
- Assorted Resistors ( 1 K $\Omega$ , 2.4 K $\Omega$ , 5.6 K $\Omega$  and 1.2 K $\Omega$ )

#### **Theory:**


Voltage and Current division allow us to simplify the task of analyzing a circuit.

**Voltage Division** allows us to calculate what fraction of the total voltage across a series string of resistors is dropped across any one resistor.

For the circuit of Figure 1, Voltage Division formulas are:


$$V_1 = \frac{R_1}{R_1 + R_2} V_S \quad (1)$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_S \quad (2)$$

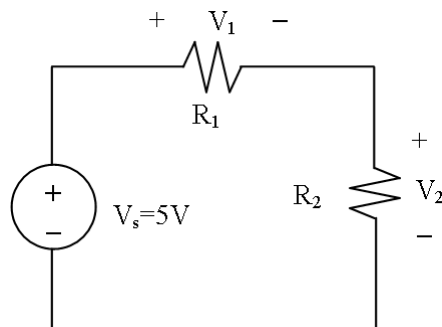

**Figure 1.** Voltage Divider

**Current Division** allows us to calculate what fraction of the total current into a parallel string of resistors flows through any one of the resistors.

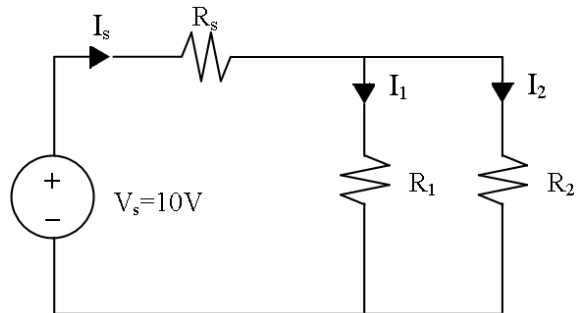

**Figure 2.** Current Divider

For the circuit of Figure 2, Current Division formulas are:

$$I_1 = \frac{R_2}{R_1 + R_2} I_s \quad (3)$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_s \quad (4)$$


### Procedure:

1. Verifying the voltage division:
  - a) Construct the circuit as shown in Figure 1. Measure the voltages  $v_1$  and  $v_2$  by choosing  $R_1 = 5.6 \text{ K}\Omega$ ,  $R_2 = 1.2 \text{ K}\Omega$  and setting the variable power supply voltage  $V_s = 5\text{V}$ . Repeat this step for  $R_1 = R_2 = 5.6 \text{ K}\Omega$  and note down the measurements.
  - b) Calculate the voltages  $V_1$  and  $V_2$  by using the formulas (1) and (2) in each case.
  - c) Compare the results from steps 1a and 1b.
2. Verifying the current division:
  - a) Construct the circuit as shown in figure 2. Measure the currents  $I_s$ ,  $I_1$  and  $I_2$  by choosing  $R_1 = 2.4 \text{ K}\Omega$ ,  $R_2 = 5.6 \text{ K}\Omega$  and  $R_s = 1 \text{ K}\Omega$ . Set the variable power supply voltage at  $V_s = 10 \text{ V}$ . Repeat this step by using  $R_1 = R_2 = 2.4 \text{ K}\Omega$  and note down the measurements.
  - b) Calculate the currents  $I_1$  and  $I_2$  by using the formulas (3) and (4).

c) Compare the results from steps 2a and 2b.

**Questions for Lab Report:**



1. How well did the measured outputs and calculated outputs compare? Explain any difference.
2. Can you apply current division to obtain  $I_1$  and  $I_2$  for the circuit shown in the figure below? Explain briefly.

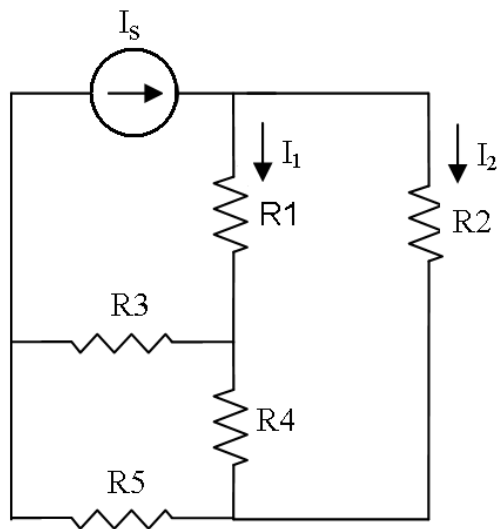

**Figure 3.**


## SOME EXAMPLES

### VOLTAGE MEASUREMENT DETAILS OF FIG.1

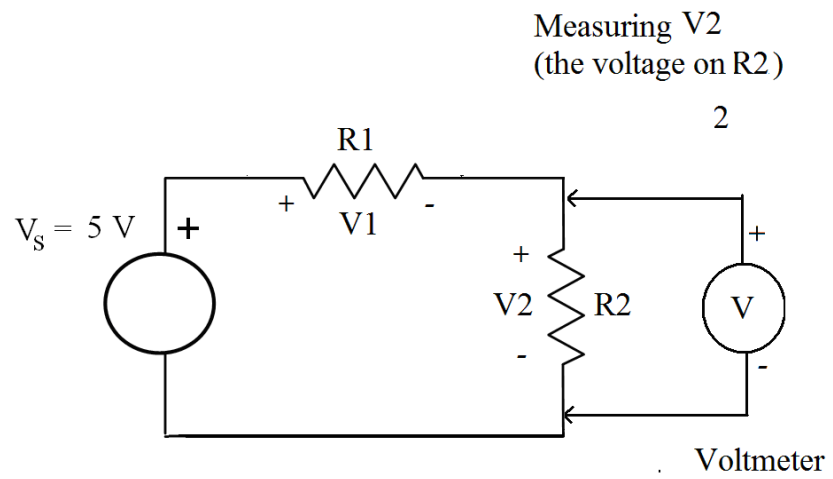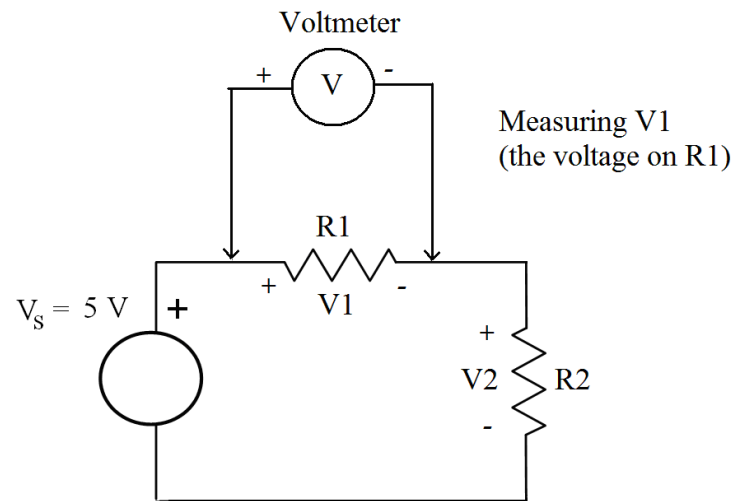

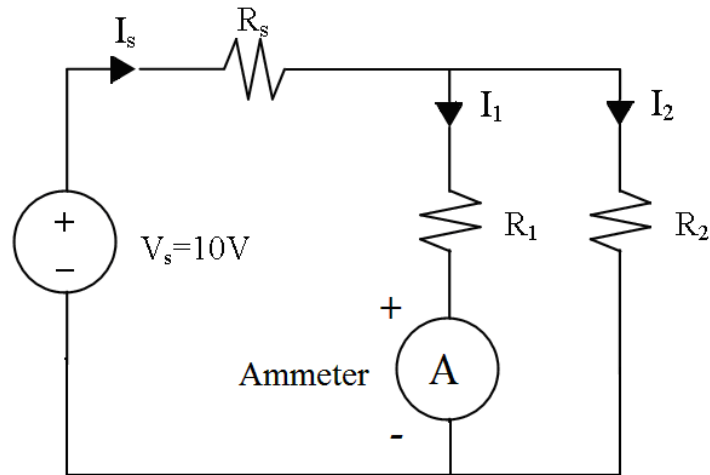
## CURRENT MEASUREMENT DETAILS ON FIG.2

**Measuring  $I_1$**  (the current thru  $R_1$ ) using an Ammeter  
( Digital Multimeter running in Ammeter Position)




Note: The ammeter above can also be placed before the resistor  $R_1$

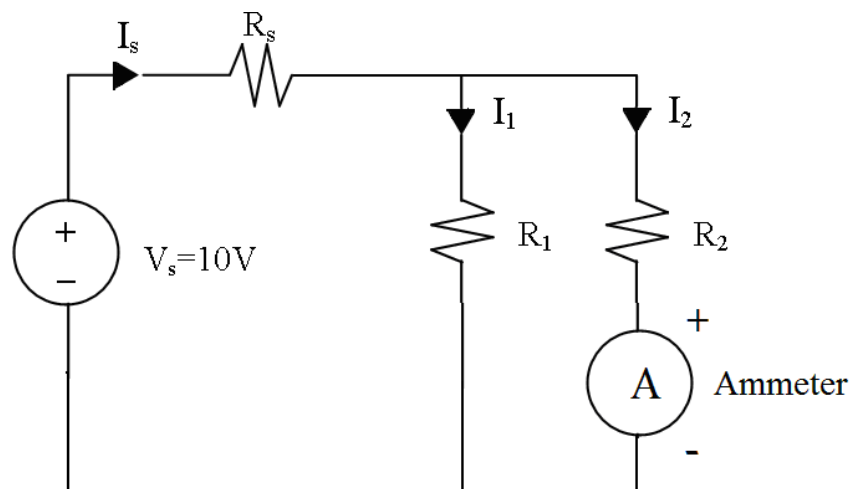**Measuring  $I_2$**  (the current thru  $R_1$ ) using an Ammeter



Note: The ammeter above can also be placed before the resistor  $R_2$

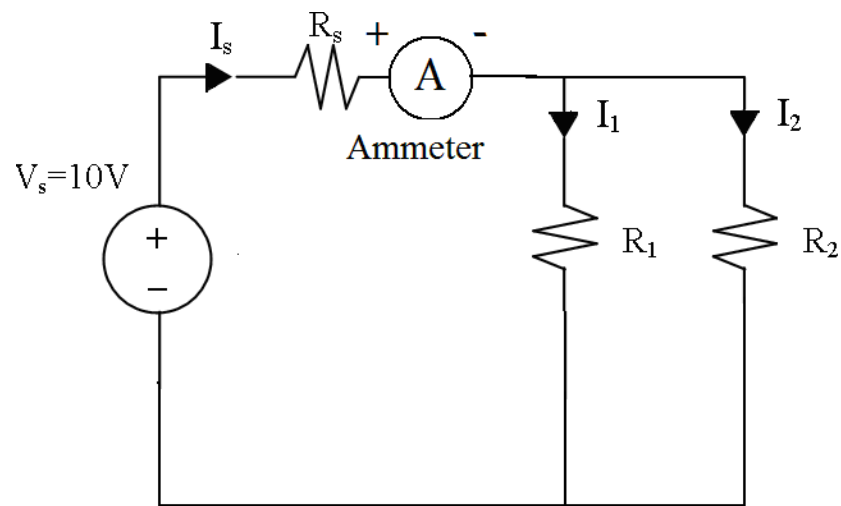Measuring the total current  $I_s$  (or the supply current)



Note: The following is another alternative when measuring  $I_s$

