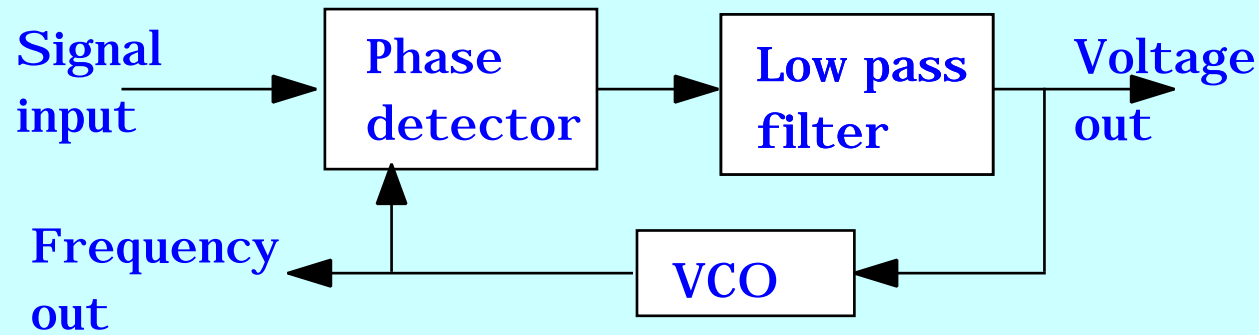


# Phase Locked Loops - PLL

---

- **frequency selective feedback system**

wide use in FM detectors, stereo demodulators, tone decoders, frequency synthesisers, frequency synchronisation,...



- **Voltage Controlled Oscillator**

in feedback loop

reference oscillation, with frequency dependent on DC voltage

- **Phase detector**

compares periodic input signal with output of VCO and adjusts in response

- **Low pass filter**

generates correction voltage from phase detector output

# PLL operation

- **No signal present**

error voltage = 0

VCO "free runs" at  $f_0$

- **Apply periodic signal at  $f_s$**


$f_s$   $f_0$

phase comparison with VCO generates error voltage...

...which forces VCO to synchronise with  $f_s$

PLL "locks" onto input frequency

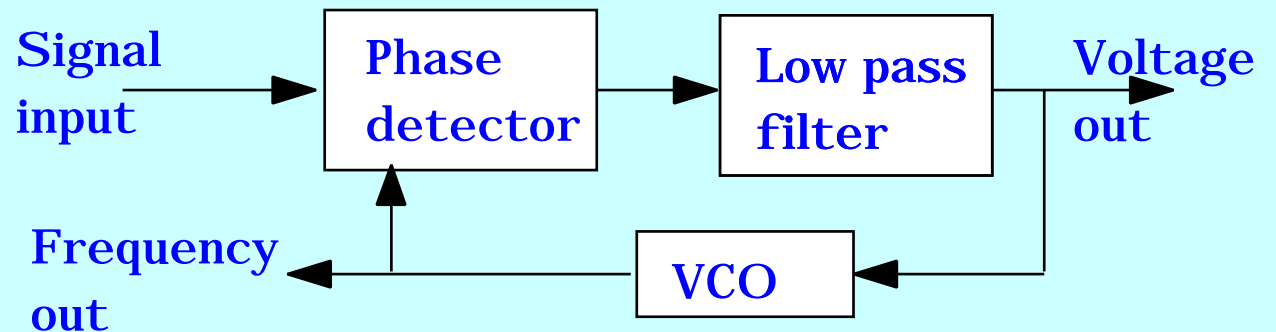VCO frequency identical to input frequency, but with phase difference



- **If input frequency varies slowly, PLL will remain locked**

will track input frequency

eg input clock with jitter (phase noise), PLL will "clean up" clock

FM radio: audio signal much lower frequency than carrier

voltage output will follow audio

# Phase sensitive detection

- Mix input and reference signals

$$V \sim \sin \omega_0 t \cdot \sin \omega_s t$$

produces two components

$$f \sim 2f_0$$

$f = f_0$  ie low frequency

- pass through low pass filter


$$\gg 1/f$$

produces error voltage


- actual method different

$$V_{\text{error}} = A \cos \theta$$

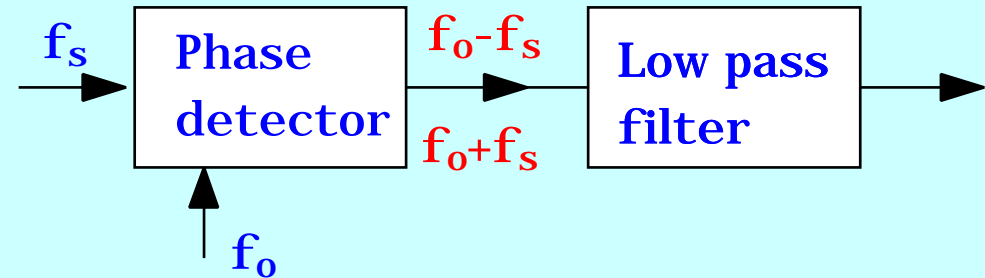cos dependence not ideal for real applications




VCO output

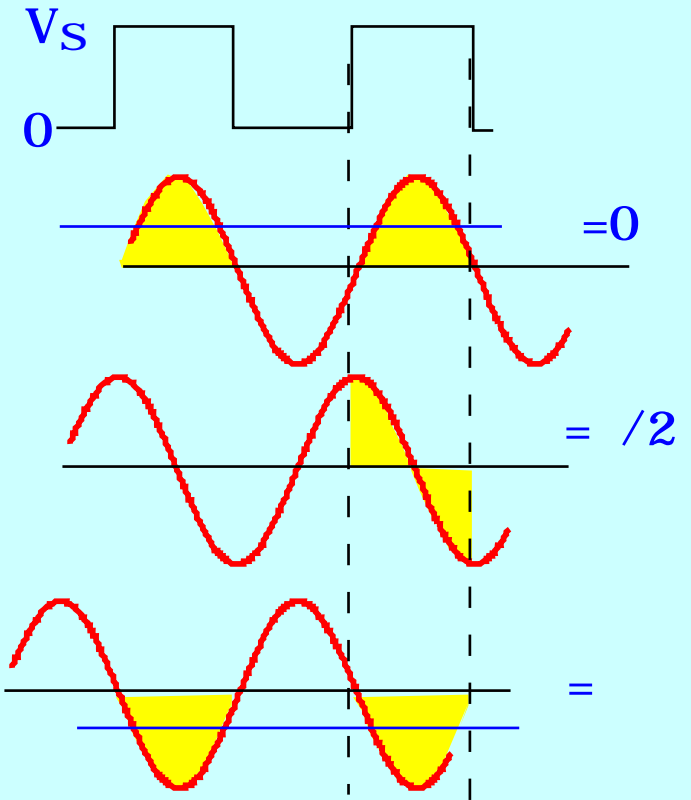


# Improved phase detector

- Transform sine wave to square wave

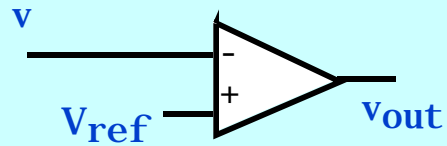

$$V_{ref} = (v_{max} - v_{min})/2$$

or input may already be pulsed


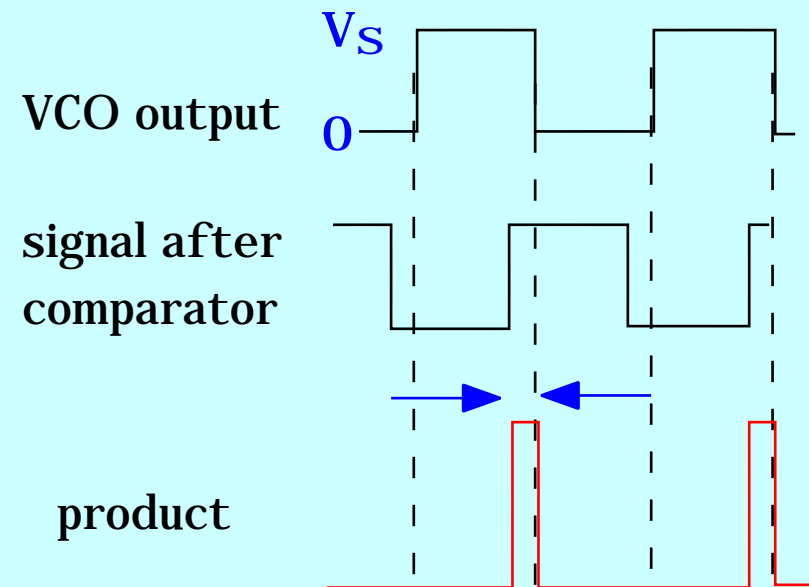


# Voltage Controlled Oscillator VCO

- ideal VCO behaviour

- moderate frequency example

nMOS = switch

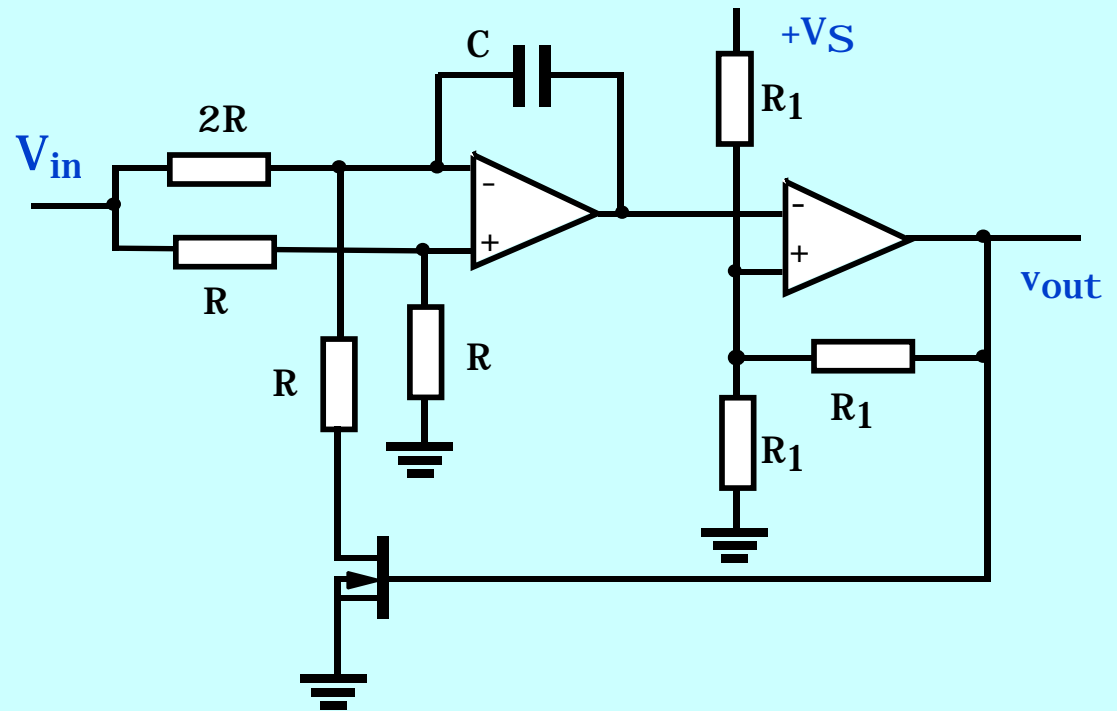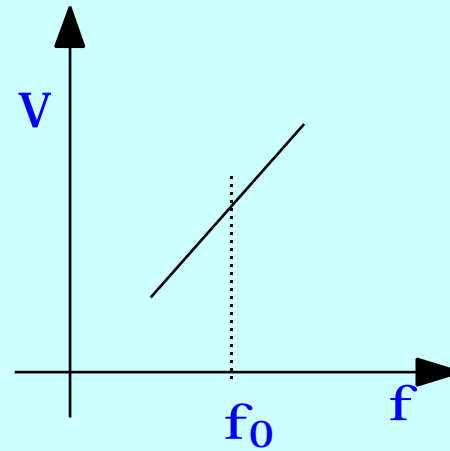

# PLL operation

---


- For phase locking, require  $f_s \approx f_0$   
=> sensitive to finite range of frequencies
- Capture range  
frequency range over which PLL can lock on signal
- Lock range  
frequency range over which PLL can track input variation
- Role of low pass filter - decreasing bandwidth (increasing  $\tau$ )  
slows capture process, increases time to lock  
decreases capture range  
once locked, greater immunity to high frequency interference  
transient response to sudden changes in frequency within capture range becomes underdamped

# PLL applications (i)

---

- **FM demodulation**


PLL tracks variation in frequency

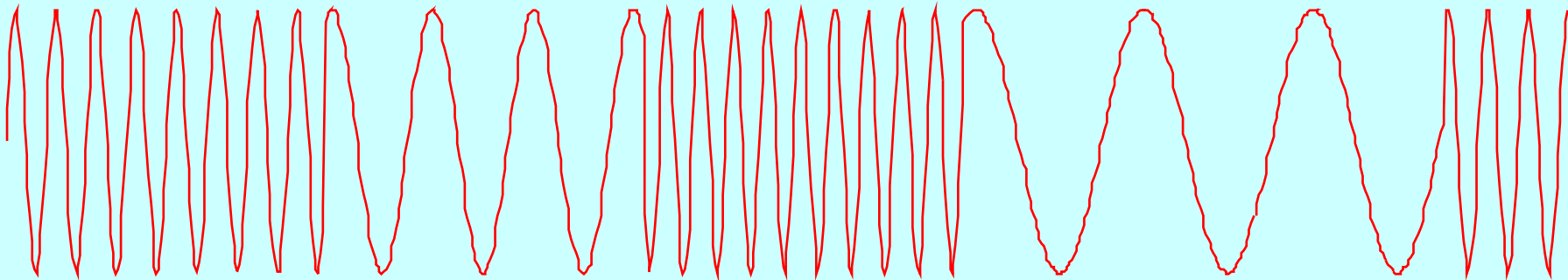

also used in Frequency-shift keying - where mark/space ratio changes, not  $f$

- **AM detection**

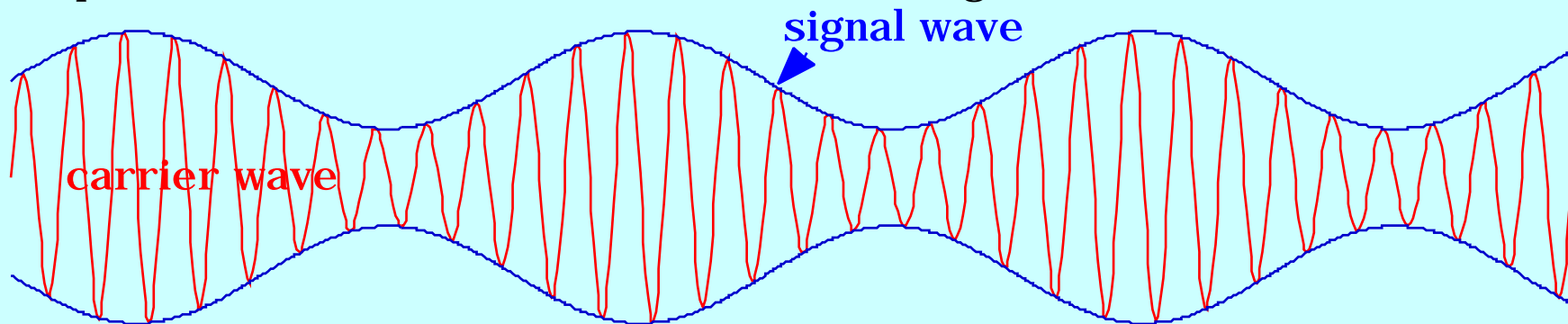if input is sinusoidal, then PLL can demodulate signal from carrier



## PLL applications (ii)


---

- **Frequency synchronisation and signal conditioning**

a poor oscillator can be locked to good reference signal - eg colour TV  
remove out-of-range interference, ie phase jitter

- **Synchronisation for control**

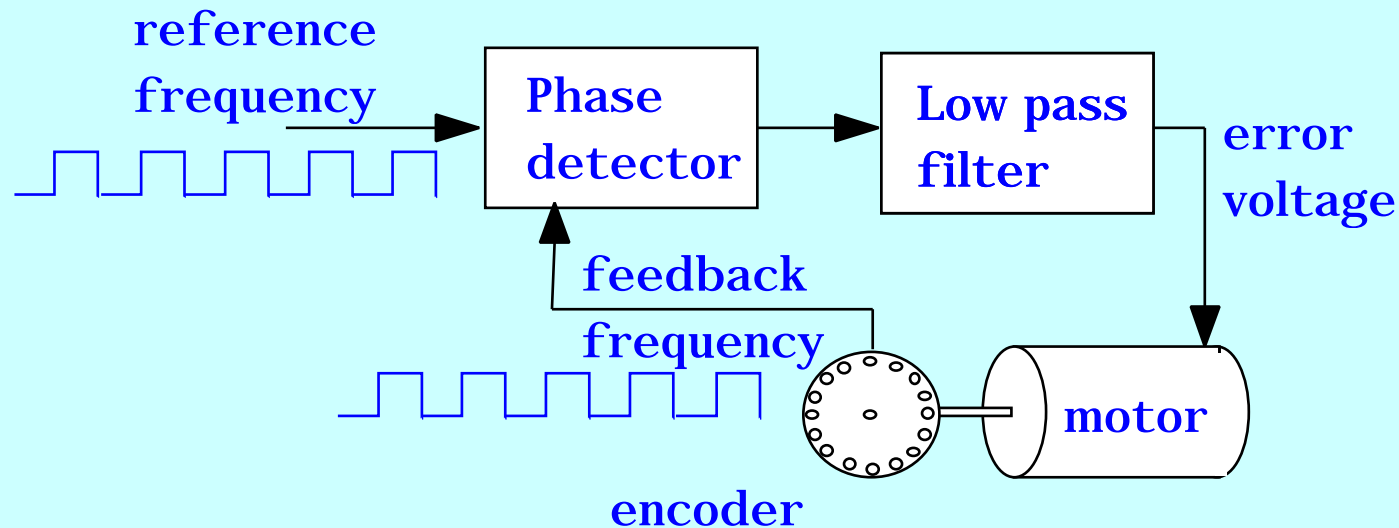eg motor speed - required for many applications  
eg CD player





## PLL applications (iii)

---

- **Frequency synthesis**

multiply reference frequency by  $N$ , by dividing output in feedback loop

- **Frequency translation**

by adjusting response to out of phase signal at input, can offset by small  $\Delta f$

- **Tone or carrier detection**

simply detect if a given frequency is present with magnitude above threshold  
useful eg in stereo decoders, modem