

# Steps for D.C. Analysis of BJT Circuits

To analyze BJT circuit with D.C. sources, we **must** follow these **five steps**:

1. **ASSUME** an operating mode
2. **ENFORCE** the equality conditions of that mode.
3. **ANALYZE** the circuit with the enforced conditions.
4. **CHECK** the inequality conditions of the mode for consistency with original assumption. If consistent, the analysis is complete; if inconsistent, go to step 5.
5. **MODIFY** your original assumption and repeat all steps.

Let's look at each step in **detail**.

## 1. **ASSUME**

We can **ASSUME** Active, Saturation, or Cutoff!

## 2. ENFORCE

### Active

For **active** region, we must ENFORCE **two equalities**.

a) Since the base-emitter junction is **forward** biased in the active region, we ENFORCE these equalities:

$$V_{BE} = 0.7 \text{ V} \quad (\text{npn})$$

$$V_{EB} = 0.7 \text{ V} \quad (\text{pnp})$$

b) We likewise know that in the **active** region, the base and collector currents are directly proportional, and thus we ENFORCE the equality:

$$i_C = \beta i_B$$

Note we can **equivalently** ENFORCE this condition with either of the the equalities:

$$i_C = \alpha i_E \quad \text{or} \quad i_E = (\beta + 1) i_B$$

## Saturation

For **saturation** region, we must likewise **ENFORCE two equalities**.

a) Since the base-emitter junction is **forward** biased, we again **ENFORCE** these equalities:

$$V_{BE} = 0.7 \text{ V} \quad (\text{npn})$$

$$V_{EB} = 0.7 \text{ V} \quad (\text{pnp})$$

b) Likewise, since the collector base junction is **reverse** biased, we **ENFORCE** these equalities:

$$V_{CB} = -0.5 \text{ V} \quad (\text{npn})$$

$$V_{BC} = -0.5 \text{ V} \quad (\text{pnp})$$

Note that from **KVL**, the above two **ENFORCED** equalities will require that these equalities **likewise** be true:

$$V_{CE} = 0.2 \text{ V} \quad (\text{npn})$$

$$V_{EC} = 0.2 \text{ V} \quad (\text{pnp})$$

Note that for saturation, you need to explicitly ENFORCE any **two** of these **three** equalities—the third will be ENFORCED automatically (via KVL)!!

To avoid **negative** signs (e.g.,  $V_{CB} = -0.5$ ), I typically ENFORCE the **first** and **third** equalities (e.g.,  $V_{BE} = 0.7$  and  $V_{CE} = 0.2$ ).

### Cutoff

For a BJT in cutoff, both *pn* junctions are **reverse** biased—no current flows! Therefore we ENFORCE these equalities:

$$i_B = 0$$

$$i_C = 0$$

$$i_E = 0$$

## 3. ANALYZE

### Active

The task in D.C. analysis of a BJT in **active** mode is to find **one** unknown **current** and **one** additional unknown **voltage**!

a) In addition the relationship  $i_C = \beta i_B$ , we have a **second** useful relationship:

$$i_E = i_C + i_B$$

This of course is a consequence of KCL, and is true **regardless** of the BJT mode.

But think about what this means! We have **two** current equations and **three** currents (i.e.,  $i_E, i_C, i_B$ )—we only need to determine **one** current and we can then immediately find the other two!

**Q:** *Which current do we need to find?*

**A:** Doesn't matter! For a BJT operating in the active region, if we know **one** current, we know them **all**!

**b)** In addition to  $V_{BE} = 0.7$  ( $V_{EB} = 0.7$ ), we have a **second** useful relationship:

$$V_{CE} = V_{CB} + V_{BE} \quad (\text{nnp})$$

$$V_{EC} = V_{EB} + V_{BC} \quad (\text{pnp})$$

This of course is a consequence of KVL, and is true **regardless** of the BJT mode.

Combining these results, we find:

$$V_{CE} = V_{CB} + 0.7 \quad (\text{nnp})$$

$$V_{EC} = 0.7 + V_{BC} \quad (\text{pnp})$$

But think about what **this** means! If we find **one** unknown voltage, we can immediately determine the **other**.

Therefore, a D.C. analysis problem for a BJT operating in the active region reduces to:

find one of these values

$$i_B, i_C, \text{ or } i_E$$

and find one of these values

$$V_{CE} \text{ or } V_{CB} \quad (V_{EC} \text{ or } V_{BC})$$

### Saturation

For the saturation mode, we know **all** the BJT voltages, but know nothing about BJT **currents**!

Thus, for an analysis of circuit with a BJT in saturation, we need to find any **two** of the **three** quantities:

$$i_B, i_C, i_E$$

We can then use **KCL** to find the third.

### Cutoff

Cutoff is a bit of the **opposite** of saturation—we know **all** the BJT **currents** (they're all **zero**!), but we know **nothing** about BJT **voltages** !

Thus, for an analysis of circuit with a BJT in cutoff, we need to find any **two** of the **three** quantities:

$$V_{BE}, V_{CB}, V_{CE} \quad (\text{npn})$$

$$V_{EB}, V_{BC}, V_{EC} \quad (\text{pnp})$$

We can then use **KVL** to find the third.

#### 4. CHECK

You do not know if your D.C. analysis is correct unless you **CHECK** to see if it is consistent with your original assumption!

**WARNING!**-Failure to **CHECK** the original assumption will result in a **SIGNIFICANT REDUCTION** in credit on exams, regardless of the accuracy of the analysis !!!

**Q:** *What exactly do we CHECK?*

**A:** We **ENFORCED** the mode **equalities**, we **CHECK** the mode **inequalities**.

#### Active

We must **CHECK two** separate inequalities after analyzing a circuit with a BJT that we **ASSUMED** to be operating in **active** mode. One inequality involves BJT **voltages**, the other BJT **currents**.

a) In the **active** region, the Collector-Base Junction is "off" (i.e., **reverse** biased). Therefore, we must **CHECK** our analysis results to see if they are **consistent** with:

$$V_{CB} > 0 \quad (\text{nnp})$$

$$V_{BC} > 0 \quad (\text{pnp})$$

Since  $V_{CE} = V_{CB} + 0.7$ , we find that an **equivalent** inequality is:

$$V_{CE} > 0.7 \quad (\text{nnp})$$

$$V_{EC} > 0.7 \quad (\text{pnp})$$

We need to check **only** one of these two inequalities (**not both!**).

b) In the active region, the Base-Emitter Junction is "on" (i.e., **forward** biased). Therefore, we must **CHECK** the results of our analysis to see if they are **consistent** with:

$$i_B > 0$$

Since the active mode constants  $\alpha$  and  $\beta$  are **always** positive values, **equivalent** expressions to the one above are:

$$i_C > 0 \quad \text{and} \quad i_E > 0$$

In other words, we need to **CHECK** and see if **any** one of the currents is positive—if one is positive, they are **all** positive!

### Saturation

Here we must **CHECK** inequalities involving BJT **currents**.

a) We know that for saturation mode, the ratio of collector current to base current will be **less than beta!** Thus we **CHECK**:

$$i_C < \beta i_B$$

b) We know that **both** *pn* junctions are **forward** biased, hence we **CHECK** to see if all the **currents are positive**:

$$i_B > 0$$

$$i_C > 0$$

$$i_E > 0$$

## Cutoff

For **cutoff** we must **CHECK** two BJT voltages.

a) Since the EBJ is **reverse biased**, we **CHECK**:

$$V_{BE} < 0 \quad (\text{nnp})$$

$$V_{EB} < 0 \quad (\text{pnp})$$

b) Likewise, since the CBJ is also **reverse biased**, we **CHECK**:

$$V_{CB} > 0 \quad (\text{nnp})$$

$$V_{BC} > 0 \quad (\text{pnp})$$

If the results of our analysis are consistent with **each** of these inequalities, then we have made the **correct** assumption! The numeric results of our analysis are then likewise correct. We can stop working!

However, if **even one** of the results of our analysis is **inconsistent** with active mode (e.g., currents are negative, or  $V_{CE} < 0.7$ ), then we have made the **wrong** assumption! Time to move to step 5.

## 5. *MODIFY*

If one or more of the BJTs are **not** in the active mode, then it must be in either **cutoff** or **saturation**. We must change our assumption and start **completely** over!

In general, **all** of the results of our previous analysis are incorrect, and thus must be **completely** scraped!