



The MOSFET as an Amplifier

Operation and small signal model

Dr. Alaa El-Din Hussein

March 21, 2008



Outline

- 1 Basic Operation
- 2 Large Signal Operation
- 3 MOSFET Amplifier Biasing
- 4 MOSFET Small Signal Operation
- 5 Small Signal Model



Outline

- 1 Basic Operation
- 2 Large Signal Operation
- 3 MOSFET Amplifier Biasing
- 4 MOSFET Small Signal Operation
- 5 Small Signal Model



The Transistor as An Amplifier

How it works?



Basic Idea

- Step 1: Set the transistor at a certain DC level (**BIASING**)
- Step 2: Inject a small signal to the input and get a bigger output (**COUPLING**)

Important

- Biasing point will determine AC Gain, I/P Impedance, O/P Impedance, and Maximum Output Swing



The Transistor as An Amplifier

How it works?



Basic Idea

- Step 1: Set the transistor at a certain DC level (**BIASING**)
- Step 2: Inject a small signal to the input and get a bigger output (**COUPLING**)

Important

- Biasing point will determine AC Gain, I/P Impedance, O/P Impedance, and Maximum Output Swing



The Transistor as An Amplifier

How it works?



Basic Idea

- Step 1: Set the transistor at a certain DC level (**BIASING**)
- Step 2: Inject a small signal to the input and get a bigger output (**COUPLING**)

Important

- Biasing point will determine AC Gain, I/P Impedance, O/P Impedance, and Maximum Output Swing



The Transistor as An Amplifier

How it works?



Basic Idea

- Step 1: Set the transistor at a certain DC level (**BIASING**)
- Step 2: Inject a small signal to the input and get a bigger output (**COUPLING**)


Important

- Biasing point will determine AC Gain, I/P Impedance, O/P Impedance, and Maximum Output Swing





Outline

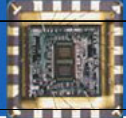
- 1 Basic Operation
- 2 Large Signal Operation**
- 3 MOSFET Amplifier Biasing
- 4 MOSFET Small Signal Operation
- 5 Small Signal Model





Large Signal Operation

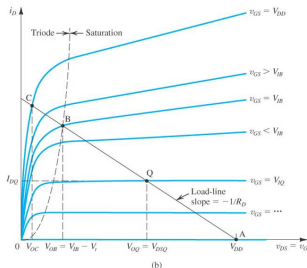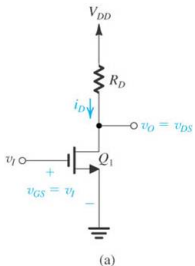

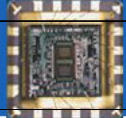- If $v_I < V_t$, the transistor is OFF and we are at point A
- If v_I increased the transistor will be in saturation region A-B
- $v_o = v_{DS} = V_{DD} - R_D \cdot i_D$ as $v_I \uparrow \rightarrow v_o \downarrow$
- If v_I increased beyond point B, the transistor enters triode region B-C





Large Signal Operation

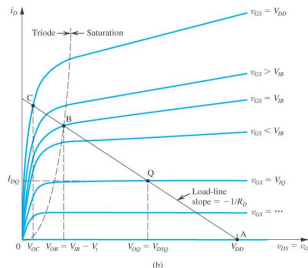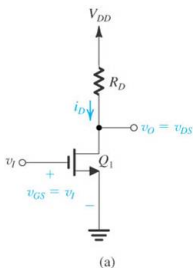

- If $v_I < V_t$, the transistor is OFF and we are at point A
- If v_I increased the transistor will be in saturation region A-B
- $v_o = v_{DS} = V_{DD} - R_D \cdot i_D$ as $v_I \uparrow \rightarrow v_o \downarrow$
- If v_I increased beyond point B, the transistor enters triode region B-C





Large Signal Operation

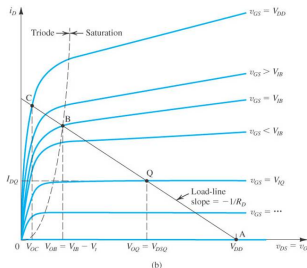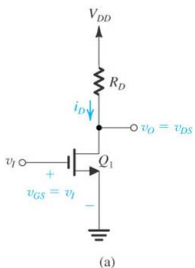

- If $v_I < V_t$, the transistor is OFF and we are at point A
- If v_I increased the transistor will be in saturation region A-B
- $v_o = v_{DS} = V_{DD} - R_D \cdot i_D$ as $v_I \uparrow \rightarrow v_o \downarrow$
- If v_I increased beyond point B, the transistor enters triode region B-C





Large Signal Operation

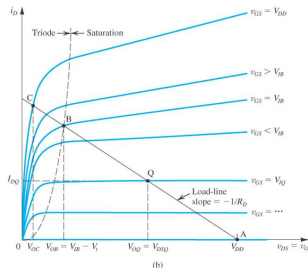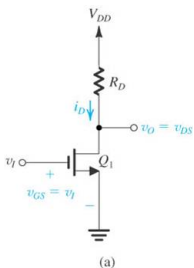


- If $v_I < V_t$, the transistor is OFF and we are at point A
- If v_I increased the transistor will be in saturation region A-B
- $v_o = v_{DS} = V_{DD} - R_D \cdot i_D$ as $v_I \uparrow \rightarrow v_o \downarrow$
- If v_I increased beyond point B, the transistor enters triode region B-C


Large Signal Operation

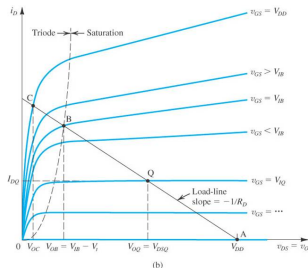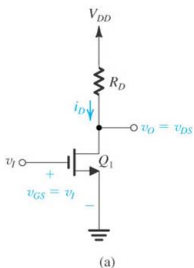

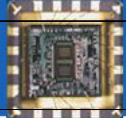
- If $v_I < V_t$, the transistor is OFF and we are at point A
- If v_I increased the transistor will be in saturation region A-B
- $v_o = v_{DS} = V_{DD} - R_D \cdot i_D$ as $v_I \uparrow \rightarrow v_o \downarrow$
- If v_I increased beyond point B, the transistor enters triode region B-C




Large Signal Operation

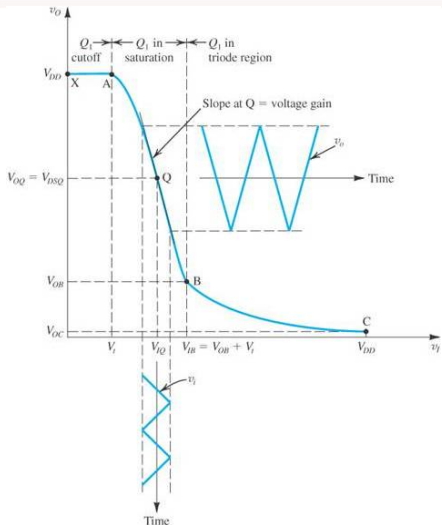

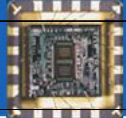
- For small signal the amplification will be linear
- To work as a switch the transistor will work either at points A, or point C (will be studied later)




Large Signal Operation

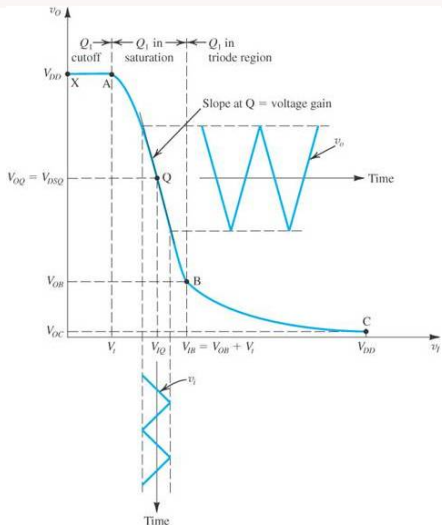

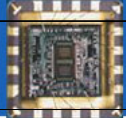- For small signal the amplification will be linear
- To work as a switch the transistor will work either at points A, or point C (will be studied later)



Large Signal Operation

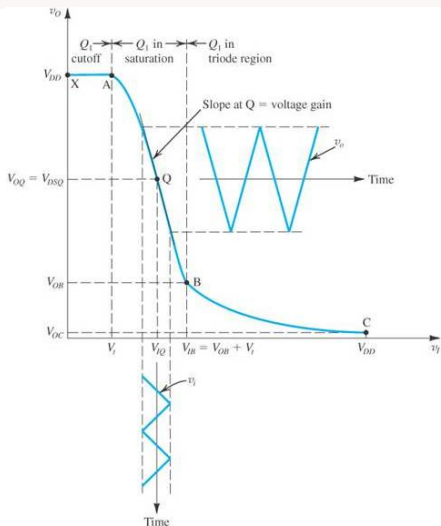


- For small signal the amplification will be linear
- To work as a switch the transistor will work either at points A, or point C (will be studied later)



Large Signal Operation

Maximum Symmetrical Swing

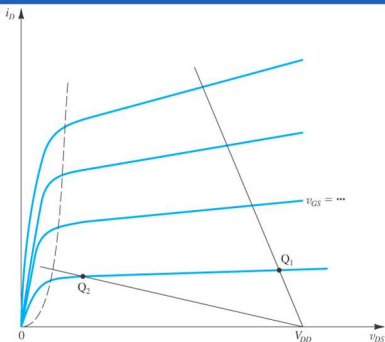


Notes

- Please note the shown two load lines and corresponding bias points.
- Bias point Q_1 does not leave sufficient room for positive signal swing at the drain (too close to V_{DD}).
- Bias point Q_2 is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.



Large Signal Operation

Maximum Symmetrical Swing

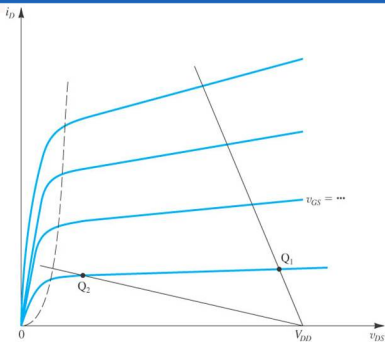


Notes

- Please note the shown two load lines and corresponding bias points.
- Bias point Q_1 does not leave sufficient room for positive signal swing at the drain (too close to V_{DD}).
- Bias point Q_2 is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.



Large Signal Operation

Maximum Symmetrical Swing

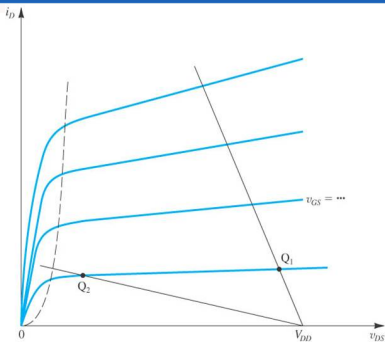


Notes

- Please note the shown two load lines and corresponding bias points.
- Bias point Q_1 does not leave sufficient room for positive signal swing at the drain (too close to V_{DD}).
- Bias point Q_2 is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.



Large Signal Operation

Example

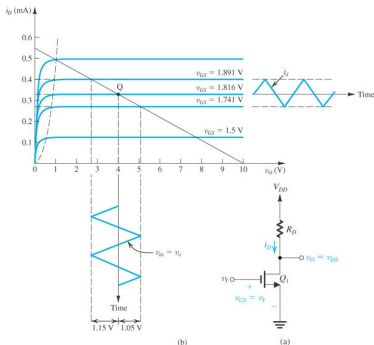


Notes

- The input is a triangular signal with $V_{PP} = 150\text{mV}$.
- From the shown figure: $\text{Gain} = \frac{\Delta v_O}{\Delta v_I} = -\frac{2.2}{0.15} = -14.7\text{V/V}$



Large Signal Operation

Example

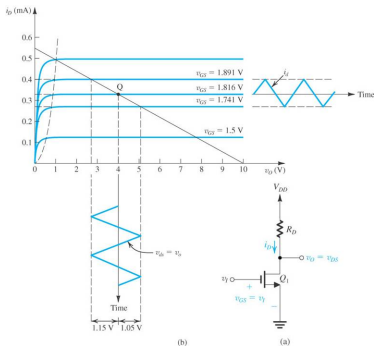


Notes

- The input is a triangular signal with $V_{PP} = 150\text{mV}$.
- From the shown figure: $\text{Gain} = \frac{\Delta v_O}{\Delta v_I} = -\frac{2.2}{0.15} = -14.7\text{V/V}$



Large Signal Operation

Example

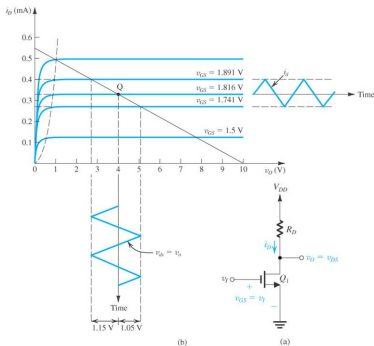

Notes

- The input is a triangular signal with $V_{PP} = 150\text{mV}$.
- From the shown figure: $\text{Gain} = \frac{\Delta v_O}{\Delta v_I} = -\frac{2.2}{0.15} = -14.7\text{V/V}$



Outline

- 1 Basic Operation
- 2 Large Signal Operation
- 3 MOSFET Amplifier Biasing**
- 4 MOSFET Small Signal Operation
- 5 Small Signal Model



MOSFET Amplifier Biasing

Biasing Methods

Several Biasing schemes are available for MOSFET amplifiers. Each of them will have its cons and pros. The mostly common schemes are:

Biasing Schemes

- Fixed V_{GS} Biasing.
- Source Resistance Feedback Biasing.
- Drain Feedback Biasing.
- Constant Current Biasing.



MOSFET Amplifier Biasing

Biasing Methods

Several Biasing schemes are available for MOSFET amplifiers. Each of them will have its cons and pros. The mostly common schemes are:

Biasing Schemes

- Fixed V_{GS} Biasing.
- Source Resistance Feedback Biasing.
- Drain Feedback Biasing.
- Constant Current Biasing.



MOSFET Amplifier Biasing

Biasing Methods

Several Biasing schemes are available for MOSFET amplifiers. Each of them will have its cons and pros. The mostly common schemes are:

Biasing Schemes

- Fixed V_{GS} Biasing.
- Source Resistance Feedback Biasing.
- Drain Feedback Biasing.
- Constant Current Biasing.



MOSFET Amplifier Biasing

Biasing Methods

Several Biasing schemes are available for MOSFET amplifiers. Each of them will have its cons and pros. The mostly common schemes are:

Biasing Schemes

- Fixed V_{GS} Biasing.
- Source Resistance Feedback Biasing.
- Drain Feedback Biasing.
- Constant Current Biasing.



MOSFET Amplifier Biasing

Biasing Methods

Several Biasing schemes are available for MOSFET amplifiers. Each of them will have its cons and pros. The mostly common schemes are:


Biasing Schemes

- Fixed V_{GS} Biasing.
- Source Resistance Feedback Biasing.
- Drain Feedback Biasing.
- Constant Current Biasing.




MOSFET Amplifier Biasing

Fixed V_{GS} Biasing

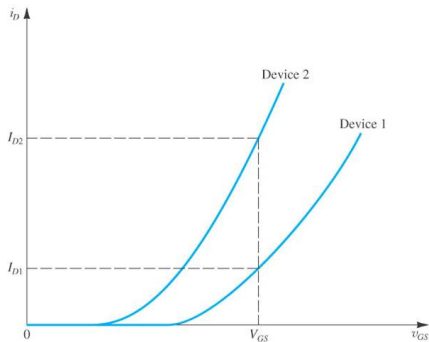


Notes

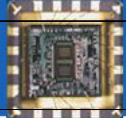- Please note that changing the device may result in a large change in the drain current and hence the operating point and the amplifier performance.



MOSFET Amplifier Biasing

Fixed V_{GS} Biasing

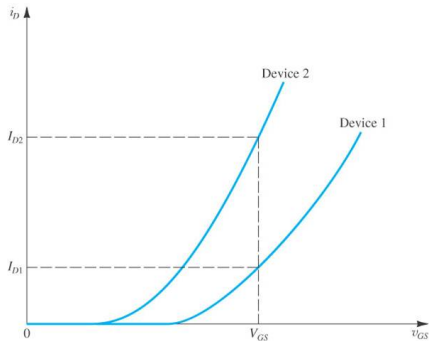


Notes

- Please note that changing the device may result in a large change in the drain current and hence the operating point and the amplifier performance.



MOSFET Amplifier Biasing

Source Resistance Feedback Biasing

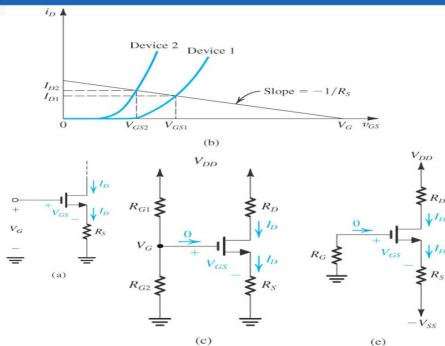


Notes

- Please note that changing the device will result in a reduced change in the drain current compared to the fixed $V_G S$.
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single supply as in (c) or dual supplies as in (e).




MOSFET Amplifier Biasing

Source Resistance Feedback Biasing

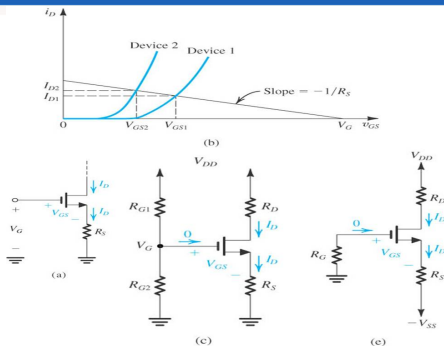


Notes

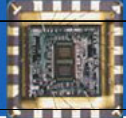- Please note that changing the device will result in a reduced change in the drain current compared to the fixed V_{GS} .
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single supply as in (c) or dual supplies as in (e).




MOSFET Amplifier Biasing

Source Resistance Feedback Biasing

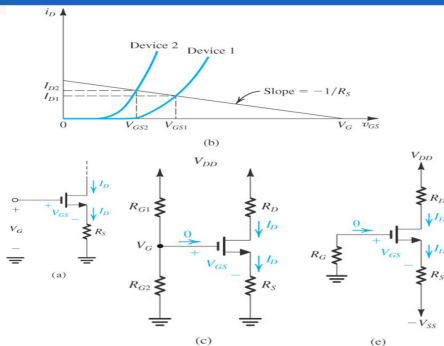


Notes

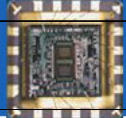- Please note that changing the device will result in a reduced change in the drain current compared to the fixed $V_G S$.
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single supply as in (c) or dual supplies as in (e).



MOSFET Amplifier Biasing

Source Resistance Feedback Biasing

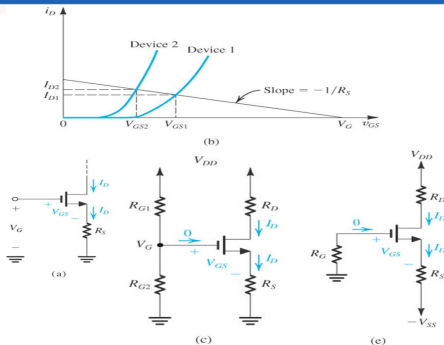


Notes

- Please note that changing the device will result in a reduced change in the drain current compared to the fixed $V_G S$.
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single supply as in (c) or dual supplies as in (e).




MOSFET Amplifier Biasing

Drain Feedback Biasing

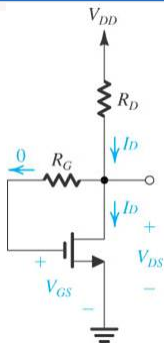


Notes

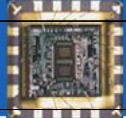- Please note that the transistor is always in saturation as $V_{GS} = V_{DS}$
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single/dual supply.



MOSFET Amplifier Biasing

Drain Feedback Biasing

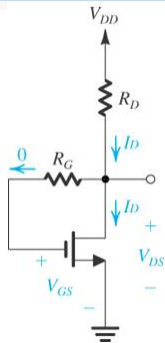


Notes

- Please note that the transistor is always in saturation as $V_{GS} = V_{DS}$
- If I_D is increased (e.g. by temperature) V_{GS} will increase and V_{DS} will decrease stabilizing I_D
- It could utilize single/dual supply.




MOSFET Amplifier Biasing

Drain Feedback Biasing

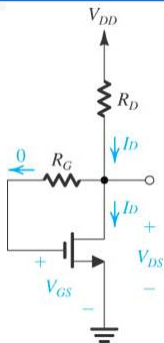


Notes

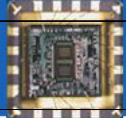- Please note that the transistor is always in saturation as $V_{GS} = V_{DS}$
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single/dual supply.



MOSFET Amplifier Biasing

Drain Feedback Biasing

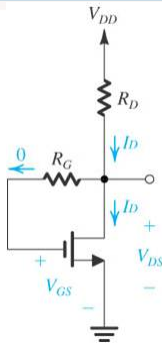


Notes

- Please note that the transistor is always in saturation as $V_{GS} = V_{DS}$
- If I_D is increased (e.g. by temperature) V_S will increase and V_{GS} will decrease stabilizing I_D
- It could utilize single/dual supply.



MOSFET Amplifier Biasing

Constant Current Biasing

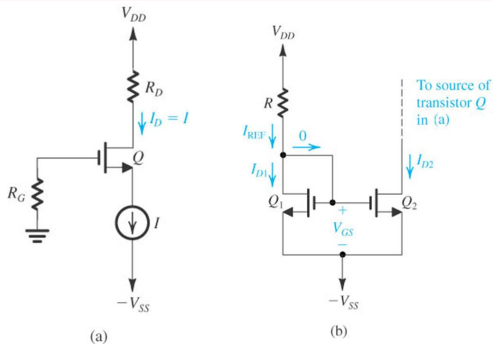


Notes

- Please note that the drain current will be independent of the amplifier transistor.
- the current source is constructed of a current mirror as shown in (b)
- Dual supplies are usually needed.



MOSFET Amplifier Biasing

Constant Current Biasing

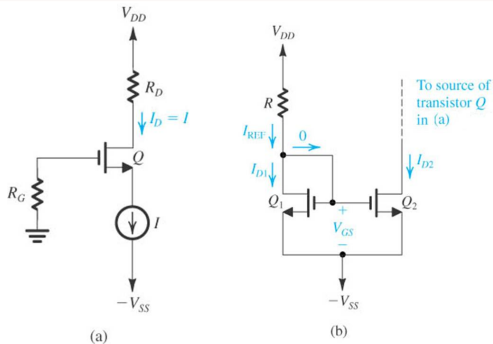


Notes

- Please note that the drain current will be independent of the amplifier transistor.
- the current source is constructed of a current mirror as shown in (b)
- Dual supplies are usually needed.



MOSFET Amplifier Biasing

Constant Current Biasing

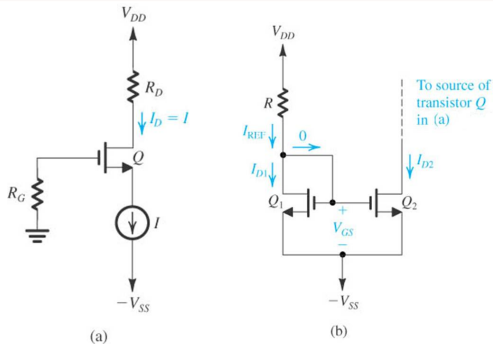


Notes

- Please note that the drain current will be independent of the amplifier transistor.
- the current source is constructed of a current mirror as shown in (b)
- Dual supplies are usually needed.



MOSFET Amplifier Biasing

Constant Current Biasing

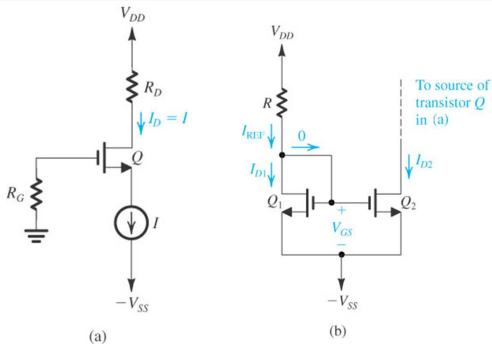


Notes

- Please note that the drain current will be independent of the amplifier transistor.
- the current source is constructed of a current mirror as shown in (b)
- Dual supplies are usually needed.




Outline

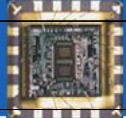- 1 Basic Operation
- 2 Large Signal Operation
- 3 MOSFET Amplifier Biasing
- 4 MOSFET Small Signal Operation**
- 5 Small Signal Model



MOSFET Small Signal Operation

Basic Operation


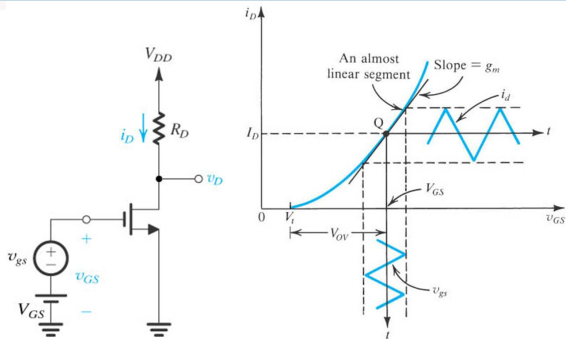


Notes

- v_{GS} represents the total voltage (D.C+A.C), V_{GS} represents the D.C only (Q-Point), and v_{gs} represents the A.C only (small signal).
- For small signal the characteristic is linear.
- The DC biasing is important to set the small signal parameters (e.g. g_m)
- Can you think what will happen if the DC is removed?

MOSFET Small Signal Operation

Basic Operation

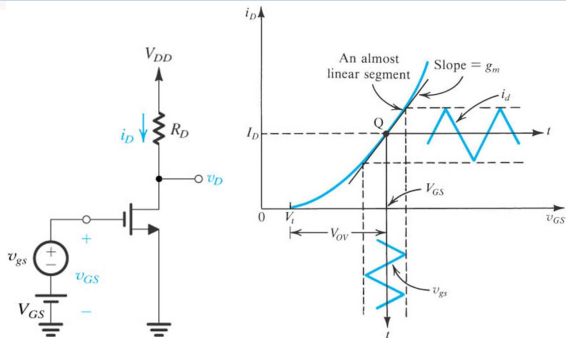
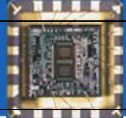


Notes

- v_{GS} represents the total voltage (D.C+A.C), V_{GS} represents the D.C only (Q-Point), and v_{gs} represents the A.C only (small signal).
- For small signal the characteristic is linear.
- The DC biasing is important to set the small signal parameters (e.g. g_m)
- Can you think what will happen if the DC is removed?


MOSFET Small Signal Operation

Basic Operation

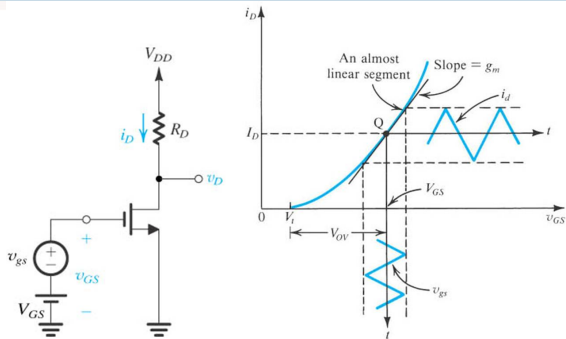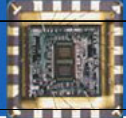


Notes

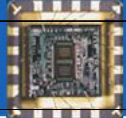- v_{GS} represents the total voltage (D.C+A.C), V_{GS} represents the D.C only (Q-Point), and v_{gs} represents the A.C only (small signal).
- For small signal the characteristic is linear.
- The DC biasing is important to set the small signal parameters (e.g. g_m)
- Can you think what will happen if the DC is removed?




MOSFET Small Signal Operation

Basic Operation

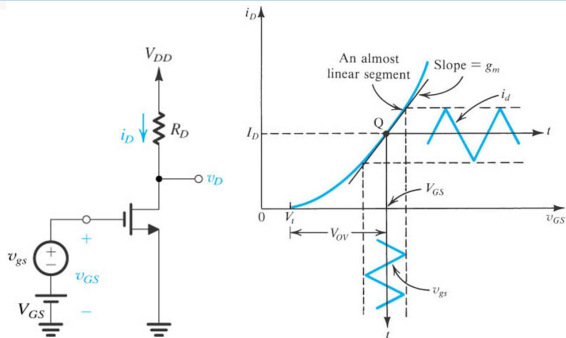


Notes

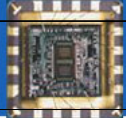- v_{GS} represents the total voltage (D.C+A.C), V_{GS} represents the D.C only (Q-Point), and v_{gs} represents the A.C only (small signal).
- For small signal the characteristic is linear.
- The DC biasing is important to set the small signal parameters (e.g. g_m)
- Can you think what will happen if the DC is removed?




MOSFET Small Signal Operation

Example

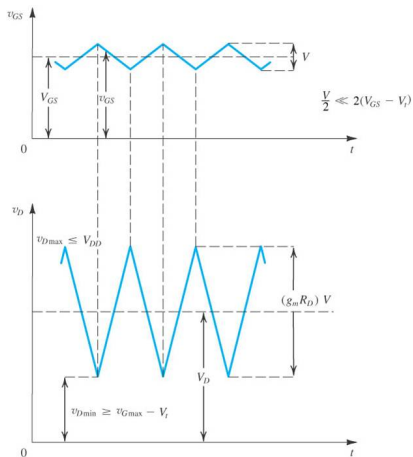


Notes

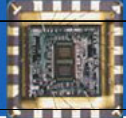- From the figure, the gain equals $g_m \cdot R_D$
- $v_{Dmax} = V_{DD}$
- $v_{Dmin} = V_{Gmax} - V_t$ to ensure saturation operation.




MOSFET Small Signal Operation

Example

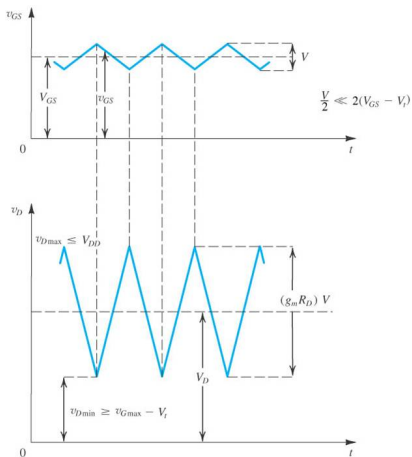


Notes

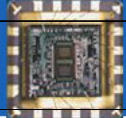- From the figure, the gain equals $g_m \cdot R_D$
- $v_{Dmax} = V_{DD}$
- $v_{Dmin} = V_{Gmax} - V_t$ to ensure saturation operation.



MOSFET Small Signal Operation

Example

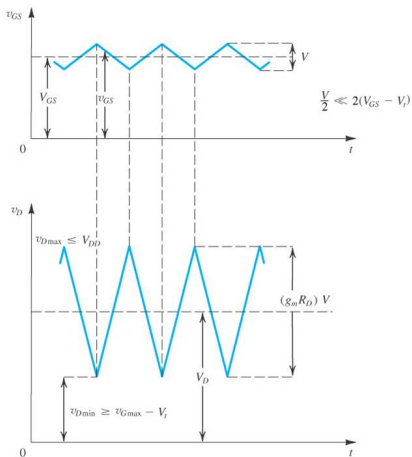


Notes

- From the figure, the gain equals $g_m \cdot R_D$
- $v_{Dmax} = V_{DD}$
- $v_{Dmin} = V_{Gmax} - V_t$ to ensure saturation operation.



MOSFET Small Signal Operation

Example

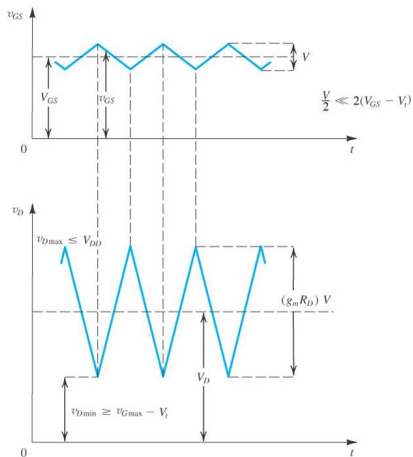

Notes

- From the figure, the gain equals $g_m \cdot R_D$
- $v_{Dmax} = V_{DD}$
- $v_{Dmin} = V_{Gmax} - V_t$ to ensure saturation operation.




Outline

- 1 Basic Operation
- 2 Large Signal Operation
- 3 MOSFET Amplifier Biasing
- 4 MOSFET Small Signal Operation
- 5 Small Signal Model**



MOSFET Small Signal Model

y-parameters

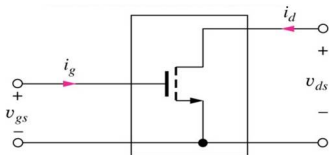

Using 2-port y-parameter network,

$$i_g = y_{11} v_{gs} + y_{12} v_{ds}$$

$$i_d = y_{21} v_{gs} + y_{22} v_{ds}$$

The port variables can represent either time-varying part of total voltages and currents or small changes in them away from Q-point values.

$$y_{11} = \left. \frac{i_g}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\partial i_G}{\partial v_{GS}} \right|_{Q\text{-point}} = 0$$

$$y_{12} = \left. \frac{i_g}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\partial i_G}{\partial v_{DS}} \right|_{Q\text{-point}} = 0$$


$$y_{21} = \left. \frac{i_d}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{Q\text{-point}} = \frac{2I_D}{V_{GS} - V_{TN}}$$

$$y_{22} = \left. \frac{i_d}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{Q\text{-point}} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}}$$



MOSFET Small Signal Model

Small Signal Parameters

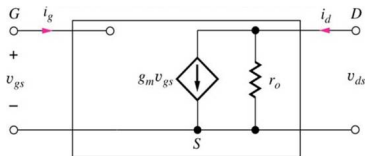

- Since the gate is insulated from the channel by gate-oxide, the input resistance of the transistor is infinite.
- Small-signal parameters are controlled by the Q-point.

Transconductance:

$$g_m = y_{21} = \frac{I_D}{\frac{V_{GS} - V_{TN}}{2}} = \sqrt{2K_n I_D}$$

Output resistance:

$$r_o = \frac{1}{y_{22}} = \frac{1}{\lambda + V_{DS}} \approx \frac{1}{\lambda I_D}$$



MOSFET Small Signal Model

Small Signal Condition

The drain current in the saturation region is given by:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2$$

$$\therefore i_D = I_D + i_d = \frac{K_n}{2} \left[(V_{GS} - V_{TN})^2 + 2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2 \right]$$

$$\therefore i_d = \frac{K_n}{2} [2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2]$$


For linearity, i_d should be proportional to v_{gs} , that means

$$v_{gs} \ll 2(V_{GS} - V_{TN})$$

Change in drain current that corresponds to small-signal operation is:


$$\frac{i_d}{I_D} = \frac{g_m}{I_D} v_{gs} = \frac{2v_{gs}}{V_{GS} - V_{TN}} \ll 4$$

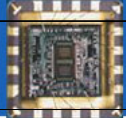If we considered \ll means 0.1 then $i_d/I_D \approx 0.4$




MOSFET Small Signal Model

T-Equivalent Small Signal Model


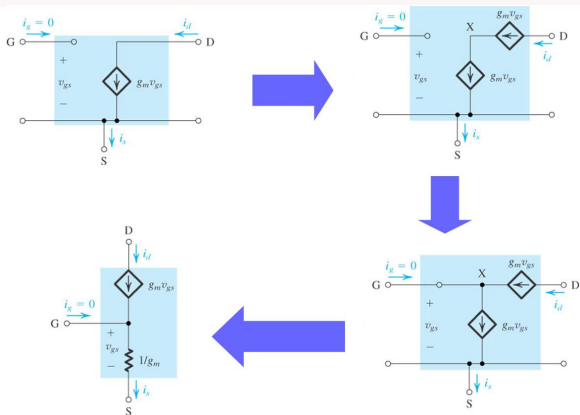


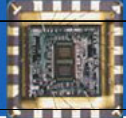- The T-model may be obtained as shown
- It may ease the analysis if source resistance is exist



MOSFET Small Signal Model

T-Equivalent Small Signal Model with r_o

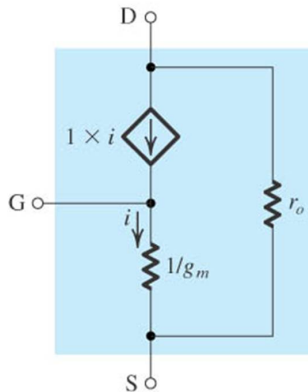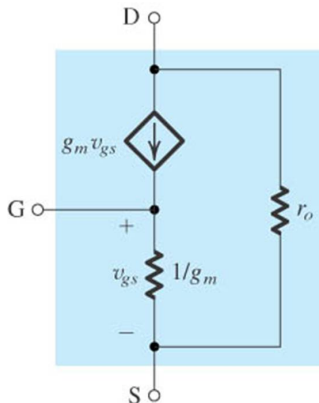

■ r_o may be added as shown