

Digital Logic

Appendix A

Boolean Algebra

Gates

Combinatorial Circuits

Sequential Circuits

19.9.2000

Copyright Teemu Kerola 2000

1

Boolean Algebra

- George Boole
 - ideas 1854
- Claude Shannon,
 - apply to circuit design, 1938 (piirisuunnittelu)
- Describe digital circuitry function
 - programming language?
- Optimise given circuitry
 - use algebra (Boolean algebra) to manipulate (Boolean) expressions into simpler expressions

19.9.2000

Copyright Teemu Kerola 2000

2

Boolean Algebra

- Variables: A, B, C
- Values: TRUE (1), FALSE (0)
- Basic logical operations:
 - binary: AND (\bullet), OR (+) $A \bullet B = AB$ $B + C$
 - unary: NOT ($\bar{}$) \bar{A} (ja, tai, ei)
- Composite operations, equations
 - precedence: NOT, AND, OR
 - parenthesis $D = A + \bar{B} \bullet C = A + ((\bar{B})C)$

19.9.2000

Copyright Teemu Kerola 2000

3

Boolean Algebra

- Other operations
 - NAND $A \text{ NAND } B = \text{NOT}(A \text{ AND } B) = \overline{AB}$
 - NOR $A \text{ NOR } B = \text{NOT}(A \text{ OR } B) = \overline{A + B}$
- Truth tables
 - What is the result of the operation?

Table A.1

	Q	
AND	0	1
0	0	0
1	0	1

19.9.2000

Copyright Teemu Kerola 2000

4

Postulates, Identities in Boolean Algebra

- How can I manipulate expressions?
 - Simple set of rules?
- Basic identities
 - commutative laws
 - distributive laws
 - identity elements
 - inverse elements
 - associative laws
 - DeMorgan's theorem

Table A.2

(vaihdantalait)
(osittelulait)
(identiteetit)
(vasta-alkiot)
(liitääntälait)
(DeMorganin laki)

19.9.2000

Copyright Teemu Kerola 2000

5

Gates

(portit)

- Fundamental building blocks
 - easy to build
 - implement basic Boolean algebra operations
- Combine to build more complex circuits
 - memory, adder, multiplier
- 1-3 inputs, 1 output
 - Fig. A.1
 - AND
- Gate delay
 - change inputs, new output available after gate delay

Fig. A.1



(viive)

19.9.2000

Copyright Teemu Kerola 2000

6

Functionally Complete Set


- Can build all basic gates (and, or, not) from a smaller set of gates

– and, or, not (trivial!)

– and, not

• OR?
 
$$A + B = \overline{\overline{A} \cdot \overline{B}}$$



OR

– or, not

– nand

Fig A.2

– nor

Fig A.3

Combinational Circuits ₍₃₎

(yhdistelmä-
piirit)

- Interconnected set of gates
 - change input, wait for gate delays, new output
- Output is Boolean function of input signals
 - m (binary, Boolean) inputs
 - n (binary, Boolean) outputs
- Described in three ways
 - Boolean equations (one for each output)

$$F = \overline{ABC} + \overline{ABC} + ABC$$

– truth table

Table A.3

– graphical symbols describe implementation
with gates and wires

Fig A.4

Simplify Presentation (and Implementation) ⁽³⁾

- Boolean equations

- Sum of products form (SOP)

$$F = \overline{ABC} + \overline{ABC} + ABC$$

Fig A.4

- Product of sums form (POS)

$$F = (A + B + C) \bullet (A + B + \overline{C}) \bullet (\overline{A} + B + C) \\ \bullet (\overline{A} + B + \overline{C}) \bullet (\overline{A} + \overline{B} + \overline{C})$$

Fig A.5

Boolean
algebra

Which presentation is better?

- Fewer gates? Smaller area on chip?
Smaller circuit delay? Faster?

Algebraic Simplification

- Circuits become too large to handle?
- Use basic identities to simplify Boolean expressions

$$F = \overline{ABC} + \overline{ABC} + ABC \\ = \overline{AB} + \overline{BC} = B(\overline{A} + \overline{C})$$

Fig A.5

Fig A.6

- May be difficult to do
- How to do it automatically?
- Build a program to do it “best”?

Karnaugh Map Squares

- Each square represents complete input value combination (canonical form)
 - adjacent squares differ only in one input value (wrap around)
- Square for input value combination
 $\overline{ABCD} = 1001$
- | CD: | 00 | 01 | 11 | 10 |
|-----|------|------|------|------|
| AB | 0000 | 0001 | 0011 | 0010 |
| 00 | 0100 | 0101 | 0111 | 0110 |
| 01 | 1100 | 1101 | 1111 | 1110 |
| 11 | 1000 | 1001 | 1011 | 1010 |
| 10 | | | | |
- order!!

19.9.2000

Copyright Teemu Kerola 2000

11

Karnaugh Maps

- Represent Boolean function (I.e., circuit) truth table in another way
 - each square is **one product** in sums-of-products (SOP) presentation
 - value is one (1) iff corresponding input values give value 1
 - value is function value for those input values

	CD	00	01	11	10
00				1	
01					
11		1			
10			1		


$F = \overline{AB}CD + ABCD + A\overline{B}C\overline{D}$

19.9.2000

Copyright Teemu Kerola 2000

12

Karnaugh Map Simplification

 - Starting point:
 - Adjacent squares differ only in one input variable value
-  Adjacent squares have value 1
 \downarrow
 $C \quad \bar{C}$ Input values differ only in one variable
 \downarrow
 Value of that variable is irrelevant
 (when all other input variables are fixed to corresponding values for those squares)
 \downarrow
 Can ignore that variable for those expressions

19.9.2000

Copyright Teemu Kerola 2000

13

Using Karnaugh Maps to Minimize Boolean Functions ⁽⁶⁾


Original function

$$f = \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd + ab\bar{c}\bar{d} + ab\bar{c}d + abcd + abc\bar{d} + a\bar{b}cd + a\bar{b}c\bar{d}$$

Canonical form (now already there)

Karnaugh Map

 Find smallest number of circles, each with largest number of 1's



Select parameter combinations corresponding to the circles

Get reduced function $f = bd + ac + ab$


19.9.2000

Copyright Teemu Kerola 2000

14

Impossible Input Variable Combinations

 - What if some input combinations can never occur?
 - Mark them "don't care"
 - or "d"
 - treat them as 0 or 1, whichever is best
 - more room to optimize




19.9.2000

Copyright Teemu Kerola 2000

15

 Example: Circuit to add 1 (mod 10) to 4-bit BCD decimal number $(_4)$



Truth table?

Table A.4

Karnaugh maps for W, X, Y and Z?

Fig. A.10

19.9.2000

Copyright Teemu Kerola 2000

16

Quine-McKluskey Method

- Another method to minimise Boolean expressions
- Why?
 - Karnaugh maps become complex with 6 input variables
- Quine-McKluskey method
 - tabular method
 - automatically suitable for programming
 - details skipped

19.9.2000

Copyright Teemu Kerola 2000

17

Basic Combinational Circuits

- Building blocks for more complex circuits
 - Multiplexer
 - Encoders/decoder
 - Read-Only-Memory
 - Adder

19.9.2000

Copyright Teemu Kerola 2000

18

Multiplexers ₍₂₎

- Select one of many possible inputs to output
 - black box Fig A.12
 - simple truth table Tbl A.7
 - implementation Fig A.13
- Each input “line” can be many parallel lines
 - select one of three 16 bit values Fig A.14
 - $C_{0..15}$, $IR_{0..15}$, $ALU_{0..15}$
 - simple extension to one line selection

19.9.2000

Copyright Teemu Kerola 2000

19

Encoders/Decoders

- Only one of many Encoder input or Decoder output lines can be 1
- Encode the line number as output
 - hopefully less pins (wires) needed this way
 - Example:
 - encode 8 input wires with 3 output pins
 - route 3 wires around the board
 - decode 3 wires back to 8 wires at targetFig A.15

19.9.2000

Copyright Teemu Kerola 2000

20

Read-Only-Memory (ROM) (4)

- Given input values, get output value
- Consider input as address, output as contents of memory location
- Truth tables for a ROM
 - 64 bit ROM
 - 16 words, each 4 bits wide

$$\text{Mem (7)} = 4 \quad \text{Mem (11)} = 14$$


- Implementation with decoder & or gates

19.9.2000

Copyright Teemu Kerola 2000

21

Adders (4)

 

Implementation Table A.9, Fig A.22

Build 4-bit adder from 4 1-bit adders Fig A.21

19.9.2000

Copyright Teemu Kerola 2000

22

Sequential Circuit

(sarjalliset piirit)

- Circuit has (modifiable) internal state
- Output of circuit depends (also) on internal state
 - not only from current inputs
 - output = $f(\text{input}, \text{state})$
 - new state = $f(\text{input}, \text{state})$
- Processor control, registers

19.9.2000


Copyright Teemu Kerola 2000

23

Flip-Flop

(kiikku)

 - 2 states for Q (0 or 1, true or false)
- 2 outputs Q and \bar{Q}
 - complement values
 - both always available on different pins
- Need to be able to change the state (Q)




19.9.2000

Copyright Teemu Kerola 2000

24


S-R Flip-Flop or S-R Latch ⁽⁴⁾ (laituri)

 

“Write 1” = “set S=1 for a short time” = “set” 1
0

“Write 0” = “set R=1 for a short time” = “reset”
 
$$\begin{aligned} \text{nor } (0, 0) &= 1 \\ \text{nor } (0, 1) &= 0 \\ \text{nor } (1, 0) &= 0 \\ \text{nor } (1, 1) &= 0 \end{aligned}$$



19.9.2000


Copyright Teemu Kerola 2000

25

S-R Latch Stable States ⁽³⁾

- 1 bit memory (value = value of Q)
- bi-stable, when R=S=0
 - Q=0?
 - Q=1?
 
$$\begin{aligned} \text{nor } (0, 0) &= 1 \\ \text{nor } (0, 1) &= 0 \\ \text{nor } (1, 0) &= 0 \\ \text{nor } (1, 1) &= 0 \end{aligned}$$




19.9.2000

Copyright Teemu Kerola 2000

26


S-R Latch Set (1) and Reset (0) _(n)

Write 1: $S=0 \rightarrow 1 \rightarrow 0$

 

Write 0: $R=0 \rightarrow 1 \rightarrow 0$

 $\text{nor}(0,0)=1$
 $\text{nor}(0,1)=0$
 $\text{nor}(1,0)=0$
 $\text{nor}(1,1)=0$



19.9.2000

Copyright Teemu Kerola 2000

27

Clocked Flip-Flops

- State change can happen only when clock is 1
 - more control on state changes
- Clocked S-R Flip-Flop Fig. A.26
- D Flip-Flop Fig. A.27
 - only one input D
 - $D = 1$ and CLOCK \rightarrow write 1
 - $D = 0$ and CLOCK \rightarrow write 0
- J-K Flip-Flop Fig. A.28
 - Toggle Q when $J=K=1$ Fig. A.29

19.9.2000

Copyright Teemu Kerola 2000

28

Registers (2)

- Parallel registers
 - read/write
 - CPU user registers
 - additional internal registers
- Shift Registers
 - shifts data 1 bit to the right
 - serial to parallel?
 - ALU operation?
 - rotate?

Fig. A.30

Fig. A.31

Counters (4)

- Add 1 to stored counter value
- Counter
 - parallel register plus increment circuits
- Ripple counter
 - asynchronous
 - increment least significant bit, and handle “carry” bit as far as needed
- Synchronous counter
 - modify all counter flip-flops simultaneously
 - faster, more complex, more expensive

Summary

- Boolean Algebra → Gates → Circuits
 - can implement all with NANDs or NORs
 - simplify circuits: Karnaugh, Quine-McCluskey
- Components for CPU design
 - ROM, adder
 - multiplexer, encoder/decoder
 - flip-flop, register, shift register, counter


19.9.2000

Copyright Teemu Kerola 2000

31

-- End of Appendix A: Digital Logic --

Simple processor

 

http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.html

19.9.2000

Copyright Teemu Kerola 2000

32