


Online Radio & Electronics Course

[Supplementary reading - Common emitter amplifier](#)

Course Website: <http://www.radioelectronicschool.com>

The purpose of this reading is to explain more about transistor bias and why a common emitter (CE) amplifier produces a 180 degree phase change to the input signal. Understanding this will give a better understanding of transistor operation – particularly how ‘bias’ works. We will be looking at a BJT (Bipolar Junction Transistor) in this reading but do kept in mind a CE amplifier can be made with any other active device.

Figure 1 shows a simplified diagram of a CE amplifier.

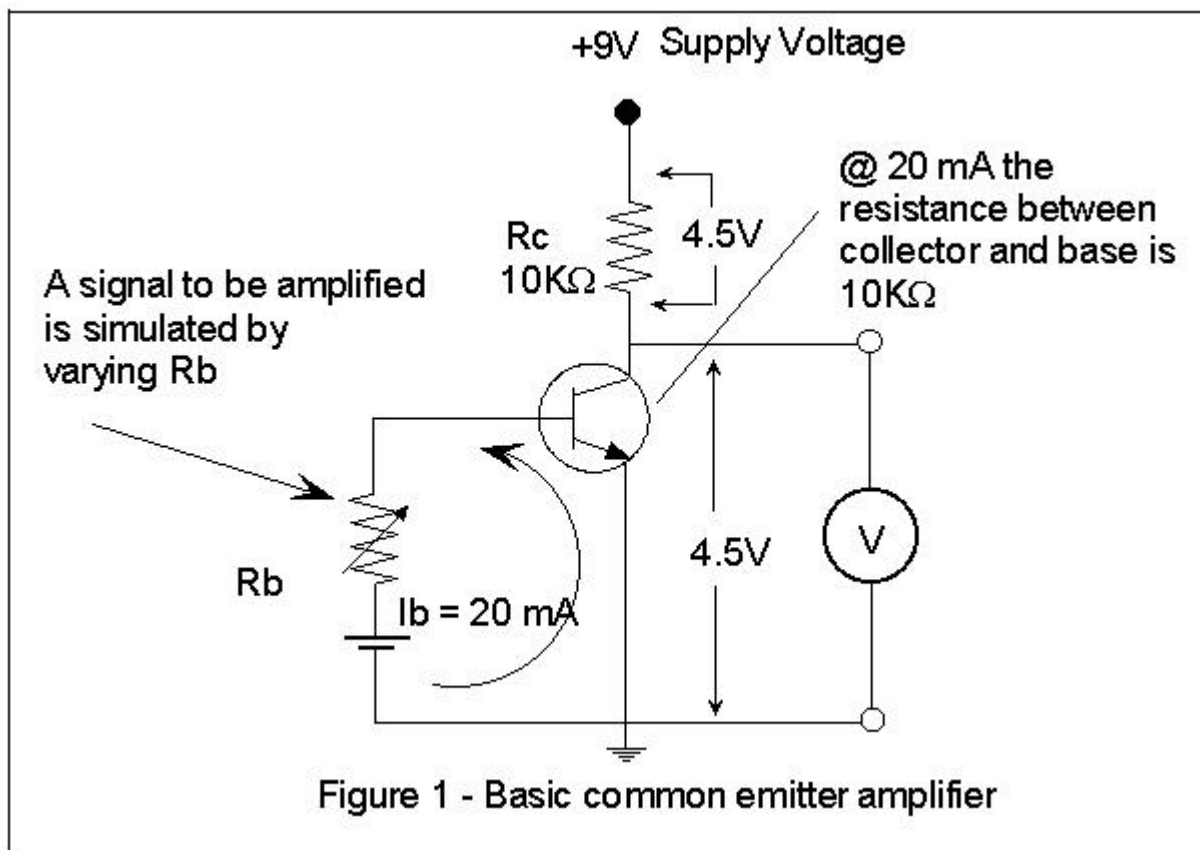

Now the values that I have placed on the diagram in figure 1 are totally arbitrary and at the same time realistic. What the actual operating voltages and currents are for a particular transistor would be determined by referring the manufactures data sheets.

In figure one the base current is supplied by a separate battery and a resistor R_b . The amount of base current (I_b) can be changed by varying R_b .

The collector of the transistor is connected to +9V via R_c . Though not shown the emitter is connect to the negative side of the 9 volt supply.

So there are two supply voltages in this diagram – the bias voltage and the main supply voltage of 9 volts. Can you tell if this transistor is connected the correct way in this circuit in terms of the battery voltages?

Both power supplies have their negative terminal connected to earth (or the emitter). What I do to determine if a transistor is drawn correctly is; I imagine I am an electron coming from negative of each power supply and see if “I” have to flow **against the arrow in the transistor symbol** to get to “my” positive side of the supply.

In figure 1 electrons must flow from earth (-9V) up into the emitter against the arrow to get to the +9V at the collector. The other supply shown is a bias voltage supplied by a battery. In the base circuit electrons flow from the negative terminal of this battery against the arrow and back to the positive terminal. The battery voltages are connected with the correct polarity to make this NPN transistor operate.


Now I have chosen an arbitrary value of 20mA for the base current. Accept this value of base current for now. The base-emitter junction is forward biased and 20 mA of base current is flowing. Since the base-emitter junction is forward biased – current will also flow from the emitter through the transistor – out of the collector – then through R_c and back to the +9V.

Since the emitter-collector circuit is in series with R_c then the sum of the voltage drops across them must equal the supply voltage of 9 volts. Again I have arbitrarily chosen an equal voltage across each. Half the supply voltage (4.5V) is across R_c and the other half (another 4.5V) is across CE – the emitter and collector.

If 4.5 volts is across R_c **and** 4.5V is across the emitter-collector of the transistor then; in this circuit with this amount of base current flowing (20mA) **the transistor could be replaced with just a 10K resistor.**

Figure 2 below shows an even more simplified (though very true) representation of the circuit in figure 1. The transistor has been replaced with a $10K\Omega$ resistor. In fact a BJT really is a **current variable resistance** or **a resistor whose resistance is determined by a current (the bias current)**. The original name first given to a transistor by its inventors was a **transfer resistor**.

Have a look at figure 2.

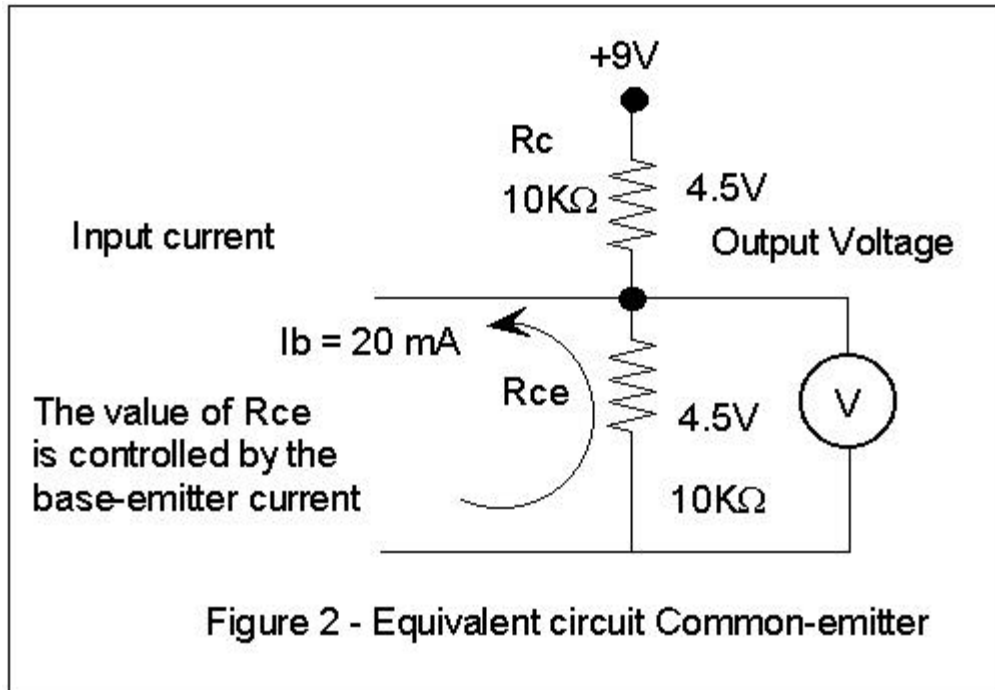

I have replaced the transistor with a resistance of 10K. This 10K resistor represents the resistance of the emitter-collector circuit. The resistance of the emitter-collector circuit can be changed by changing the bias current (now at 20mA). If more bias current were made to flow then the emitter-collector resistance of the BJT would fall and less voltage would appear across it. The sum of the voltage drop across the emitter-collector and Rc must always equal the applied voltage (9V).

So if the bias current were to **increase** – the emitter-collector resistance would **decrease** and the voltage measure from the collector to ground (emitter) would fall and the voltage across Rc would rise by the same amount.

If we were to decrease the bias current then the emitter-collector resistance would increase. If the effective emitter-collector resistance rose above 10K then more voltage would have to be measured on the voltmeter. If the emitter-collector resistance increases then the emitter-collector voltage (as measured by the meter) will rise and the voltage across Rc will decrease by the same amount. (the sum remaining 9V).

The transistor used in the common emitter configuration is really just two resistors in series as shown in figure 2. However the resistance of the transistor (between collector and emitter) is determined by the base-emitter current. Now – recall – the signal to be amplified is connected to the base-emitter circuit. The amplifier output is taken from the collector-emitter – or if you prefer – the output is taken from the collector and ground.


The way a transistor amplifies (irrespective of its configuration CE, CB, or CC) is that small changes in base-emitter current brings about large changes of emitter-collector current. **Can you see that larger current is brought about by decreasing resistance?**

You will be doing well right now if you can see that the transistor is **really** like a special resistor whose resistance is controlled by an input current.

Have a look at figure 3a – we are not concerned about ‘absolute’ values of current and voltage here as that will vary from transistor to transistor.

In figure 3a I have **increased** the base-emitter current. This means the transistor is turned on harder. It also means its collector-emitter resistance R_{ce} will decrease. The output voltage across R_{ce} or between the collector and ground must decrease.

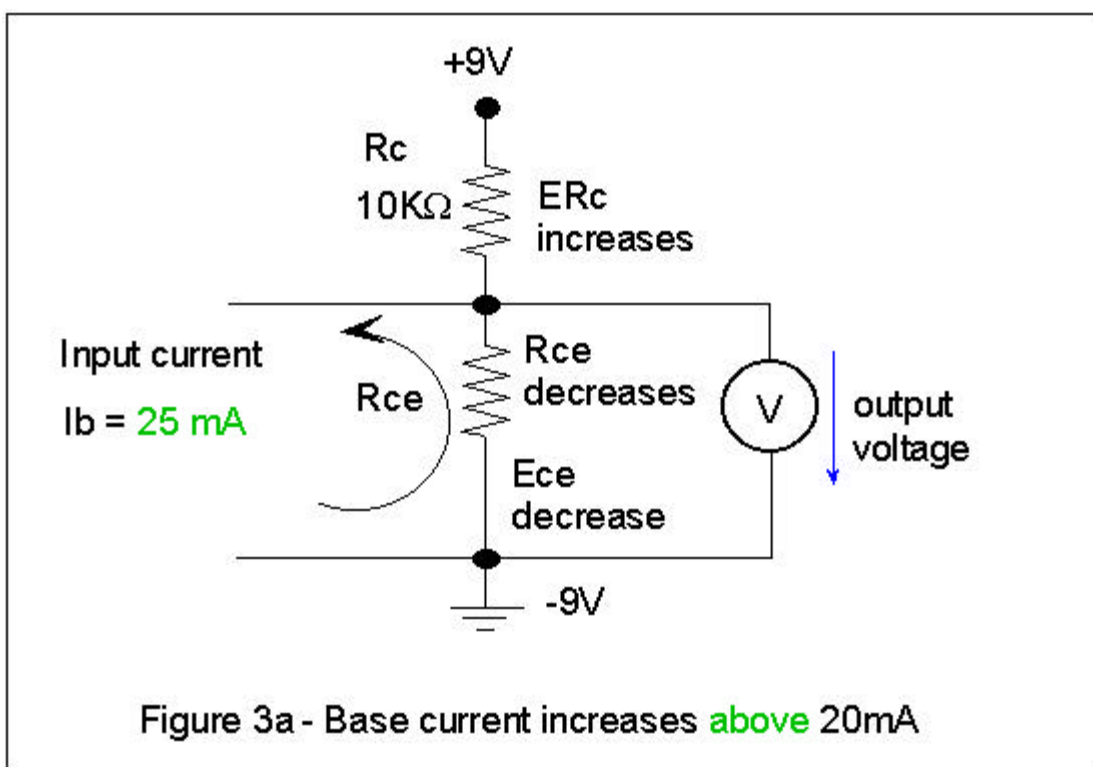
The voltage across R_c i.e. E_{Rc} increases by the same amount that E_{ce} decreases as their sum must equal the supply voltage at all times.



In figure 3b the base current is decreased. This means that the transistor will not conduct from emitter to collector as hard – the transistor is being turned towards off – its (the transistors) effective resistance between collector and emitter increase and the voltage E_{ce} must therefore increase.

When the transistor is left alone its base current will return to 20mA and the voltage

across R_{ce} will return to 4.5V.

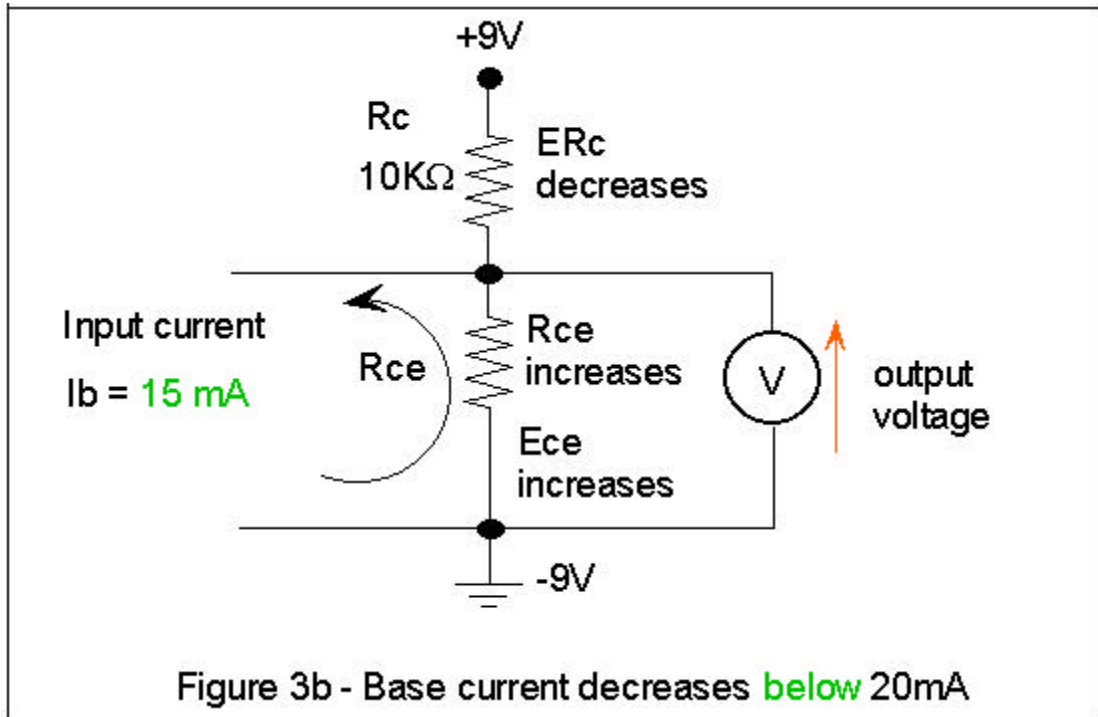

In a practical circuit this normal fixed value of the base current is called the bias or quiescent base current. We don't have a separate battery to supply bias. We also feed our input signal to be amplified to the base-emitter circuit. The input signal will either add to or subtract from the quiescent bias current. A resulting amplified output voltage will appear between the collector of the common emitter amplifier and ground.


You can see that the transistor needs DC voltages and currents in its quiescent state. The signal to be amplified may well be AC or varying DC – it does not matter. A capacitor passes AC or varying DC (well at least it appears to anyway). So capacitors called coupling capacitors are added to the input and output circuits. Coupling capacitors allow a varying current or voltage to be fed to and taken from the circuit whilst blocking the DC voltages from the transistor affecting the previous and subsequent stages.

Have a look at figure 4.

This is actually a practical amplifier. The amount of quiescent base current (the bias) is determined by the voltage divider consisting of R_1 and R_2 . As before I have arbitrarily chosen a transistor that requires a bias current of 20mA.

I have added input and output coupling capacitors.

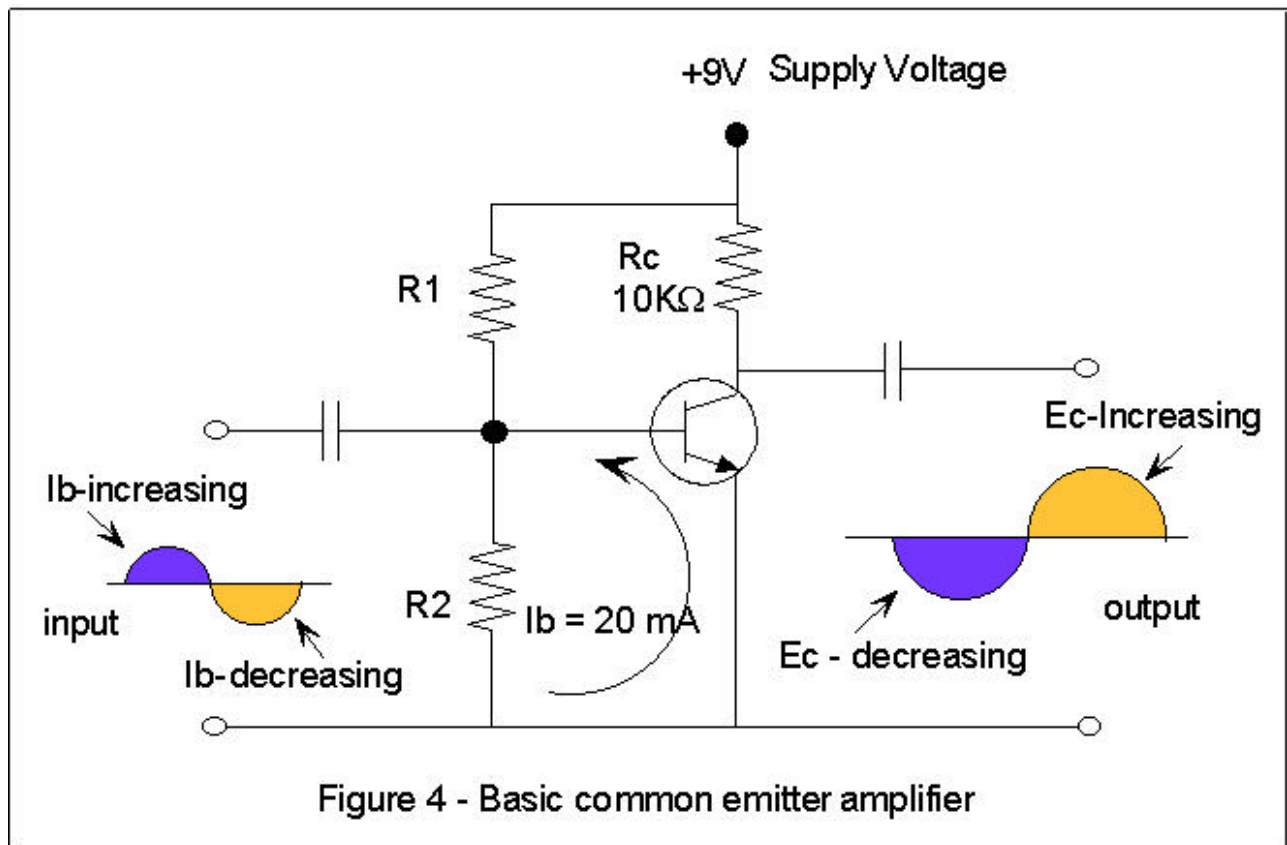The output voltage is taken from between the collector and ground and the circuit operation is as described above.



An input signal that increases the base current (makes the base more positive with respect to the emitter for NPN) will cause the output voltage to fall as shown in blue. A input signal which causes the base current to decrease will cause the output voltage to rise.

So you can see that the amplified output is 180 degrees out of phase with the input. This phase shift is of no consequence when it comes to the intelligence or information contained in the signal being amplified. The phase change matters when we use feedback in circuits though this is an advanced topic. The output of the CE amplifier if fed back to the input would be 'negative feedback'.

I am often asked what the purpose of R_c is. If R_c were not present; firstly too much emitter collector current would flow and the transistor would be destroyed. As important; without R_c there would be no output – if we removed R_c and connect the collector to the +9V supply then the voltage between emitter and collector would always remained 9V. R_c is essential as it forms a voltage divider with the internal resistance of the transistor (R_{ce}). Changes in signal cause R_{ce} to change in resistance and the voltage change thereby produced across R_{ce} is the output voltage.

We could add an emitter resistance (R_e) to this circuit – as discussed in the reading on semiconductors a small resistance in the emitter lead (say 1K in this circuit) will prevent thermal runaway. If we do add a emitter resistance we also add an emitter bypass capacitor across R_e . The reactance of the bypass capacitor is typically $1/10^{\text{th}}$ the resistance of R_e at the lowest operating frequency.

Okay – well you should now see why a CE amplifier cause a 180 degree phase shift and you should also have more of an understanding of transistor bias.

There are simple design formulas for choosing all the values in a CE amplifier like all other amplifiers. You also would need access the data tables of the transistor. In practice 99% of the time experimenters, hobbyists and even engineers work from existing circuits – why recalculate the circuit when one is available.

Can you tell if the applied voltages to the circuit are correct. The examiner may reverse a polarity and expect to see this – for example in the above circuit $-9V$ could be connected to the collector.

Can you identify the active device used? Can you identify that it is a CE circuit? Identify voltage divider bias? Emitter stabilisation and bypassing. To lessor extent be aware that there is a 180 degree phase change between output and input in a CE amplifier. CE amplifiers have a relatively low input impedance and a moderately high output impedance – the low input impedance is usually well suited for many microphones used in radio communications and electronics.

Last revised 11 September 2000

Free for non-commercial use but must not be published without permission.

Copyright © 1999-2001 Ron Bertrand VK2DQ

Email: ron@radioelectronicschool.com