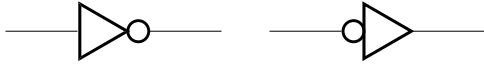


Properties of Digital Integrated Circuits

Most important elements: Inverter and Noninverter

Inverter Symbols



Noninverter Symbols



Idealized Inverter and Voltage Transfer Characteristics(VTCs)

