




# Chapter 2

## Diode Applications

- In general, approximate model of diode is used in applications because of non-ideal real life conditions (tolerance, temperature effect, etc) never allow an ideal case to be applied
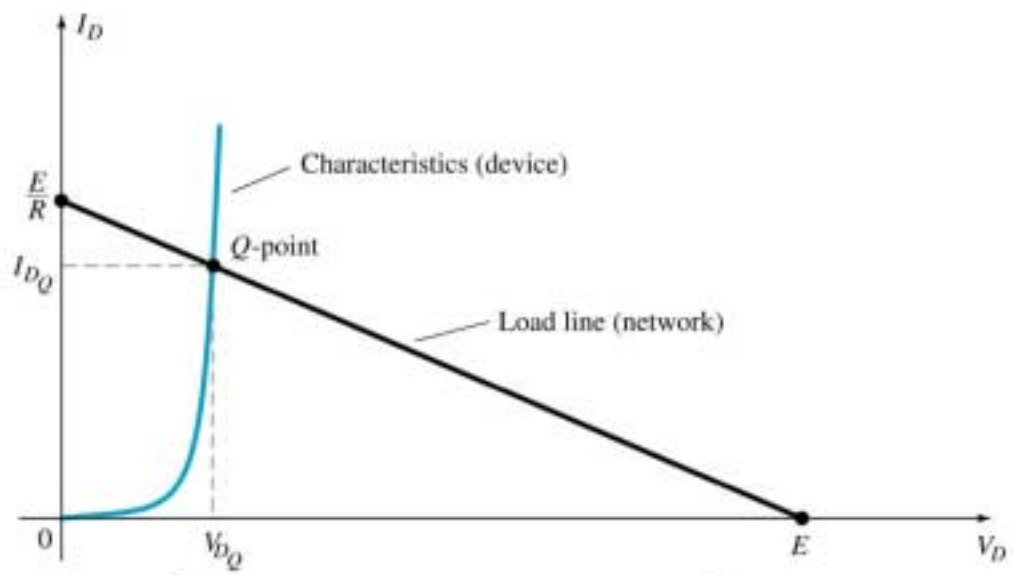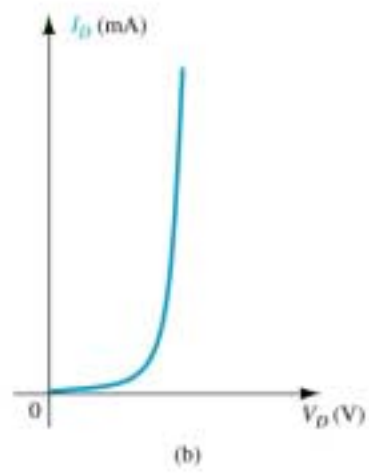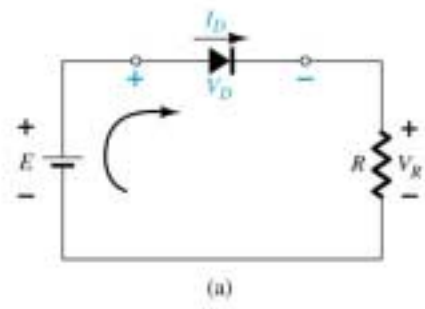
# Load Line Analysis

- The load of a circuit determines the point or the region of operation of a diode (or device)
- The method: A line is drawn on the characteristic of the device
- The intersection point gives the point of operation



# Load Line Analysis



- In the above figure, E has to be in the forward bias direction and  $> V_T$  of the diode, in order for the current to flow. Using KVL:
- $-E + V_D + V_R = 0$
- $E = V_D + V_R = V_D + I_D R$
- Notice: Variables  $V_D$ ,  $I_D$  are same in the above equation
- For  $V_D=0$ :  $I_D = E/R$
- For  $I_D=0$ :  $E = V_D + I_D R$

# Load Line Analysis

- The intersection point is called Q point
- Same solution can be found by using nonlinear diode equation
- We can avoid heavy math using load line analysis.
- Exp from notes 1
- Exp from notes 2
- Exp from notes 3

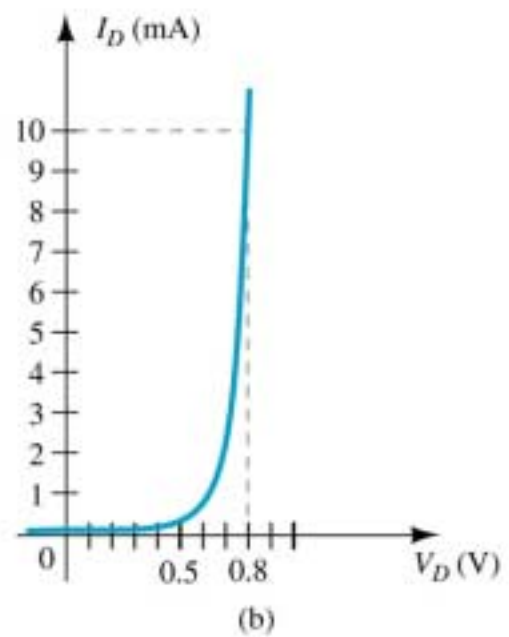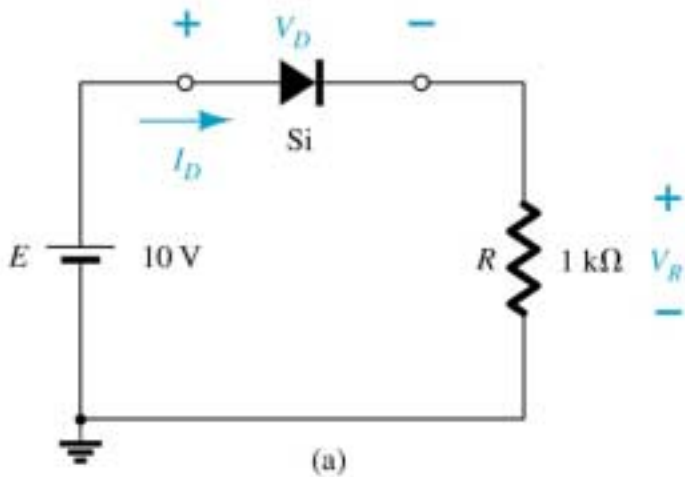
# Example 1

- For below figure, determine  $V_{DQ}$ ,  $I_{DQ}$  and  $V_R$



# Solution


- Refer to notes for the solution

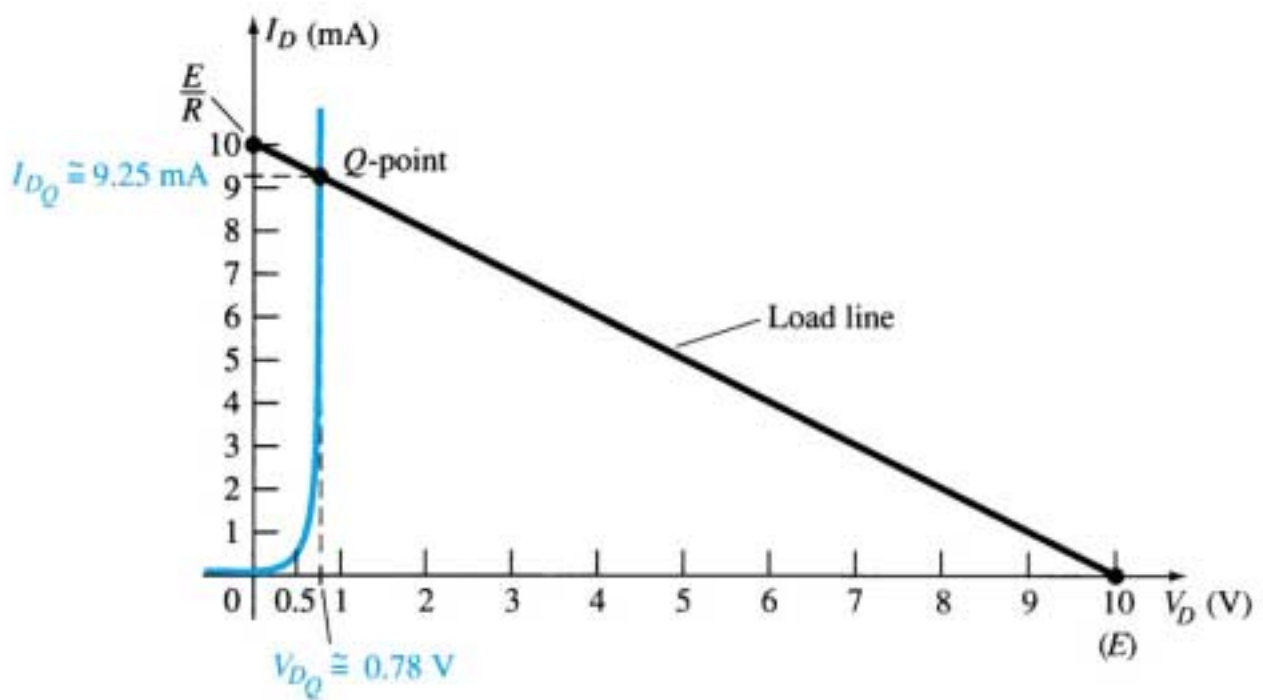
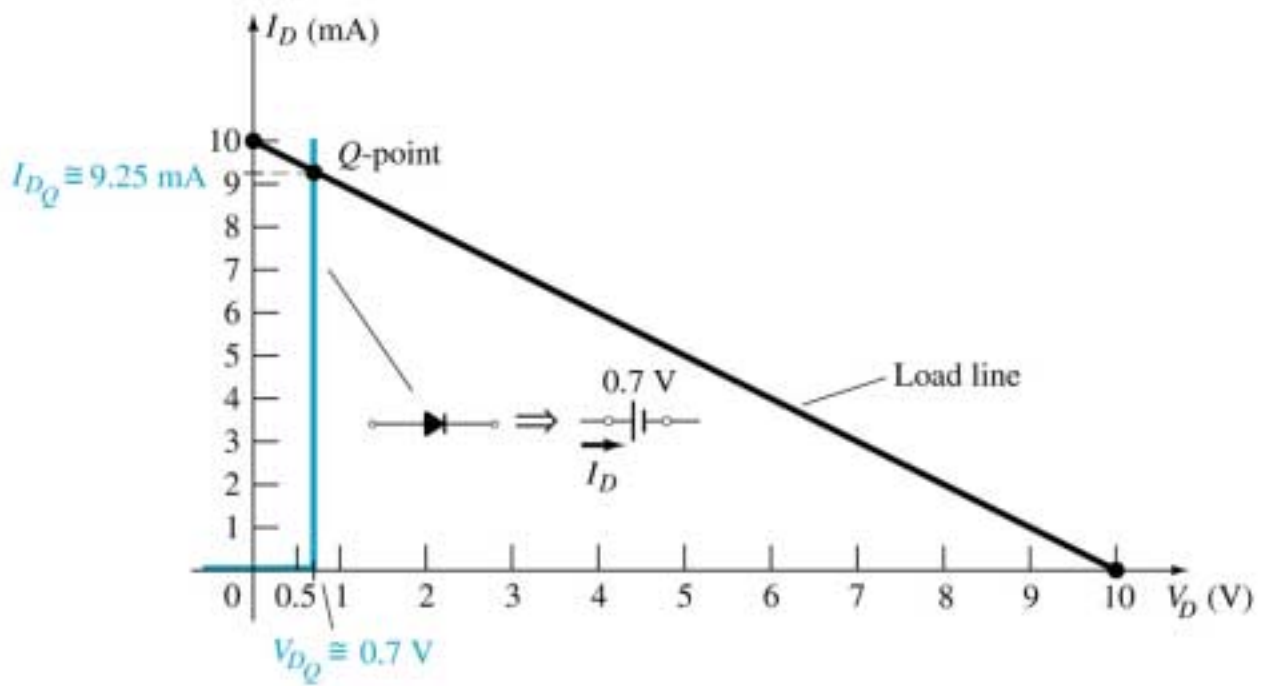
## Example 2

- Repeat the previous example using approximate model of the Si diode
- Solution: Refer to notes and see the next figure






Solution to Example 2.
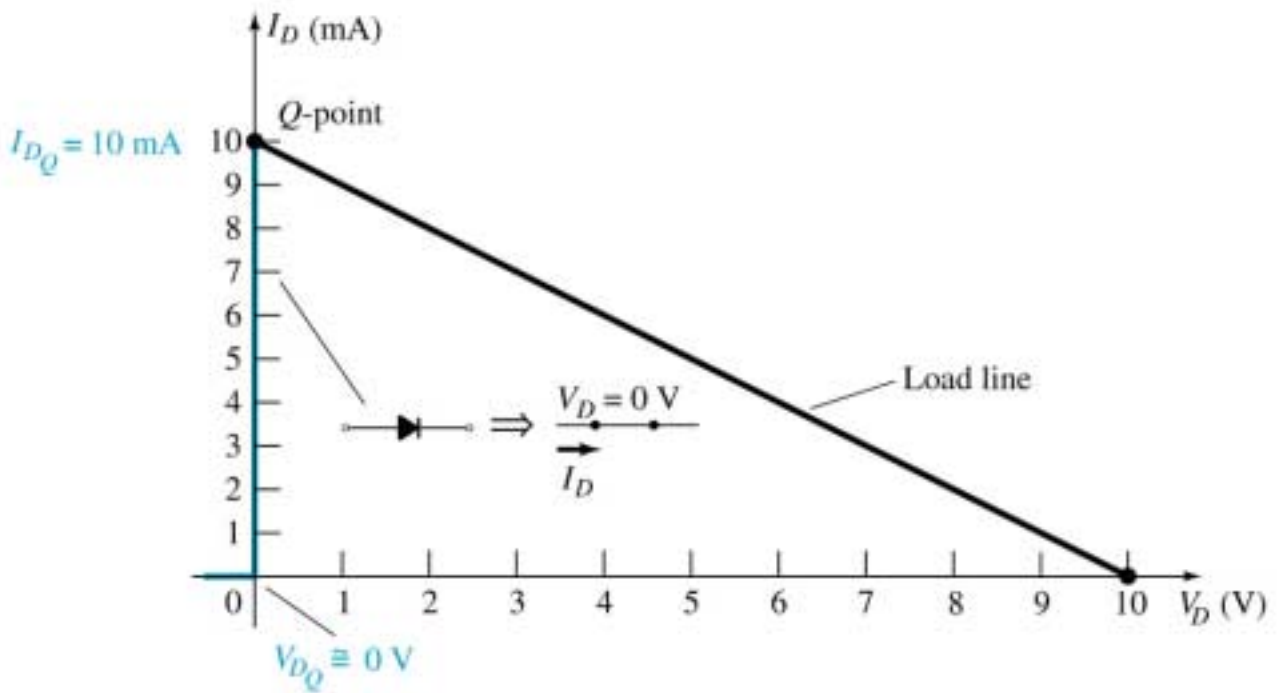
## Example 3

- Repeat the same example using ideal model of the diode
- Solution: Refer to notes and see next figure





Solution to example 3 using ideal model

# Diode Approximations


- As an engineer, we will generally use approximate models to avoid extensive mathematical calculations
- This is achieved by using approximate model of a device whenever it is possible
- Approximate model of diodes are given in Table 2.1
- Also see Figure 2.11
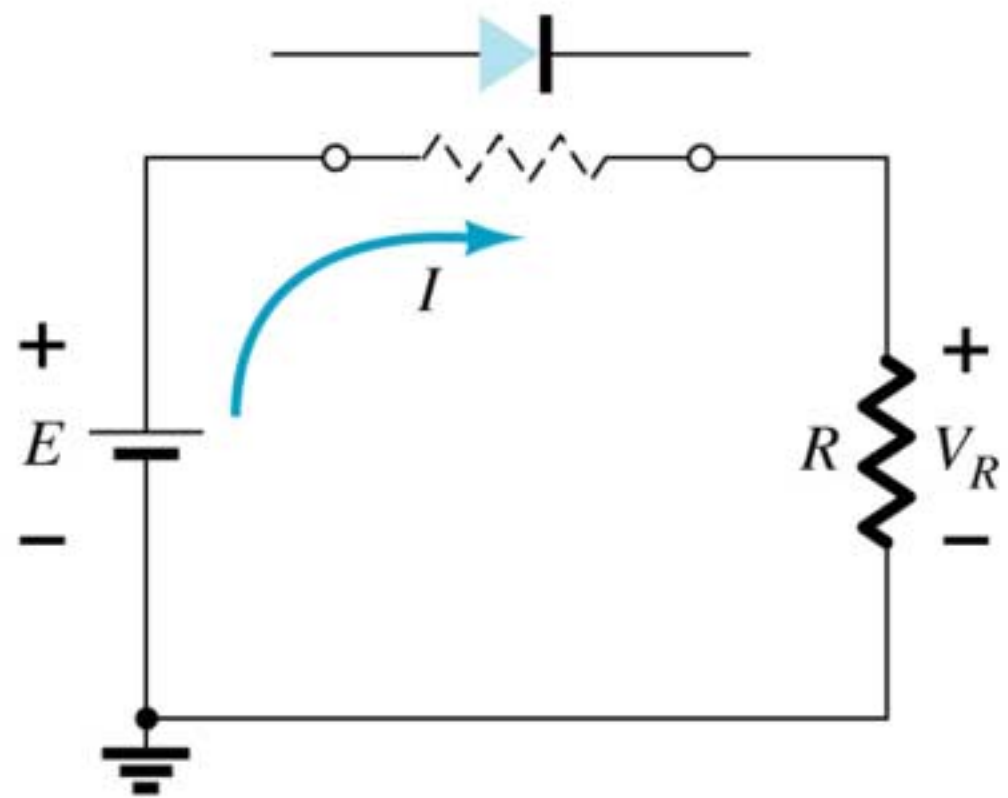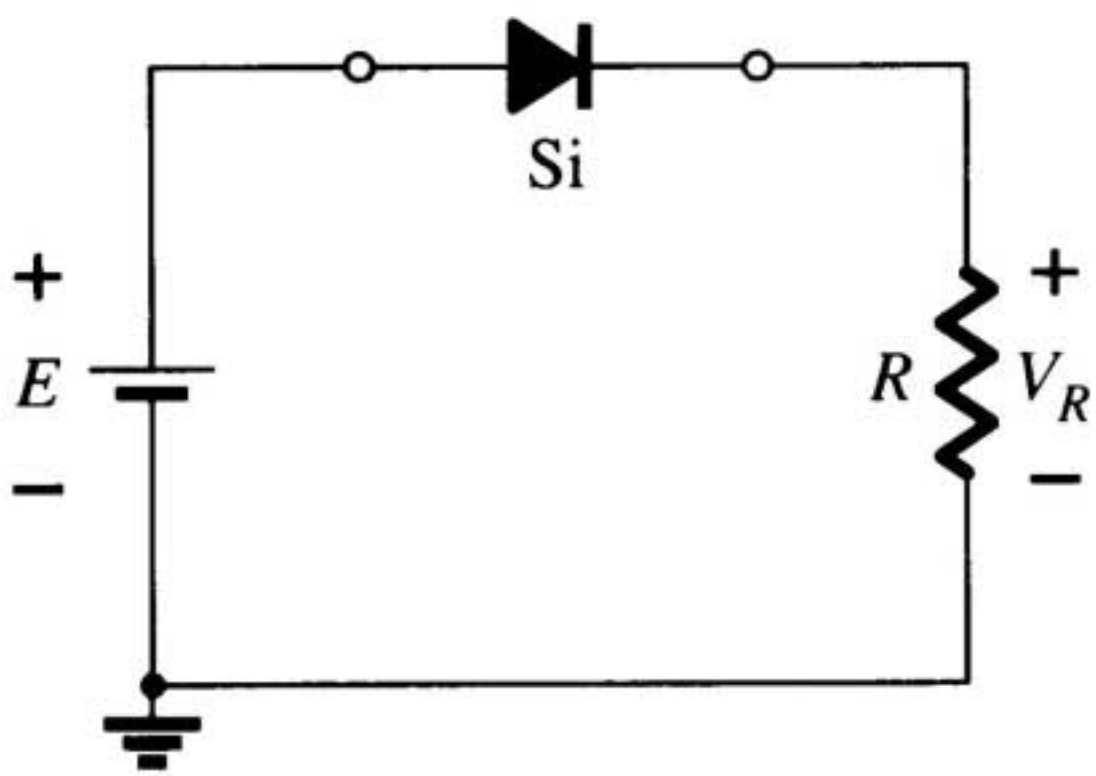
# Series Diode Config. with DC Inputs

- When connected to voltage sources in series, the diode is on if the applied voltage is in the direction of forward-bias and it is greater than the  $V_T$  of the diode
- When a diode is on, we can use the approximate model for the on state
- See next two figures




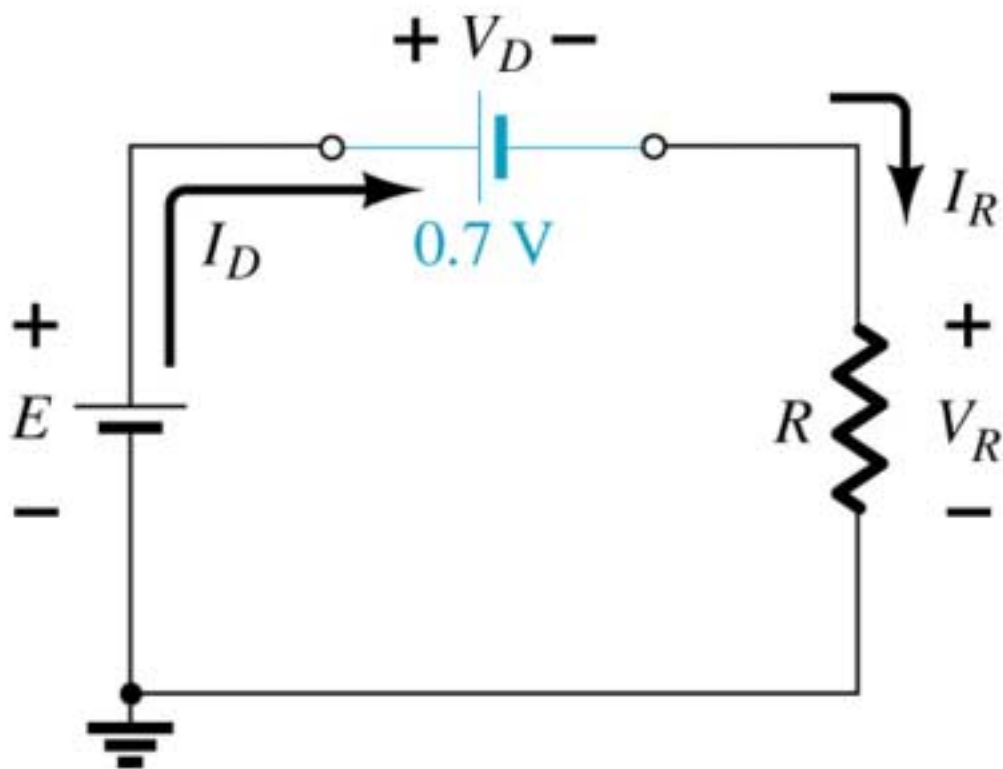
Using equivalent model of the diode in the forward-bias region


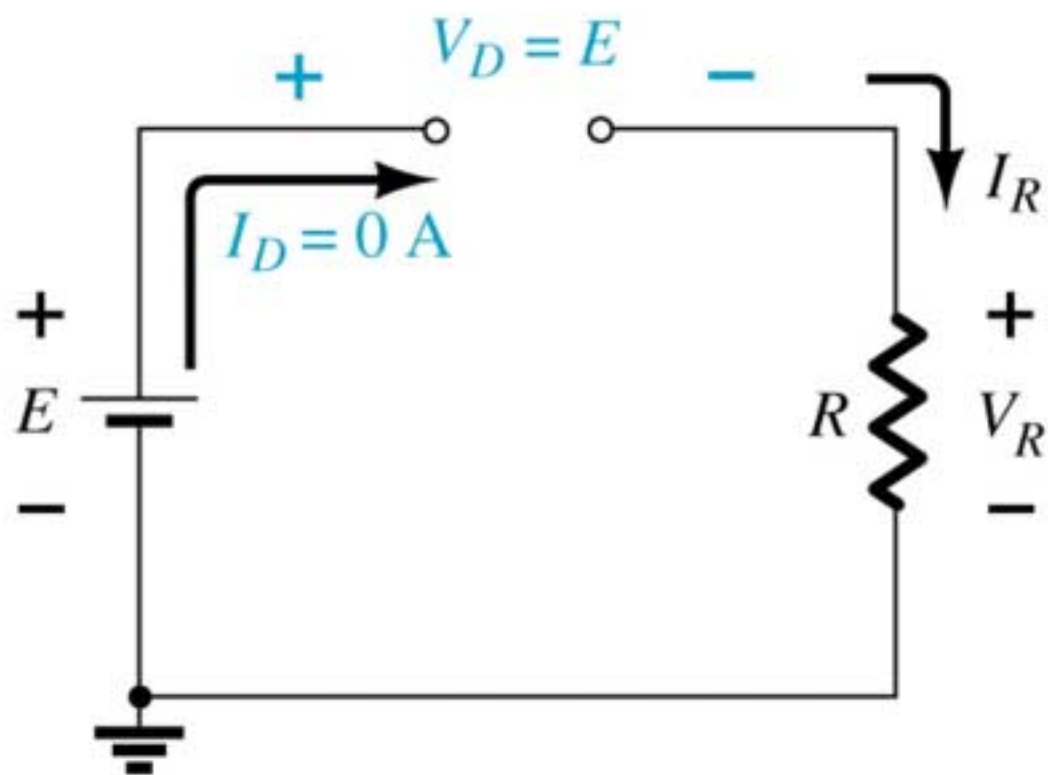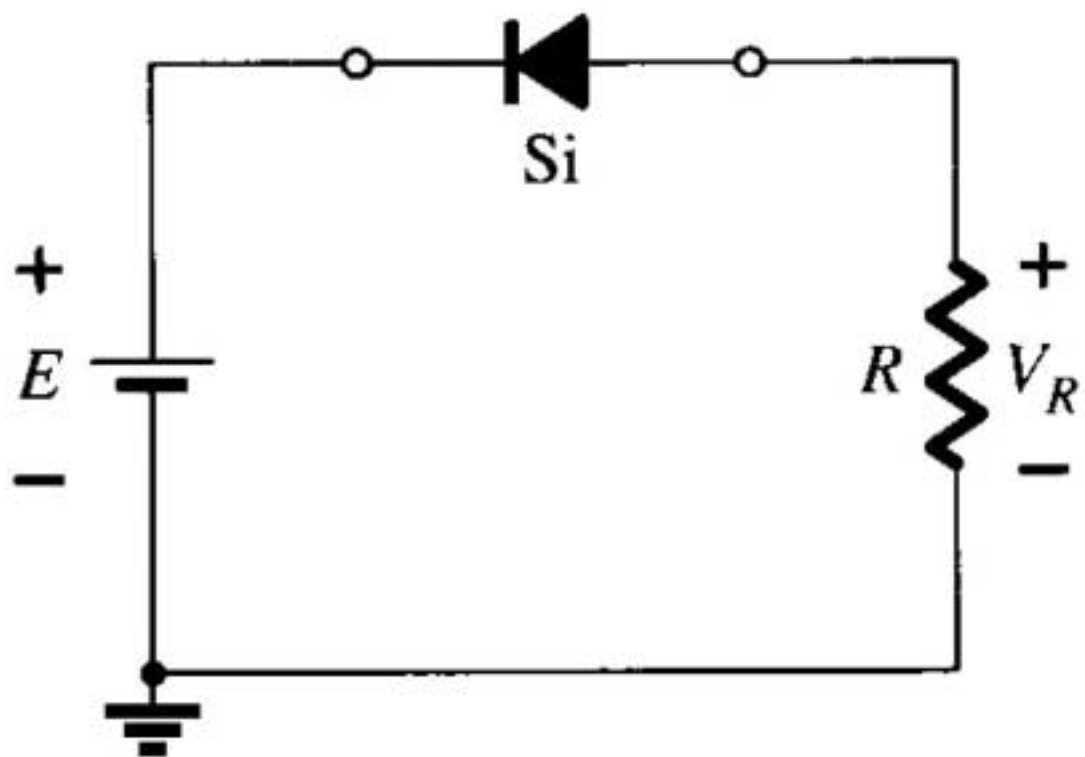
# Series Diode Config. with DC Inputs


- Here,  $V_D = V_T$ ,  $V_R = E - V_T$
- $I_D = I_R = V_R / R$
- When the diode is in the off state, the model for the off state is used
- See two figures
- Here,  $V_D = E$ ,  $V_R = 0$ ,  $I_D = 0$
- Keep in mind that KVL has to be satisfied under all conditions
- Exp from notes 1,2,3,4,5





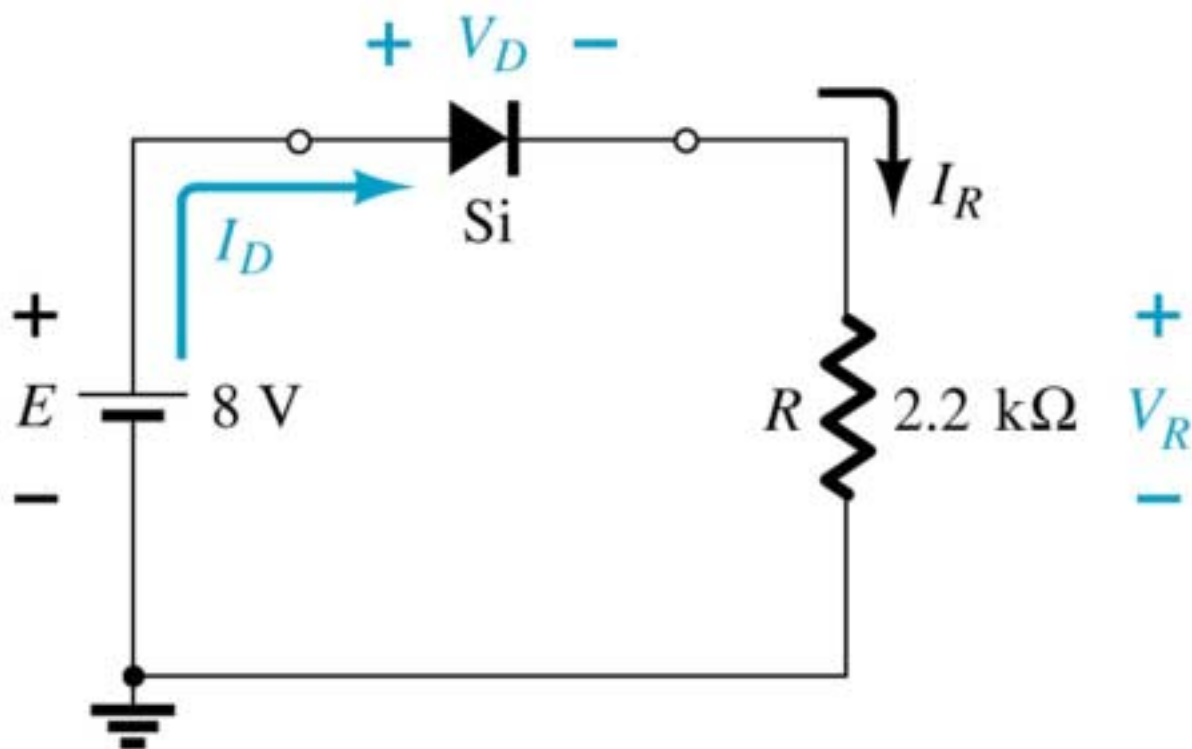
# Example 4

- For the figure below, determine  $V_D$ ,  $I_D$ , and  $V_R$
- Refer to notes for the solution



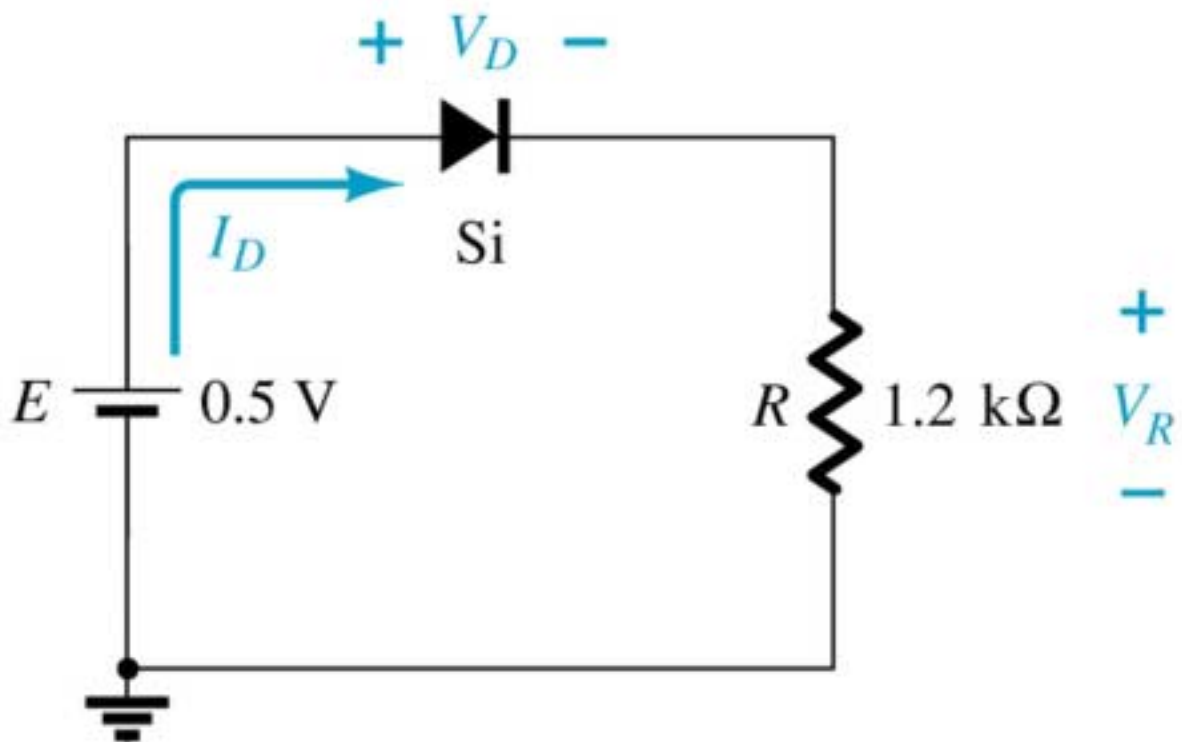
# Example 5

- For the figure below, determine  $V_D$ ,  $I_D$ , and  $V_R$
- Refer to notes for the solution



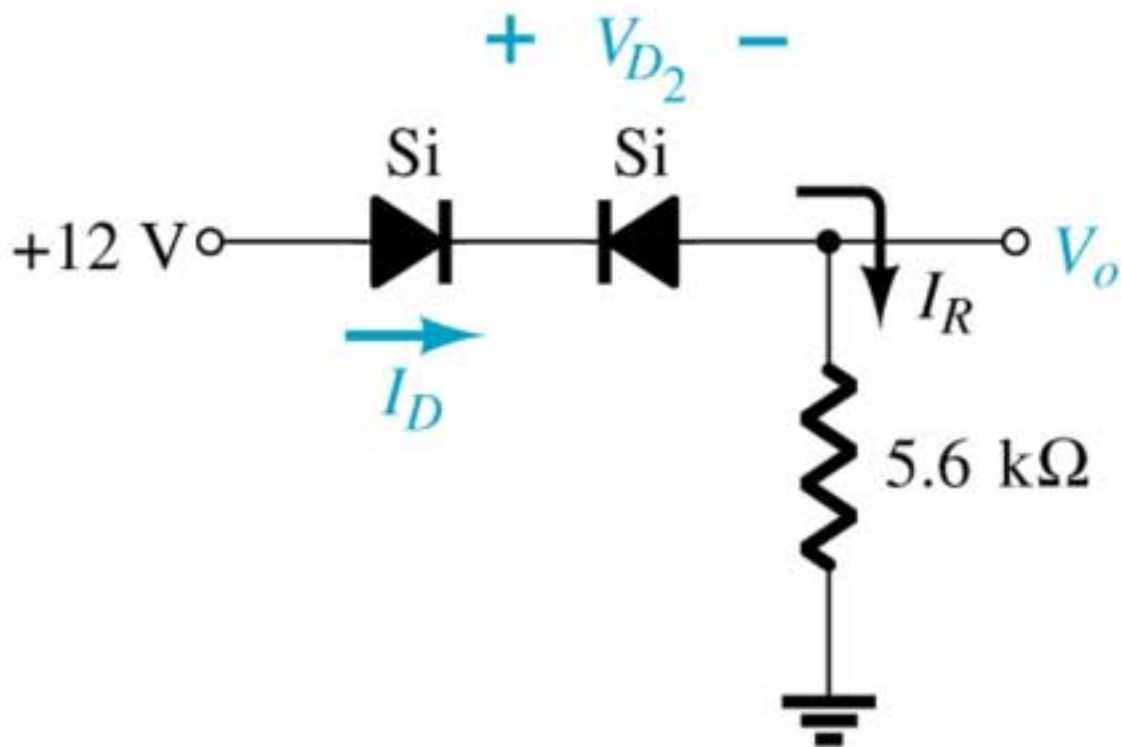
# Example 6

- Determine  $V_{D2}$ ,  $I_D$  and  $V_o$  for the figure below
- Refer notes for the solution



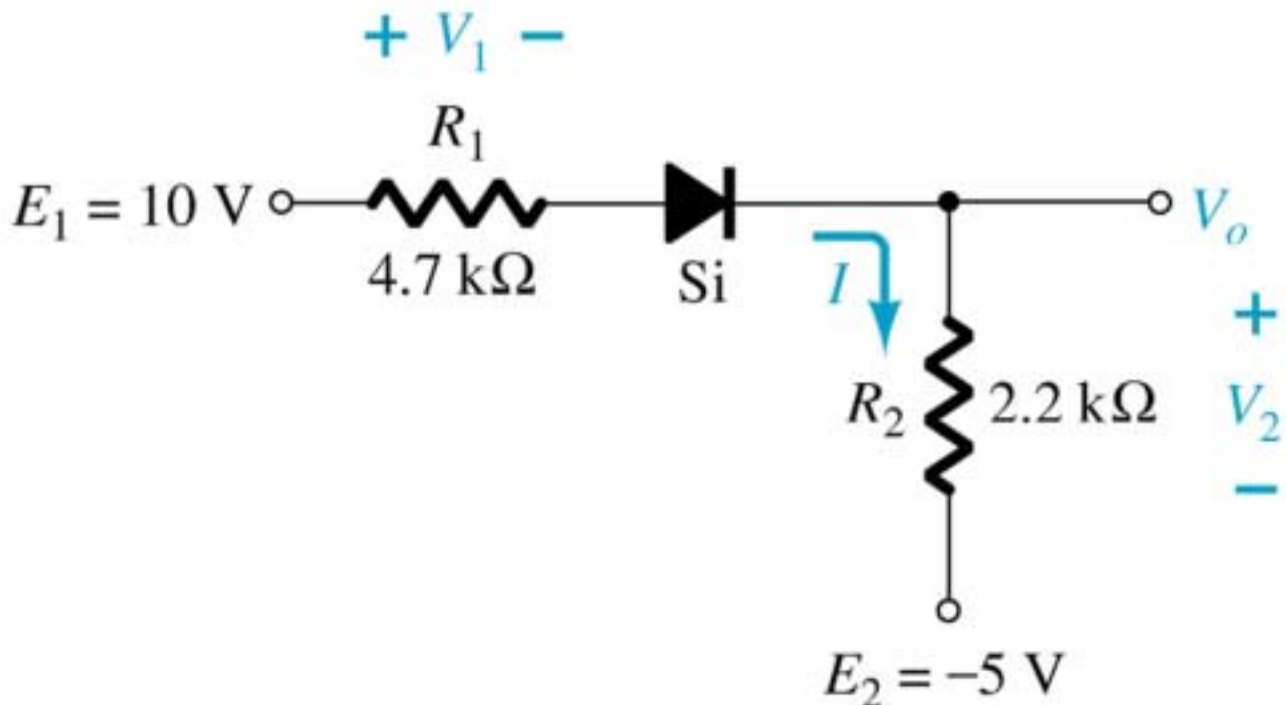
# Example 7


- Determine  $I_1$ ,  $V_1$ ,  $V_2$  and  $V_0$  for the figure below
- Refer to notes for the solution


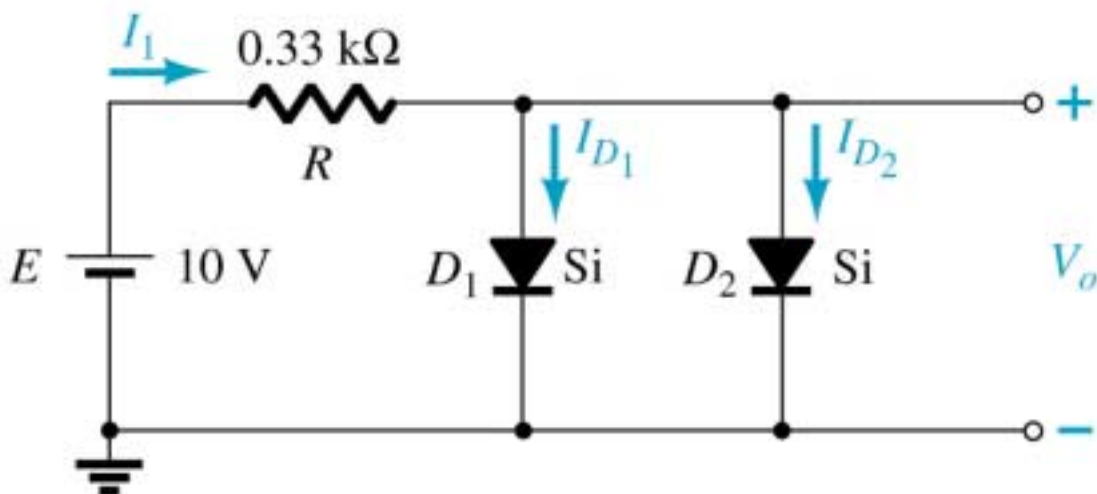
## Parallel Diode Configurations

- Determine  $I_1$ ,  $V_{D1}$ ,  $V_{D2}$  and  $V_o$  for the parallel diode circuit in below figure
- Refer to notes for the solution




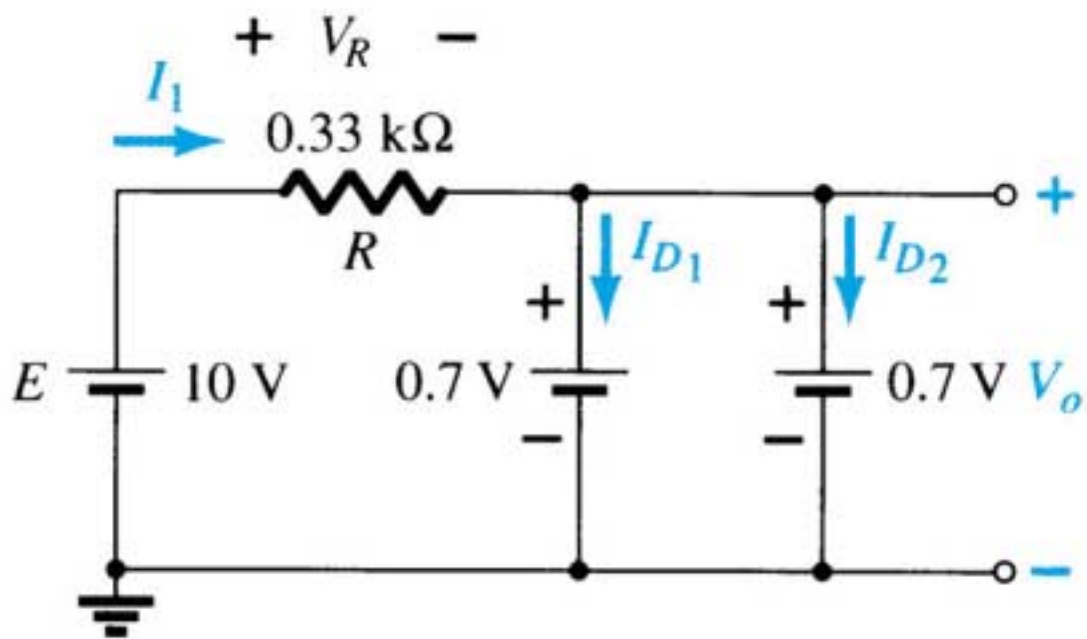

Determining unknown quantities
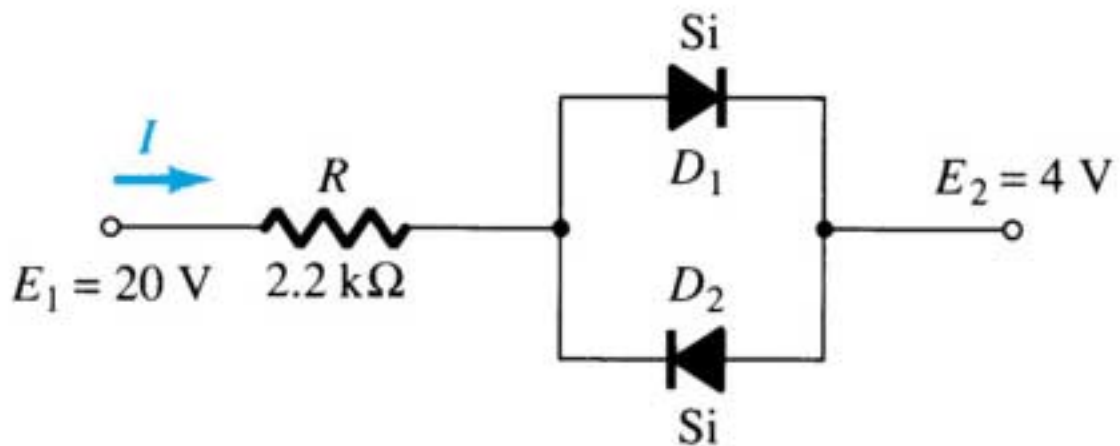
# Example 9


- Determine the current  $I$  for the circuit below
- Refer to notes for the solution





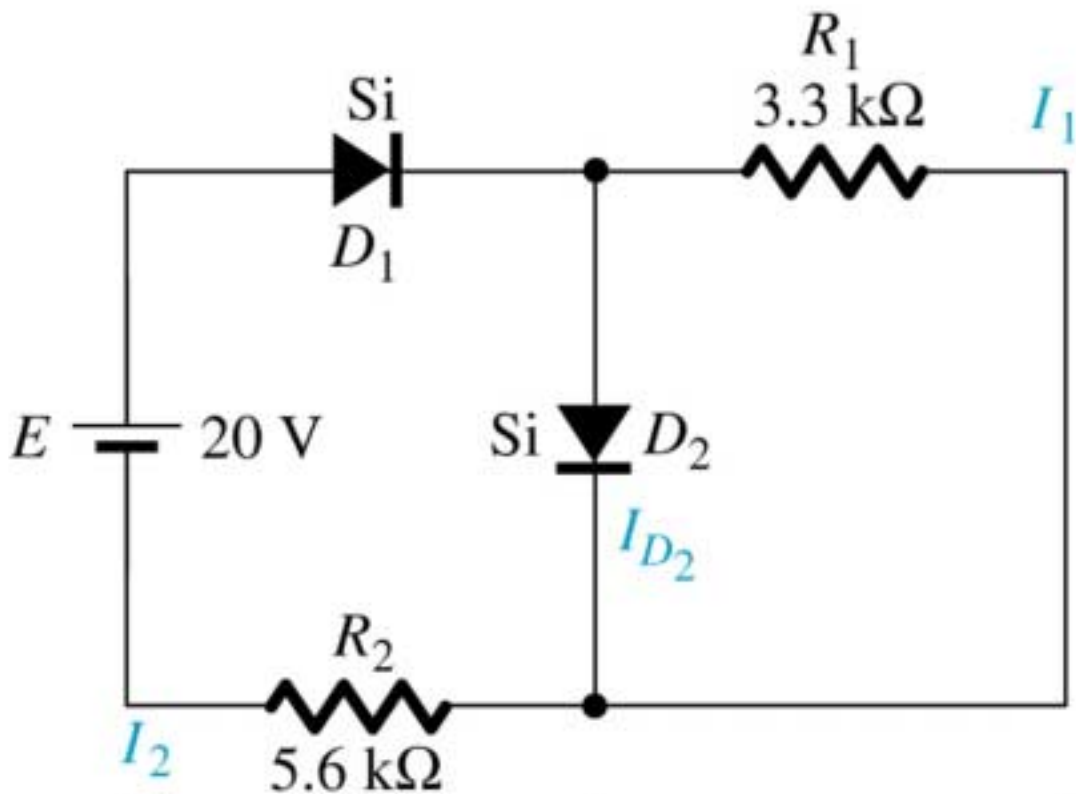
# Example 10

- Determine  $I_1$ ,  $I_2$ , and  $I_D$  for the figure below
- Refer to notes for the solution



# Example 10


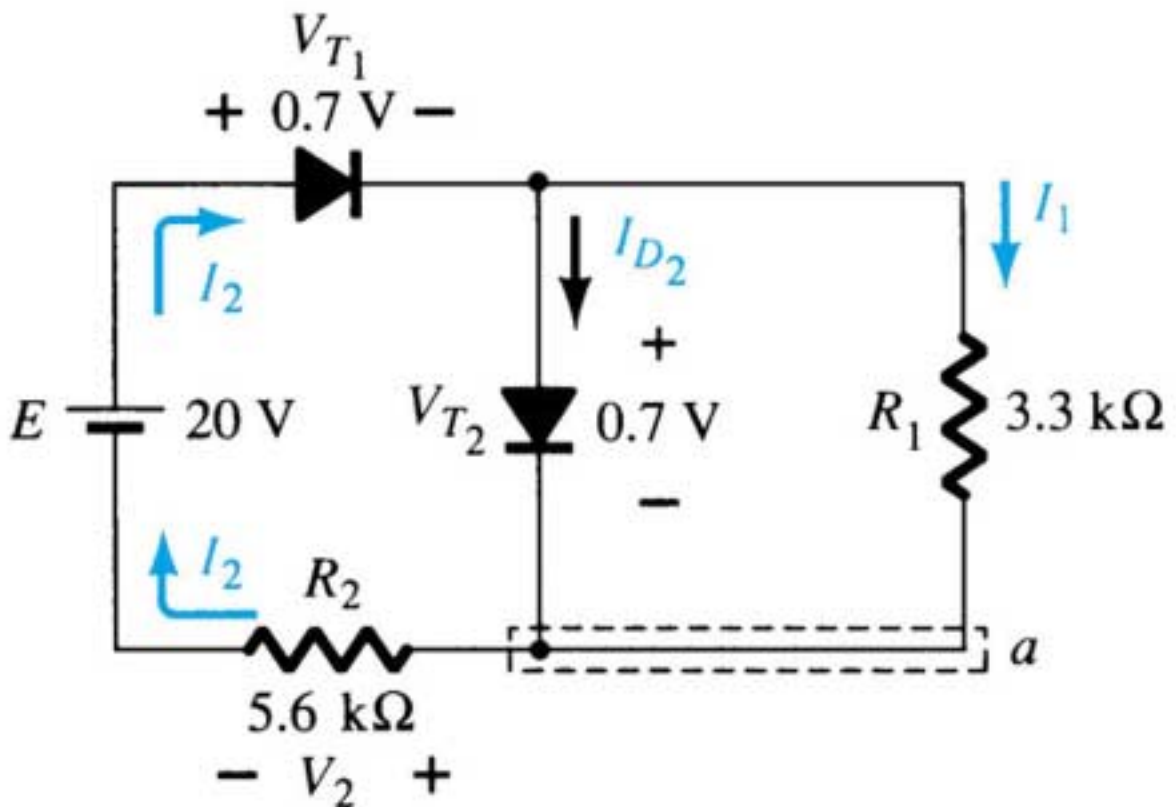




Determining the unknown quantities for the above example

# Sinusoidal Inputs: Half-wave Rectifier

- We expand our analysis to include time varying signals
- Such a network is shown as in the next figure
- This circuit is called half-wave rectifier
- For the positive and negative cycles, the circuit is approximated as in below
- See following 2 figures


# Half-wave Rectifier

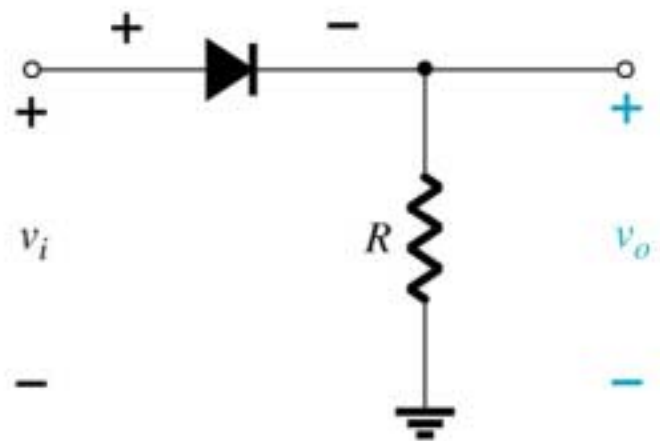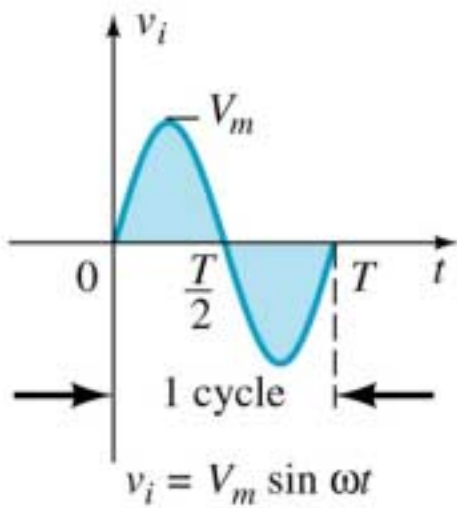

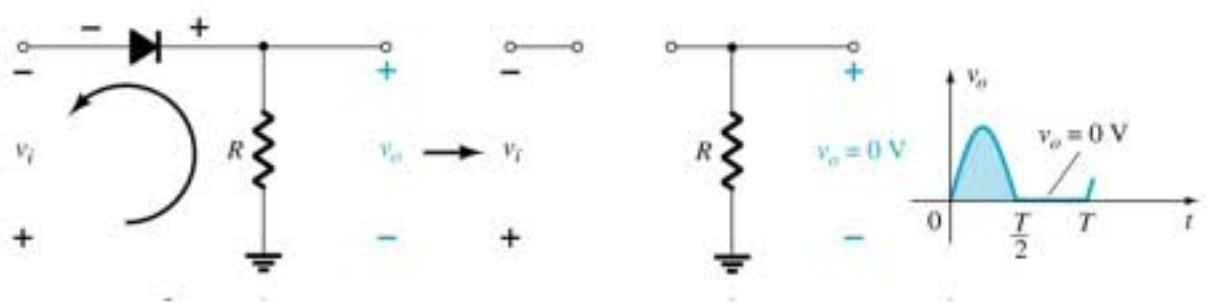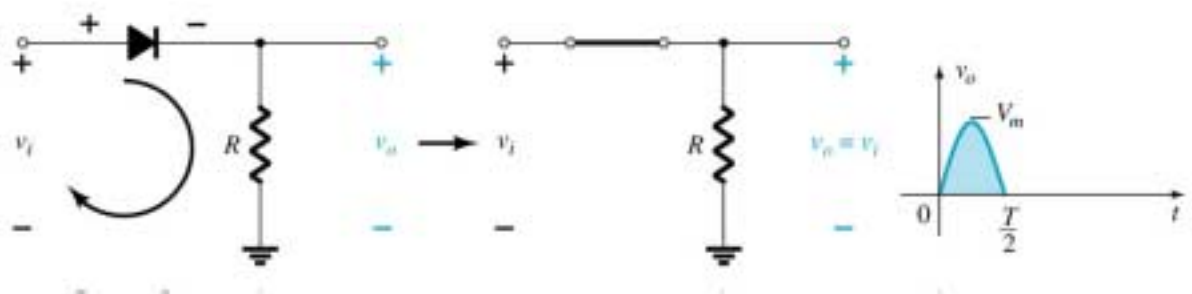
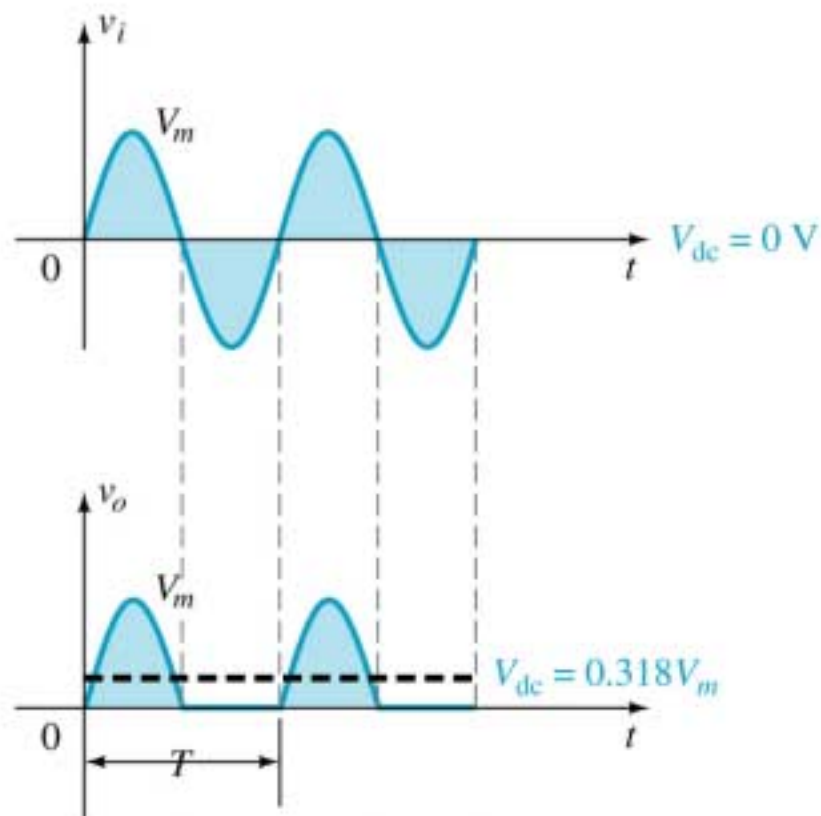
# Half-wave Rectifier

- The total effect of diode on the output signal is given in below




# Half-wave Rectifier

- For the half-wave rectified signal:

$$V_{dc} = 0.318 V_m$$

- If the effect of  $V_T$  is also considered, the output of the system will as below
- $V_{dc} = 0.318 (V_m - V_T)$
- See next Figure
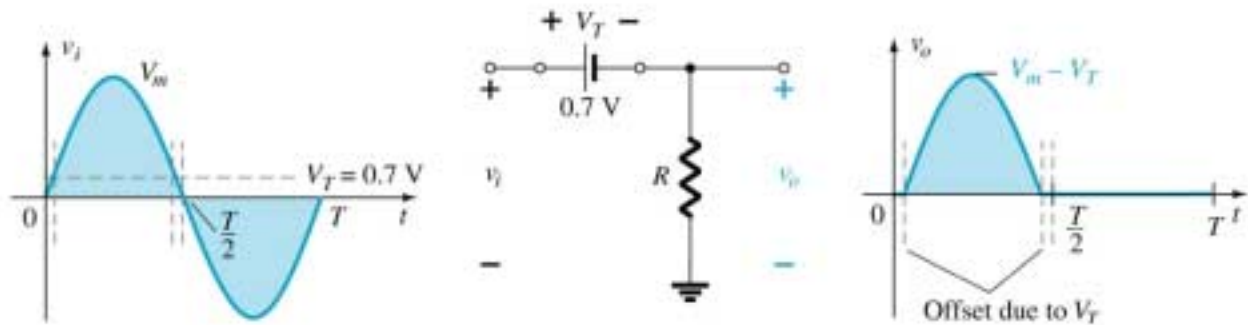
# Effect of $V_T$ on half-wave rectified signal





# PIV rating of Half-wave Rectifiers

- PIV rating is very important consideration for rectifier circuits
- For the half-wave rectifier:
- $PIV \geq V_m$

# Full-wave Rectifiers

## Bridge Networks

- The dc level obtained from a sinusoidal input to the half-wave rectifier can be improved to 100% using full wave rectifiers
- Bridge networks are used for this purpose
- See Figure 2.54
- For positive and negative cycles, network acts as below
- See Figures 2.55 – 2.58