

BRIDGES
IMPEDANCE MEASUREMENT

Experiment # 4

EE 312

Basic Electronics Instrumentation Laboratory

Fall 2000

September 20, 2000

OBJECTIVES:

- The first objective of this experiment is to learn how to use bridges used to measure values for Resistance R, Capacitance C, & Inductance L
- The second objective is to determine the **precision, accuracy and probable error** in the measured values.

In this experiment, you will learn to measure:

Resistance	using a	Wheatstone Bridge,
Capacitance	using a	Desauty Bridge*,
Inductance	using a	Maxwell Bridge.

* The name Desauty could not be found in IEEE Standard Dictionary of Electrical & Electronics Terms, IEEE-Std-100-1992.

Components:

① Isolation Transformer (1:1)

② Four Resistance Boxes

- a) Heathkit Precision Box c) EICO Industrial Box
- b) Industrial Precision Box d) Heathkit Substitution Box

3 Two Capacitance Boxes & Two Capacitors

- a) Precision Box c) Unknown Capacitor
- b) Substitution Box d) 200 μ F Capacitor

4 1mH Inductor

0

Experiment # 4

Part I- Resistance Measurement

- Wheatstone Bridge

Part II- Capacitance Measurement


- DeSauty Bridge

Part III- Inductance Measurement

- Maxwell Bridge

At balance $I = 0$

$$Z1 \cdot Z4 = Z2 \cdot Z3$$

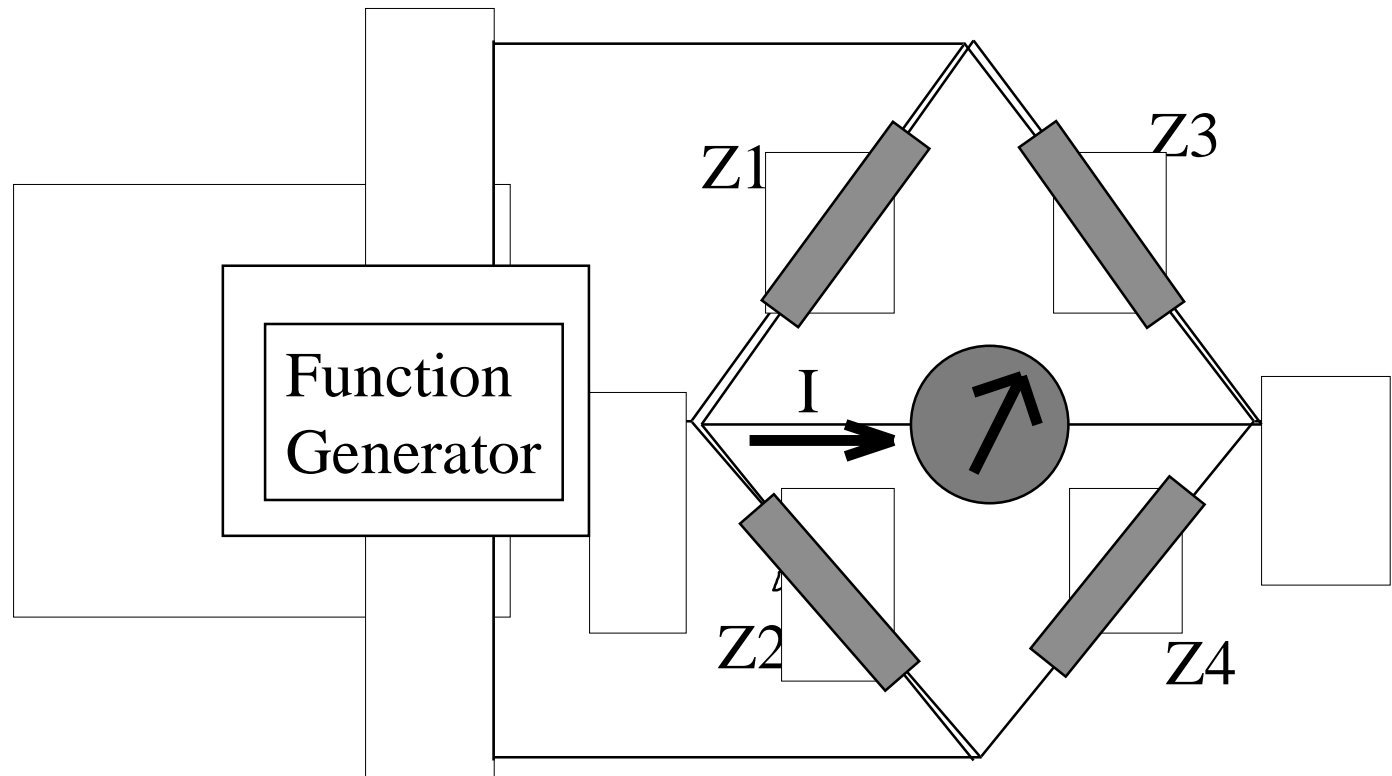

At balance $I = 0$


The voltages on each side of the meter must be equal. Thus

$$V(FG) \times Z2 / (Z1 + Z2) = \\ V(FG) \times Z4 / (Z3 + Z4)$$

Cross multiply and simplify to obtain

$$Z2 \cdot Z3 = Z1 \cdot Z4$$

Part I- Resistance Measurement

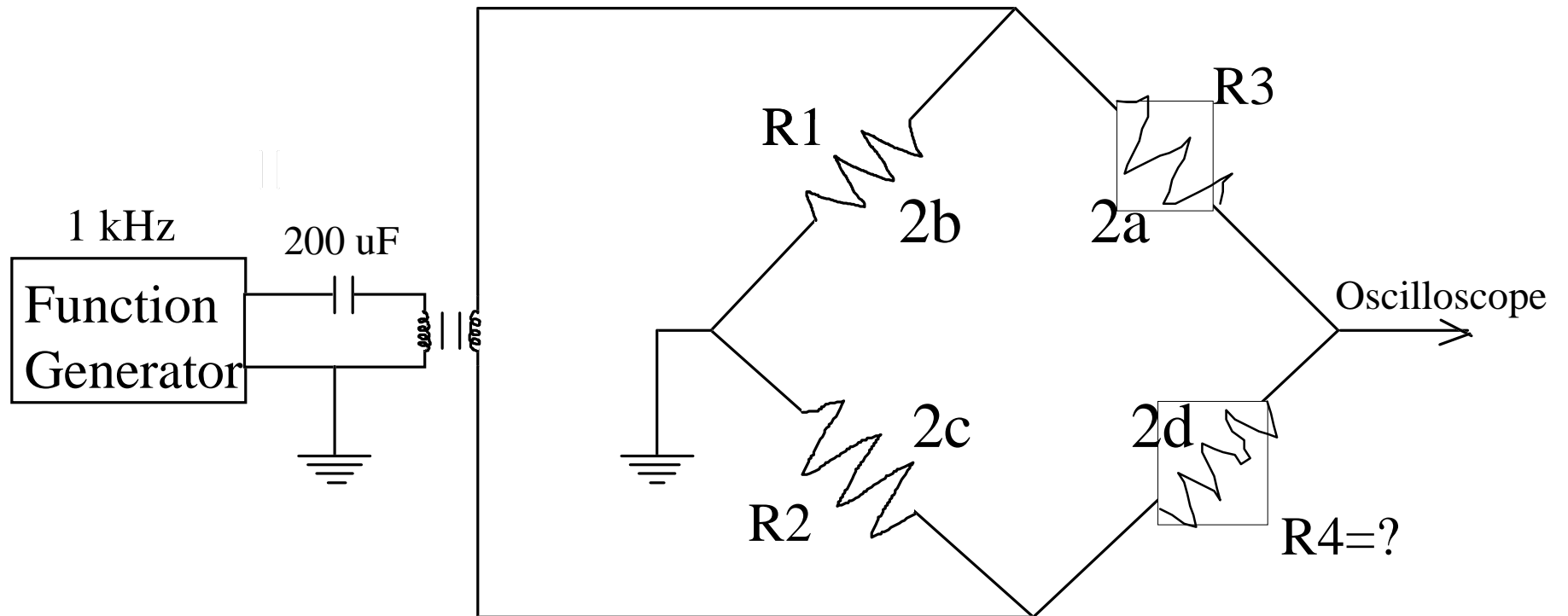

$$Z2 \cdot Z3 = Z1 \cdot Z4$$

$$R2 \cdot R3 = R1 \cdot R4$$


$$R4 = R3 \times (R2/R1)$$

$$R4 = R3 \div (R1/R2)$$


If R3 is viewed as the standard, then the unknown R4 equals the standard multiplied by the ratio R2/R1 or divided by the ratio of R1/ R2. The sharpest null is obtained by keeping the ratio R2/R1 = 1. However, this can be done only if a standard equal to the unknown is available.

Record values for R1, R2, R3, & R4.

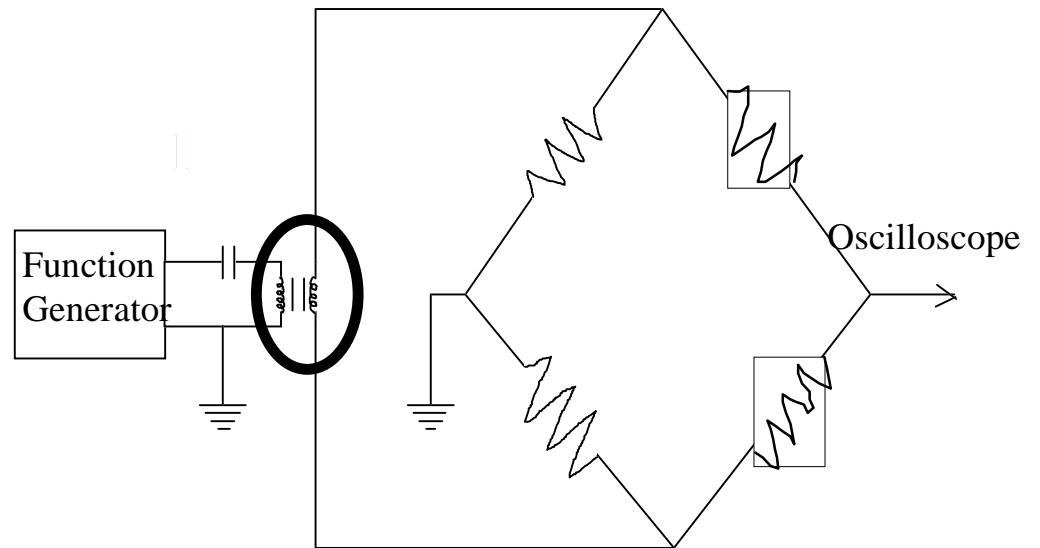- Transformer between the function generator and the bridge is used to isolate **grounding** of the bridge circuit as shown. This, in turn, makes possible the use of a single channel of the oscilloscope instead of a differential mode for balancing the bridge.




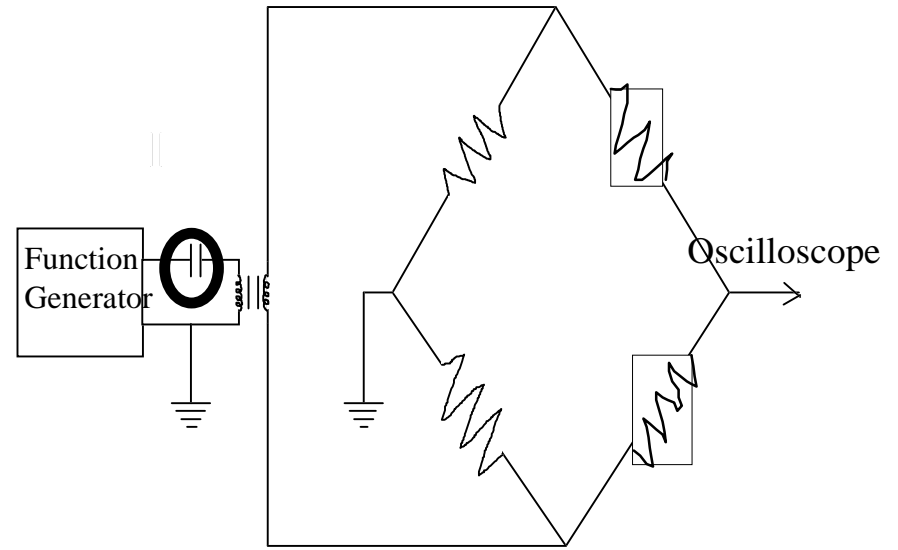- The capacitor between the function generator and the transformer is used to prevent accidental dc bias to the transformer and electrical shock if a lead is disconnected.



$$V (t) = L \times \frac{d I}{d t}$$

Part II- Capacitance Measurement

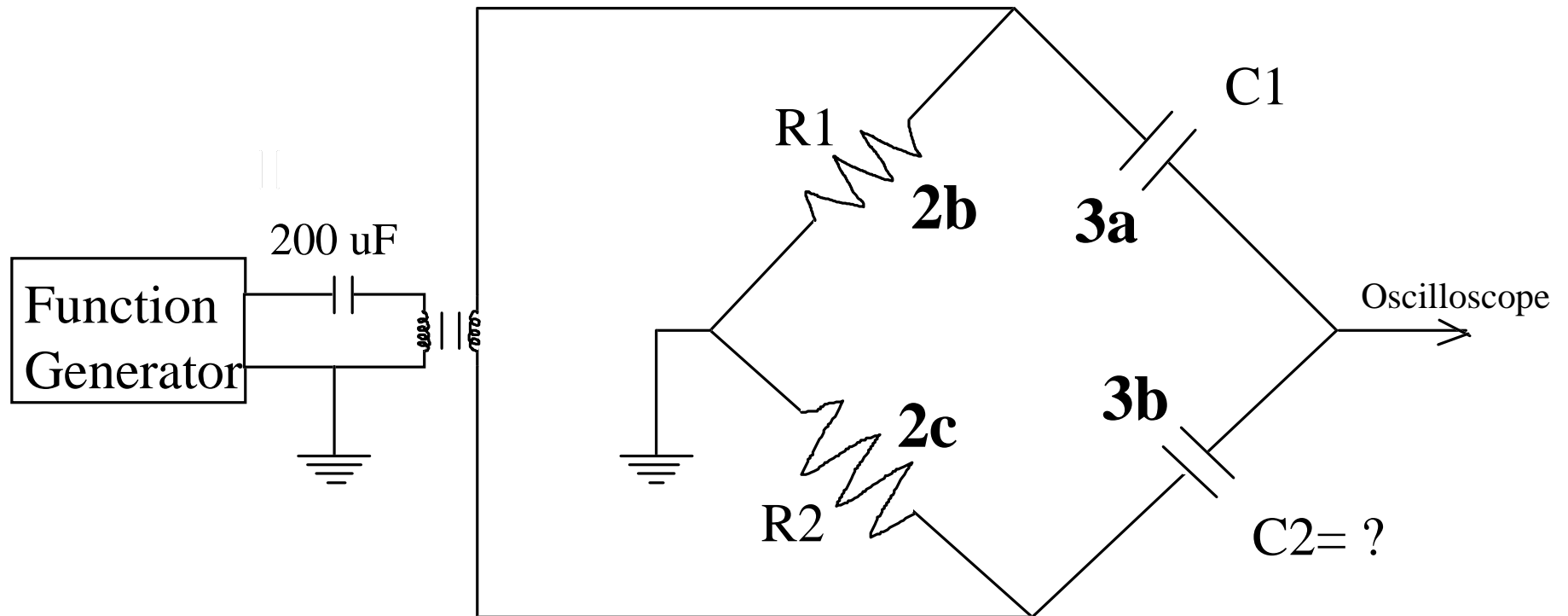

$$Z_2 \cdot Z_3 = Z_1 \cdot Z_4$$

$$R_2 \cdot (1/j\omega C_1) = R_1 \cdot (1/j\omega C_2) \quad \& \quad R_2 C_2 = R_1 C_1$$

$$C_2 = C_1 \times (R_1/R_2)$$


$$C_2 = C_1 \div (R_2/R_1)$$


If C_1 is viewed as the standard, then the unknown C_2 equals the standard multiplied by the ratio R_1/R_2 or divided by the ratio of R_2/R_1 . The sharpest null is obtained by keeping the ratio $R_2/R_1 = 1$. However, this can be done only if a standard equal to the unknown is available.

Record values for R_1 , R_2 , C_1 , & C_2 .

A capacitor of unknown (to you) value will be supplied by an instructor. Measure the value of this capacitance and then find out from the instructor what the actual value is.


Part III- Inductance Measurement

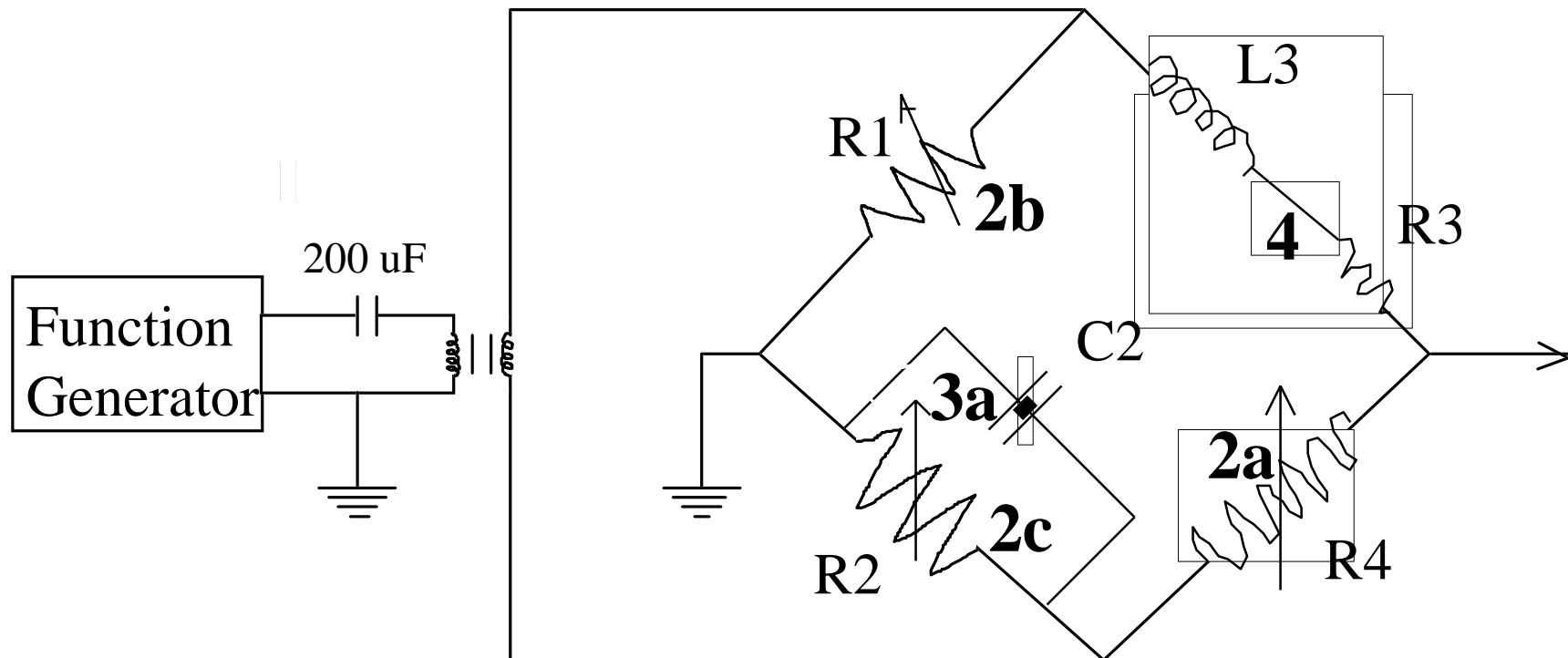

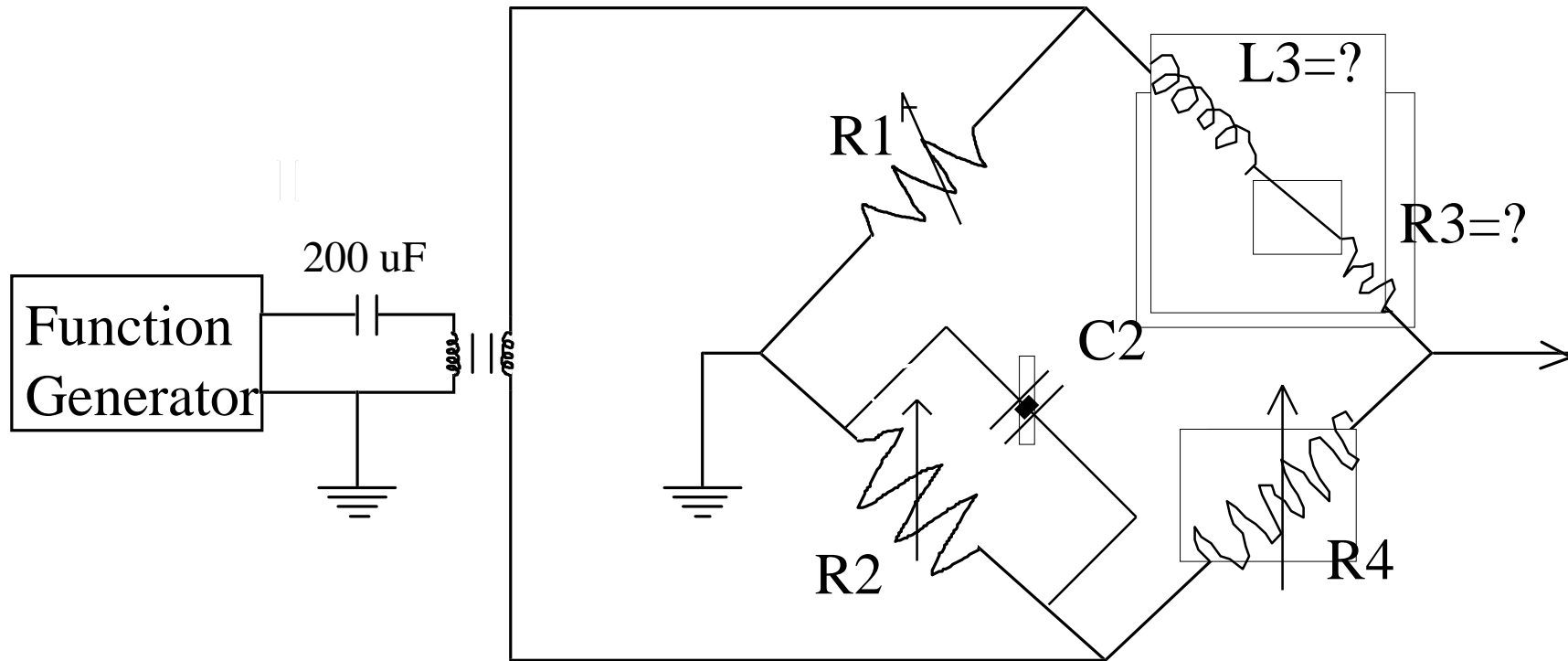

- Measure the values for inductance $L3$ of an unknown inductor and its internal resistance $R3$. The nominal inductance equals 1 mH.
 - Measure the dc value for the resistance $R3$ of the inductor with a Fluke DMM. Skin effect could cause the ac resistance to increase as the ac frequency increases.
- Can you explain skin effect?


$$Z_1 \times Z_4 = Z_2 \times Z_3$$

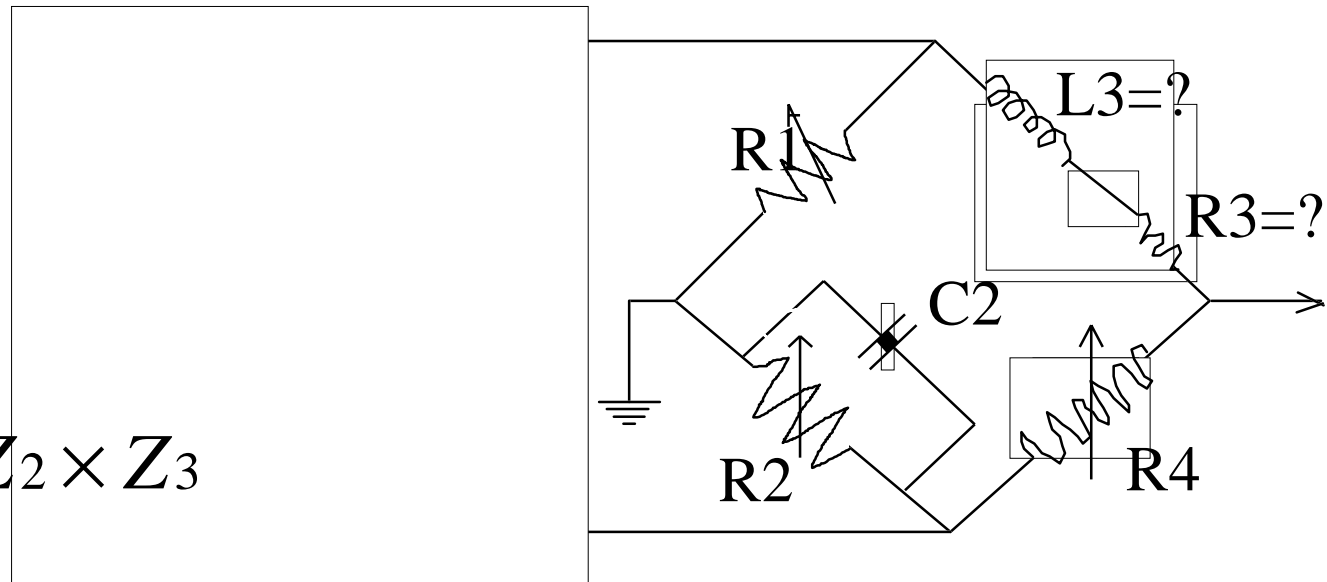

$$R_1 \times R_4 = (R_3 + j \cdot L_3 \cdot \omega) \cdot \left(\frac{1}{\left(\frac{1}{R_2} + j \cdot \omega \cdot C_2 \right)} \right)$$
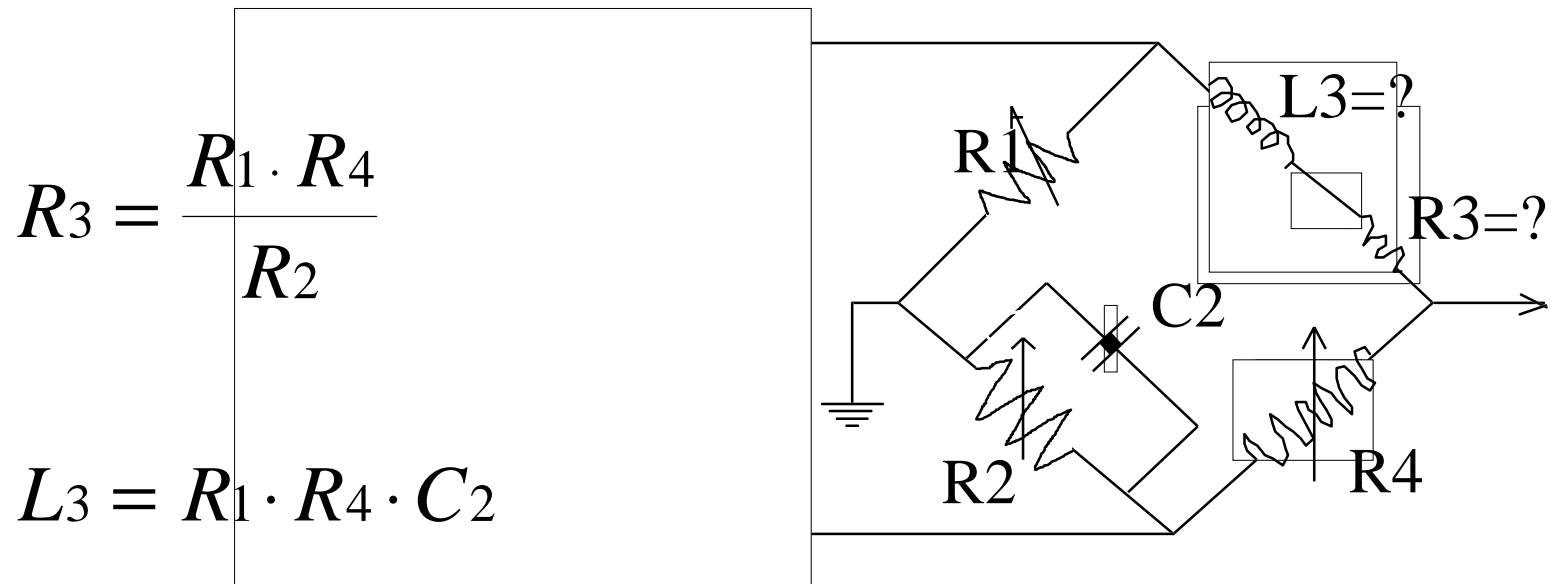
$$R_1 \cdot R_4 + \boxed{j} \cdot \omega \cdot R_1 \cdot R_2 \cdot R_4 \cdot C_2 = R_2 \cdot R_3 + \boxed{j} \cdot \omega \cdot R_2 \cdot \boxed{L_3}$$





- Keep C_2 & R_4 constant .
- Vary R_1 & R_2 until balance reached.

New Task for 2000

- : Eliminate the isolation transformer & repeat Maxwell Bridge Exp. using CRO Differential Measurement Technique.

No Report for Experiment 4 Bridges

Since there is no report, your Laboratory Notebook (LN) should be done carefully and should include discussion and conclusions.

The weighting factor for the Laboratory Notebook grade_for E4 will be higher than that for E3.