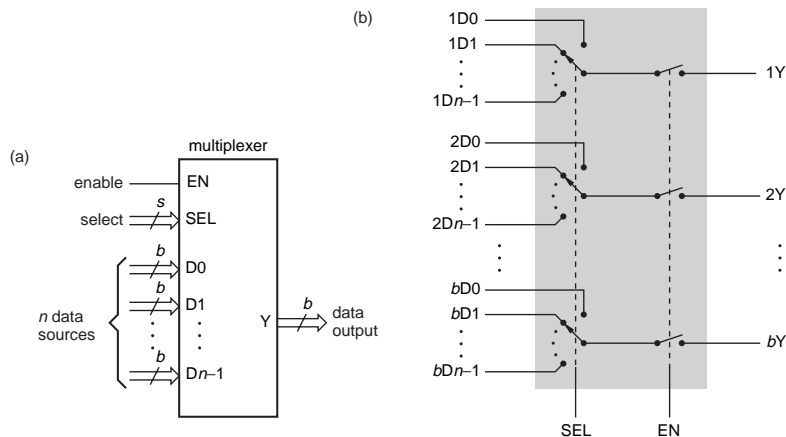


Multiplexers


A multiplexer is a (one-directional) digital switch.



Parameters for n -input b -output mux:

- b outputs
- n inputs per output
- $\lceil \log_2 n \rceil$ select signals

74x157 quad 2-to-1 mux

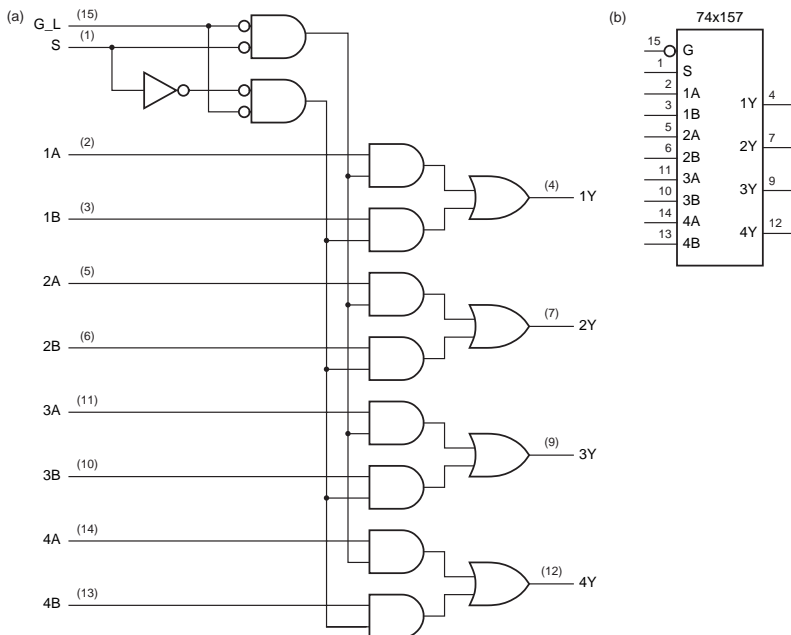

Typical muxes in Xilinx library: M2_1, M8_1E

Multiplexer truth tables

This is same as truth table for M2_1E (except enable active level).

Inputs		Outputs			
G_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

Table 5-35
Truth table for a 74x157 2-input, 4-bit multiplexer.

The 8-input 74x151 corresponds to M8_1E with an extra output.

Inputs				Outputs	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'


Table 5-34
Truth table for a 74x151 8-input, 1-bit multiplexer.

October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6-3

74x151 8-to-1 mux

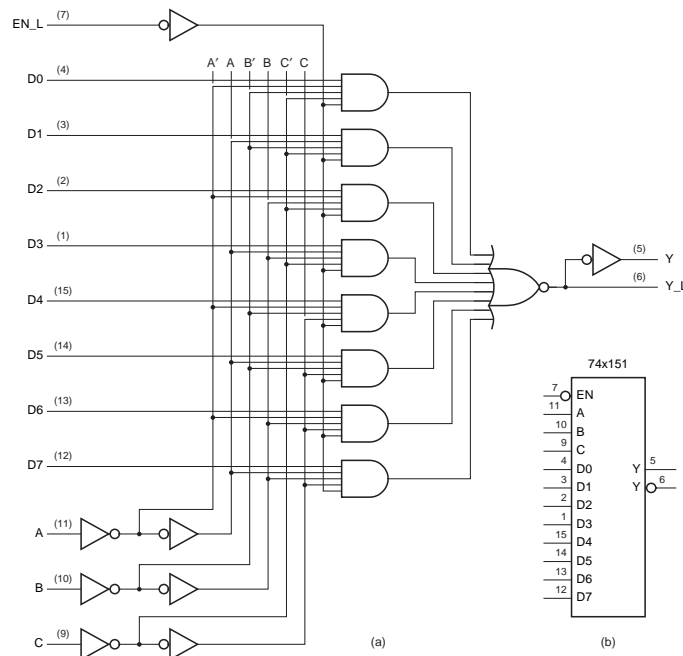


October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6-4

Expanding multiplexers

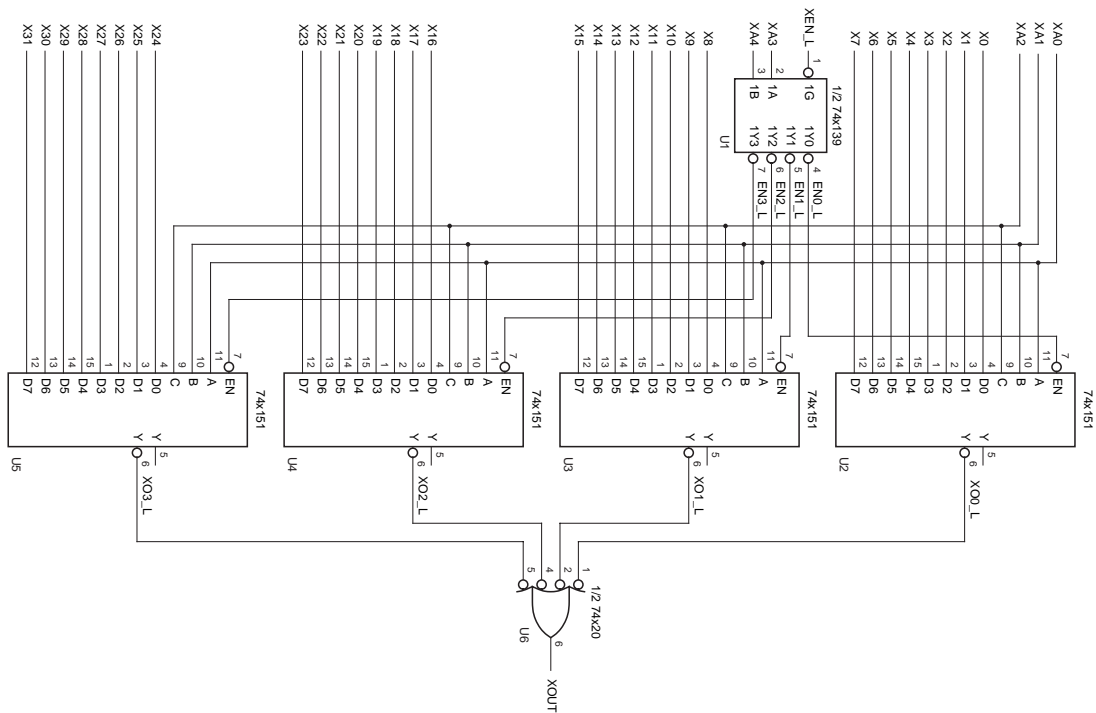


October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6-5

Encoders

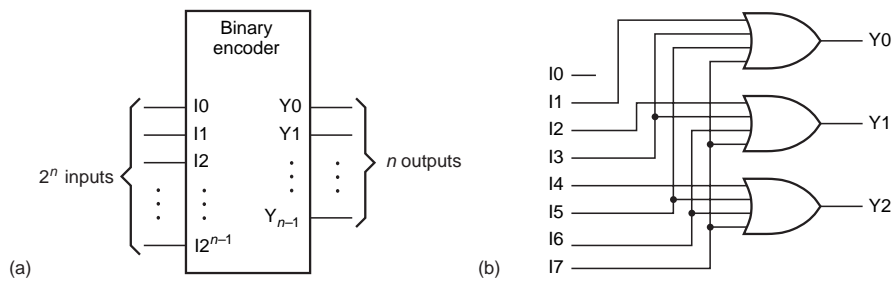Encoder converts input signals to more useful, usually more compact, representation. Most common encoder is 2^n -to- n binary encoder.



Equations for 8-to-3 encoder:

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_0 = I_1 + I_3 + I_5 + I_7$$


October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6-6

Encoder application

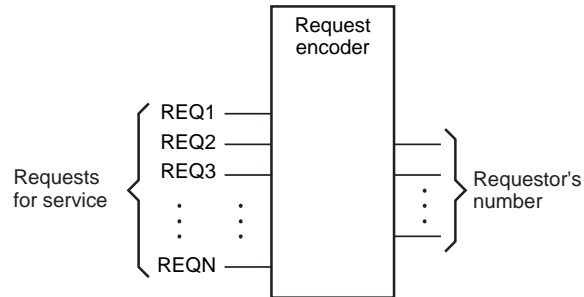Typical application: produce the index of “the” signal that is active.



If more than one signal can be active, highest priority signal is selected.

A more advanced encoder might output indexes of highest two active signals.


An even more advanced encoder might remember previous requests and change priorities.

October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6–7

Priority encoder

 

$$H7 = I7$$

$$H6 = I6 * /I7$$

$$H5 = I5 * /I6 * /I7$$

$$H4 = I4 * /I5 * /I6 * /I7$$

$$H3 = I3 * /I4 * /I5 * /I6 * /I7$$

$$H2 = I2 * /I3 * /I4 * /I5 * /I6 * /I7$$

$$H1 = I1 * /I2 * /I3 * /I4 * /I5 * /I6 * /I7$$

$$A2 = H4 + H5 + H6 + H7$$

$$A1 = H2 + H3 + H6 + H7$$

$$A0 = H1 + H3 + H5 + H7$$

$$IDLE = /(I0 + \dots + I7)$$


October 15, 2002

EE 121: Digital Design Laboratory

Lecture 6–8


74x148 priority encoder

Table 5-23 Truth table for a 74x148 8-input priority encoder.

 

Inputs								Outputs					
EI_L	I0_L	I1_L	I2_L	I3_L	I4_L	I5_L	I6_L	I7_L	A2_L	A1_L	A0_L	GS_L	EO_L
1	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	1	0	1
0	x	x	x	x	x	0	1	1	0	1	0	0	1
0	x	x	x	x	0	1	1	1	0	1	1	0	1
0	x	x	x	0	1	1	1	1	1	0	0	0	1
0	x	0	1	1	1	1	1	1	1	1	0	0	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0


Cascaded priority encoders

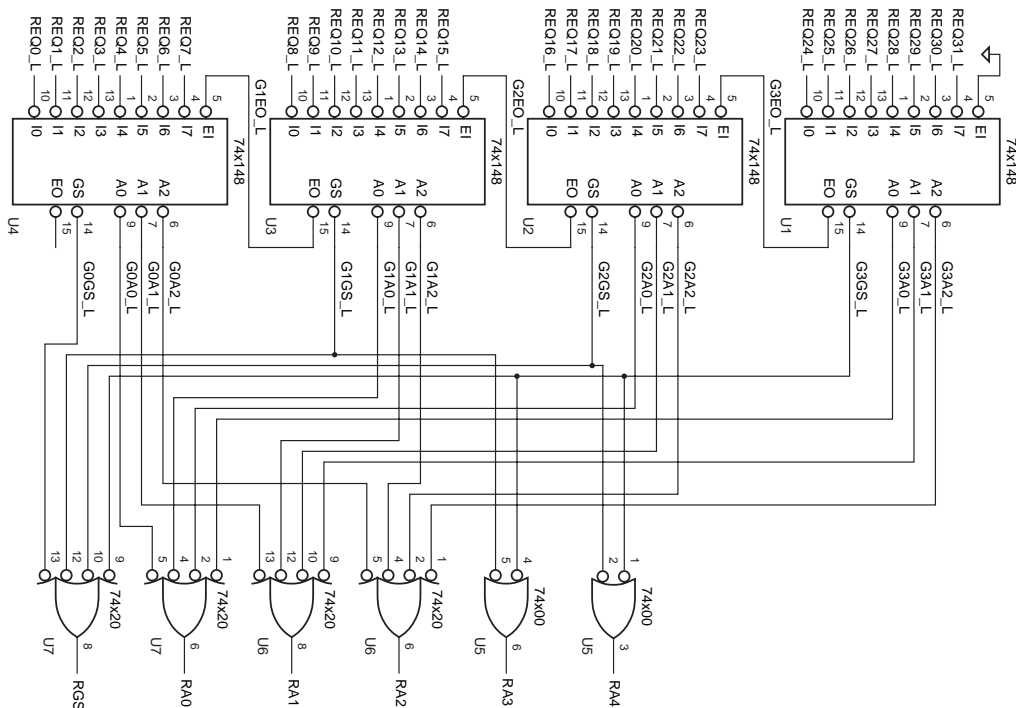

Comparators

A one-bit comparator is the same as the XNOR or equivalence function (note that NXOR would be a better name than XNOR):
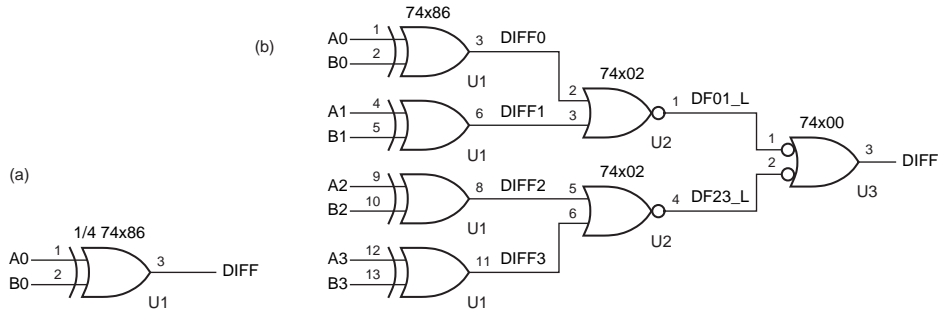
$$\text{XNOR}(X, Y) = X \cdot Y + X' \cdot Y' = (X \cdot Y' + X' \cdot Y)'$$




An n-bit comparator determines if two n-bit signal vectors are equal:

$$\text{EQ}(X[1 : n], Y[1 : n]) = (X_1 = Y_1) \cdot (X_2 = Y_2) \cdot \dots \cdot (X_n = Y_n)$$

Magnitude comparators

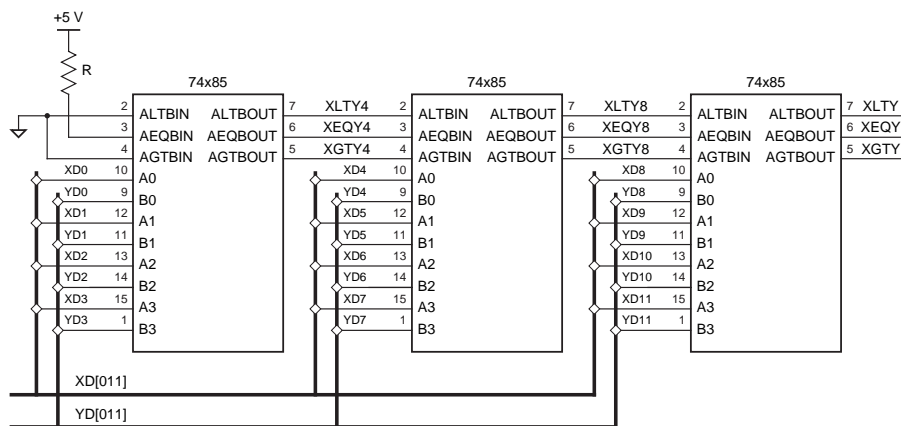Comparator components are designed to be cascadable.



Xilinx library includes, among others, COMP8 (equality comparator) and COMP8 and COMP8C (magnitude comparators).