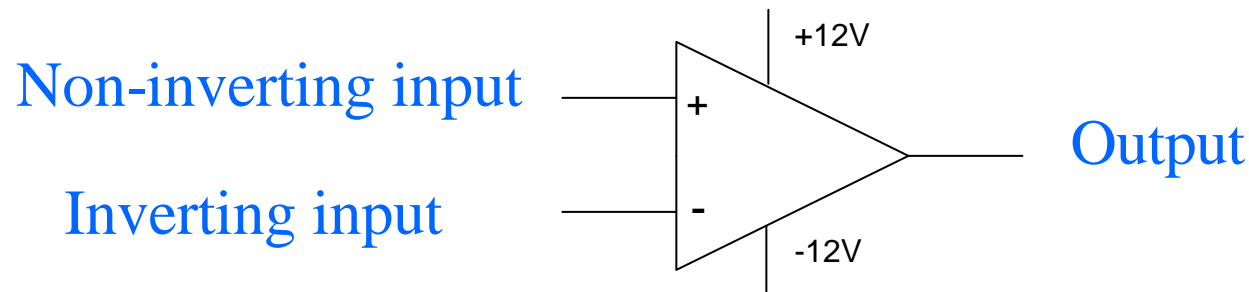




Operational Amplifiers



- Before digital computers became so universal, analog computers were popular for solving problems such as differential equations.
- The basic building block of the analog computer is the *operational amplifier*.
- The outstanding characteristic of the op-amp is its high gain — typically 10^5 to 10^6 which is much greater than can be obtained from a single transistor.





Model of Op-Amp

- The operational amplifier is always connected to supply voltages
- Typically split supplies of $\pm 12\text{V}$ or $\pm 15\text{V}$ are used
- By convention, these supply connections are usually omitted from schematic diagrams
- A model of a real op-amp is given below
- Note that R_{in} is typically very large (say $10\text{M}\Omega$) and R_{out} is typically small (say 25Ω). The open-loop gain, A , is of the order of 10^6

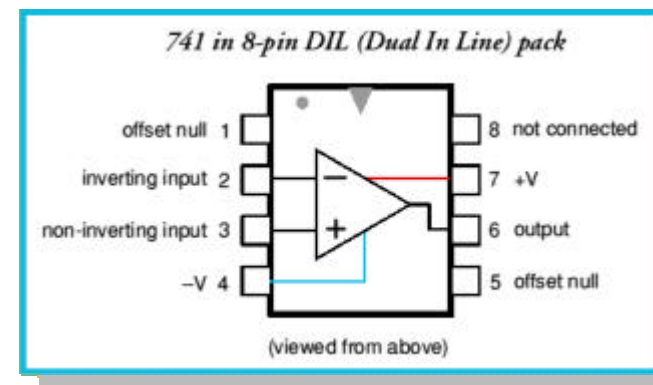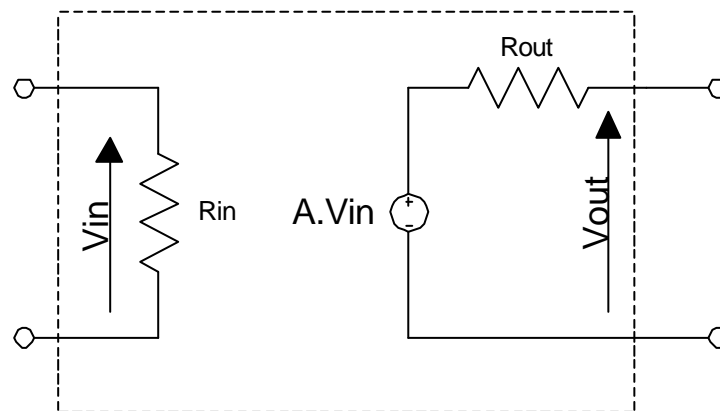




Comments

- An ideal op-amp would have infinite gain, infinite input resistance, and zero output resistance
- We will mainly use the ideal model for simple analysis. The approximation is quite good for real op-amps in many practical cases.
- In particular, we will assume infinite input resistance, and zero output resistance.
- We will assume a large gain A and take the limits of performance as A tends to infinity.



Inverting Amplifier

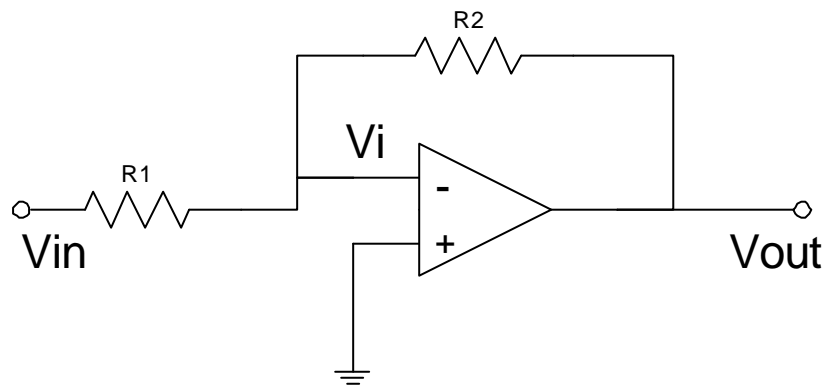

$$\frac{V_{out}}{V_{in}} = -\frac{R2}{R1}$$

Since infinite input resistance, current through R1 must equal current through R2

$$\frac{V_{in} - V_i}{R1} = \frac{V_i - V_{out}}{R2}$$

$$V_i - V_{out} = \frac{R2}{R1}(V_{in} - V_i)$$

But $V_{out} = -AV_i$, so

$$-\left(\frac{1}{A} + 1\right)V_{out} = \frac{R2}{R1}\left(V_{in} + \frac{V_{out}}{A}\right)$$

$$-\left(\frac{1}{A} + 1 + \frac{R2}{A.R1}\right)V_{out} = \frac{R2}{R1}V_{in}$$

For A tending to infinity, bracketed term approaches 1

$$\frac{V_{out}}{V_{in}} = -\frac{R2}{R1}$$



Virtual Earth


- In the example, note that as A tends to infinity, the voltage on the inverting input tends to zero
 - with very high gain (approaching infinity) the voltage at the inverting input must be zero or else the output voltage would also be very large
- Thus in this configuration we say that the inverting input is a *virtual earth* point. That is, its potential is zero but it is not physically connected to earth.
- The virtual earth concept makes analysis quite easy.



Summer

- The following circuit can be used to add/subtract voltages to perform arithmetic

Virtual earth

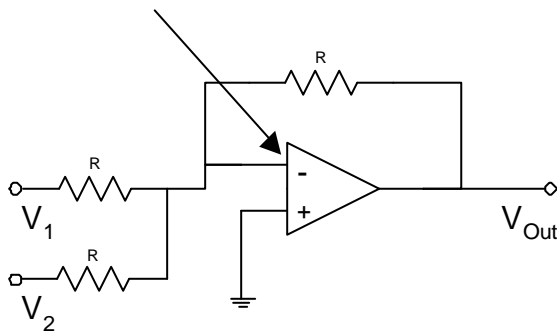

Sum of currents into virtual earth point must equal zero

$$\frac{V_1}{R} + \frac{V_2}{R} + \frac{V_{out}}{R} = 0$$

$$V_{out} = -(V_1 + V_2)$$


$$V_{out} = -(V_1 + V_2)$$

Note the negative sign on the output



Non-Inverting Amplifier

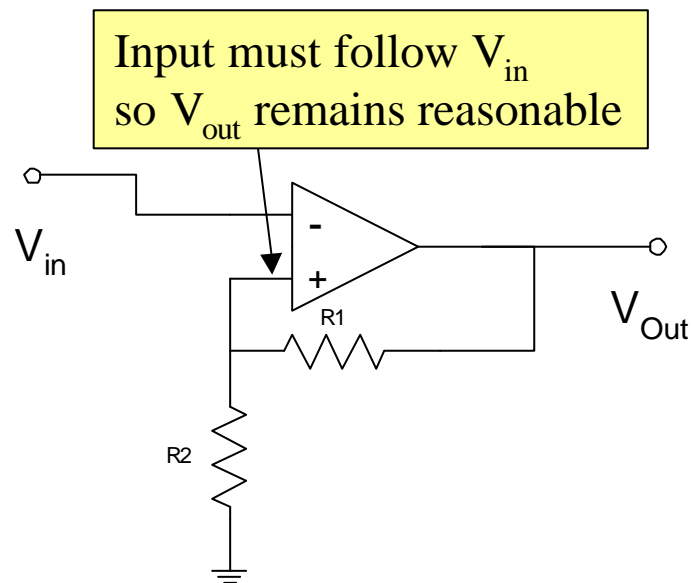- We can also configure the op-amp as a non-inverting amplifier




$$\frac{R2}{R1 + R2} V_{out} = V_{in}$$
$$\frac{V_{out}}{V_{in}} = \frac{R1 + R2}{R2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R1 + R2}{R2}$$



Integrator

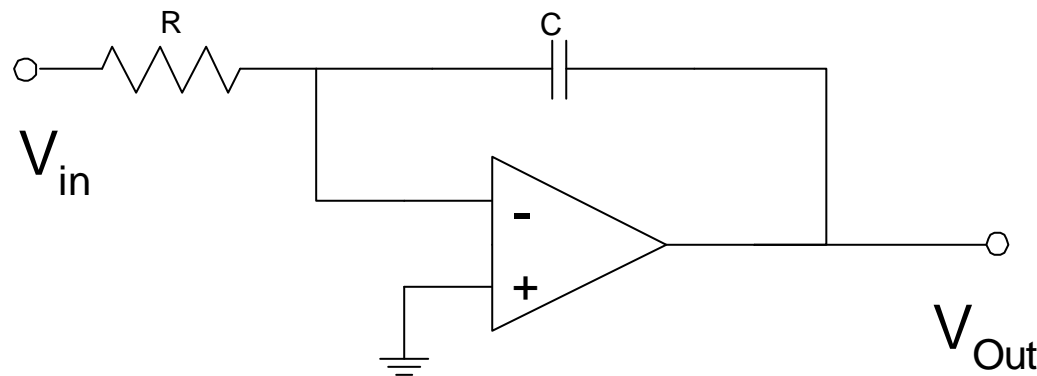- The following circuit acts as an inverting integrator



$$\frac{V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$

$$\frac{dV_{out}}{dt} = -V_{in} \frac{1}{RC}$$


$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$



Differentiator

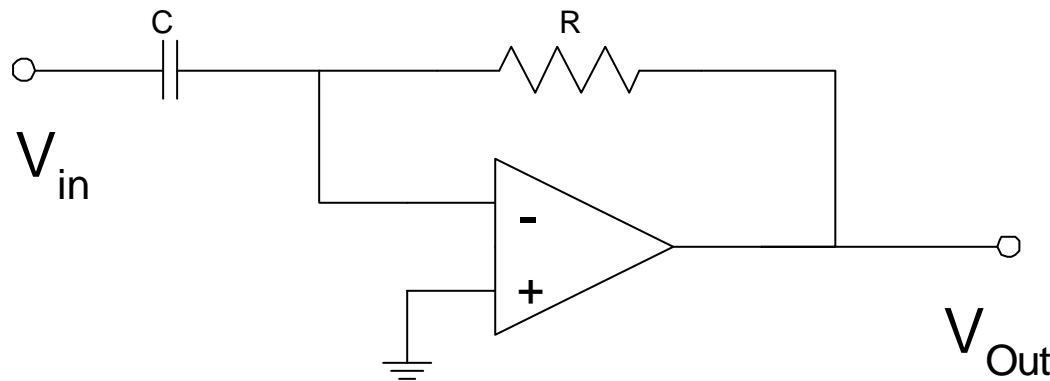- The following circuit acts as an inverting differentiator



$$\frac{V_{out}}{R} + C \frac{dV_{in}}{dt} = 0$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$