



# Energy Storage of Capacitor

- Capacitors do not dissipate power, but store energy when charging and restore it to the circuit when discharging.
- How much energy does a capacitor store?

$$E = \int_0^T P dt = \int_0^T V I dt = \int_0^T V C \frac{dV}{dt} dt$$

RHS allows us to integrate wrt  $V$  instead of  $T$ , but we must change the upper limit of integration to the final capacitor voltage  $V_T$  at  $t=T$

$$E = \int_0^{V_T} C V dv = \frac{1}{2} C V_T^2$$

**In general, just use  
the formula**

$$E = \frac{1}{2} C V^2$$




# Parallel Capacitors

- Recall that capacitance is given by

$$C = \frac{Q}{V}$$

where  $Q$  is the charge and  $V$  is the applied voltage.

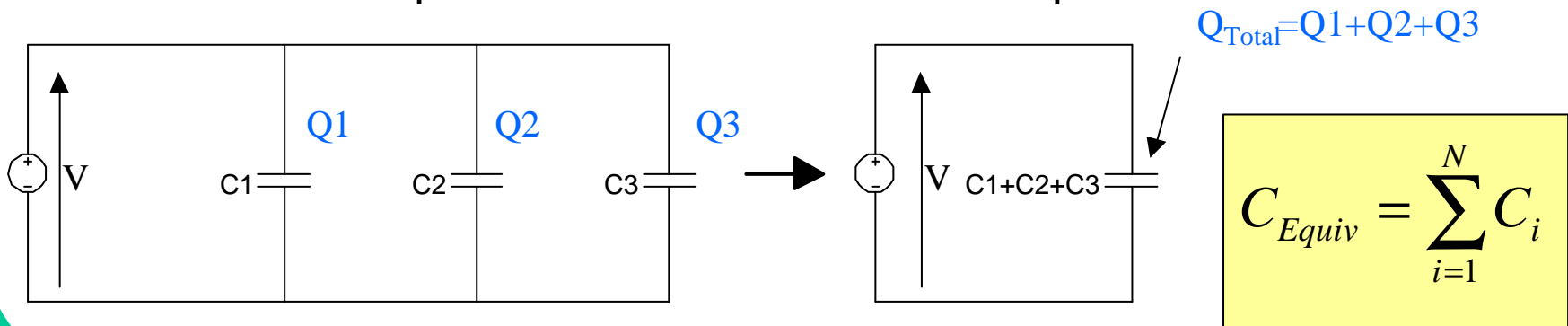
- Thus if capacitors are placed in parallel, the total charge stored will sum and hence the equivalent capacitance will just be the sum of the capacitances of the individual capacitors.




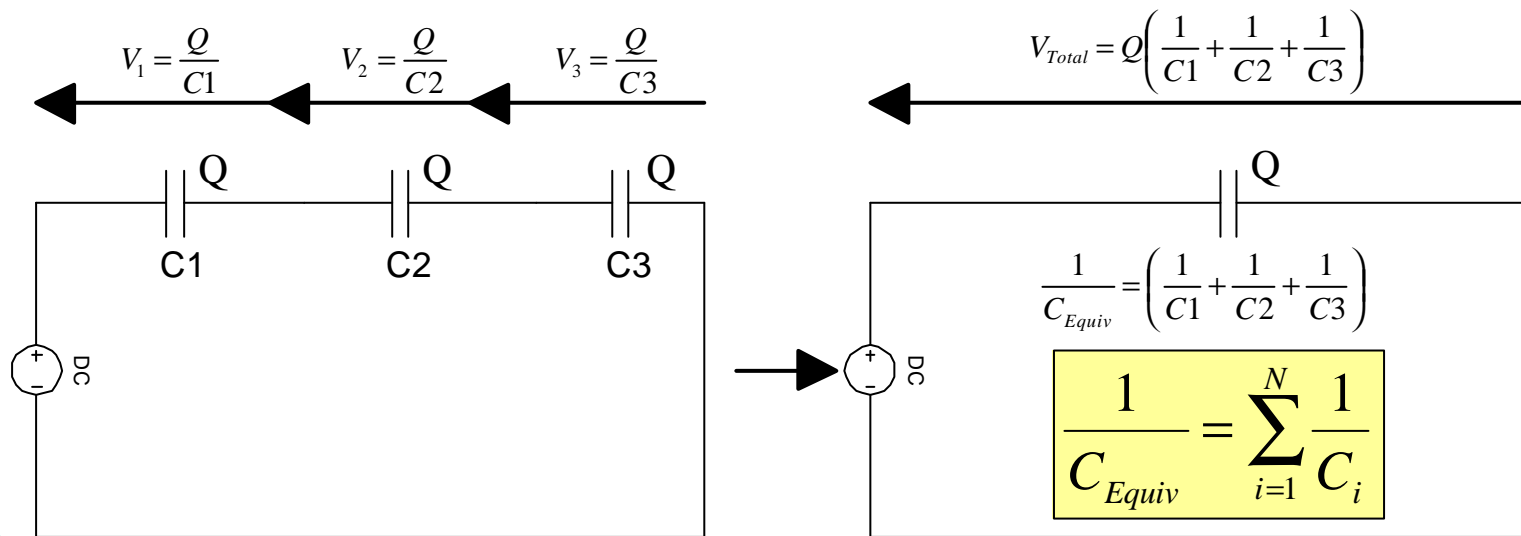
# Series Capacitors

- If a current,  $I$ , is passed through a set of series capacitors over a period of time,  $T$ , each will acquire the same charge  $Q=IT$ .
- Each capacitor,  $C_i$ , will exhibit a voltage,  $V_i=Q/C_i$ .






# Parallel and Series Capacitors

- In other words
  - Capacitors in parallel are combined like the formula for resistors in series
  - Capacitors in series are combined like the formula for resistors in parallel
- Non-standard capacitance values can be made by combining standard value capacitors in parallel and series.


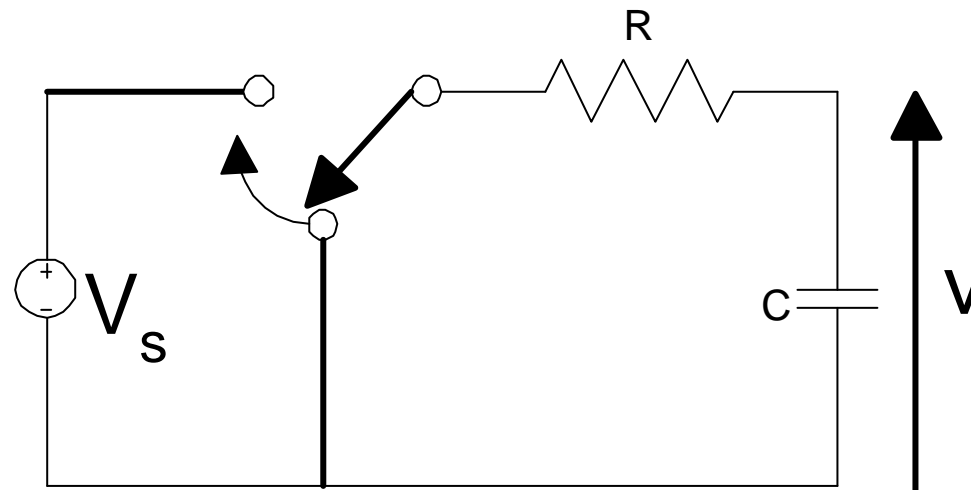
# Behavior of Simple RC Circuit


- Consider that the switch has been in the position shown for a long time so that the capacitor is completely discharged.
- The switch moves to the other position at time  $t=0$ . What is the behaviour of the voltage,  $v$ , across the capacitor?




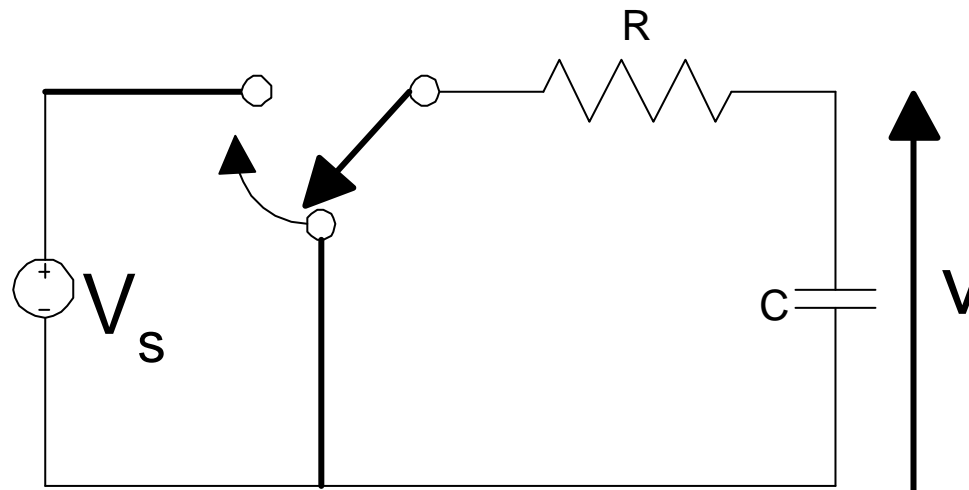
# Simple RC Circuit

- Initially, there will be no charge on the capacitor (hence no voltage across it) and a current of  $i=V_s/R$  will flow through the resistor
- As the capacitor charges, the voltage across the capacitor will rise and the current will decrease.
- Eventually, the capacitor will become completely charged to the voltage  $V_s$  and no current will flow at all.





# Differential Equations

- Using Kirchoff's Voltage Law we have

$$-V_s + iR + \frac{q}{C} = 0 \quad (1)$$

where  $i=i(t)$  and  $q=q(t)$  are the instantaneous current and charge respectively

- Differentiating wrt  $t$  yields

$$R \frac{di}{dt} + \frac{1}{C} i = 0 \Rightarrow i = -RC \frac{di}{dt} \quad (2)$$

- Since this equation says that  $i(t)$  is simply a scalar,  $-RC$ , times  $di/dt$ , we guess that  $i(t)$  must take the form of an exponential function. (Recall that the derivative of  $e^x$  wrt  $x$  is also  $e^x$ )
- Thus to solve (2),  $i(t)$  must take the form where  $A$  is a scalar constant

$$i = A e^{-\frac{t}{RC}}$$



## Solution to Equations

$$i = Ae^{-\frac{t}{RC}}$$

- We solve for A by substituting back into (1) at time  $t=0$ .

$$-V_s + iR + \frac{q}{C} = 0 \quad (1)$$

at time  $t = 0$ ,  $q = 0$ , and  $i = Ae^{-\frac{t}{RC}} = A$ , yielding

$$-V_s + AR = 0 \quad (1)$$

- Thus  $A=V_s/R$  and the final solution is


$$i = \frac{V_s}{R} e^{-\frac{t}{RC}}$$





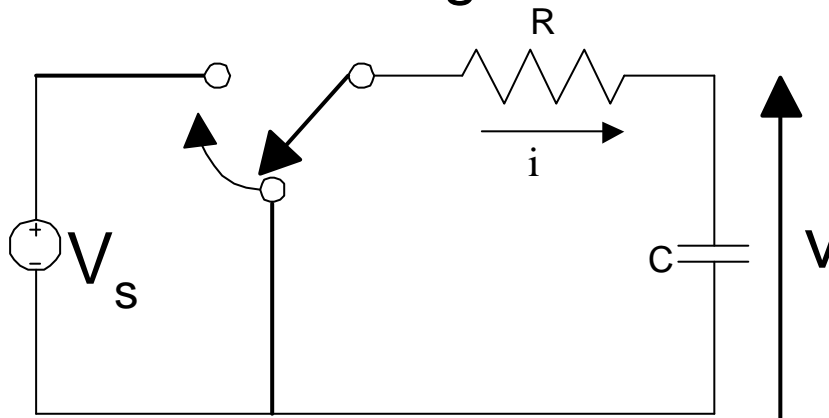
# Capacitor Voltage

- The voltage across the capacitor,  $v$ , is given by  $V_s$  minus the voltage across the resistor given by  $V_R=iR$


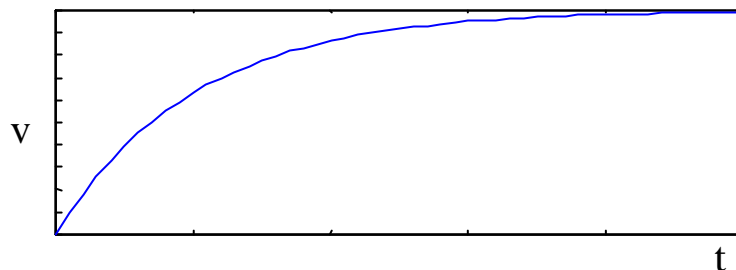
$$\begin{aligned} v &= V_s - iR \\ &= V_s - \frac{V_s}{R} e^{-\frac{t}{RC}} R \\ &= V_s \left( 1 - e^{-\frac{t}{RC}} \right) \end{aligned}$$




$$v = V_s \left( 1 - e^{-\frac{t}{RC}} \right)$$


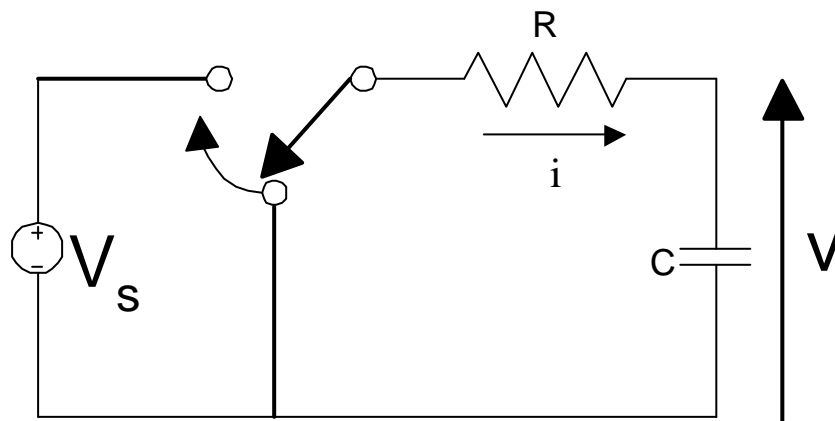
# Final Voltages and Currents

- The quantity  $RC$  is called the time constant of the circuit denoted by the Greek symbol,  $\tau$ , (Tau)
- The time constant has the units of time (seconds).




$$v = V_s \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$i = \frac{V_s}{R} e^{-\frac{t}{\tau}}$$


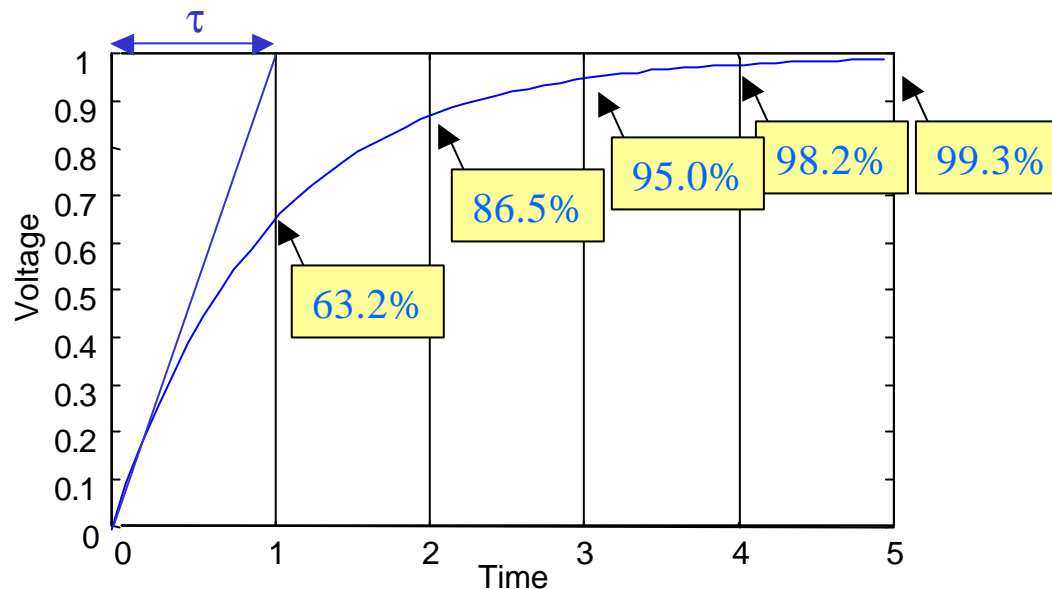
# Voltage Characteristics

- If we plot normalised voltage (fraction of supply voltage) across the capacitor against time expressed in multiples of the time constants,  $\tau = RC$ , we obtain the following graph.




After  $t=\tau$  time constant we obtain 63.2% of final voltage. After  $t=5\tau$ , we obtain 99.3% of the final voltage

Initial slope is  $V_s/\tau$ .  
This is a quick way to estimate  $\tau$  on an oscilloscope.


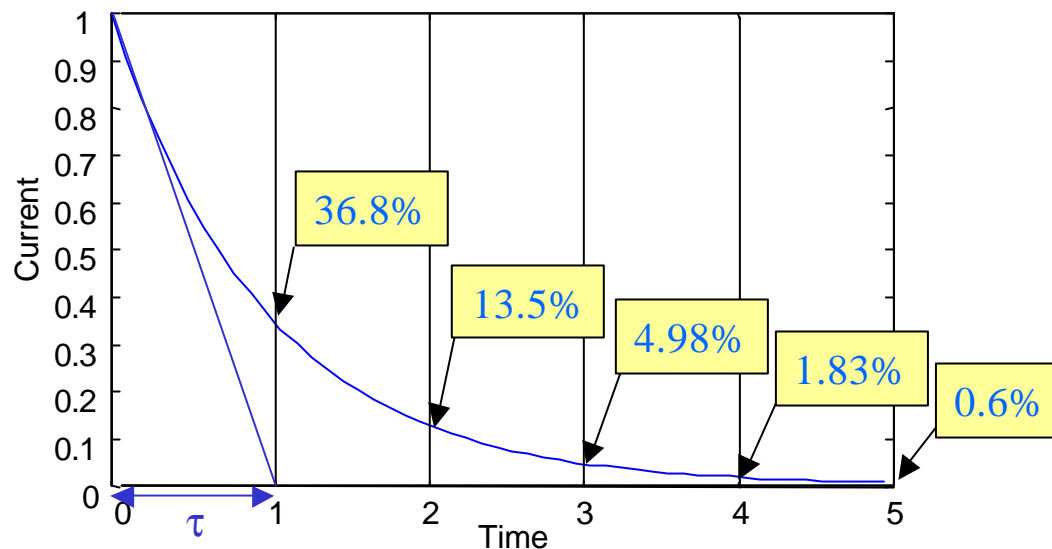
# Current Characteristics

Similarly, If we plot normalised current (fraction of initial current,  $i_0$ ) through the capacitor against time expressed in multiples of the time constants,  $\tau = RC$ , we obtain the following graph.



After  $t=\tau$  time constant we obtain 36.8% of initial current. After  $t=5\tau$ , we obtain 0.6% of the initial current

Initial slope is  $i_0/\tau$ . This is a quick way to estimate  $\tau$  on an oscilloscope.