
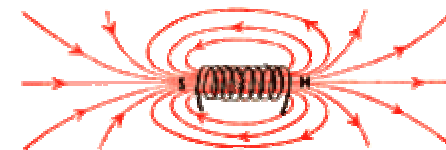


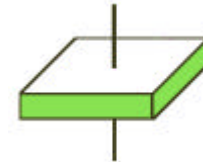

Inductor Energy Storage

- Both capacitors and inductors are energy storage devices
- They do not dissipate energy like a resistor, but store and return it to the circuit depending on applied currents and voltages
- In the capacitor, energy is stored in the electric field between the plates
- In the inductor, energy is stored in the magnetic field around the inductor





Energy Storage Formula

- We write

$$P = IV = I \left(L \frac{dI}{dt} \right)$$

- and since energy

$$E = \int_0^t P dt$$

$$E = \int_0^t IL \frac{dI}{dt} dt = \int_{I_0}^{I_t} LI dI = L \left[\frac{I^2}{2} \right]_{I_0}^{I_t}$$

- and, assuming the initial current $I_0=0$ and the final current $I_t=I$, we have


$$E = \frac{1}{2} LI^2$$

Compare with
capacitor

$$E = \frac{1}{2} CV^2$$



Series Inductors

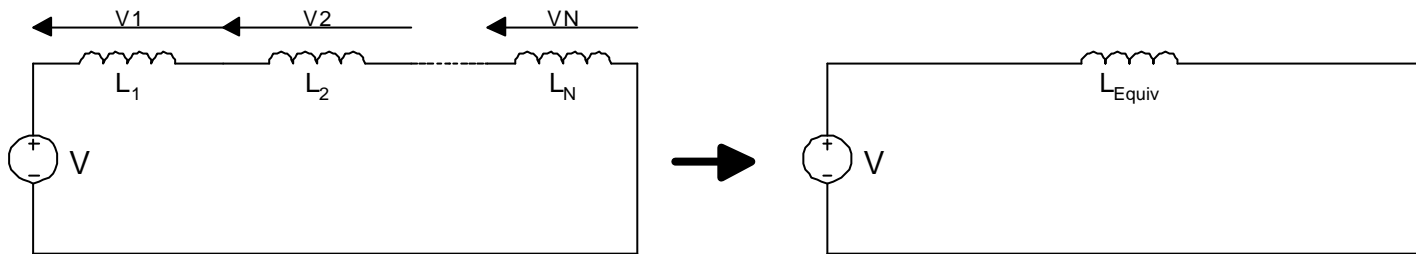

$$\begin{aligned} V &= V_1 + V_2 + \dots + V_N \\ &= L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + \dots + L_N \frac{dI}{dt} \\ &= (L_1 + L_2 + \dots + L_N) \frac{dI}{dt} \end{aligned}$$


$$V = L_{\text{Equiv}} \frac{dI}{dt}$$

$$\therefore L_{\text{Equiv}} = L_1 + L_2 + \dots + L_N$$

- So inductors in series add like resistors in series



Parallel Inductors

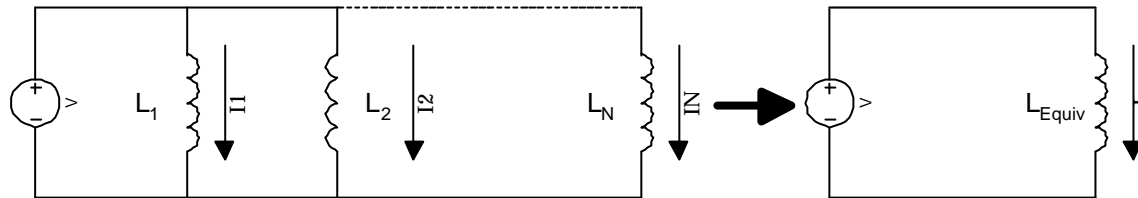

For any inductor r on the left

$$V = L_r \frac{dI_r}{dt} \Rightarrow I_r = \frac{1}{L_r} \int_0^t V dt \quad [+I_r(0) = 0 \text{ assumed}]$$

$$I = \frac{1}{L_{\text{Equiv}}} \int_0^t V dt$$

$$I = \sum_{r=1}^N \left(\frac{1}{L_r} \int_0^t V dt \right) = \sum_{r=1}^N \frac{1}{L_r} \left(\int_0^t V dt \right)$$


$$\frac{1}{L_{\text{Equiv}}} = \sum_{i=1}^N \frac{1}{L_i}$$

- So inductors in parallel add like resistors in parallel



Behaviour of Simple RL Circuits

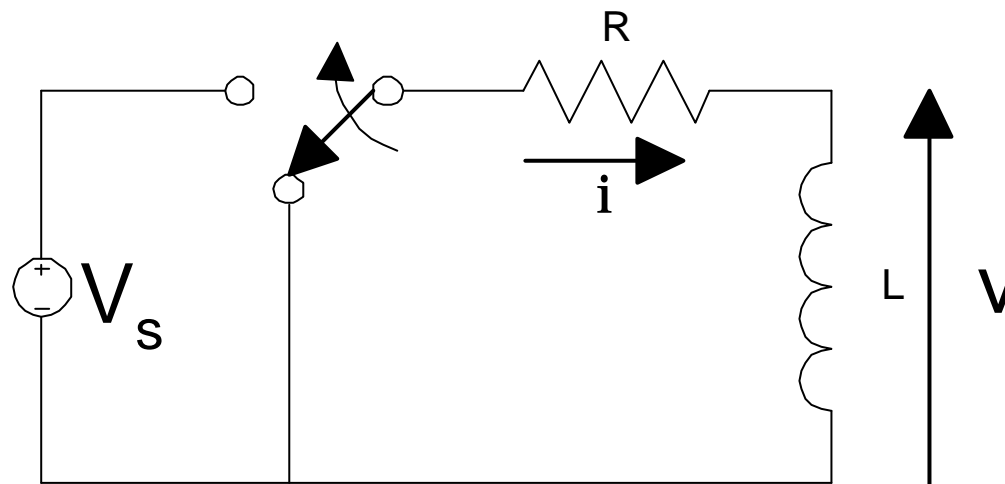- Consider that the switch has been in the position shown for a long time so that no current is flowing.
- The switch moves to the other position at time $t=0$. What is the behaviour of the voltage, v , across the inductor?






Simple RL Circuit

Initially, there will be no current through the inductor because the inductor will create a voltage to oppose a step change in current. Hence a voltage of V_s will initially appear across the inductor.

As the current increases, the voltage across the inductor will decrease.

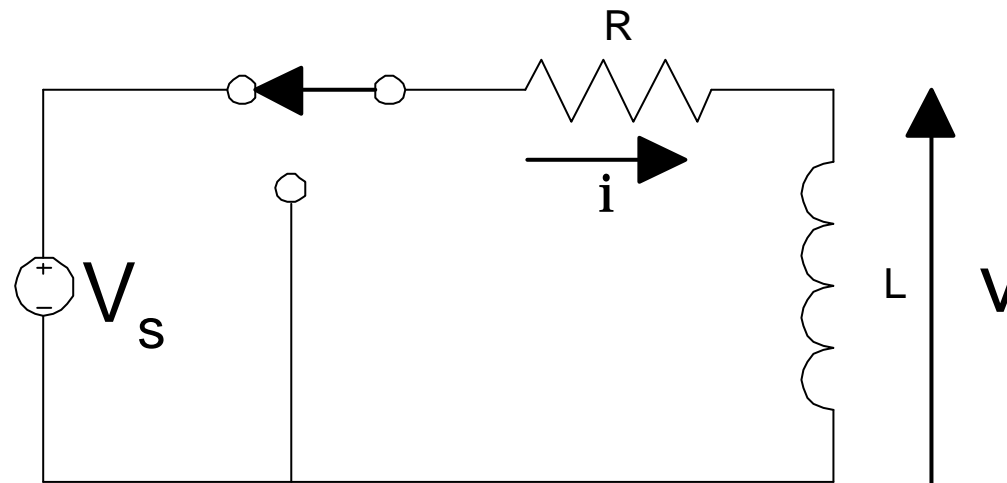Eventually, a steady current of V_s/R will be reached and v will fall to zero.





Analysis of RL Circuit

- Assume the inductor is not storing energy at $t=0$ (no current)
- KVL for this circuit yields

$$V_s = Ri + L \frac{di}{dt}$$

We know the solution has the form

$$i(t) = I_A + I_B e^{-\frac{t}{\tau}}$$

Initial and final boundary values yields

$$I_{\text{initial}} = I_A + I_B = 0; I_{\text{final}} = I_A = \frac{V_s}{R}$$

$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\frac{t}{\tau}} \quad (*)$$



Final Solution

- Now we just need to determine the time constant τ
- Differentiating (*) yields

$$\frac{di}{dt} = \frac{1}{t} \frac{V_s}{R} e^{-\frac{t}{\tau}} = \frac{1}{t} \left(\frac{V_s}{R} - i \right)$$

Backsubstitution into the KVL equation yields

$$V_s = Ri + \frac{L}{t} \left(\frac{V_s}{R} - i \right)$$

$$V_s - Ri = \frac{L}{Rt} (V_s - Ri)$$


$$t = \frac{L}{R}$$

$$i(t) = \frac{V_s}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$



Current Characteristics

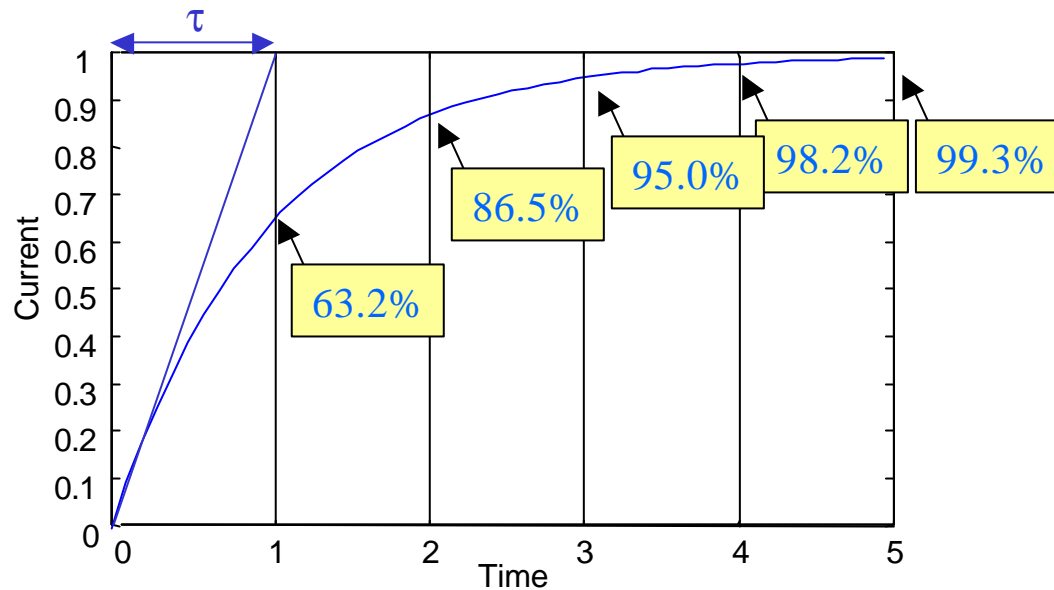If we plot normalised current (fraction of final current $I_0 = V_s/R$) through the inductor against time expressed in multiples of the time constants, $\tau = L/R$, we obtain the following graph.




After $t = \tau$ we obtain 63.2% of the final current. After $t = 5\tau$, we obtain 99.3% of the final current

Initial slope is I_0/τ .
This is a quick way to estimate τ on an oscilloscope.



Voltage Characteristics

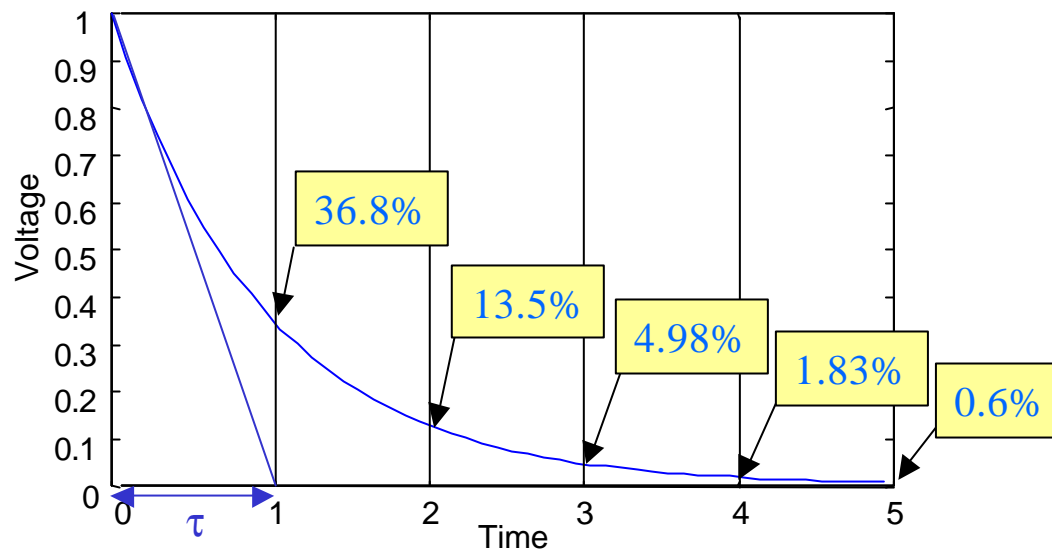Similarly, If we plot normalised voltage (fraction of supply voltage, V_s) across the inductor against time expressed in multiples of the time constant, $\tau = L/R$, we obtain the following graph.



After $t=\tau$ we obtain 36.8% of supply voltage.
After $t=5\tau$, we obtain 0.6% of the supply voltage

Initial slope is V_s/τ .
This is a quick way to estimate τ on an oscilloscope.