

Power conversion circuits

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

Resources and methods for learning about these subjects (list a few here, in preparation for your research):

Question 1

Describe what a *dynamotor* is, and what its purpose might be in an electrical system.
[file 01098](#)

Answer 1

A *dynamotor* is a special type of electromechanical machine intended to convert one form of electrical power into another, using a common magnetic field and rotating element.

Notes 1

The answer here is purposely vague, as I want students to research the details themselves.

Question 2

What is a *DC-DC converter* circuit, and what applications might such a circuit be used for?
[file 01097](#)

Answer 2


A "DC-DC converter" is a circuit that transforms a DC voltage either up or down, generally with an inverse transformation in current. Applications include supplying DC power to load devices where the main power source is DC, but of the wrong voltage.

Notes 2

In many cases, DC-DC converters find use in large systems that were not designed well (i.e. with proper DC voltages provided by a common AC-DC supply circuit). However, converter circuits do have more legitimate uses, including applications where *isolation* is required between two DC circuits. Ask your students what "electrical isolation" is any why it might be important.

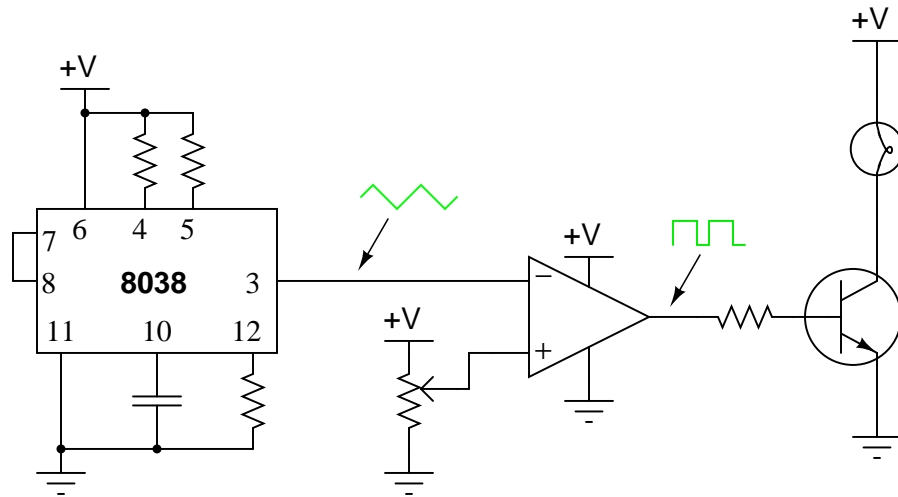Question 3

This circuit uses an 8038 waveform generator IC (integrated circuit) to produce a "sawtooth" waveform, which is then compared against a variable DC voltage from a potentiometer:



The result is a pulse waveform to the base of the power transistor, of the same frequency as the sawtooth waveform. Normally in circuits such as this, the frequency is at least several hundred Hertz.

Explain what happens to the brightness of the lamp when the potentiometer wiper is moved closer to +V, and when it is moved closer to ground.

[file 01105](#)

Answer 3


The lamp glows brighter as the duty cycle of the pulse waveform increases, and visa-versa.

Notes 3

This question is a good review of comparator operation, and it introduces the concept of *duty cycle*, if your students have not encountered it before. Ask your students to explain how and why the duty cycle changes as the potentiometer wiper is moved. Ask them to explain why the lamp's brightness changes with duty cycle, and whether or not this is an efficient method of power control.

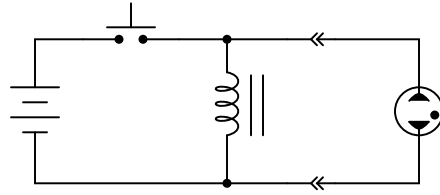Question 4

This circuit generates a pulse of DC voltage sufficient to energize the neon lamp, every time the switch is opened:




Describe the principle of operation for this simple circuit, and also how it could be modified to produce *continuous high-voltage* DC power.

Hint: how does a common AC-DC power supply circuit convert *pulses* of rectified DC into a relatively "smooth" DC output?

[file 01100](#)

Answer 4

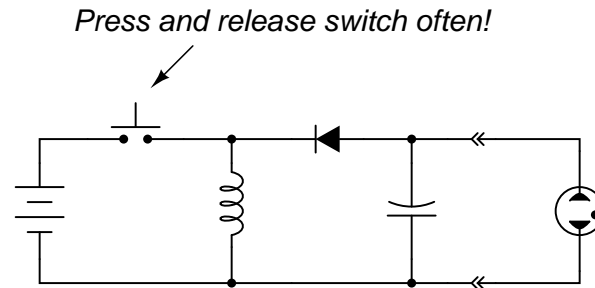


Follow-up question: how would you recommend we "automate" this circuit so that a person does not have to keep pressing and releasing the switch for it to generate a continuous DC output voltage?

Notes 4

Ask your students to explain their solutions for "automating" the switch's action. Prepare yourself for some creative answers!

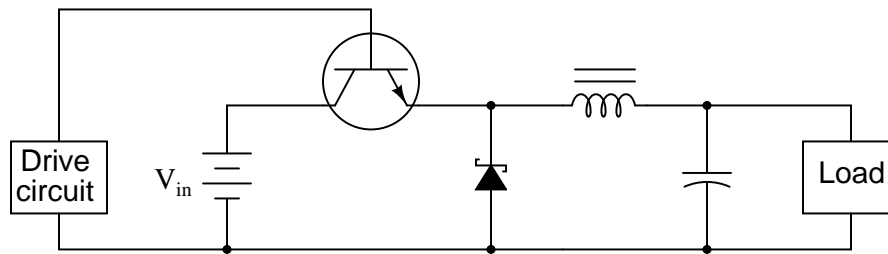Question 5

The schematic diagram shown here is for a "buck" converter circuit, a type of DC-DC "switching" power conversion circuit:




In this circuit, the transistor is either fully on or fully off; that is, driven between the extremes of saturation or cutoff. By avoiding the transistor's "active" mode (where it would drop substantial voltage while conducting current), very low transistor power dissipations can be achieved. With little power wasted in the form of heat, "switching" power conversion circuits are typically very efficient.


Trace all current directions during both states of the transistor. Also, mark the inductor's voltage polarity during both states of the transistor.

[file 01102](#)

Answer 5

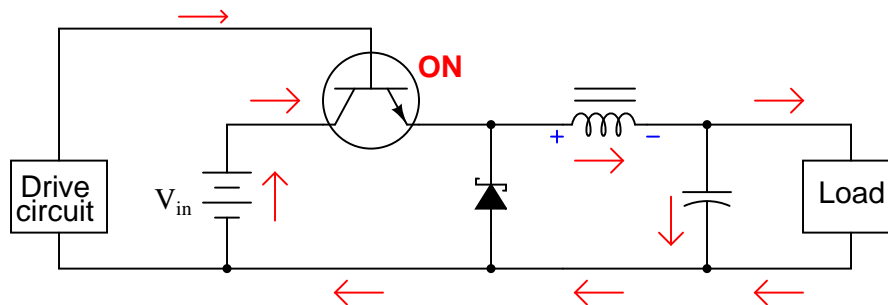

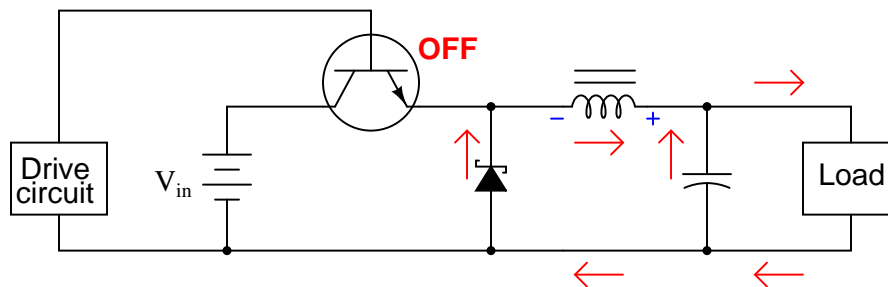Note: all currents shown using conventional flow notation




Follow-up question: how does the load voltage of this converter relate to the supply (battery) voltage? Does the load receive more or less voltage than that provided by the battery?

Challenge question: why do you suppose a Schottky diode is used in this circuit, as opposed to a regular (PN) rectifying diode?

Ask your students why they think this circuit is called a *buck* converter. "Buck" usually refers to something that is in opposition. What is being opposed in this circuit?

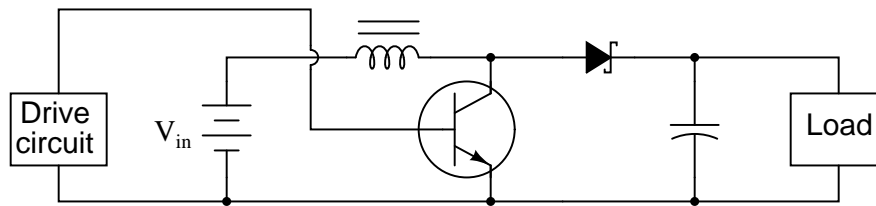Question 6

The schematic diagram shown here is for a "boost" converter circuit, a type of DC-DC "switching" power conversion circuit:




In this circuit, the transistor is either fully on or fully off; that is, driven between the extremes of saturation or cutoff. By avoiding the transistor's "active" mode (where it would drop substantial voltage while conducting current), very low transistor power dissipations can be achieved. With little power wasted in the form of heat, "switching" power conversion circuits are typically very efficient.


Trace all current directions during both states of the transistor. Also, mark the inductor's voltage polarity during both states of the transistor.

[file 01103](#)

Answer 6

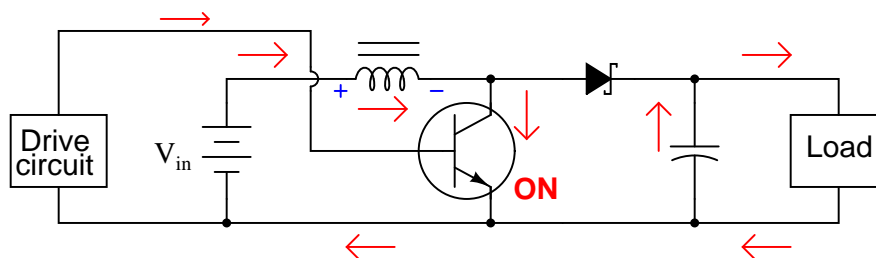

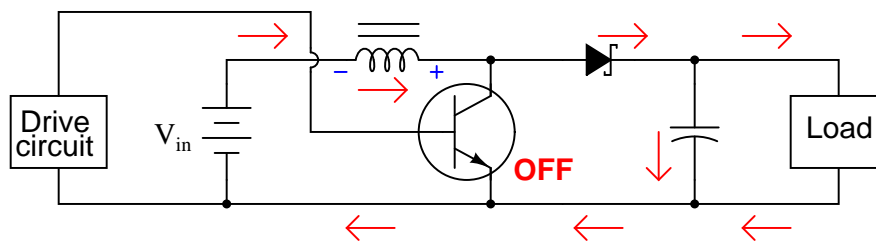Note: all currents shown using conventional flow notation



Follow-up question: how does the load voltage of this converter relate to the supply (battery) voltage? Does the load receive more or less voltage than that provided by the battery?


Challenge question: why do you suppose a Schottky diode is used in this circuit, as opposed to a regular (PN) rectifying diode?

Notes 6

Ask your students why they think this circuit is called a *boost* converter. "Boost" usually refers to something that is aiding something else. What is being aided in this circuit?

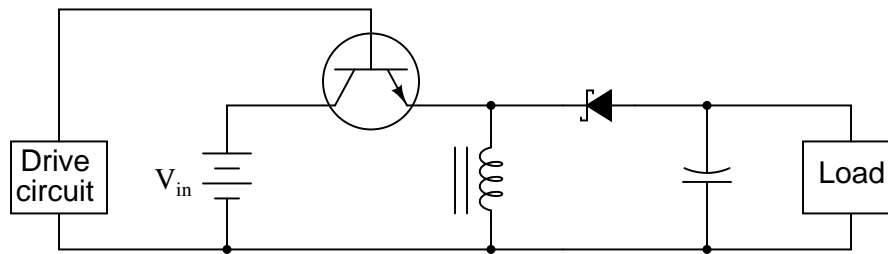Question 7

The schematic diagram shown here is for an *"inverting" converter circuit*, a type of DC-DC "switching" power conversion circuit:





In this circuit, the transistor is either fully on or fully off; that is, driven between the extremes of saturation or cutoff. By avoiding the transistor's "active" mode (where it would drop substantial voltage while conducting current), very low transistor power dissipations can be achieved. With little power wasted in the form of heat, "switching" power conversion circuits are typically very efficient.

Trace all current directions during both states of the transistor. Also, mark the inductor's voltage polarity during both states of the transistor.

[file 02285](#)

Answer 7

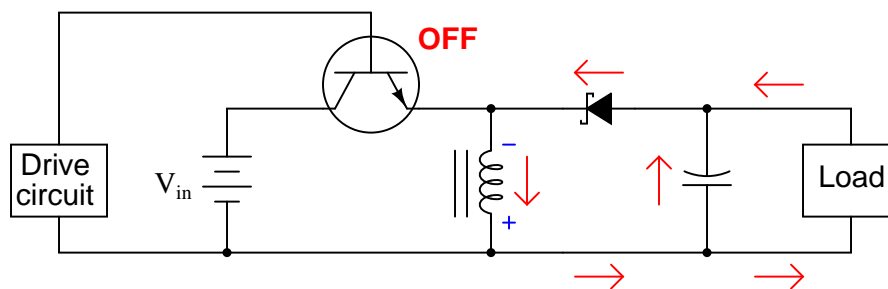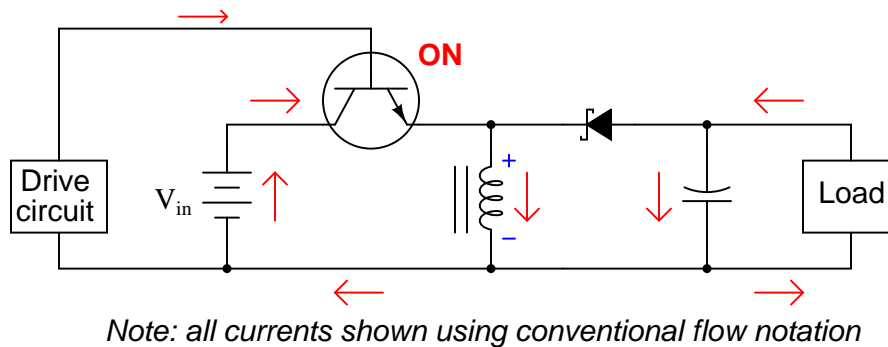


Notes 7

Ask your students why they think this circuit is called an *inverting* converter.

Although it may not be evident from viewing the circuit schematic, this converter circuit is capable of stepping voltage up *or* down, making it quite versatile.

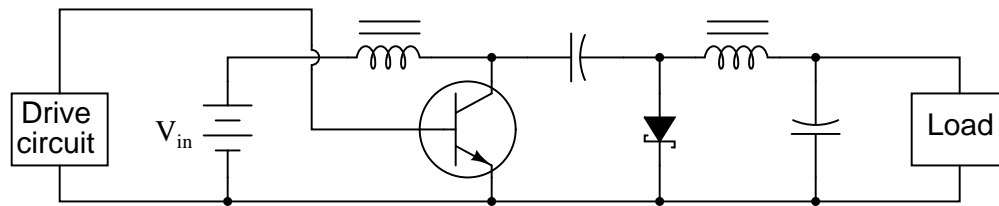Question 8

The schematic diagram shown here is for a "Cuk" converter circuit, a type of DC-DC "switching" power conversion circuit:




In this circuit, the transistor is either fully on or fully off; that is, driven between the extremes of saturation or cutoff. By avoiding the transistor's "active" mode (where it would drop substantial voltage while conducting current), very low transistor power dissipations can be achieved. With little power wasted in the form of heat, "switching" power conversion circuits are typically very efficient.


Trace all current directions during both states of the transistor. Also, mark the both inductors' voltage polarities during both states of the transistor.

[file 02478](#)

Answer 8

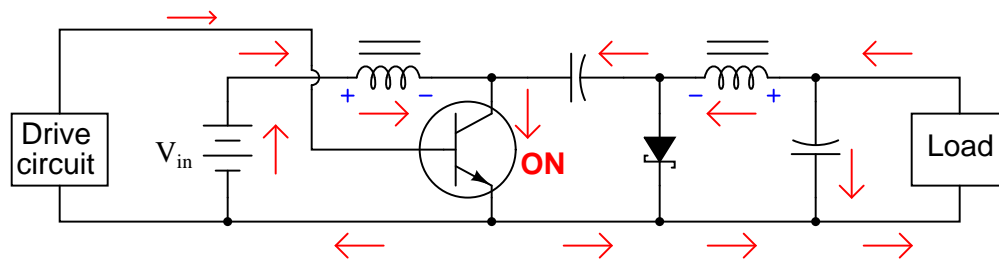

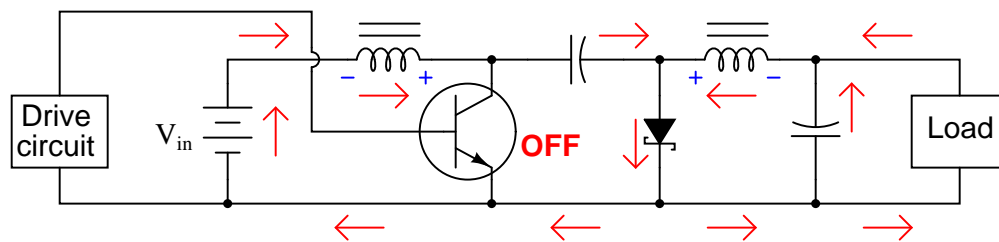Note: all currents shown using conventional flow notation




Follow-up question: how does the load voltage of this converter relate to the supply (battery) voltage? Does the load receive more or less voltage than that provided by the battery?

Notes 8

The "strange" name of this circuit comes from the last name of the engineer who invented it! For more information, consult the writings of Rudy Severns on the general topic of switch-mode power conversion circuits.

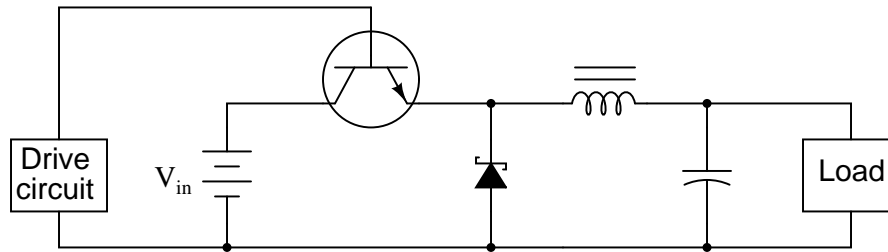Question 9

Predict how the operation of this buck converter circuit will be affected as a result of the following faults. Consider each fault independently (i.e. one at a time, no multiple faults):



- Drive circuit fails with a constant "low" (0 volts) output signal:
- Drive circuit fails with a constant "high" (+V) output signal:
- Diode fails shorted:
- Inductor fails open:
- Capacitor fails shorted:

For each of these conditions, explain *why* the resulting effects will occur.

[file 03732](#)

Answer 9


- Drive circuit fails with a constant "low" (0 volts) output signal: *Output voltage falls to zero after capacitor discharges.*
- Drive circuit fails with a constant "high" (+V) output signal: *Output voltage rises to become approximately equal to V_{in} .*
- Diode fails shorted: *Output voltage falls to zero, then transistor fails due to overheating.*
- Inductor fails open: *Output voltage falls to zero after capacitor discharges.*
- Capacitor fails shorted: *Output voltage falls to zero immediately.*

Notes 9

The purpose of this question is to approach the domain of circuit troubleshooting from a perspective of knowing what the fault is, rather than only knowing what the symptoms are. Although this is not necessarily a realistic perspective, it helps students build the foundational knowledge necessary to diagnose a faulted circuit from empirical data. Questions such as this should be followed (eventually) by other questions asking students to identify likely faults based on measurements.

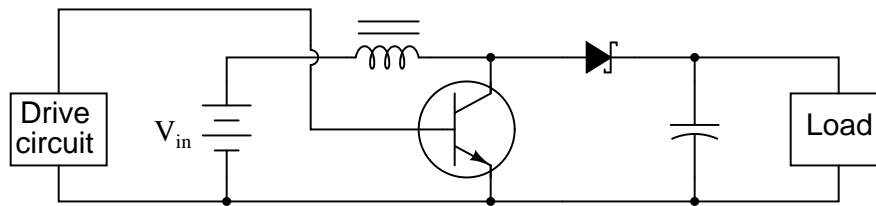Question 10

Predict how the operation of this boost converter circuit will be affected as a result of the following faults. Consider each fault independently (i.e. one at a time, no multiple faults):



- Drive circuit fails with a constant "low" (0 volts) output signal:
- Drive circuit fails with a constant "high" (+V) output signal:
- Diode fails shorted:
- Inductor fails open:
- Capacitor fails shorted:

For each of these conditions, explain *why* the resulting effects will occur.
[file 03733](#)

Answer 10

- Drive circuit fails with a constant "low" (0 volts) output signal: *Output voltage rises to become approximately equal to V_{in} .*
- Drive circuit fails with a constant "high" (+V) output signal: *Output voltage falls to zero after capacitor discharges.*
- Diode fails shorted: *Output voltage exhibits very large "ripple" as the voltage repeatedly falls to zero and spikes back up each drive cycle, transistor may fail due to overheating.*
- Inductor fails open: *Output voltage falls to zero after capacitor discharges.*
- Capacitor fails shorted: *Output voltage falls to zero immediately.*


Notes 10

The purpose of this question is to approach the domain of circuit troubleshooting from a perspective of knowing what the fault is, rather than only knowing what the symptoms are. Although this is not necessarily a realistic perspective, it helps students build the foundational knowledge necessary to diagnose a faulted circuit from empirical data. Questions such as this should be followed (eventually) by other questions asking students to identify likely faults based on measurements.

Question 11

So-called *linear* regulator circuits work by adjusting either a series resistance or a shunt resistance to maintain output voltage at some fractional value of input voltage:

"Linear" regulator circuit types

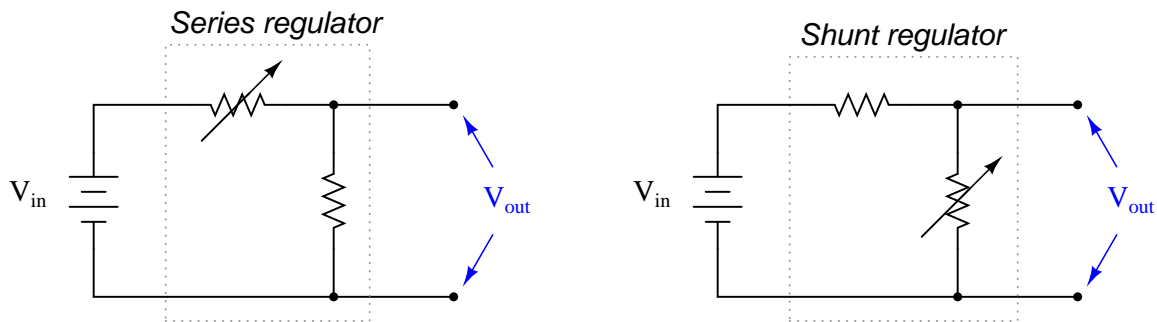

Typically, these variable resistances are provided by transistors rather than actual rheostats, which would have to be manually controlled.

Explain why a *switching* regulator circuit would perform the same task as a linear regulator circuit at a much greater efficiency. Also, identify which type(s) of switching regulator circuit would be best suited for the task of reducing an input voltage to a lesser output voltage.

[file 02162](#)

Answer 11

A *buck* regulator circuit functions in nearly the same manner as a transformer: stepping voltage down while stepping current up. Ideally, switching regulator circuits waste zero energy, unlike (resistive) linear regulator circuits.

Follow-up question: which type of linear regulator circuit does the traditional *zener diode voltage regulator* belong to, series or shunt?



Notes 11

In the process of analyzing switching regulator functionality, it is easy for students to overlook the purpose for why they exist at all. Discuss the importance of power conversion efficiency, especially for electronic applications that are battery powered.

An important point to emphasize in this question is that most of the switching "regulator" circuits first shown to students are not actually regulators at all, but merely *converters*. A switching converter circuit does not become a regulator circuit until a feedback control is added. Such controls are usually too complex to introduce at the very beginning, so they are typically omitted for simplicity's sake. However, students should realize the difference between a switching *regulator* circuit and a mere switching *converter* circuit, lest they believe the converter to be capable of more than it is.

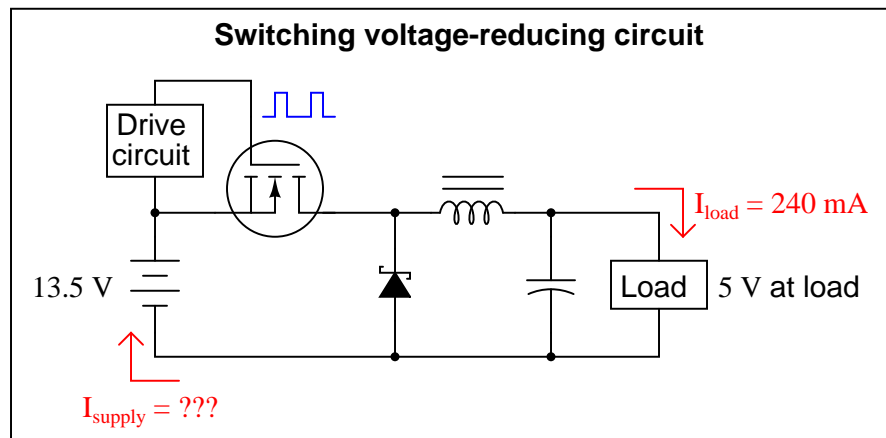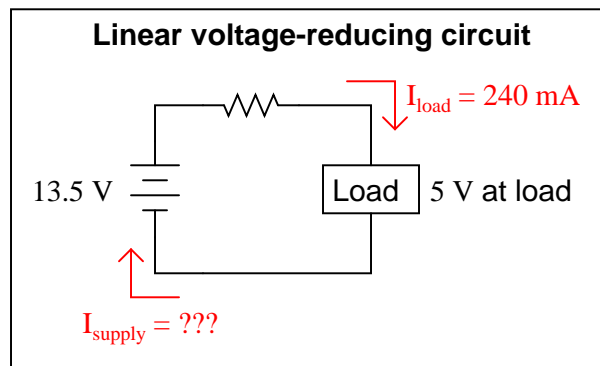Question 12

Shown here are two voltage-reducing circuits: both reducing a supply voltage of 13.5 volts down to 5 volts for a load.



Calculate the average supply current (I_{supply}) for both of these circuits. Assume that the switching circuit has negligible power losses in the transistor, inductor, capacitor, and diode. If the 13.5 volt source were an electrochemical battery, which battery would last longer powering the same load?

[file 02479](#)

Answer 12

The battery supplying the linear circuit must source 240 mA, while the battery supplying the switching circuit must only source an average current of 88.9 mA.

Follow-up question: calculate the power efficiency of the linear circuit, and comment on why it is so different from the switching circuit.

Explain to your students that switching power conversion circuits are very efficient: typically 85 to 95 percent! It should be rather obvious which battery will last longer, and why. This is precisely why switching regulator circuits (DC-DC converters with a feedback network to stabilize output voltage) are used in place of linear regulator circuits (zener diode based) in many battery-powered electronic applications.

In essence, switching converter circuits act like DC transformers, able to step voltage down (or up), with current inversely proportional. Of course, the Law of Energy Conservation holds for switching circuits just as it does for transformers, and students may find this Law the easiest way to perform supply/load current calculations knowing the supply and load voltages:


$$P_{out} \approx P_{in}$$

$$V_{in}I_{in} \approx V_{out}I_{out}$$

If time permits, you might want to show your students a datasheet for a power converter controller, showing them how integrated circuits exist to precisely control the switching of MOSFETs for power converter circuits just like this.

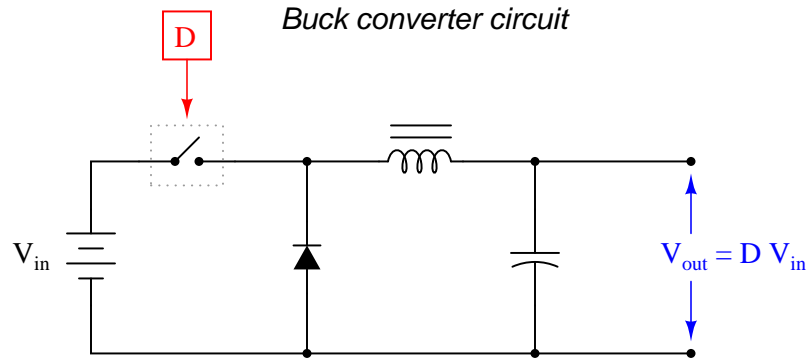Question 13

The output voltage of a *buck converter* circuit is a function of the input voltage and the duty cycle of the switching signal, represented by the variable D (ranging in value from 0% to 100%), where $D = \frac{t_{on}}{t_{on} + t_{off}}$:



Based on this mathematical relationship, calculate the output voltage of this converter circuit at these duty cycles, assuming an input voltage of 40 volts:

- $D = 0\%$; $V_{out} =$
- $D = 25\%$; $V_{out} =$
- $D = 50\%$; $V_{out} =$
- $D = 75\%$; $V_{out} =$
- $D = 100\%$; $V_{out} =$

file 02158

Answer 13

- $D = 0\%$; $V_{out} = 0$ volts
- $D = 25\%$; $V_{out} = 10$ volts
- $D = 50\%$; $V_{out} = 20$ volts
- $D = 75\%$; $V_{out} = 30$ volts
- $D = 100\%$; $V_{out} = 40$ volts


Notes 13

The calculations for this circuit should be very straightforward.

Note that the switching element in the schematic diagram is shown in generic form. It would never be a mechanical switch, but rather a transistor of some kind.

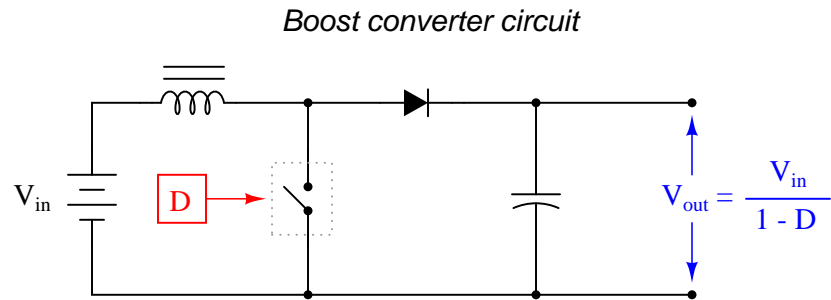Question 14

The output voltage of a *boost converter* circuit is a function of the input voltage and the duty cycle of the switching signal, represented by the variable D (ranging in value from 0% to 100%), where $D = \frac{t_{on}}{t_{on} + t_{off}}$:



Based on this mathematical relationship, calculate the output voltage of this converter circuit at these duty cycles, assuming an input voltage of 40 volts:

- $D = 0\%$; $V_{out} =$
- $D = 25\%$; $V_{out} =$
- $D = 50\%$; $V_{out} =$
- $D = 75\%$; $V_{out} =$
- $D = 100\%$; $V_{out} =$

file 02159

Answer 14

- $D = 0\%$; $V_{out} = 40$ volts
- $D = 25\%$; $V_{out} = 53.3$ volts
- $D = 50\%$; $V_{out} = 80$ volts
- $D = 75\%$; $V_{out} = 160$ volts
- $D = 100\%$; $V_{out} = 0$ volts


Notes 14

The calculations for this circuit should be straightforward, except for the last calculation with a duty cycle of $D = 100\%$. Here, students must take a close look at the circuit and not just follow the formula blindly.

Note that the switching element in the schematic diagram is shown in generic form. It would never be a mechanical switch, but rather a transistor of some kind.

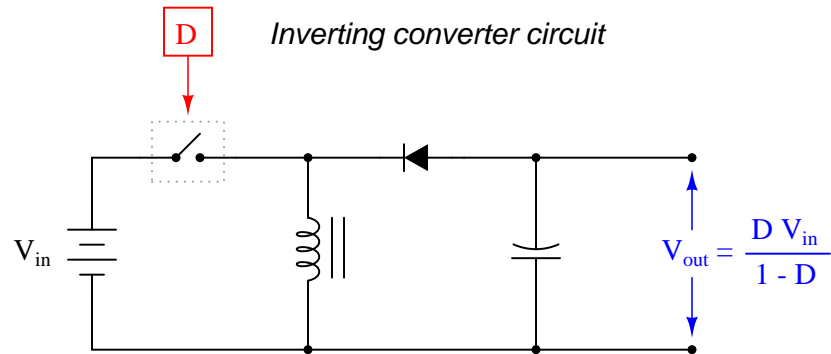Question 15

The output voltage of an *inverting converter* circuit is a function of the input voltage and the duty cycle of the switching signal, represented by the variable D (ranging in value from 0% to 100%), where $D = \frac{t_{on}}{t_{on} + t_{off}}$:



Based on this mathematical relationship, calculate the output voltage of this converter circuit at these duty cycles, assuming an input voltage of 40 volts:

- $D = 0\%$; $V_{out} =$
- $D = 25\%$; $V_{out} =$
- $D = 50\%$; $V_{out} =$
- $D = 75\%$; $V_{out} =$
- $D = 100\%$; $V_{out} =$

file 02160

Answer 15

- $D = 0\%$; $V_{out} = 0$ volts
- $D = 25\%$; $V_{out} = 13.3$ volts
- $D = 50\%$; $V_{out} = 40$ volts
- $D = 75\%$; $V_{out} = 120$ volts
- $D = 100\%$; $V_{out} = 0$ volts


Notes 15

The calculations for this circuit should be straightforward, except for the last calculation with a duty cycle of $D = 100\%$. Here, students must take a close look at the circuit and not just follow the formula blindly.

Note that the switching element in the schematic diagram is shown in generic form. It would never be a mechanical switch, but rather a transistor of some kind.

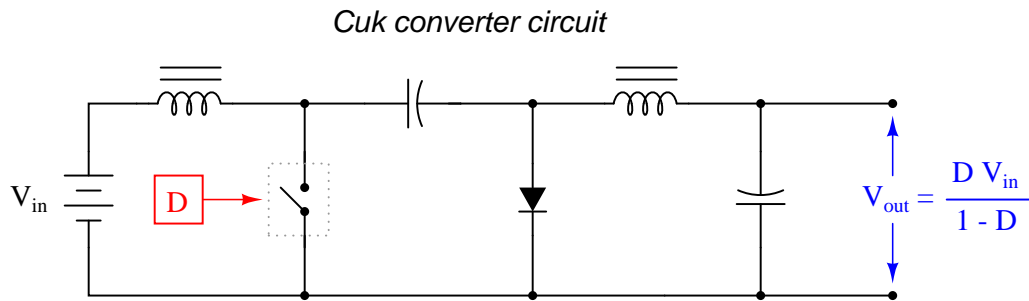Question 16

The output voltage of a *Cuk converter* circuit (named after the engineer who invented it) is a function of the input voltage and the duty cycle of the switching signal, represented by the variable D (ranging in value from 0% to 100%), where $D = \frac{t_{on}}{t_{on} + t_{off}}$:



Based on this mathematical relationship, calculate the output voltage of this converter circuit at these duty cycles, assuming an input voltage of 25 volts:

- $D = 0\%$; $V_{out} =$
- $D = 25\%$; $V_{out} =$
- $D = 50\%$; $V_{out} =$
- $D = 75\%$; $V_{out} =$
- $D = 100\%$; $V_{out} =$

[file 02477](#)

Answer 16

- $D = 0\%$; $V_{out} = 0$ volts
- $D = 25\%$; $V_{out} = 8.33$ volts
- $D = 50\%$; $V_{out} = 25$ volts
- $D = 75\%$; $V_{out} = 75$ volts
- $D = 100\%$; $V_{out} = 0$ volts

Notes 16

The calculations for this circuit should be straightforward, except for the last calculation with a duty cycle of $D = 100\%$. Here, students must take a close look at the circuit and not just follow the formula blindly.

Note that the switching element in the schematic diagram is shown in generic form. It would never be a mechanical switch, but rather a transistor of some kind.

Astute students will note that there is no difference between the standard *inverting* converter circuit and the *Cuk* design, as far as output voltage calculations are concerned. This, however, does not mean the two circuits are equivalent in all ways! One definite advantage of the Cuk converter over the standard inverting converter is that the Cuk's input current never goes to zero during the switch's "off" cycle. This makes the Cuk circuit a "quieter" load as seen from the power source. Both inverting and buck converter circuits create a lot of electrical noise on the supply side if their inputs are unfiltered!

Question 17

The following equations solve for the output voltage of various switching converter circuits (unloaded), given the switch duty cycle D and the input voltage:

$$V_{out} = D V_{in} \quad (\text{Buck converter circuit})$$

$$V_{out} = \frac{V_{in}}{1 - D} \quad (\text{Boost converter circuit})$$

$$V_{out} = \frac{D V_{in}}{1 - D} \quad (\text{Inverting or Cuk converter circuit})$$

Manipulate each of these equations to solve for duty cycle (D) in terms of the input voltage (V_{in}) and desired output voltage (V_{out}). Remember that duty cycle is always a quantity between 0 and 1, inclusive.

[file 02161](#)

Answer 17

$$D = \frac{V_{out}}{V_{in}} \quad (\text{Buck converter circuit})$$

$$D = 1 - \left(\frac{V_{in}}{V_{out}} \right) \quad (\text{Boost converter circuit})$$

$$D = \frac{V_{out}}{V_{in} + V_{out}} \quad (\text{Inverting or Cuk converter circuit})$$



Notes 17

Given the equations for these converter circuit types solving for output voltage in terms of input voltage and duty cycle D , this question is nothing more than an exercise in algebraic manipulation.

Note to your students that all of these equations assume a condition of zero load on the converter circuit. When loads are present, of course, the output voltage will not be the same as what is predicted by these neat, simple formulae. Although these DC-DC power converter circuits are commonly referred to as "regulators," it is somewhat misleading to do so because it falsely implies a capacity for self-correction of output voltage. Only when coupled to a feedback control network are any of these converter circuits capable of actually *regulating* output voltage to a set value.

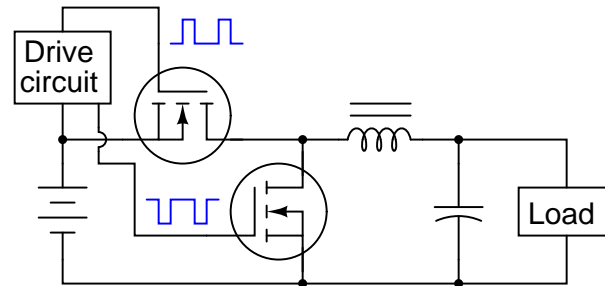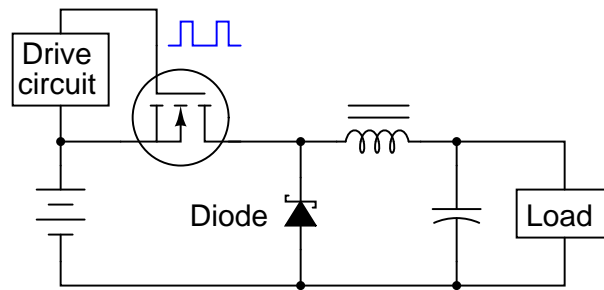Question 18

Many switching converter circuits use a switched MOSFET in place of a free-wheeling diode, like this:



The diode is a simple solution for providing the inductor a path for current when the main switching transistor is off. Why would anyone use another MOSFET in place of it, especially if this means the drive circuit has to become more complex (to drive two transistors at different times instead of just one transistor) to do the same task?

[file 02480](#)

Answer 18

A MOSFET in its enhanced mode will drop less voltage than a diode (even a Schottky diode) in this circuit, improving power efficiency.

Notes 18

It might not be obvious to some students why less voltage drop (across the MOSFET versus across the diode) has an impact on conversion efficiency. Remind them that power equals voltage times current, and that for any given current, a reduced voltage drop means reduced power dissipation. For the free-wheeling current path, less power dissipation means less power wasted, and less power that needs to be supplied by the source (for the same load power), hence greater efficiency.

Question 19

A "boost" switching converter operating at 90% efficiency delivers 50 volts to a DC load. Calculate the load current if the input voltage is 17 volts and the input current is 9.3 amps.

[file 02357](#)

Answer 19

$$I_{load} = 2.85 \text{ amps}$$

Notes 19

Calculations involving energy efficiency seem very confusing to some students. One principle that I often remind my students of is the Law of Energy Conservation, which prohibits any circuit from outputting more energy (or power) than it takes in. All too often, students mis-calculate in problems such as these, ending up with output powers greater than input powers!

Discuss problem-solving techniques, soliciting input from your students. Ideally, have individuals or groups present their techniques to the class as a whole, so you may observe their thinking processes and so that other students may learn how to become better problem-solvers.

Question 20

A "buck" switching converter operating at 85% efficiency delivers 10 amps of current at 5 volts to a DC load. Calculate the input current if the input voltage is 23 volts.

[file 02356](#)

Answer 20

$$I_{input} = 2.56 \text{ amps}$$

Notes 20

Calculations involving energy efficiency seem very confusing to some students. One principle that I often remind my students of is the Law of Energy Conservation, which prohibits any circuit from outputting more energy (or power) than it takes in. All too often, students mis-calculate in problems such as these, ending up with output powers greater than input powers!

Discuss problem-solving techniques, soliciting input from your students. Ideally, have individuals or groups present their techniques to the class as a whole, so you may observe their thinking processes and so that other students may learn how to become better problem-solvers.

Question 21

A "boost" switching converter operating at 80% efficiency delivers 178 volts at 1 amp to a DC load. Calculate the input voltage if the input current is 11 amps.

[file 02358](#)

Answer 21

$$V_{input} = 20.2 \text{ volts}$$


Notes 21

Calculations involving energy efficiency seem very confusing to some students. One principle that I often remind my students of is the Law of Energy Conservation, which prohibits any circuit from outputting more energy (or power) than it takes in. All too often, students mis-calculate in problems such as these, ending up with output powers greater than input powers!

Discuss problem-solving techniques, soliciting input from your students. Ideally, have individuals or groups present their techniques to the class as a whole, so you may observe their thinking processes and so that other students may learn how to become better problem-solvers.

Question 22

The output voltage of a buck converter is a direct function of the switching transistor's duty cycle. Specifically, $V_{out} = V_{in} \left(\frac{t_{on}}{t_{total}} \right)$. Explain how the following PWM control circuit regulates the output voltage of the buck converter:

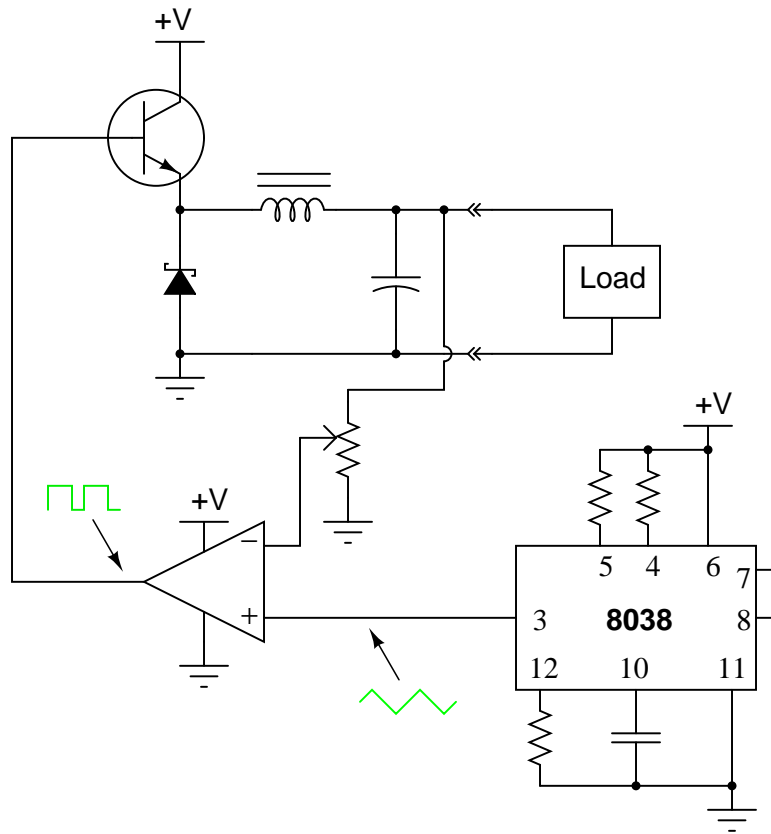

[file 01106](#)

Answer 22

If the load (output) voltage sags, the PWM circuit generates an output signal with a greater duty cycle, which then drives the power transistor to provide more voltage to the load.

Follow-up question: what is the purpose of the potentiometer in this circuit?

Notes 22

Here, students see a PWM control circuit coupled with a buck converter to provide *voltage-regulated* power conversion. Ask them what form of feedback (positive or negative?) is used in this circuit to regulate the output voltage at a steady value.

Let your students know that the PWM and feedback functions for switching regulator circuits are often provided in a single, application-specific integrated circuit rather than by a collection of discrete components and IC's as shown in the question.

Question 23

The energy efficiency (η) of switching converter circuits typically remains fairly constant over a wide range of voltage conversion ratios. Describe how a switching *regulator* circuit (controlling load voltage to a pre-set value) "appears" to a power source of changing voltage if the regulator's load is constant. In other words, as the input voltage changes, what does the input current do?

[file 02359](#)

Answer 23

The input current of a switching regulator is *inversely* proportional to the input voltage when powering a constant load, appearing as a *negative impedance* to the power source.

Notes 23


"Negative impedance" and "negative resistance" are phrases that may not be addressed very often in a basic electronics curriculum, but they have important consequences. If students experience difficulty understanding what the meaning of "negative" impedance is, remind them of this mathematical definition for impedance:

$$Z = \frac{dV}{dI}$$


One of the unintended (and counter-intuitive) consequences of a circuit element with negative impedance can be *oscillation*, especially when the input power circuit happens to contain substantial inductance.

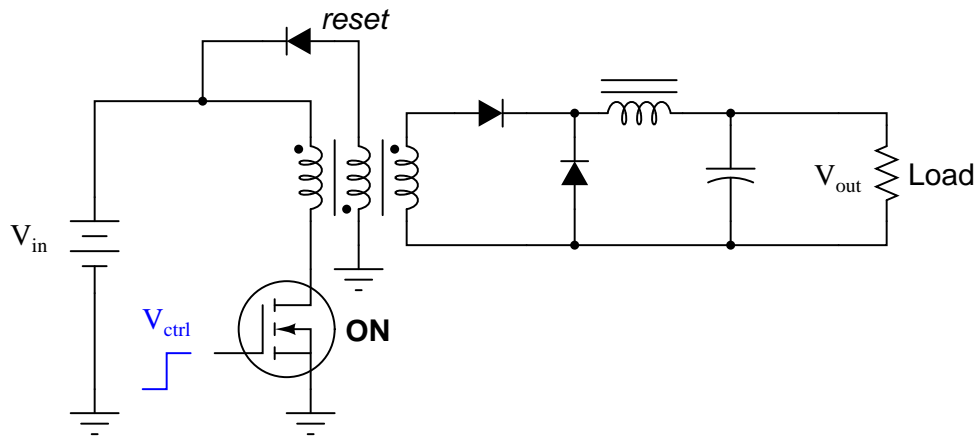Question 24

The following DC-DC converter circuit is called a *forward converter*. It is called this because the energy transfer from input to output occurs while the transistor is conducting, not while it is off. Verify this feature of the circuit by tracing current through all portions of it while the transistor is on:




Now, trace current through the circuit while the transistor is off, and explain the purpose of the *reset* winding in the transformer:

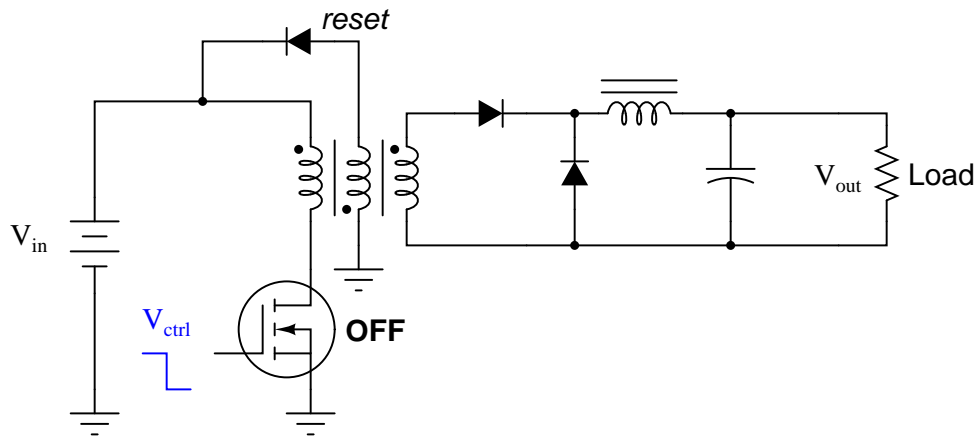

[file 03724](#)

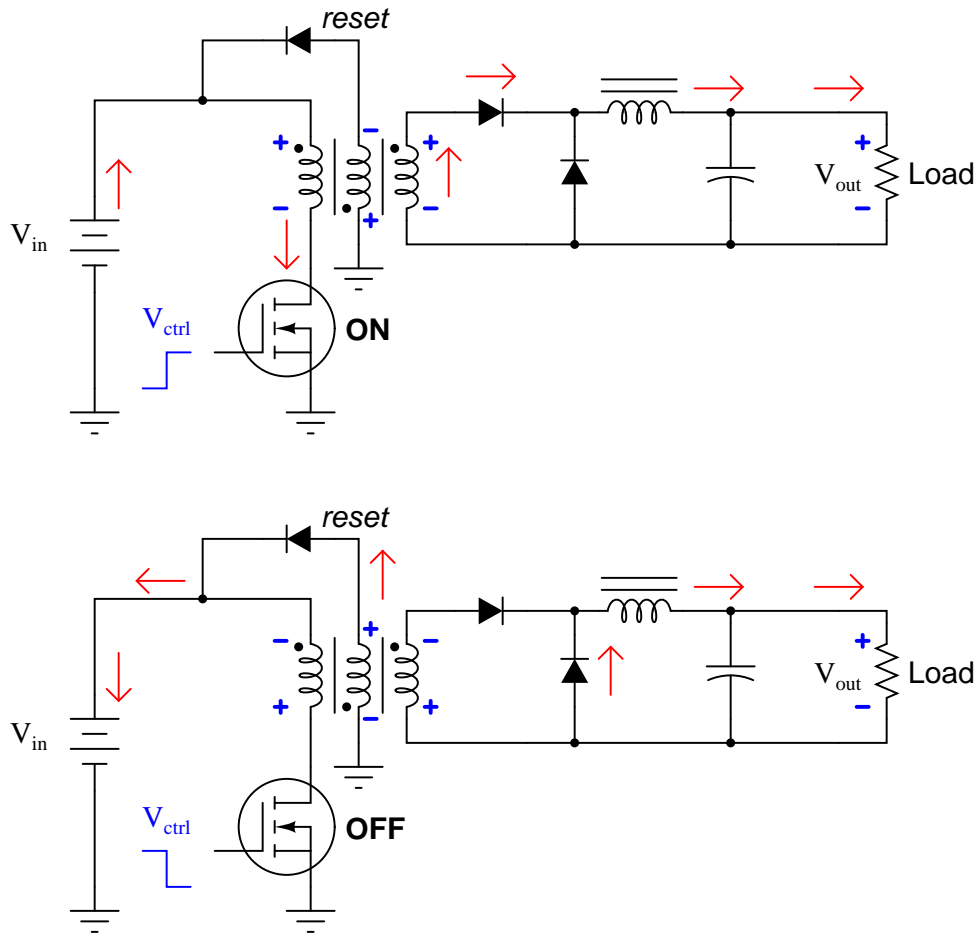In the following schematics, conventional flow notation has been used to denote direction of currents:



The purpose of the reset winding is to rid the transformer core of stored energy during the off cycle. If this were not done, the transformer core's magnetic flux levels would reach saturation after just a few on/off cycles of the transistor.

This question is a great review of the "dot convention" used in transformer schematic symbols.

Question 25

While simple "brute-force" AC-DC power supply circuits (transformer, rectifier, filter, regulator) are still used in a variety of electronic equipment, another form of power supply is more prevalent in systems where small size and efficiency are design requirements. This type of power supply is called a *switching power supply*.

Explain what a "switching power supply" is, and provide a schematic diagram of one for presentation and discussion. (Hint: most electronic computers use "switching" power supplies instead of "brute force" power supplies, so schematic diagrams should not be difficult to find.)

[file 01107](#)

Answer 25

I'll let you do all the research for this question!

Notes 25

While many "switching" power supply circuits will be too complex for beginning electronics students to fully understand, it will still be a useful exercise to analyze such a schematic and identify the major components (and functions).

Ask your students why "switching" power supplies are smaller and more efficient than "brute force" designs. Ask your students to note the type of transformer used in switching power supplies, and contrast its construction to that of line-frequency power transformers.

Question 26

Suppose a friend of yours recently purchased an off-road vehicle. This friend also purchased a military-surplus spotlight, which he thinks would be a great accessory for off-road illumination at night. The only problem is, the spotlight is rated for 24 volts, while the electrical system in his vehicle is 12 volt.

Your friend asks you to engineer a solution for powering the 24-volt spotlight with the 12 volts available on his vehicle. Of course, you are not allowed to modify the vehicle's electrical system (change it to 24 volt generator, battery, starter motor, etc.), because it is new and still under warranty. What do you recommend to your friend?

Draw a component-level schematic diagram of your solution to this problem.

file 01099

Answer 26

While there are several different methods which could be used here to transform 12 volts into 24 volts, I will not reveal any of them here, lest I spoil the fun for you!


Notes 26

Students may be inclined to give easy answers to this problem ("use a DC-DC converter!"), but the purpose of it is for students to explore solutions at the *component level*. Even if they do not yet understand how the circuitry works, they should be able to find complete solutions in their research, or at least enough schematics for sections of the conversion process for them to engineer a complete solution.

Remind your students that this is a powerful spotlight they're going to have to power! Their conversion system may have to handle hundreds of watts.

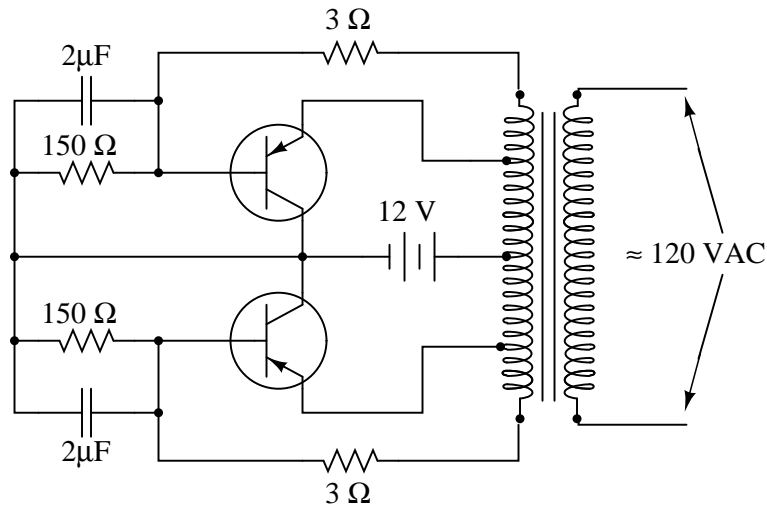Question 27

Describe the purpose and function of this circuit:



The 120 volt AC output provided by this circuit is definitely *not* sinusoidal, and the circuit's frequency varies with load. Can you think of any way(s) to improve these aspects of the circuit (you need not show details of your design modifications)?

[file 01101](#)

Answer 27

This is an *inverter* circuit.


Be prepared to explain what each of the transistors does, and how the transformer is able to function with DC power on its primary winding.

Notes 27


This particular schematic was derived from a Triad brand transformer application, part number TY-75A. Recommended transistors were Delco 2N278, Bendix 2N678, Clevite 2N1146, and Delco 2N173. Slight variations in resistor and capacitor sizes may result in better performance. The 3 Ω resistors should have power ratings of at least 5 watts each, and the 150 Ω resistors should be rated for at least 20 watts each.

$\int f(x) dx$ Calculus alert!

Electronic power conversion circuits known as *inverters* convert DC into AC by using transistor switching elements to periodically reverse the polarity of the DC voltage. Usually, inverters also increase the voltage level of the input power by applying the switched-DC voltage to the primary winding of a step-up transformer. You may think of an inverter's switching electronics as akin to double-pole, double-throw switch being flipped back and forth many times per second:

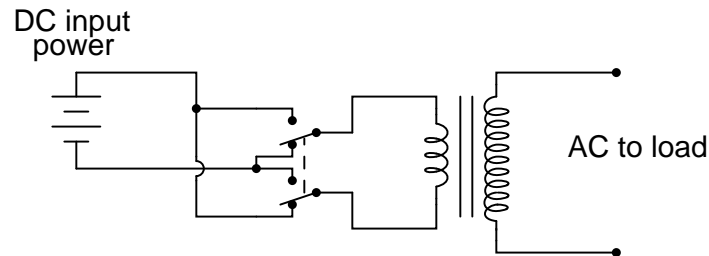


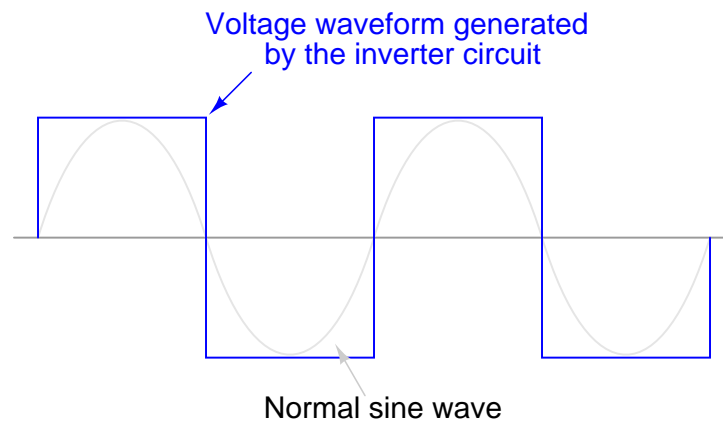The first commercially available inverters produced simple square-wave output:




However, this caused problems for most power transformers designed to operate on sine-wave AC power. When powered by the square-wave output of such an inverter, most transformers would *saturate* due to excessive magnetic flux accumulating in the core at certain points of the waveform's cycle. To describe this in the simplest terms, a square wave possesses a greater *volt-second product* than a sine wave with the same peak amplitude and fundamental frequency.

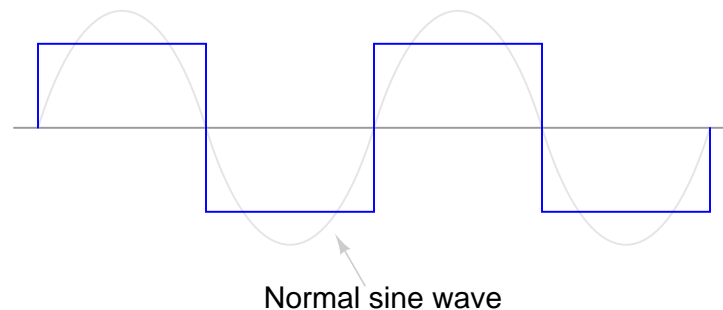
This problem could be avoided by decreasing the peak voltage of the square wave, but then some types of powered equipment would experience difficulty due to insufficient (maximum) voltage:



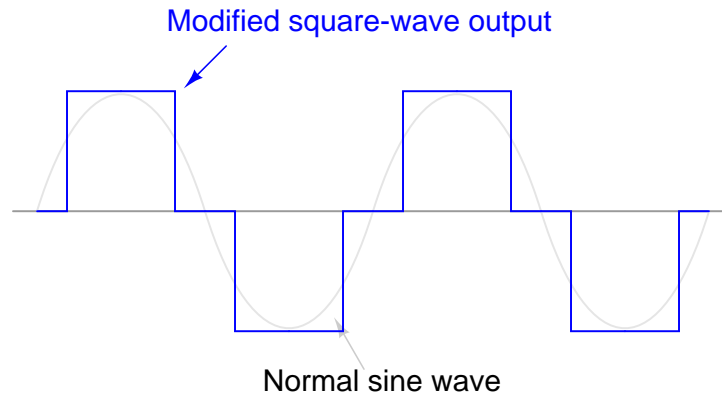A workable solution to this dilemma turned out to be a modified duty cycle for the square wave:



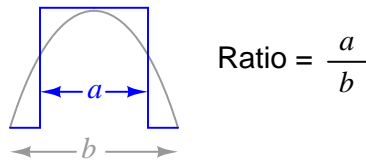Calculate the fraction of the half-cycle for which this modified square wave is "on," in order to have the same volt-second product as a sine wave for one-half cycle (from 0 to π radians):



Hint: it is a matter of calculating the respective *areas* underneath each waveform in the half-cycle domain.

[file 01489](#)

Answer 28

$$\text{Fraction} = \frac{2}{\pi} \approx 0.637$$


Challenge question: prove that the duty cycle fraction necessary for the square wave to have the same *RMS value* as the sine wave is exactly $\frac{1}{2}$. Hint: the volts-squared-second product of the two waveforms must be equal for their RMS values to be equal!

Notes 28

This problem is a great example of how integration is used in a very practical sense. Even if your students are unfamiliar with calculus, they should at least be able to grasp the concept of equal volt-second products for the two waveforms, and be able to relate that to the amount of magnetic flux accumulating in the transformer core throughout a cycle.

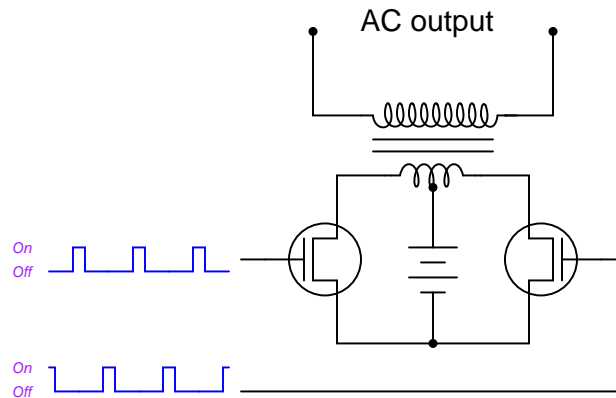
Question 29

A common topology for DC-AC power converter circuits uses a pair of transistors to switch DC current through the center-tapped winding of a step-up transformer, like this:



Note: protective devices to guard against transient overvoltages have been omitted from this diagram for simplicity!

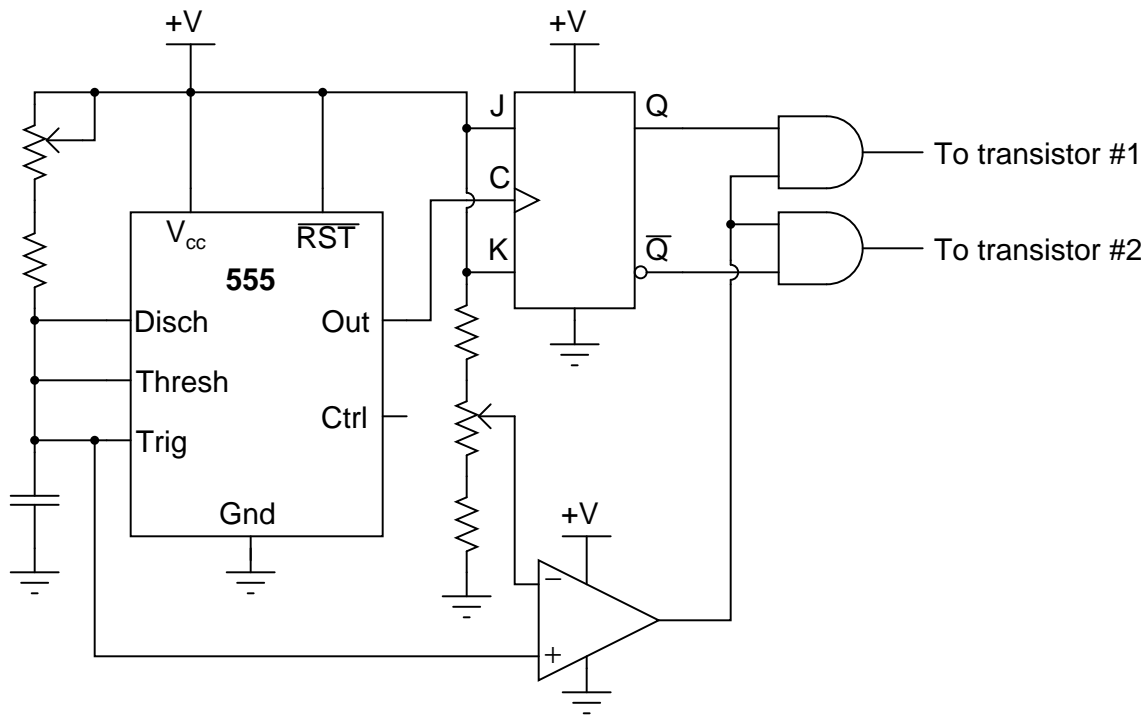
In order for this form of circuit to function properly, the transistor "firing" signals must be precisely synchronized to ensure the two are never turned on simultaneously. The following schematic diagram shows a circuit to generate the necessary signals:




Explain how this circuit works, and identify the locations of the frequency control and pulse duty-cycle control potentiometers.

file 03452

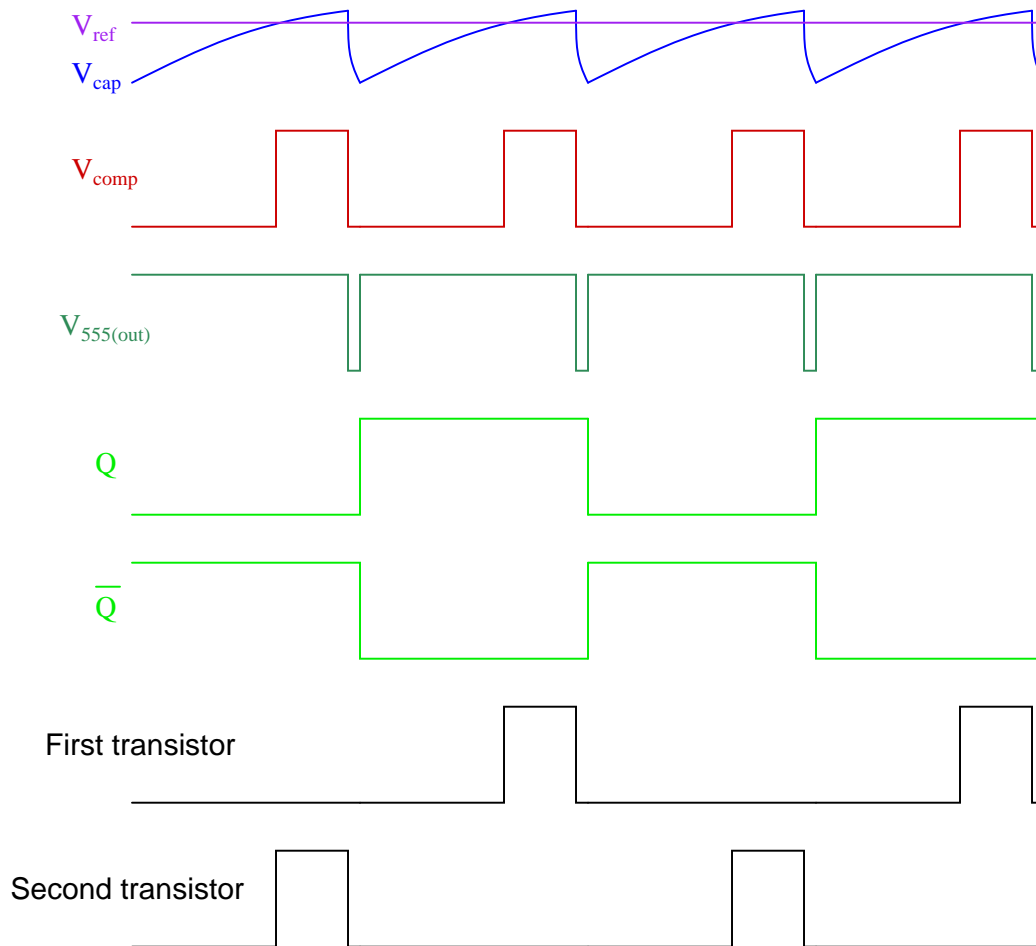A timing diagram is worth a thousand words:



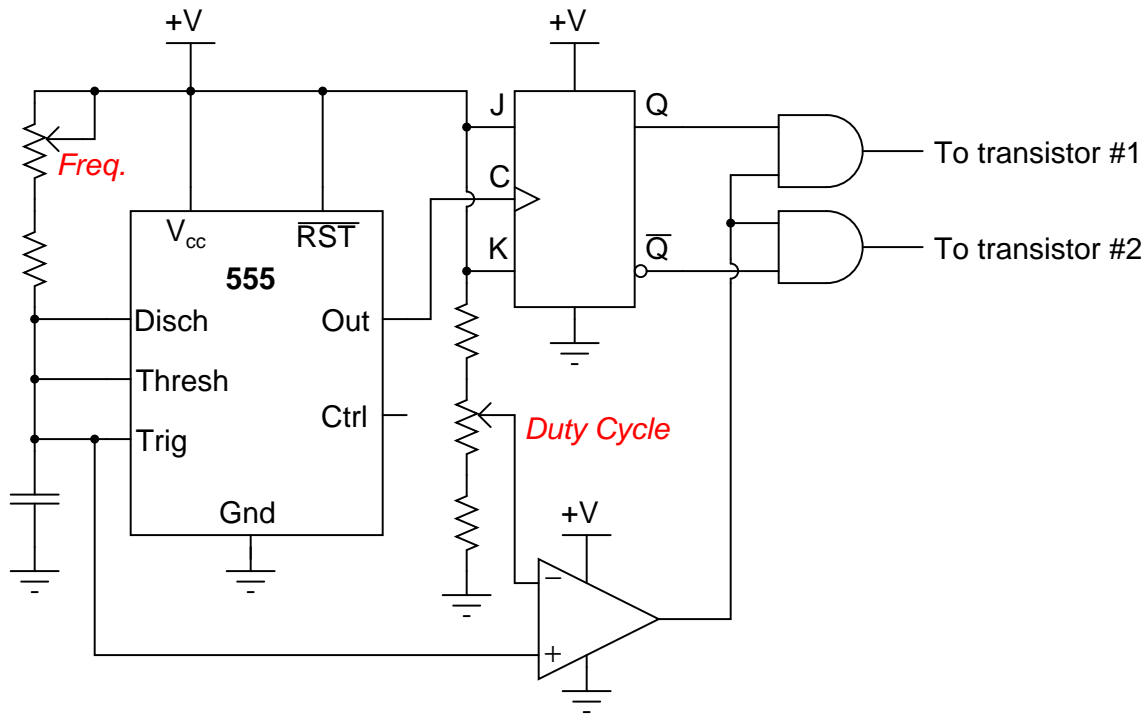- V_{ref} = DC reference voltage set by duty cycle potentiometer
- V_{cap} = Voltage measured at top terminal of the 555's capacitor
- V_{comp} = Comparator output voltage
- $V_{555(out)}$ = 555 timer output voltage
- Q = Noninverted output of J-K flip-flop
- \bar{Q} = Inverted output of J-K flip-flop



Follow-up question: which direction would you have to move the frequency potentiometer to increase the output frequency of this circuit? Which direction would you have to move the duty cycle potentiometer to increase that as well?

Challenge question: suppose you were prototyping this circuit without the benefit of an oscilloscope. How could you test the circuit to ensure the final output pulses to the transistors are never simultaneously in the "high" logic state? Assume you had a parts assortment complete with light-emitting diodes and other passive components.

Notes 29

This question is an exercise in schematic diagram and timing diagram interpretation. By the way, I have built and tested this circuit and I can say it works very well.

Don't just sit there! Build something!!

Learning to mathematically analyze circuits requires much study and practice. Typically, students practice by working through lots of sample problems and checking their answers against those provided by the textbook or the instructor. While this is good, there is a much better way.

You will learn much more by actually *building and analyzing real circuits*, letting your test equipment provide the "answers" instead of a book or another person. For successful circuit-building exercises, follow these steps:

1. Carefully measure and record all component values prior to circuit construction, choosing resistor values high enough to make damage to any active components unlikely.
2. Draw the schematic diagram for the circuit to be analyzed.
3. Carefully build this circuit on a breadboard or other convenient medium.
4. Check the accuracy of the circuit's construction, following each wire to each connection point, and verifying these elements one-by-one on the diagram.
5. Mathematically analyze the circuit, solving for all voltage and current values.
6. Carefully measure all voltages and currents, to verify the accuracy of your analysis.
7. If there are any substantial errors (greater than a few percent), carefully check your circuit's construction against the diagram, then carefully re-calculate the values and re-measure.

When students are first learning about semiconductor devices, and are most likely to damage them by making improper connections in their circuits, I recommend they experiment with large, high-wattage components (1N4001 rectifying diodes, TO-220 or TO-3 case power transistors, etc.), and using dry-cell battery power sources rather than a benchtop power supply. This decreases the likelihood of component damage.

As usual, avoid very high and very low resistor values, to avoid measurement errors caused by meter "loading" (on the high end) and to avoid transistor burnout (on the low end). I recommend resistors between 1 k Ω and 100 k Ω .

One way you can save time and reduce the possibility of error is to begin with a very simple circuit and incrementally add components to increase its complexity after each analysis, rather than building a whole new circuit for each practice problem. Another time-saving technique is to re-use the same components in a variety of different circuit configurations. This way, you won't have to measure any component's value more than once.

[file 00505](#)

Answer 30

Let the electrons themselves give you the answers to your own "practice problems"!

It has been my experience that students require much practice with circuit analysis to become proficient. To this end, instructors usually provide their students with lots of practice problems to work through, and provide answers for students to check their work against. While this approach makes students proficient in circuit theory, it fails to fully educate them.

Students don't just need mathematical practice. They also need real, hands-on practice building circuits and using test equipment. So, I suggest the following alternative approach: students should *build* their own "practice problems" with real components, and try to mathematically predict the various voltage and current values. This way, the mathematical theory "comes alive," and students gain practical proficiency they wouldn't gain merely by solving equations.

Another reason for following this method of practice is to teach students *scientific method*: the process of testing a hypothesis (in this case, mathematical predictions) by performing a real experiment. Students will also develop real troubleshooting skills as they occasionally make circuit construction errors.

Spend a few moments of time with your class to review some of the "rules" for building circuits before they begin. Discuss these issues with your students in the same Socratic manner you would normally discuss the worksheet questions, rather than simply telling them what they should and should not do. I never cease to be amazed at how poorly students grasp instructions when presented in a typical lecture (instructor monologue) format!

A note to those instructors who may complain about the "wasted" time required to have students build real circuits instead of just mathematically analyzing theoretical circuits:

What is the purpose of students taking your course?

If your students will be working with real circuits, then they should learn on real circuits whenever possible. If your goal is to educate theoretical physicists, then stick with abstract analysis, by all means! But most of us plan for our students to do something in the real world with the education we give them. The "wasted" time spent building real circuits will pay huge dividends when it comes time for them to apply their knowledge to practical problems.

Furthermore, having students build their own practice problems teaches them how to perform *primary research*, thus empowering them to continue their electrical/electronics education autonomously.

In most sciences, realistic experiments are much more difficult and expensive to set up than electrical circuits. Nuclear physics, biology, geology, and chemistry professors would just love to be able to have their students apply advanced mathematics to real experiments posing no safety hazard and costing less than a textbook. They can't, but you can. Exploit the convenience inherent to your science, and *get those students of yours practicing their math on lots of real circuits!*