

**White LED Step-Up Regulator**




The EL7513 is a constant current boost regulator specially designed for white LEDs. It can drive up to 5 LEDs in series or 12 LEDs in parallel/series configuration. Up to 91% of efficiency can be achieved.

The EL7513 is available in a thin SOT-23 package with maximum height of 1mm vs 1.45mm for a regular SOT-23 package.

The brightness of the LEDs is adjusted through a voltage level on the CNTL pin. When the level falls below 0.1V, the chip goes into shut-down mode and consumes less than 1µA of current.

The complete demo board schematic diagram is shown in Figure 1. Only D<sub>2</sub>-D<sub>5</sub> is stuffed.

Only D<sub>2</sub>-D<sub>5</sub> is stuffed.

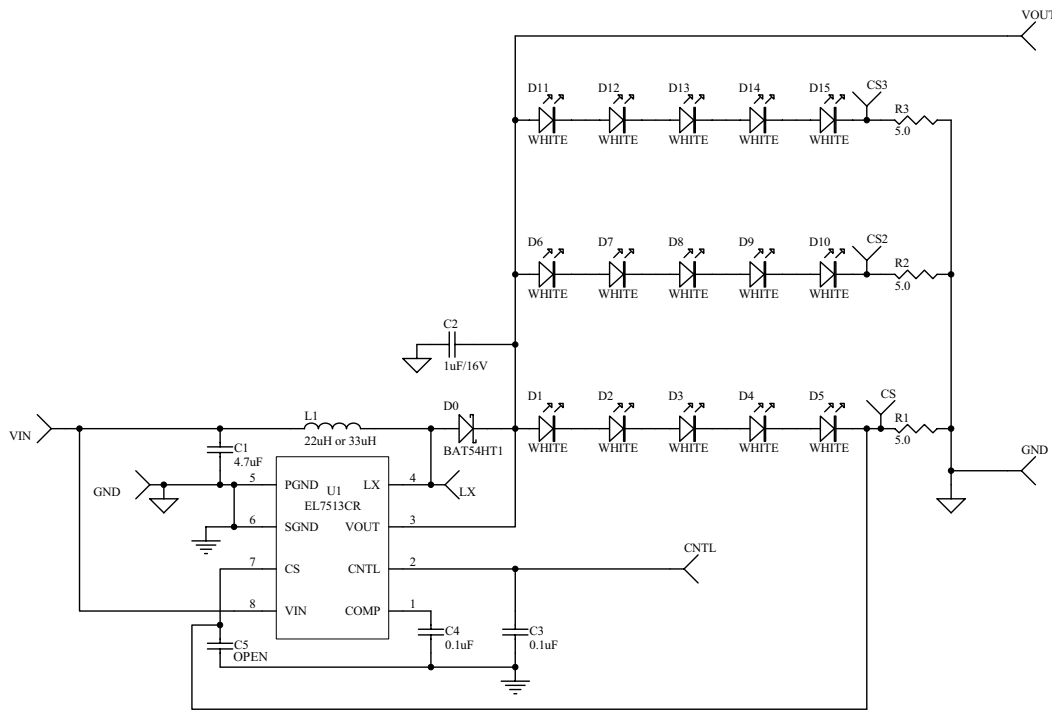

**FIGURE 1. DEMO BOARD SCHEMATIC**

**Demo Board Bill of Materials**

REFERENCE DESIGNATOR	VALUE	PACKAGE	MAX HEIGHT (mm)	MANUFACTURER	MANUFACTURER'S PN	MANUFACTURER'S PHONE NUMBER
C1	4.7µF/6.3V	0805	1.25	TDK	C2012X5R0J475K	847-803-6100
C2	1µF/16V	0805	1.25	TDK	C2012X5R1C105K	847-803-6100
C3	0.1µF	0603		Any		
C4	OPEN	0603		Any		
C5	0.1µF	0603		Any		
D0	BAT54HT1	SOD323	1	Any		
R1, R2, R3	4.99Ω	0603				
L1	33µH		1	Coilcraft	LPO1704-333M	847-639-6400
U1	EL7513	SOT23-8	1	Intersil	EL7513	888-ELANTEC

## Input Voltage

This demo board is intended for  $V_{IN} = 2.7$  to  $5.5V$ . However, with higher voltage rating input and output capacitors ( $C_1$  and  $C_2$ ), it can be used for higher input voltage up to  $13.5V$ .

## Brightness Control

The relationship between the LED current and CNTL voltage level is as follows:

$$I_{LED} = \frac{V_{CNTL}}{13.33 \times R_1}$$

When  $R_1$  is  $5\Omega$ ,  $1V$  of  $V_{CNTL}$  conveniently sets  $I_{LED}$  to  $15mA$ . The range of  $V_{CNTL}$  is  $250mV$  to  $5.5V$ .

## Component Selection

The input and output capacitors are not very important for the converter to operate normally. The input capacitance is normally  $2.22\mu F$  -  $4.7\mu F$ , output capacitance  $0.22\mu F$  -  $1\mu F$ , depending on number of LEDs with 3 LEDs,  $0.22\mu F$  is sufficient. Higher capacitances are allowed to reduce the voltage/ current ripple, but at added cost. Use X5R or X7R ceramic type (for its good temperature characteristics) capacitors with correct voltage rating and maximum allowed height.

When choosing an inductor, make sure the inductor can handle the average and peak currents giving by following formulas:

$$I_{LAVG} = \frac{I_O \times V_O}{0.8 \times V_{IN}}$$

$$I_{LPK} = I_{LAVG} + \frac{1}{2} \times \Delta I_L$$

$$\Delta I_L = \frac{V_{IN} \times (V_O - V_{IN})}{L \times V_O}$$

Where  $\Delta I_L$  is the peak-to-peak inductor current ripple,  $L$  inductance in  $\mu H$ .

A wide range of inductance ( $6.8\mu H$  -  $68\mu H$ ) can be used for the converter to function correctly. However, try different values of inductor in the same series to see which generates best efficiency.

The diode should be Schottky type with minimum reverse voltage of  $20V$ . The diode's peak current is the same as inductor's peak current, the average current is  $I_O$ , and RMS current is:

$$I_{DRMS} = \sqrt{I_{LAVG} \times I_O}$$

Ensure the diode's ratings exceed these current requirements.

The compensation capacitor  $C_4$  can be any value from  $4700pF$  to  $1\mu F$ .  $C_3$  and  $C_5$  are for noise filtering; they may not be needed if there is no noise interference.

## White LED Connections

One leg of LEDs connected in series will ensure all the uniformity of the brightness.  $18V$  maximum voltage enables 4-5 LEDs can be placed in series. When placing 5 LEDs in series, make sure the worst total forward voltage does not exceed  $18V$ .

## PCB Layout Considerations

The layout is very important for the converter to function properly. Power Ground ( $\downarrow$ ) and Signal Ground ( $\frac{\perp}{\perp}$ ) should be separated to ensure the high pulse current in the power ground does not interference with the sensitive signals connected to Signal Ground. Both grounds should only be connected at one point right at the chip. The heavy current paths ( $V_{IN}$ -L-LX pin-PGND, and  $V_{IN}$ -L-D-Co-PGND) should be as short as possible.

The trace connected to pin 7 (CS) is most important. The current sense resistor  $R_1$  should be very close to the pin and when the trace is long, use a small filter cap ( $C_5$ ) close to pin 7.

The heat of the IC is mainly dissipated through the PGND pin. Maximizing the copper area around the plane is preferable. In addition, a solid ground plane is always helpful for the EMI performance.

**Demo Board Layout**

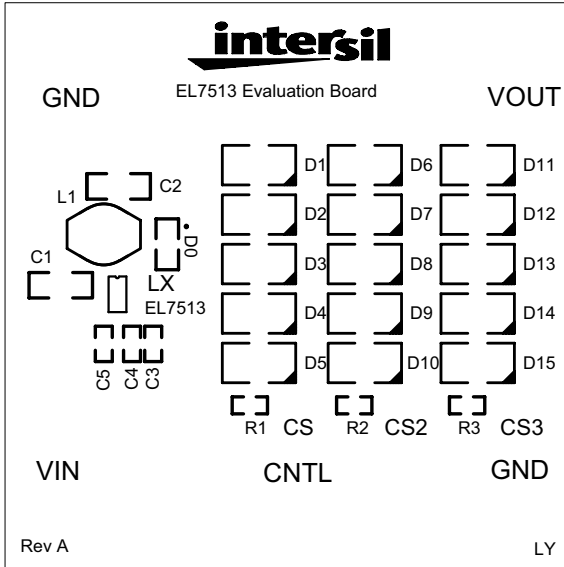


FIGURE 2. SILKSCREEN

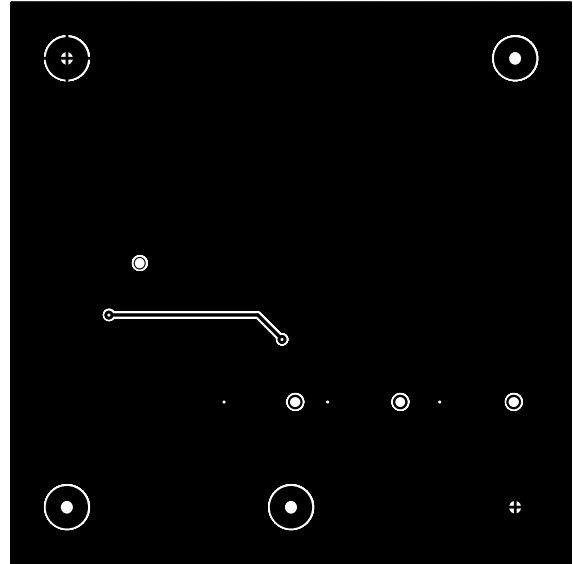


FIGURE 4. BOTTOM LAYER

**Demo Board Layout (continued)**

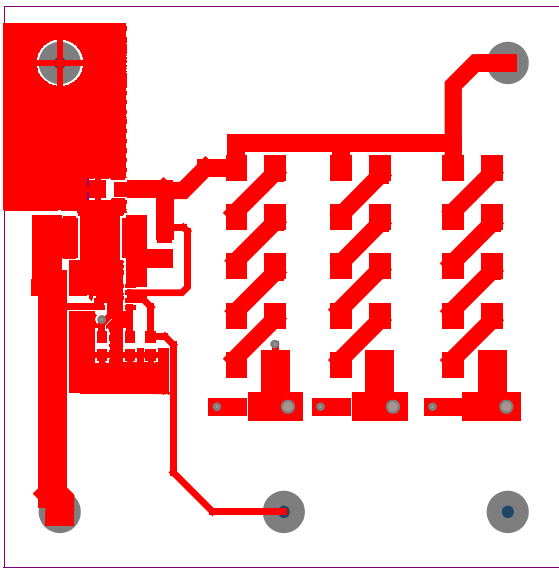


FIGURE 3. TOP LAYER

All Intersil U.S. products are manufactured, assembled and tested utilizing ISO9000 quality systems. Intersil Corporation's quality certifications can be viewed at [www.intersil.com/design/quality](http://www.intersil.com/design/quality)

*Intersil products are sold by description only. Intersil Corporation reserves the right to make changes in circuit design, software and/or specifications at any time without notice. Accordingly, the reader is cautioned to verify that data sheets are current before placing orders. Information furnished by Intersil is believed to be accurate and reliable. However, no responsibility is assumed by Intersil or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Intersil or its subsidiaries.*

For information regarding Intersil Corporation and its products, see [www.intersil.com](http://www.intersil.com)