

SOME USEFUL ELECTRIC CIRCUITS

1 The twin-T Bridge

The twin-T bridge shown in *Fig. 1* is frequently used as a feedback element in selective amplifiers, oscillators and for many other purposes. It consists of two T-circuits connected in parallel. The analysis of this circuit is best carried out by transforming both T into equivalent Π -connection and connecting them parallel as shown in *Fig. 2*, where

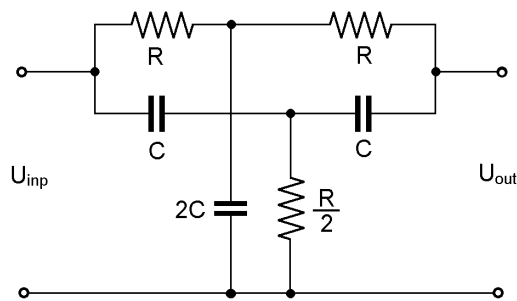


Fig. 1

$$Z_A = 2(R + j\omega CR), \quad (1)$$

$$Z'_A = 2\left(\frac{1}{j\omega C} - \frac{1}{\omega^2 C^2 R}\right), \quad (2)$$

$$Z_B = Z'_B = Z_C = Z'_C = R + \frac{1}{j\omega C}, \quad (3)$$

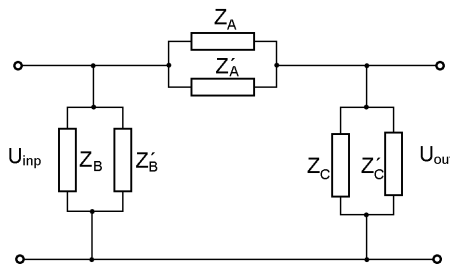


Fig. 2

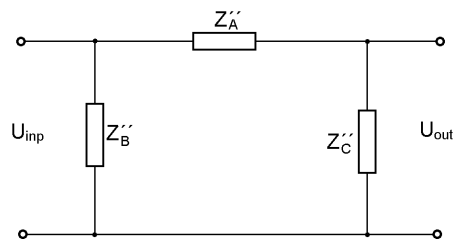


Fig. 3

(such transfiguration will be analysed in the article "Delta-star transformation").

Adding the impedances in *Fig. 2* in parallel we get a new circuit shown in *Fig. 3*, where

$$\mathbf{Z}_A'' = 2R \frac{1 + j\omega CR}{1 - \omega^2 C^2 R^2}, \quad (4)$$

$$\mathbf{Z}_B'' = \mathbf{Z}_C'' = \frac{1}{2} \left(R + \frac{1}{j\omega C} \right), \quad (5)$$

The complex transmission coefficient is

$$\mathbf{K}(\omega) = \frac{U_{out}(\omega)}{U_{inp}(\omega)} = \frac{\mathbf{Z}_C''}{\mathbf{Z}_A'' + \mathbf{Z}_C''} = \frac{1 - \omega^2 C^2 R^2}{1 - \omega^2 C^2 R^2 + j4\omega CR}. \quad (6)$$

The absolute value of the transmission coefficient is given by

$$\begin{aligned} K(\omega) &= \frac{U_{out}(\omega)}{U_{inp}(\omega)} = \left| \frac{\mathbf{Z}_C''}{\mathbf{Z}_A'' + \mathbf{Z}_C''} \right| = \frac{1 - \omega^2 C^2 R^2}{\sqrt{(1 - \omega^2 C^2 R^2)^2 + (4\omega CR)^2}} = \\ &= \frac{1 - \left(\frac{\omega}{\omega_0} \right)^2}{\sqrt{\left[1 - \left(\frac{\omega}{\omega_0} \right)^2 \right]^2 + \left(4 \frac{\omega}{\omega_0} \right)^2}}. \end{aligned} \quad (7)$$

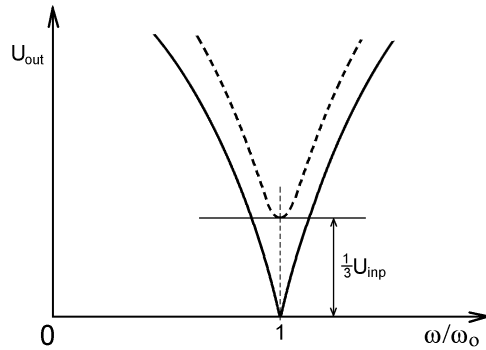


Fig. 4

where $\omega_0 = 1/(RC)$. If the resistors and capacitors in *Fig. 1* are fixed, the output voltage is dependent on the frequency of the input voltage. The dependence of $U_{out}(\omega/\omega_0)$ is shown in *Fig. 4*. We see, that there is a single frequency

$$\omega_0 = \frac{1}{RC}, \quad (8a)$$

$$f_0 = \frac{1}{2\pi RC}, \quad (8b)$$

at which the output voltage is zero. In the vicinity of this frequency the circuit behaves itself as a resonant circuit with relatively high Q-factor. The circuit is particularly useful at low frequencies, where the equivalent RLC-circuit request large values of L and C .

Another way to analyse the twin-T bridge is using the method of node voltages.

2 The bridged T

If we remove the capacitor $2C$ in the circuit of *Fig. 1*, we get a new selective element, commonly called the bridged T-filter, shown in *Fig. 5*. The analysis similar to this used in preceding case leads to an equivalent Π -connection (see *Fig. 3*), with

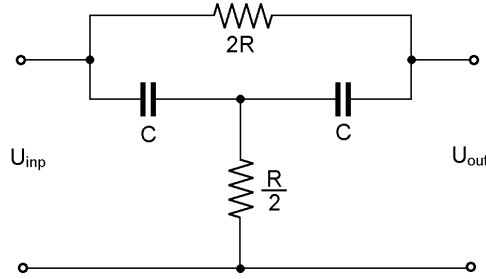


Fig. 5

$$Z''_A = 2 \frac{R + j\omega C}{1 - \omega^2 C^2 R^2 + j\omega CR}, \quad (9)$$

$$Z''_B = Z''_C = \left(R + \frac{1}{j\omega C} \right), \quad (10)$$

The complex transmission coefficient is

$$\begin{aligned} K(\omega) &= \frac{U_{out}(\omega)}{U_{inp}(\omega)} = \frac{Z''_C}{Z''_A + Z''_C} = \frac{(\omega CR)^4 + (\omega CR)^2 + 1 + j2\omega CR[(\omega CR)^2 - 1]}{(\omega CR)^4 + 7(\omega CR)^2 + 1} = \\ &= \frac{\left(\frac{\omega}{\omega_0}\right)^4 + \left(\frac{\omega}{\omega_0}\right)^2 + 1 + j2\frac{\omega}{\omega_0} \left[\left(\frac{\omega}{\omega_0}\right)^2 - 1\right]}{\left(\frac{\omega}{\omega_0}\right)^4 + 7\left(\frac{\omega}{\omega_0}\right)^2 + 1}. \end{aligned} \quad (11)$$

where

$$\omega_0 = \frac{1}{RC}, \quad (12)$$

From the expression (11) is obvious, that the output voltage is real if $\omega = \omega_0 = 1/(RC)$, and at this frequency approaches minimum, which is

$$U_{out.min} = \frac{1}{3}U_{inp}. \quad (13)$$

The dependence $U_{out}(\omega \omega_0)$ is shown in Fig. 4 (dashed curve).

3 Delta-star transformation

The passive three terminal network consisting of three impedances Z_A , Z_B and Z_C as shown in Fig. 1a, is said to form a delta (Δ) – connection. The passive three terminal network consisting of three impedances Z_1 , Z_2 and Z_3 as shown in Fig. 1b, is said to form a star (Υ) – connection. The two circuits are equivalent if their respective input, output and transfer impedance are equal.

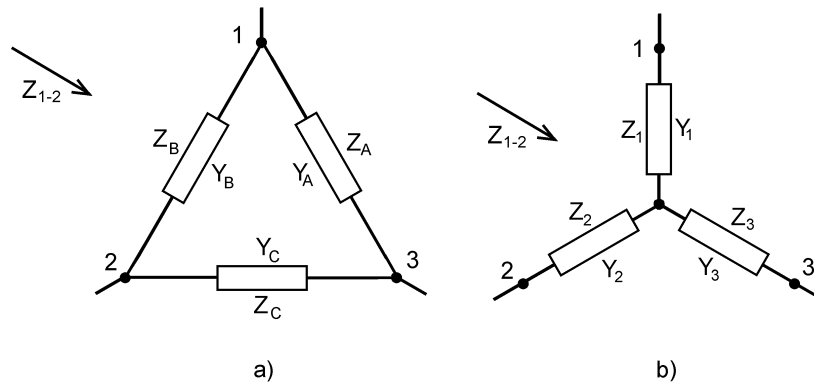


Fig. 1

Assuming open circuit conditions, we get from Figs. 1a, 1b:

Impedance	Delta	Star
Z_{1-2}	$= \frac{Z_B(Z_A + Z_C)}{Z}$	$= Z_1 + Z_2$
Z_{2-3}	$= \frac{Z_C(Z_A + Z_B)}{Z}$	$= Z_2 + Z_3$
Z_{3-1}	$= \frac{Z_A(Z_B + Z_C)}{Z}$	$= Z_1 + Z_3$

where

$$Z = Z_A + Z_B + Z_C .$$

Rearranging the above equations gives

$$Z_1 + Z_2 = \frac{Z_A Z_B}{Z} + \frac{Z_B Z_C}{Z} , \quad (1)$$

$$Z_2 + Z_3 = \frac{Z_B Z_C}{Z} + \frac{Z_C Z_A}{Z} , \quad (2)$$

$$Z_3 + Z_1 = \frac{Z_C Z_A}{Z} + \frac{Z_A Z_B}{Z} . \quad (3)$$

Subtracting Eq. (2) from Eq. (1)

$$Z_1 - Z_3 = \frac{Z_A Z_B}{Z} - \frac{Z_C Z_A}{Z} , \quad (4)$$

Adding Eq. (3) and Eq. (4) gives

$$Z_1 = \frac{Z_A Z_B}{Z} , \quad (4)$$

similarly

$$Z_2 = \frac{Z_B Z_C}{Z} , \quad (6)$$

and

$$Z_3 = \frac{Z_C Z_A}{Z} . \quad (7)$$

The reverse transformation of “star network” into “delta” is best carried out by using impedances replaced by admittances, and short circuiting one pair of corresponding terminals in each network at a time. Thus from *Figs. 1a, 1b* we get:

Short - circuited

terminals	Delta	Star
1-3	$Y_{1-2} = Y_B + Y_C$	$= \frac{Y_2(Y_3 + Y_1)}{Y}$
2-3	$Y_{1-3} = Y_A + Y_B$	$= \frac{Y_1(Y_2 + Y_3)}{Y}$
1-2	$Y_{2-3} = Y_C + Y_A$	$= \frac{Y_3(Y_1 + Y_2)}{Y}$

where

$$Y = Y_1 + Y_2 + Y_3 .$$

Solving for “delta” impedances:

$$Y_A = \frac{Y_3 Y_1}{Y} , \quad (8)$$

$$Y_B = \frac{Y_1 Y_2}{Y} , \quad (9)$$

$$Y_C = \frac{Y_2 Y_3}{Y}, \quad (10)$$

in terms of impedances

$$Z_A = Z_3 + Z_1 + \frac{Z_3 Z_1}{Z_2}, \quad (11)$$

$$Z_B = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}, \quad (12)$$

$$Z_C = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}. \quad (13)$$

A.T.